

ECE 100 (Spring 2021) - Quiz #2

(Format: 2 questions, 50 minutes)

Name: _____

Student ID: _____

Score: _____ out of 50

Instructions:

1. Register for the quiz (if you are seeing this, you should have already registered)
2. Once you register for the midterm, you will have 50 minutes to complete Quiz #2.
3. After the midterm, you have 15 minutes to submit and upload your quiz to CCLE (under "Week 8 → Quiz #2").
4. Please fill out this 'End-of-Quiz' survey to acknowledge that you have completed the quiz and submitted your answer sheet to CCLE:
<https://forms.gle/ygYR56REKELkUXoE6>

Rules:

- Quiz is closed book. No computers, cell phones, etc.
- 1-page cheat sheet
- Scientific calculator allowed.
- Box all of your answers & show your work.
- **If you have questions on the exam, please DO NOT post on Piazza. Email instructor(s) directly.**

Quiz Start Time:

Wednesday, May 19th @ 6:00pm PDT

Note: Once you register for the quiz, you will have 1h 5m to complete & upload your results. (50 minutes to take the exam, 15 minutes to upload).

End Time:

Thursday, May 20th @ 5:59pm PDT (answer sheet must be submitted by this time)

No late submissions

Problem 1: Phasors (15 points)


(a) Given $i_1(t) = 4\cos(\omega t + 30^\circ)$ and $i_2(t) = 5\sin(\omega t - 20^\circ)$, solve for

$i_T(t) = i_1(t) + i_2(t)$. (4 points)

(b) Using the phasor approach, determine the current $i(t)$ in a circuit described by the following 2nd order differential equation. (5 points)

$$4i + 8 \int i \, dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

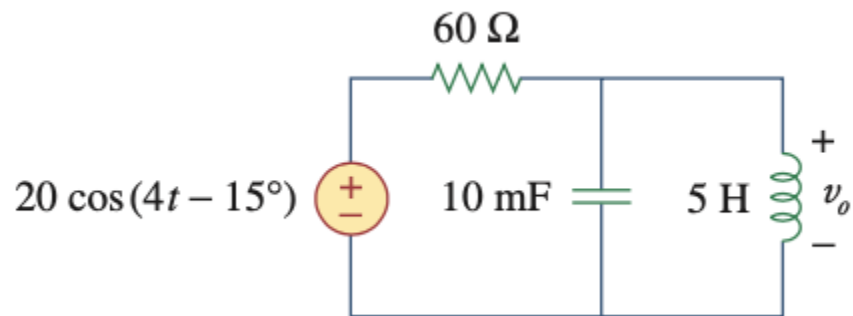
(c) Determine $v_o(t)$ in the following circuit. (5 points)



(d) What type of filter can be constructed using the circuit topology shown in part (c)? (1 point)

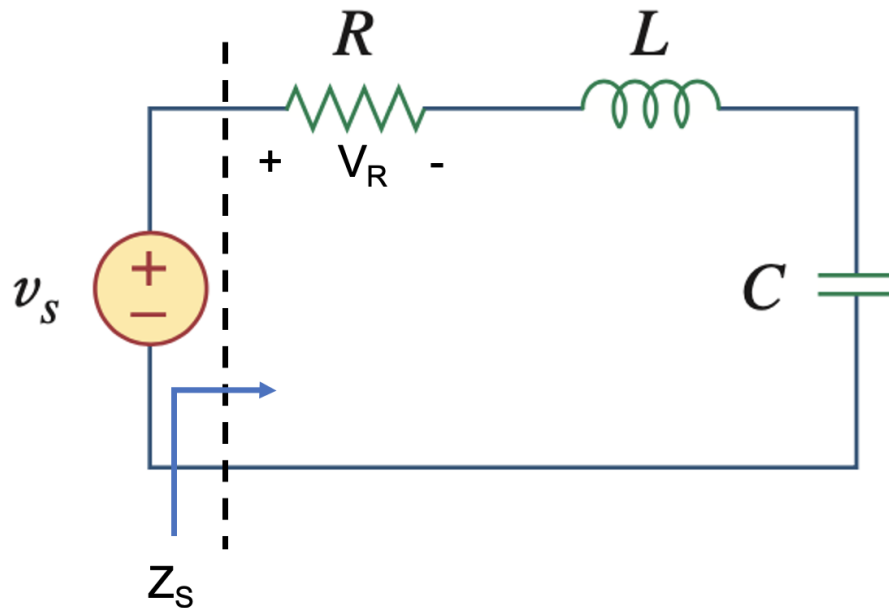Problem 2: Resonance (35 points)

Consider the series RLC circuit shown below. The source voltage is given as $V_s(t) = V_m \sin(\omega t)$.



(a) Solve for the voltage $V_R(t)$ in the time domain using 2nd order differential equations. You may neglect the complementary solution.

(4 points)

Hint: Start by writing the differential equation for the current flowing through the circuit, $i(t)$. Neglecting the complementary solution, you may consider a particular solution of the form $i_p(t) = A \times e^{j\omega t}$.

(b) Solve for the voltage $V_R(t)$ using the concept of phasors and complex impedances. (4 points)

(c) Solve for the impedance seen by the source, Z_s . (2 points)

(d) Derive for the transfer function, $H(j\omega) = V_R(j\omega)/V_S(j\omega)$. (3 points)

(e) Write a set of expressions that describes the magnitude, $|H(j\omega)|$, and phase $\angle H(j\omega)$ of the transfer function derived in (d). (3 points)

(f) Draw the Bode plot of the transfer function. Show both magnitude and phase plots on two separate graphs. (3 points)

(g) What is the resonant angular frequency, ω_o ? (2 points)

(h) What is the output phase with respect to the input phase at resonance ($\omega = \omega_o$)? (2 points)

(i) What is the quality factor, Q_s , of this circuit? (2 points)

(j) What is the 3dB bandwidth of this circuit? (2 points)

(k) Plot $V_R(t)$ considering the following excitation: (3 points)

for $t < 0$: $V_s(t) = V_m \sin(\omega t)$

for $t \geq 0$: $V_s(t) = 0$

(l) What is the energy stored in the first cycle (at $t > 0$)? What is the energy during the second cycle? (3 points)

Hint: Consider a damped oscillation with an envelope of $e^{-\alpha t} = e^{-t/\tau}$ where

$$\alpha = \frac{1}{\tau} = \frac{\omega_o}{2Q_s} \text{ (is also related to the damping coefficient: } \alpha = \frac{1}{\tau} = \zeta \omega_o \text{).}$$

(m) How do you relate this to the quality factor of the circuit? (2 points)