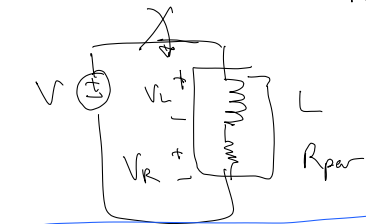




RL circuits

diff. eq.



$$V(t) = L \frac{di}{dt} + iR_{par}$$
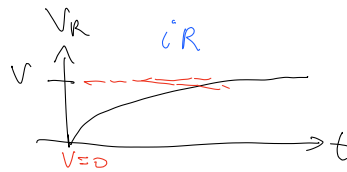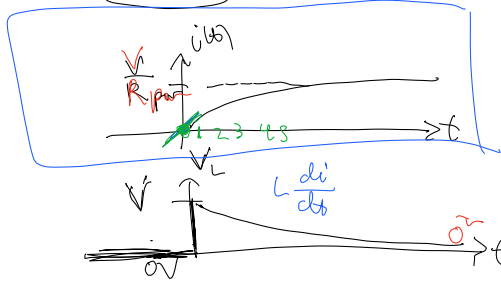
$$i(t) = \frac{V}{R_{par}} (1 - e^{-Rt/L})$$




resistance-limited circuit

$$t=0 : i=0$$

$$V_R = 0 \quad V = V_L + V_R$$

$$\rightarrow V_L = V = L_1 \frac{di}{dt}$$
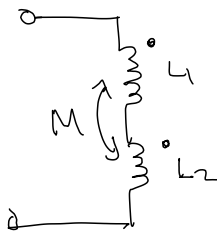
$$\frac{di}{dt} = \frac{V}{L_1} = \frac{\Delta i}{\Delta t} = \frac{10V}{L_1}$$



① aiding

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$


$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

② opposing

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$


... di1 ... di2

① aiding

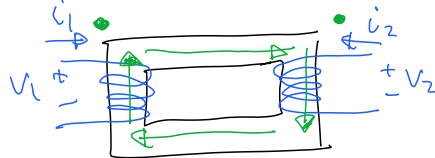

$$\phi = \phi_1 + \phi_2$$


② opposing

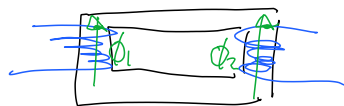


$$\phi = \phi_1 - \phi_2$$

$$V_1 = N_1 \frac{d\phi}{dt}$$

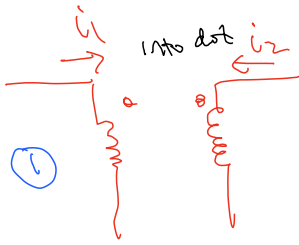
$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$







$\Rightarrow$  aiding

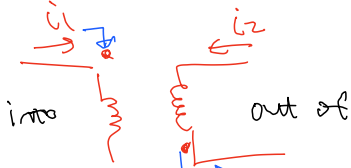




$\Rightarrow$  opposing

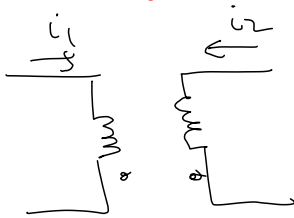


out of the dot (or both sides)

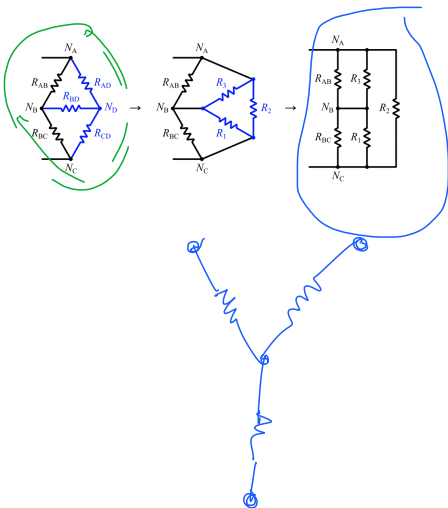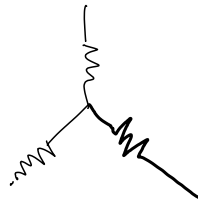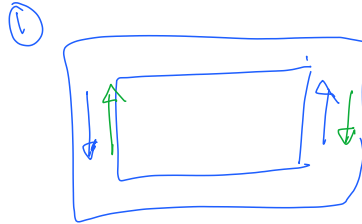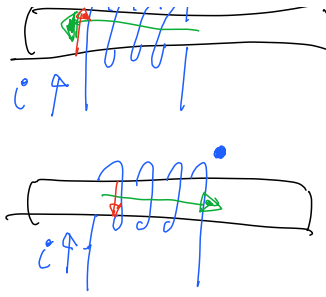



net = node

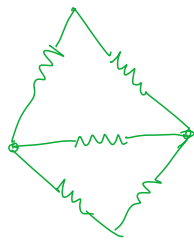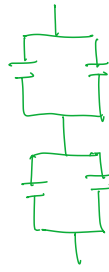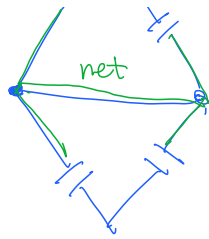

$Y \leftrightarrow \Delta$

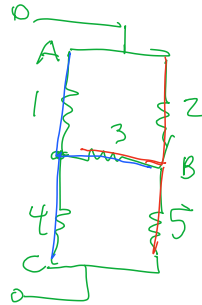

① redraw

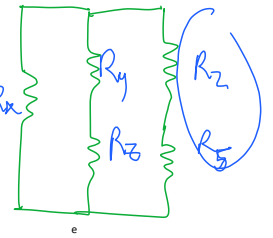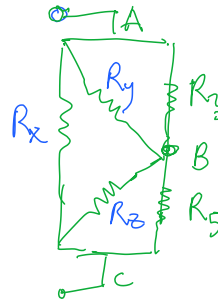


unchanged

$R_x, R_y, R_z$  be  
re-computed using  
 $\Delta \leftrightarrow Y$  transform


## Tools :

- ① KVL
- ② KCL
- ③ Ohm's Law
- ④ source transformations
- ⑤ Superposition
- ⑥ series/parallel circuits

★ KCL is more useful

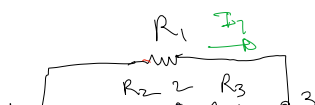

node 2: ground  
 $V_2 = 0$

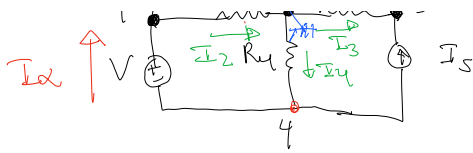

node 1:

$$I_x - I_1 - I_2 = 0$$

$$I_1 = \frac{V_1 - V_3}{R_1} \quad I_2 = \frac{V_1 - V_2}{R_2}$$

What is  $I_x$ ?


\* always defined  
I flowing into  
node = 0

\* voltage source

don't  
use  
KCL



current can be any  
value

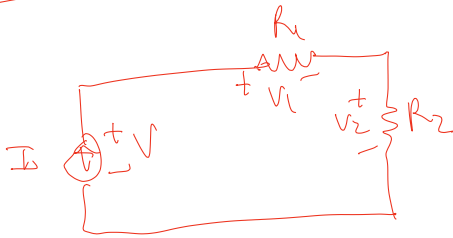



$$V - IR_1 - IR_2 = 0 \quad (KVL)$$

how would solve for V?

$$V = I(R_1 + R_2)$$

N-1 loops }  
M-1 nodes } 3 variables  
(OV)



cannot solve  
KCL @ node 1 early

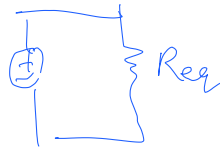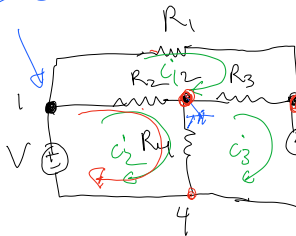


$$\text{loop \#3: } -V_s - (i_3 - i_2)R_4 - (i_3 - i_1)R_3 = 0$$


What is  $V_s$ ?

→  $V_s$  can be any value

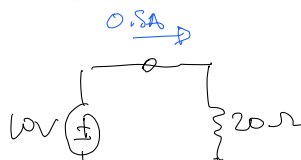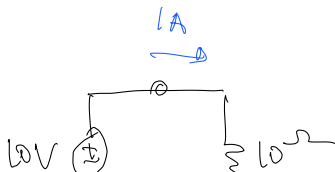

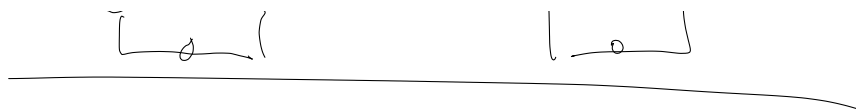

ideal transformer:

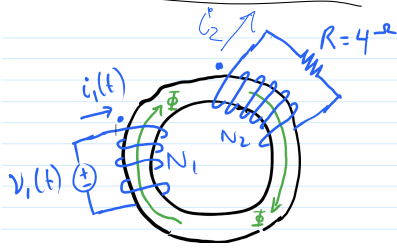

$$V_1 = N_1 \frac{d\Phi}{dt}$$


$$V_1 = L_1 \frac{di_1}{dt}$$

$$V_2 = N_2 \frac{d\Phi}{dt}$$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$V_2 = \frac{N_2}{N_1} V_1$$


$$i_2 = \frac{N_1}{N_2} i_1$$

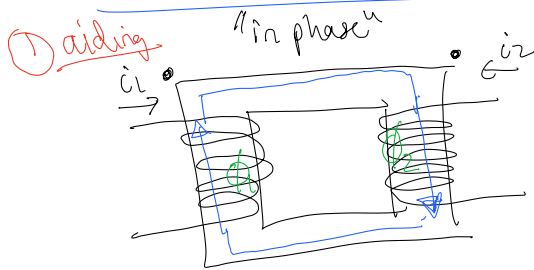

$$\Phi = \Phi_1 + \Phi_2$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
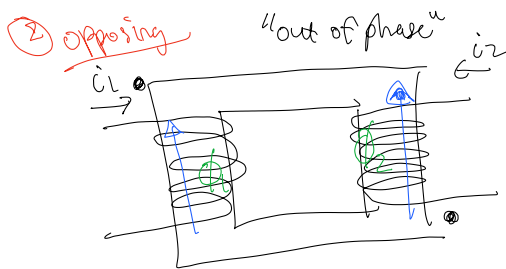
$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$



@ side 1:



$$\Phi = \Phi_1 - \Phi_2$$

@ side 2:

$$\Phi = \Phi_2 - \Phi_1$$

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

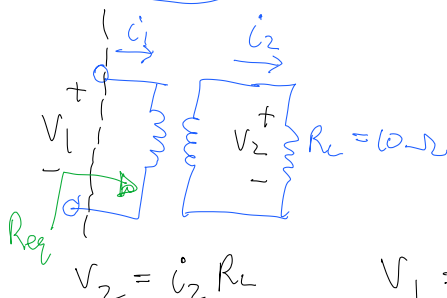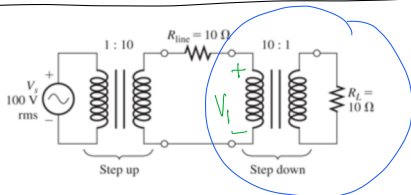
$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$



$$V_1 = \frac{N_1}{N_2} i_2 R_L$$


$$V_1 = \frac{N_1}{N_2} V_2$$

$$i_2 = \frac{N_1}{N_2} i_1$$


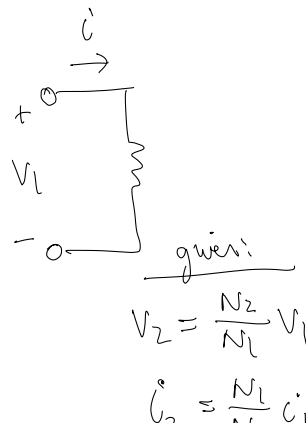


$$V_1 = \frac{N_1}{N_2} \left( \frac{N_1}{N_2} \right) i_1 R_L$$
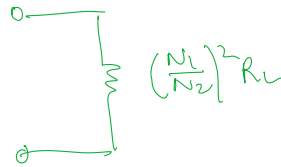
$$\frac{V_1}{i_1} = \left( \frac{N_1}{N_2} \right)^2 R_L \quad \leftarrow \quad R_{eq} = \frac{V_1}{i_1}$$




technique:  
"reflection"

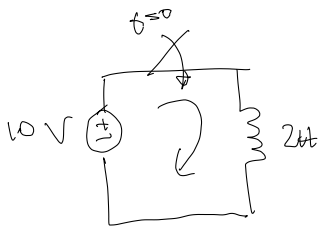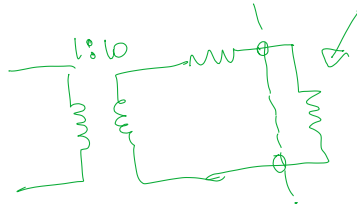

$$10V - (2H) \frac{di}{dt} = 0$$
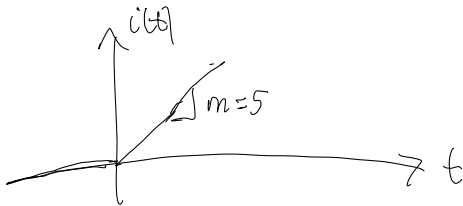
$$\frac{di}{dt} = \frac{10V}{2H} = 5 \frac{A}{s}$$





$$i(t=1s) = 5A$$



$$i(t=1000000s) = 5 \times 10^6 A$$

$$t \rightarrow \infty : i(t) \rightarrow \infty$$

differential

$$V = iR + L \frac{di}{dt}$$

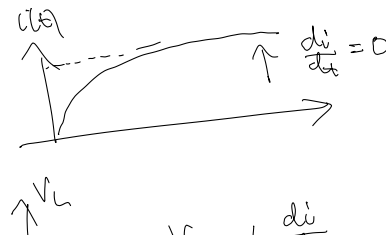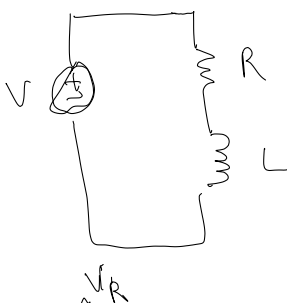

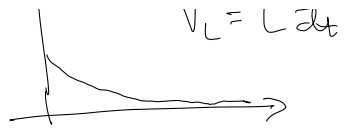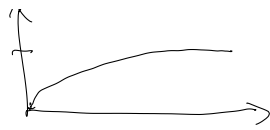

"Rising force - limited current"

---