
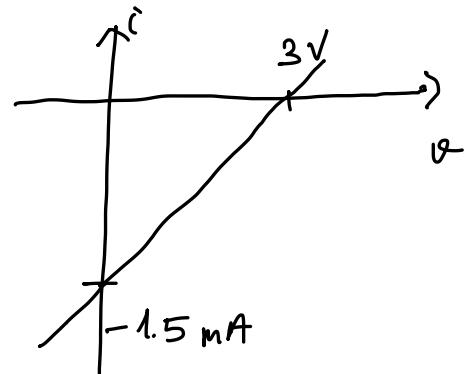


Home Work 4:

Problem 1:

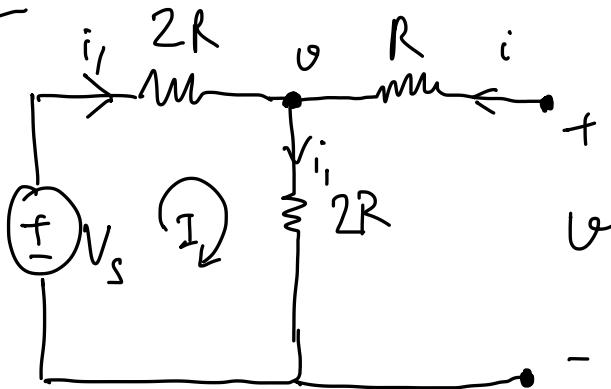

a) From the graph, we have:

$$V_o = 3V \text{ when } i = 0 \Leftrightarrow \text{open circuit} \rightarrow V_{th} = 3V$$

$$i_{sc} = -1.5 \text{ mA} \text{ when } V = 0 \Leftrightarrow \text{short circuit}$$



$$\Rightarrow Z_{th} = \left| \frac{V_o}{i_{sc}} \right| = \left| \frac{3V}{1.5 \times 10^{-3} A} \right| = 2 \times 10^3 (\Omega) = 2 k\Omega$$

b) When $\{i = 0, V = 3V\}$ \Rightarrow applying KVL for loop (I), we have.

$$V_s = 4Ri_1, \text{ also } V = 2Ri_1 = 3V \Rightarrow i_1 = \frac{3}{2R} (A)$$

$$\Rightarrow V_s = 4R \times \frac{3}{2R} \quad [6(V)]$$

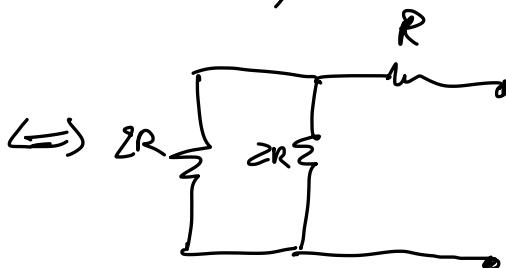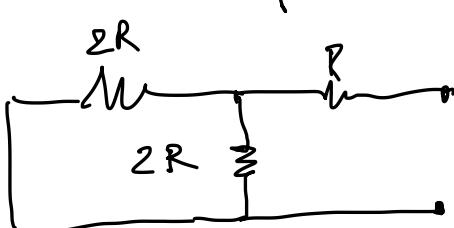* We have the new circuit when finding the Z_{th} ,
(short circuit for voltage source V_s)




$$\Rightarrow Z_{th} = (2R \parallel 2R) \text{ series } R = \frac{2R \times 2R}{2R + 2R} + R = 2R$$


From a, we know $Z_{th} = 2k\Omega \Rightarrow 2R = 2k\Omega$

$$\Rightarrow R = 1(k\Omega)$$

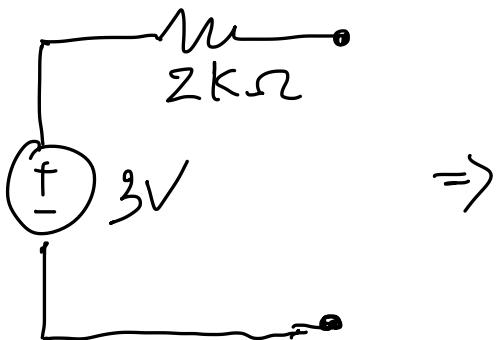c) From a & b, we have the equivalent Thevenin:



The new circuit:

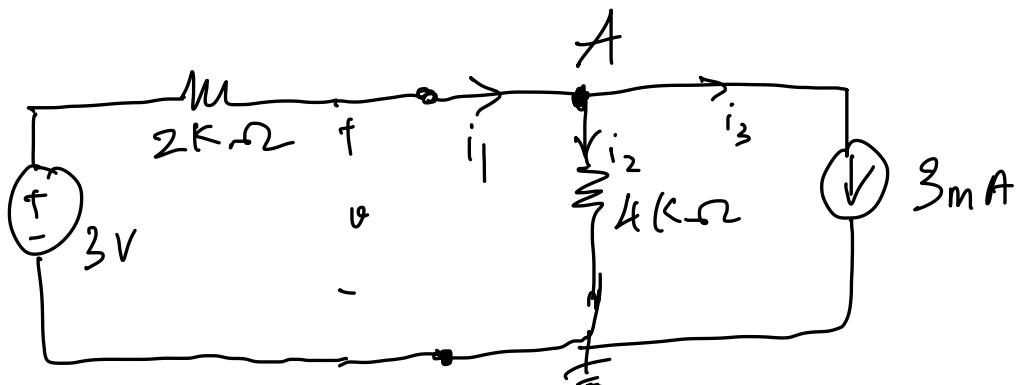


Apply KCL at $A \Rightarrow i_1 = i_2 + i_3$

$$\Rightarrow \frac{3-v}{2k\Omega} = \frac{v}{4k\Omega} + 3mA \Rightarrow \frac{3-v}{2k} - \frac{v}{4k} = 3mA$$


$$\Rightarrow 2(3-v) - v = 3 \times 4 = 12$$

$$\Rightarrow 6 - 2v - v = 12 \Rightarrow -6 = 3v \Rightarrow v = -2V$$


Problem 2 : Determine the current i :

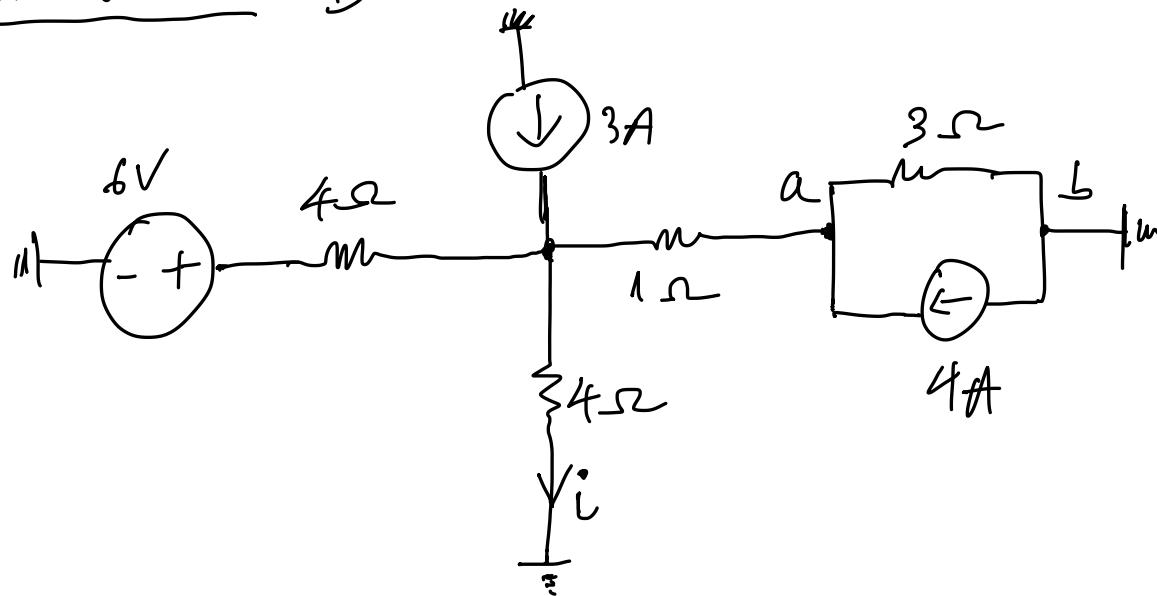

Since we have:

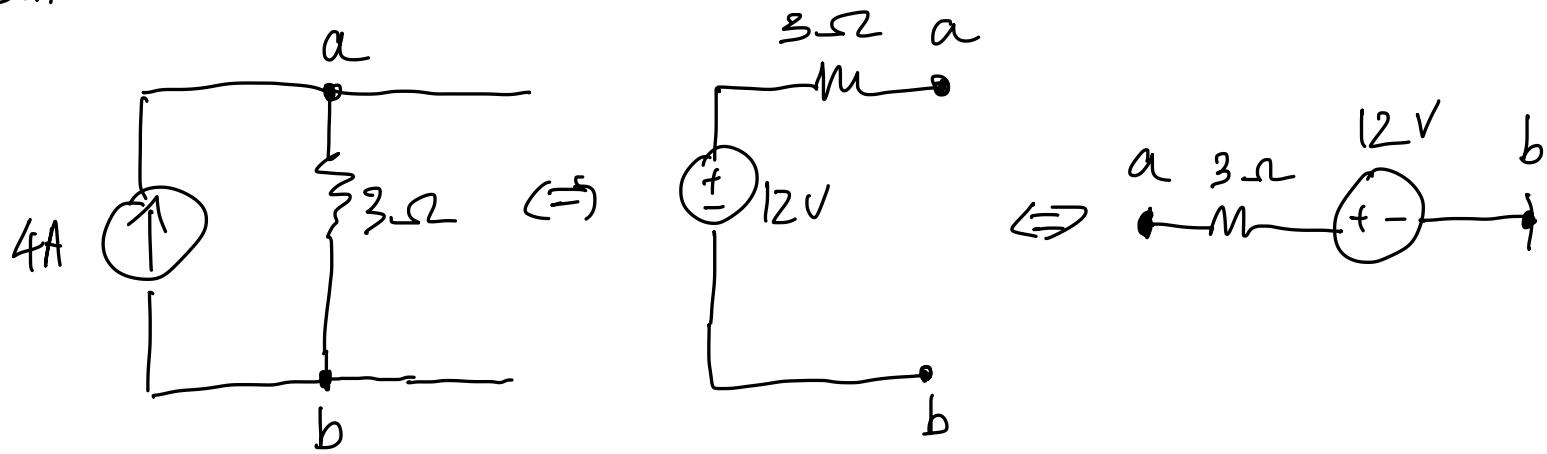

The original circuit will be equivalent:

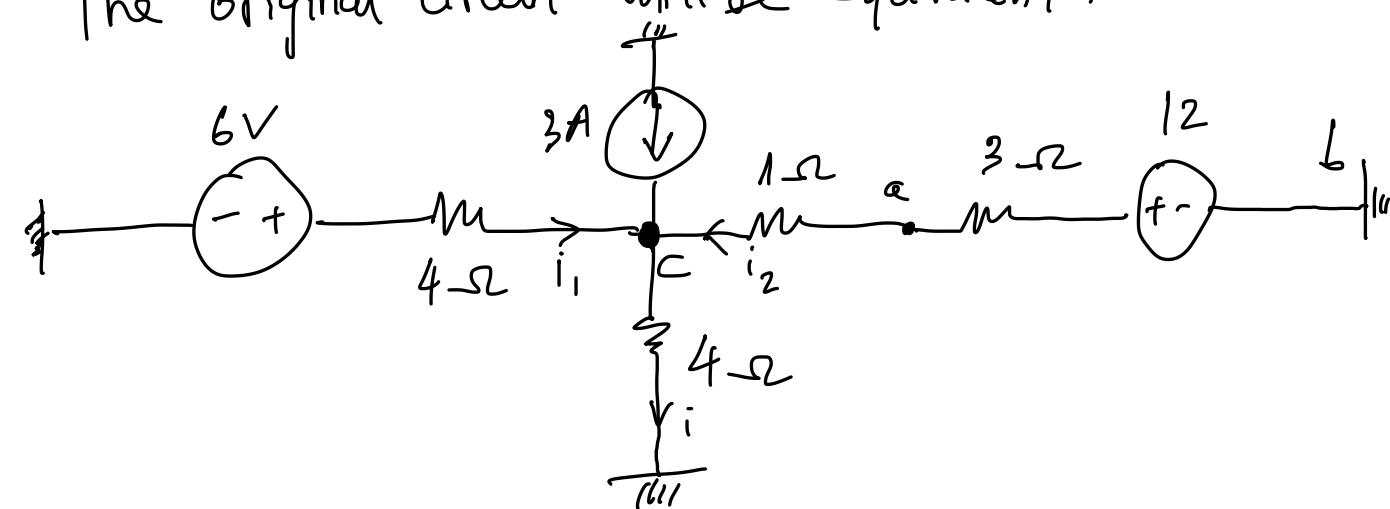

Apply KCL at C, we have: $i_1 + i_2 + 3 = i$



$$\Rightarrow \frac{6 - V_C}{4} + 3 + \frac{12 - V_C}{4} = \frac{V_C}{4}$$

$$\Rightarrow 6 - V_C + 12 + 12 - V_C = V_C$$

$$\Rightarrow 30 = 3V_C \Rightarrow V_C = 10 \text{ (V)}$$


$$\Rightarrow i = \frac{10}{4} = \boxed{2.5 \text{ A}}$$


Problem 3:

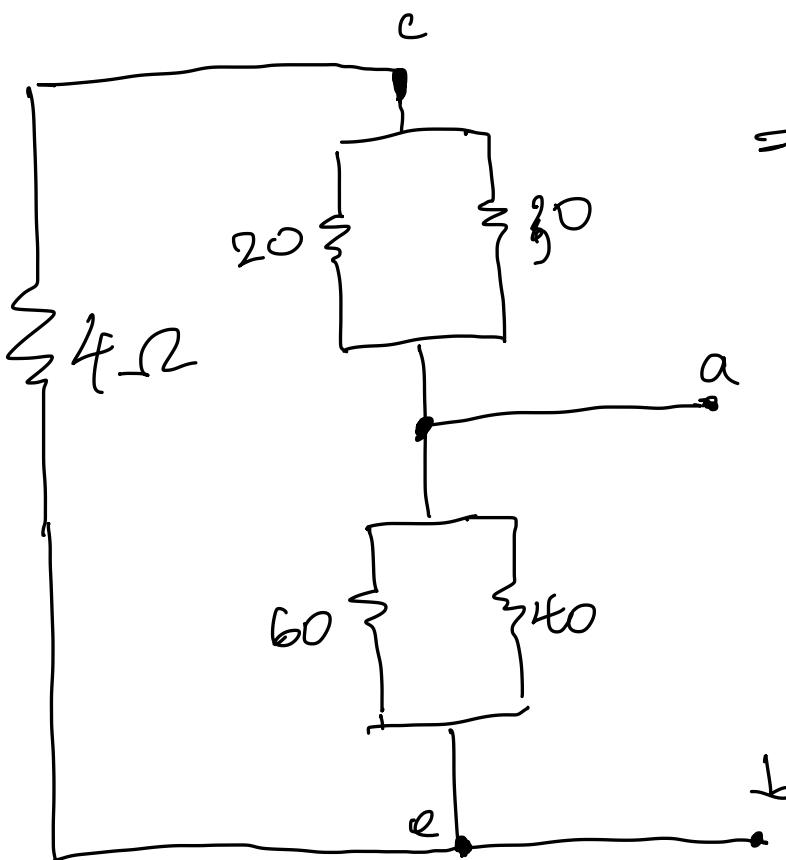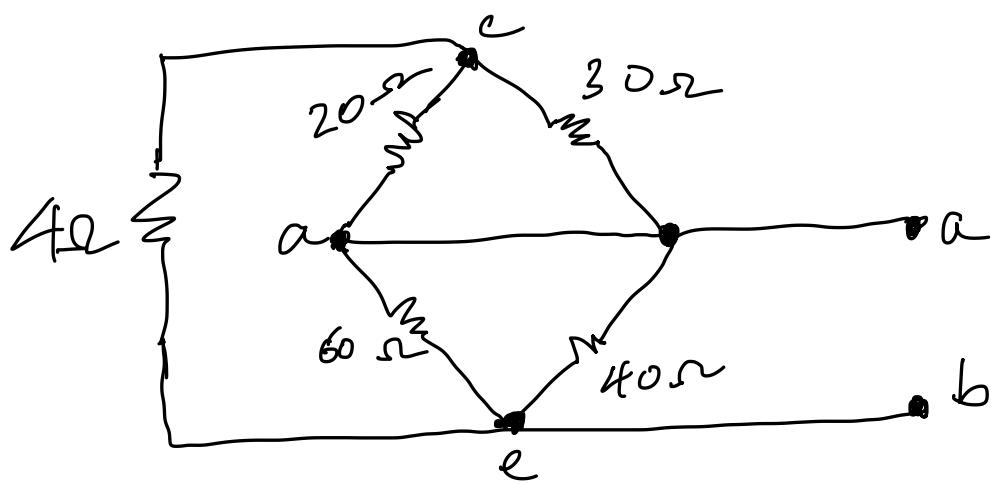

$$20 \parallel 30 \Rightarrow R_{20-30} = \frac{30 \times 20}{30 + 20} = 12\ \Omega$$

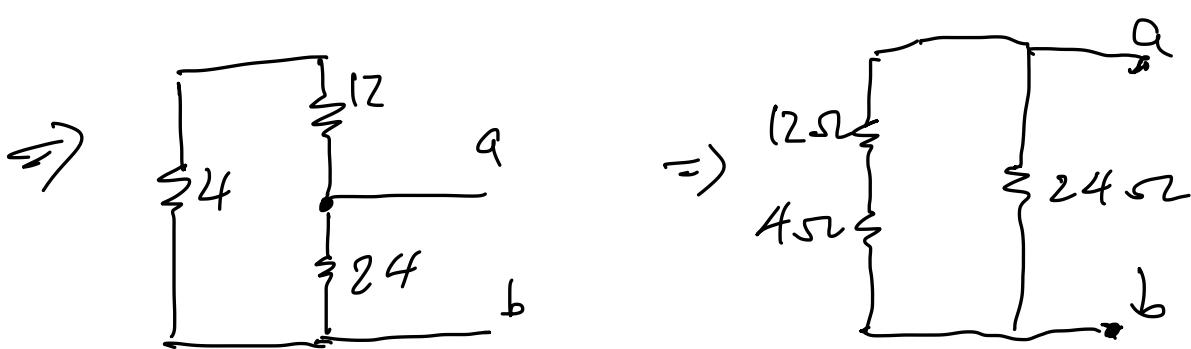
$$60 \parallel 40 \Rightarrow R_{60-40} = \frac{60 \times 40}{60 + 40} = 24\ \Omega$$



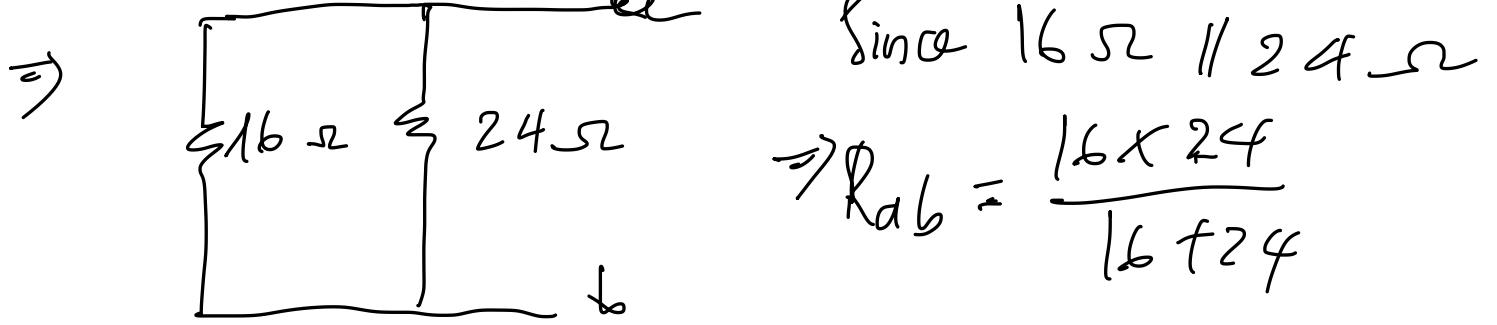

$$\Rightarrow R_{AB} = 9.6 (\Omega)$$


Problem 4: Given $R_{ab} = 23 \Omega$

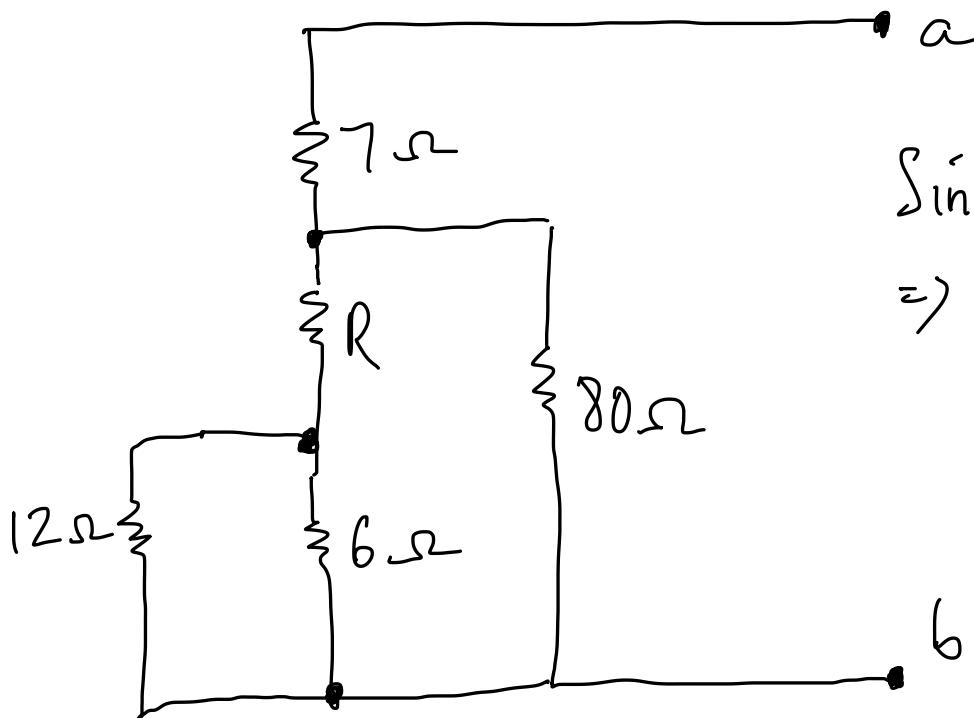

Since $12 \Omega \parallel 6 \Omega$

$$\Rightarrow R_{12-6} = \frac{12 \times 6}{12 + 6} = 4 \Omega$$

(R serves 4Ω) $\parallel 80 \Omega$

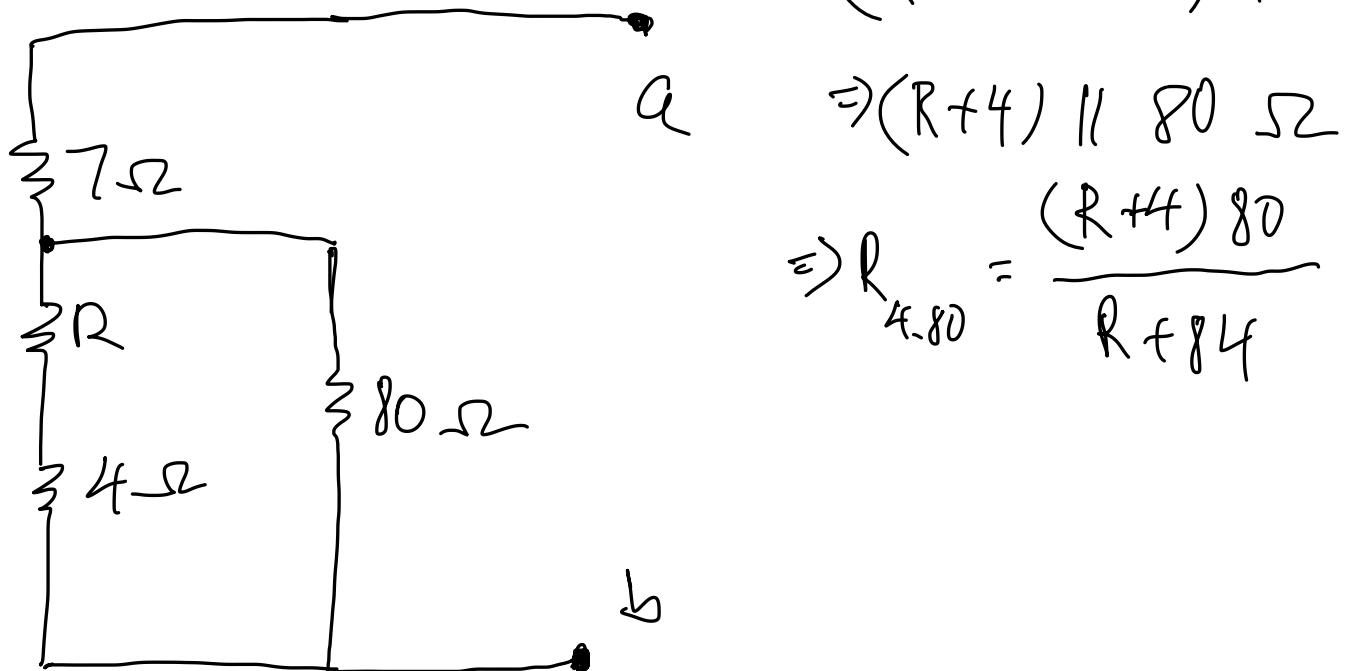

a

$\Rightarrow (R+4) \parallel 80 \Omega$

$$\Rightarrow R_{4-80} = \frac{(R+4) 80}{R+84}$$

Also R_{4-80} series $7 \Omega \Rightarrow$

$$R_{ab} = 7 + R_{4-80} = 23 (\Omega)$$

$$\Rightarrow R_{A-80} = 16 \Omega$$

$$\Rightarrow \frac{(R+4) \times 80}{R+84} = 16(\Omega)$$

$$\Rightarrow 80R + 320 = 16R + 1344$$

$$\Rightarrow 64R = 1024$$

$$\Rightarrow R = 16 (\Omega)$$

Problem 5: Given:

$$R_1 = 15 \Omega$$

$$R_2 = 5 \Omega$$


$$R_3 = 20 \Omega$$

$$R_4 = 10 \Omega$$

$$R_5 = 8 \Omega$$

$$R_6 = 4 \Omega$$

$$I_s = 5 A$$

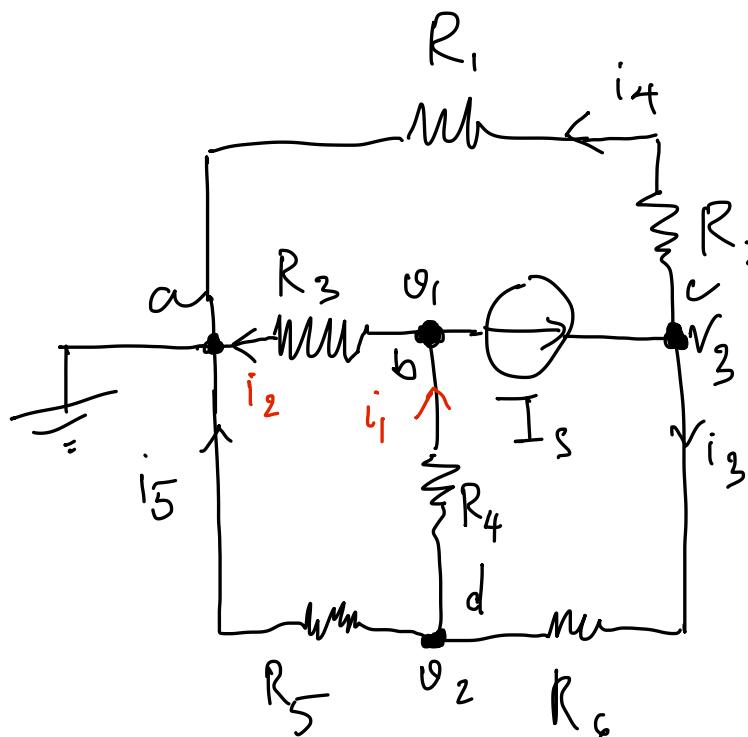

Apply KCL at b, we have:

$$i_1 = i_2 + I_s = i_2 + 5$$

$$\Rightarrow \frac{v_2 - v_1}{R_4} = \frac{v_1}{R_3} + 5$$

$$\Rightarrow \frac{v_2 - v_1}{10} = \frac{v_1}{20} + 5$$

$$\Rightarrow 2v_2 - 2v_1 = v_1 + 100$$

$$\Rightarrow 2v_2 - 3v_1 = 100 \quad (1)$$

Apply KCL at c, we have:

$$I_S = i_3 + i_4 \Rightarrow 5 = \frac{v_3 - v_2}{R_b} + \frac{v_3 - 0}{R_2 + R_1}$$

$$\Rightarrow 5 = \frac{v_3 - v_2}{4} + \frac{v_3}{20}$$

$$\Rightarrow 100 = 5v_3 - 5v_2 + v_3$$

$$\Rightarrow 6v_3 - 5v_2 = 100 \quad (2)$$

Apply KCL at a, we have:

$$i_2 + i_4 + i_5 = 0 \Rightarrow \frac{v_2}{R_S} + \frac{v_3}{R_1 + R_2} + \frac{v_1}{R_3} = 0$$

$$\Rightarrow \frac{v_2}{8} + \frac{v_3}{20} + \frac{v_1}{20} = 0$$

$$\Rightarrow 5v_2 + 2v_3 + 2v_1 = 0$$


$$\Rightarrow 2v_1 + 5v_2 + 2v_3 = 0 \quad (3)$$

From (1), (2) & (3), we have:

$$\begin{cases} -3v_1 + 2v_2 = 100 \\ -5v_2 + 6v_3 = 100 \\ 2v_1 + 5v_2 + 2v_3 = 0 \end{cases} \Rightarrow$$

$v_1 = -30.56(V)$
$v_2 = 4.167(V)$
$v_3 = 20.14(V)$

Problem 6:

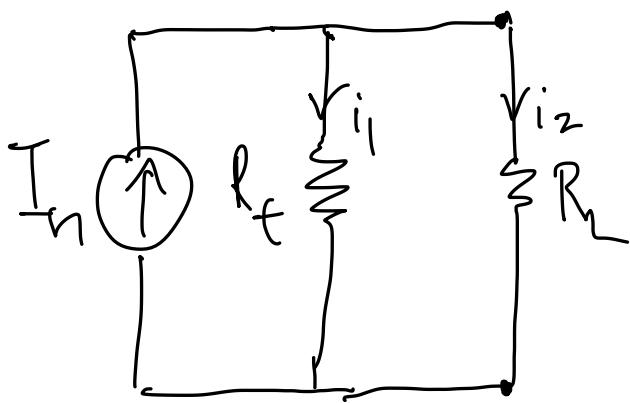

* Find expression for the power delivered to the load in term of I_n , R_t & R_L

$$i_2 = \frac{R_t}{R_t + R_L} I_n$$

(divide current)

$$\Rightarrow P_{R_L} = i_2^2 R_L = \left(\frac{R_t}{R_t + R_L} I_n \right)^2 \times R_L$$

$$\Rightarrow P_{R_L} = \frac{R_t^2 R_L}{(R_t + R_L)^2} I_n^2$$

* Assuming I_n, R_t are fixed value, R_L is variable. Show that maximum power delivered for $R_L = R_t$

let $x = R_L$, $R_t = a$ (constant), I_n constant

$$P = \frac{a^2 x}{(a+x)^2} \text{ In } (R_t = a > 0 \text{ & } R_L = x > 0)$$

since they are value of resistor

We have $\frac{dP}{dx} = a^2 \ln \left[\frac{x}{(a+x)^2} \right]'$

Also: $\left[\frac{x}{(a+x)^2} \right]' = \frac{(a+x)^2 - 2x(a+x)}{(a+x)^4}$

$$\Rightarrow \frac{dP}{dx} = 0 \Leftrightarrow (a+x)^2 - 2x(a+x) = 0$$

$$\Leftrightarrow (a+x)(a+x - 2x) = 0$$

$$\Leftrightarrow (a+x)(a-x) = 0 \Leftrightarrow \begin{cases} a = -x \text{ (reject)} \\ a = x \end{cases}$$

$$\Rightarrow \frac{dP}{dx} = 0 \Leftrightarrow a = x \Leftrightarrow R_t = R_L$$

Since $P = \frac{a^2 x}{(a+x)^2}$ will get maximum

When $\frac{dP}{dx} = 0 \Rightarrow$ the power which is delivered
for R_L will get maximum value when $R_L = R_t$.


* We have already $P = \frac{R_t^2 R_L}{(R_t + R_L)^2} \times I_n^2$

With $R_L = R_t$

$$\Rightarrow P = \frac{R_t^2 \times R_t}{4R_t^2} \times I_n^2 = \frac{R_t}{4} \times I_n^2$$

$$\Rightarrow P_{\max} = \boxed{\frac{I_n^2 R_t}{4}}$$

Problem 7:

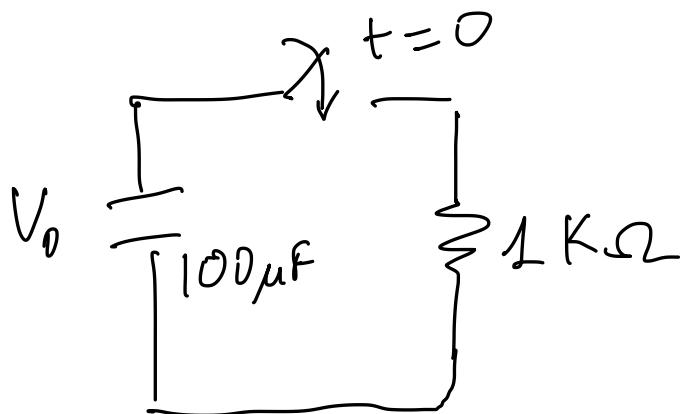


a capacitance is initially charged to 1000V

$\Rightarrow V_0 = 1000V$ at $t=0^+$
 (Since capacitor does not allow the voltage change instantaneously)

$$\Rightarrow V(0^+) = 1000V$$

Also when $t \rightarrow \infty \Rightarrow$

$$\Rightarrow V(\infty) = 0V$$

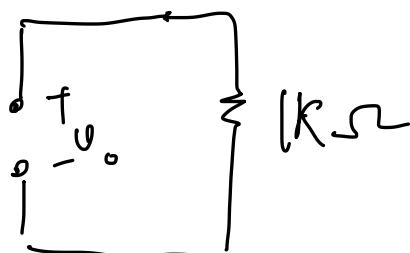

$$\text{Also: } V(t) = V(\infty) - (V(\infty) - V(0^+)) e^{-t/RC}$$

$$\Rightarrow V_C(t) = V_0 e^{-t/RC} = 1000 e^{-t/RC} (V)$$

$$R = 1000 \Omega, C = 100 \mu F = 100 \times 10^{-6} F$$

$$\Rightarrow RC = 1000 \times 100 \times 10^{-6} = 0.1$$

$$\Rightarrow V_C(t) = 1000 e^{-10t} (V)$$

$$\Rightarrow [V_C(t)]^2 = (1000)^2 e^{-20t}$$

\Rightarrow Energy of capacitor:

$$E(t) = \frac{1}{2} C [v_c(t)]^2 = \frac{1}{2} \times \underline{100} \times \underline{10^{-6}} \times \underline{1000^2} e^{-20t}$$
$$= 50 e^{-20t} \text{ (J)}$$

Since at $t=0^+$, we have the initial energy of capacitance $\Rightarrow E_0 = 50 e^0 = 50 \text{ J}$

Since 50% of the initial energy of capacitance has been dissipated in the resistance \Rightarrow the capacitance remains 50%.

\Rightarrow at t_2 , we have:

$$E(t_2) = 50 e^{-20t_2} = 50\% \text{ of } 50 \text{ J}$$
$$= 0.5 \times 50 = 25 \text{ (J)}$$

$$\Rightarrow e^{-20t_2} = \frac{25}{50} = 0.5$$


$$\Rightarrow t_2 = \frac{\ln 0.5}{-20} \Rightarrow t_2 \approx 0.03466 \text{ (s)}$$

$$\Rightarrow t_2 = 34.66 \text{ ms}$$

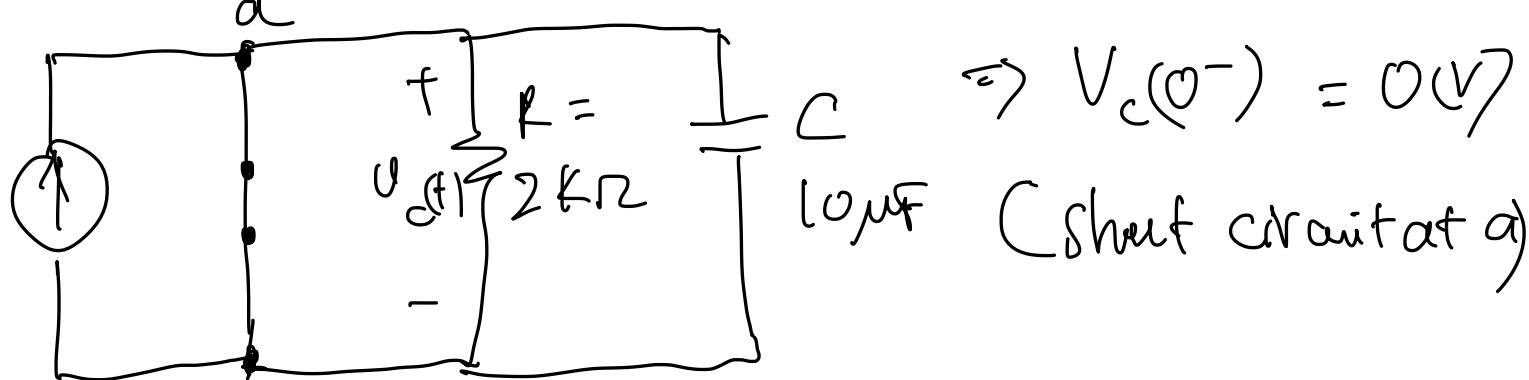Problem 3: $v_c(t)$


- * Switch was closed before $t=0$
- * open after $t=0$

At $t = 0^- \Rightarrow$ switch was closed, we have




$\Rightarrow v_c(0^+) = 0$ since the capacitor doesn't allow the voltage change instantaneously.


Then $t = 0^+$, we have:

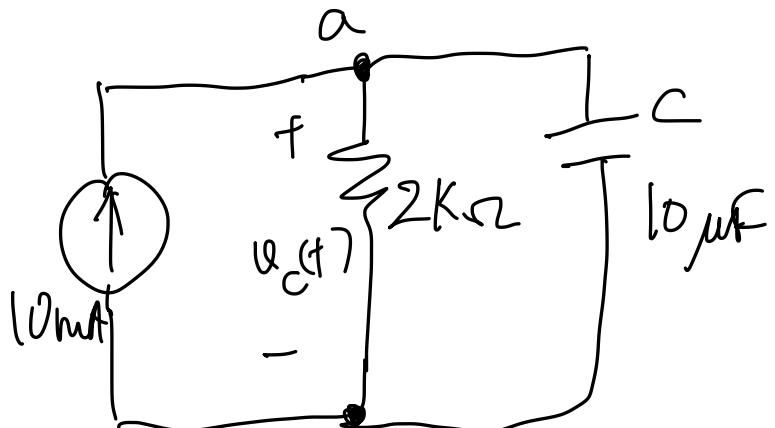


Since :

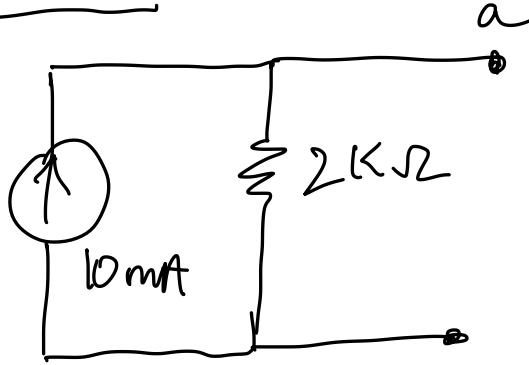


\Rightarrow

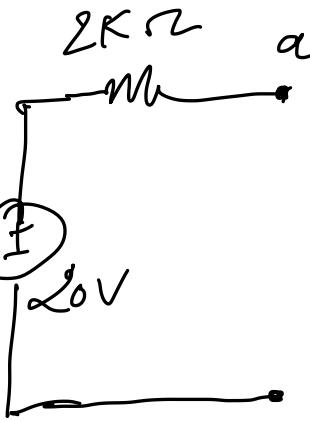

Thevenin equivalent.

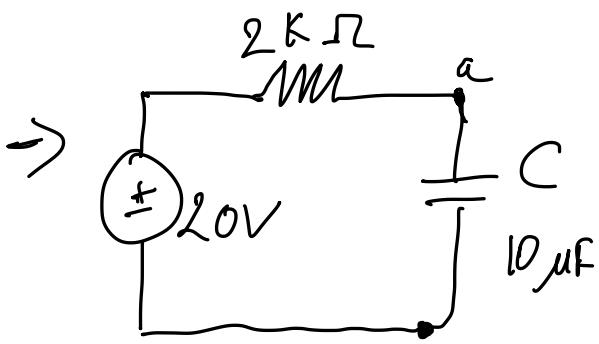

When $t \rightarrow \infty$, we have

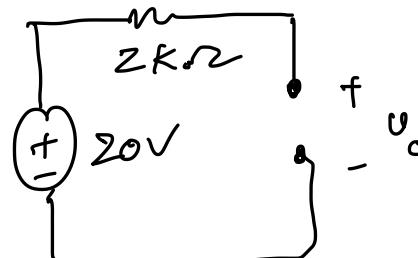

$$\Rightarrow V_c(\infty) = 20V.$$

$$A(s_0); I = RC = 2000\Omega \times 10 \times 10^{-6} = 0.02 \text{ (s)}$$


$$\Rightarrow V_d(t) = V(\infty) - (V(\infty) - V(0^+)) e^{-t/(RC)}$$

$$\Rightarrow V_c(t) = 20 - (20 - 0) e^{-50t} \quad (V)$$


$$V_c(t) = \boxed{20 - 20 e^{-50t} \quad (V)}$$

$$t=0 \Rightarrow V_c = 0$$


$$t=\infty \Rightarrow V_c = 20$$

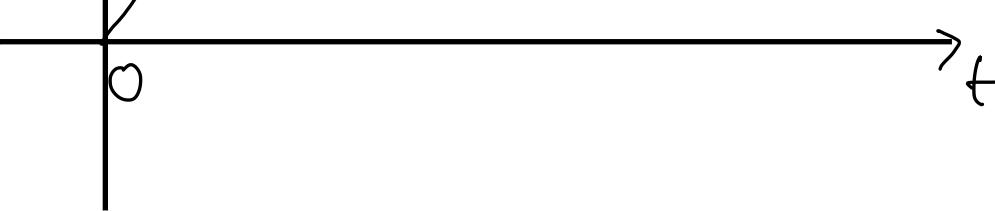

Problem 9: Determine the max of I_L

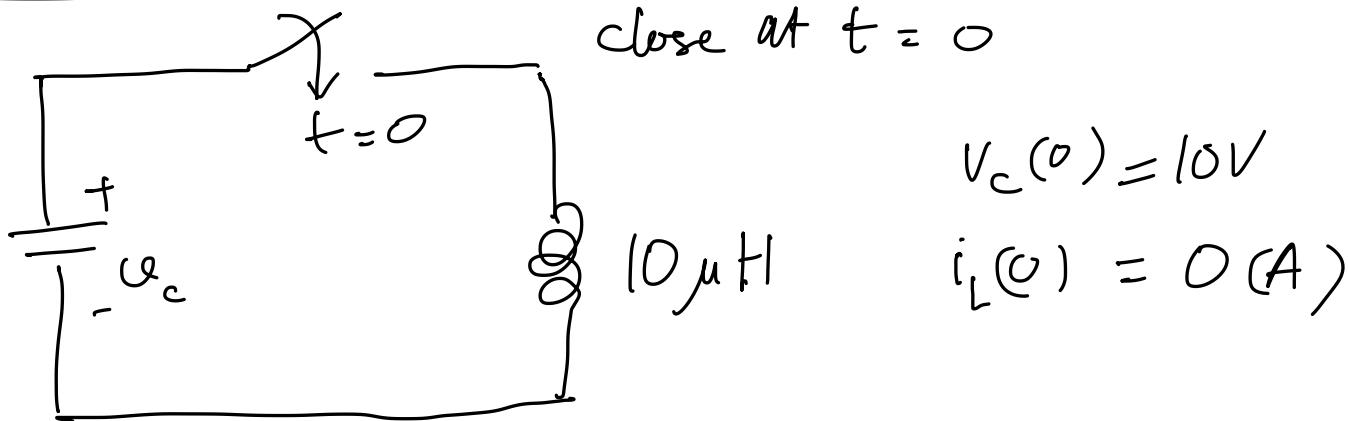

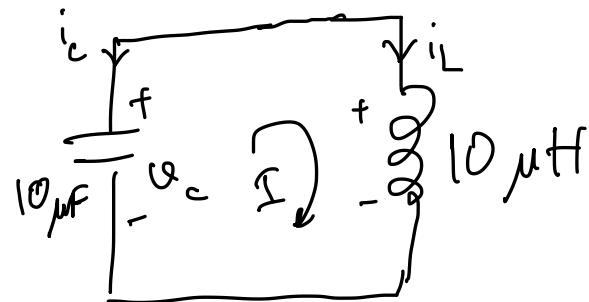Since capacitor doesn't allow the voltage change instantaneously & inductor doesn't allow the current change instantaneously $\Rightarrow V_c(0^+) = 10V$
 $i_L(0^+) = 0(A)$.



Using the energy conservation, we can have the maximum energy of L will be the same as the maximum energy of C that is initial energy of capacitance.

$$\text{Also } E_C = \frac{1}{2} C [V_{C(t)}]^2$$

In the initial time $t = 0^+$, we have

$$v_c(0^+) = 10V$$

\Rightarrow the maximum energy of capacitance:

$$E_{C_{\max}} = \frac{1}{2} C \times V^2 = \frac{1}{2} \times 10 \times 10^{-6} F \times 10^2 \\ = 0.0005 (J)$$

Beside, the energy of inductance:

$$E_L = \frac{1}{2} L [i_L(+)]^2$$

Since L is constant \Rightarrow the maximum of inductance \Leftrightarrow the maximum of current I_L

$$\Rightarrow E_{L_{\max}} = \frac{1}{2} L I_{L_{\max}}^2$$

Using the energy conservation we mentioned before, we have:

$$E_{C_{\max}} = E_{L_{\max}}$$

$$\Rightarrow \frac{1}{2} L I_{L_{\max}}^2 = 0.0005 \text{ (J)}$$


$$\Rightarrow \frac{1}{2} \times 10 \times 10^{-6} I_{L_{\max}}^2 = 0.0005$$

$$\Rightarrow I_{L_{\max}}^2 = 100$$

$$\Rightarrow I_{L_{\max}} = 10 \text{ (A)}$$

Problem 10: For a long time prior to $t=0$, the switch closed. Find v_c prior $t=0 \Rightarrow t \rightarrow 0^-$

Prior to $t=0 \Leftrightarrow$ We have:

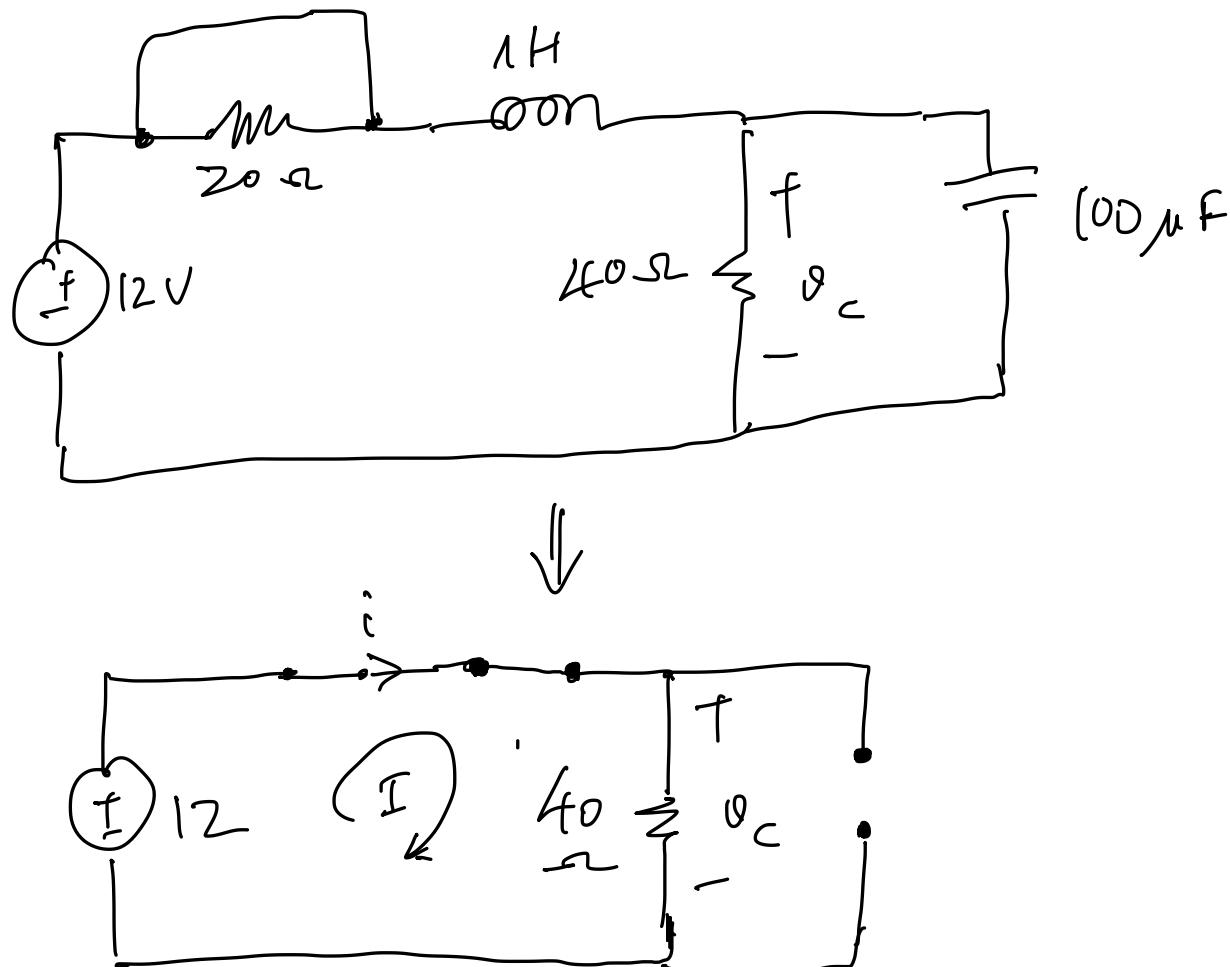


Apply KVL for $I \Rightarrow Iz = 40i \Rightarrow i = \frac{Iz}{40} (A)$
 $\Rightarrow i = 0.3 (A)$

$$\Rightarrow v_c = 40 \text{ } \Omega \times \frac{12}{40} = 12 (\text{V})$$


$$\Rightarrow v_c(0^-) = 12 \text{ V} \quad \& \quad i_L(0^-) = 0.3 (\text{A})$$

After opening the switch, We Have:

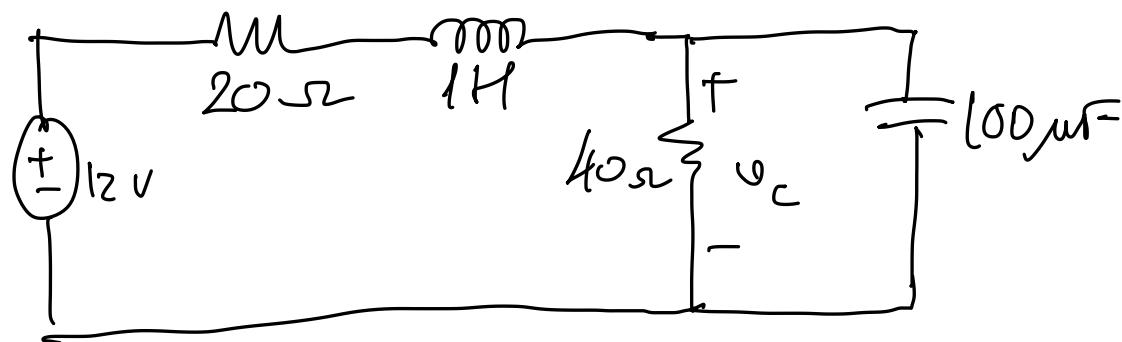

Since capacitor doesn't allow the voltage change instantaneously & inductor doesn't allow the current change instantaneously $\Rightarrow v_c(0^+) = 12V$
 $i_L(0^+) = 0.3(A)$

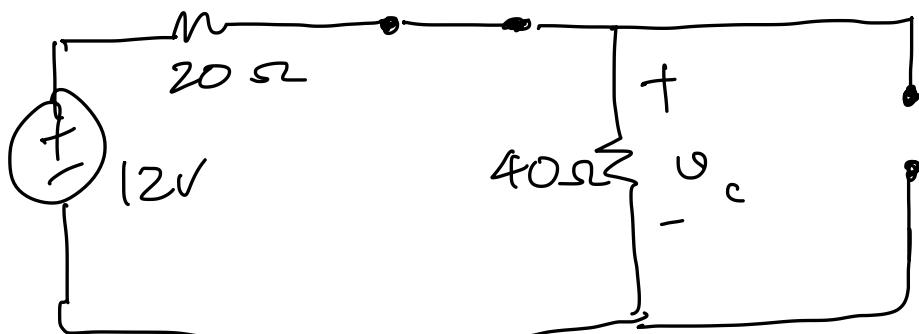After open switch for a long time, We Have:



$$\Rightarrow v_c = \frac{40}{20+40} \times 12 = 8V \quad (\text{Voltage divider})$$

$$\Rightarrow v_c(\infty) = 8V$$