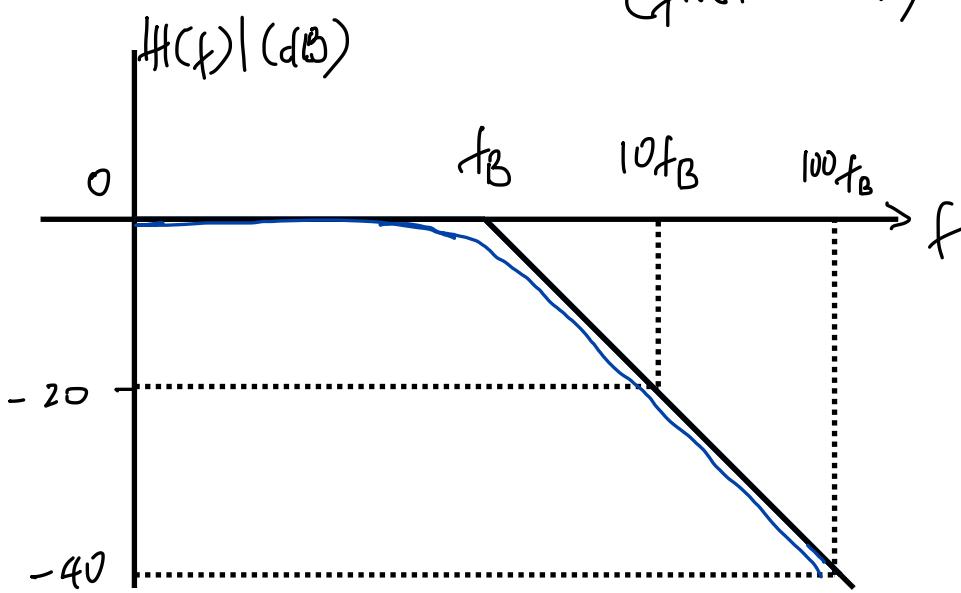



What Ho - HW 7

Problem 1:


a) i) low-pass: Example expected frequency:
(first-order)



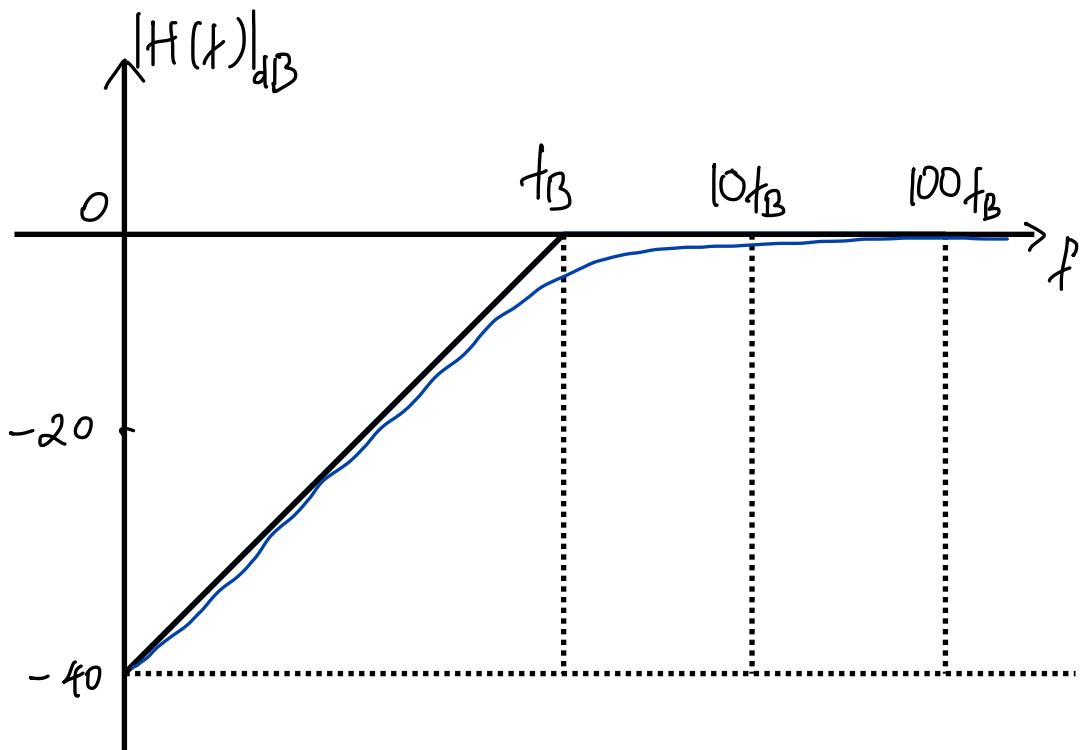
ii) High pass: Example expected frequency: (first-order)



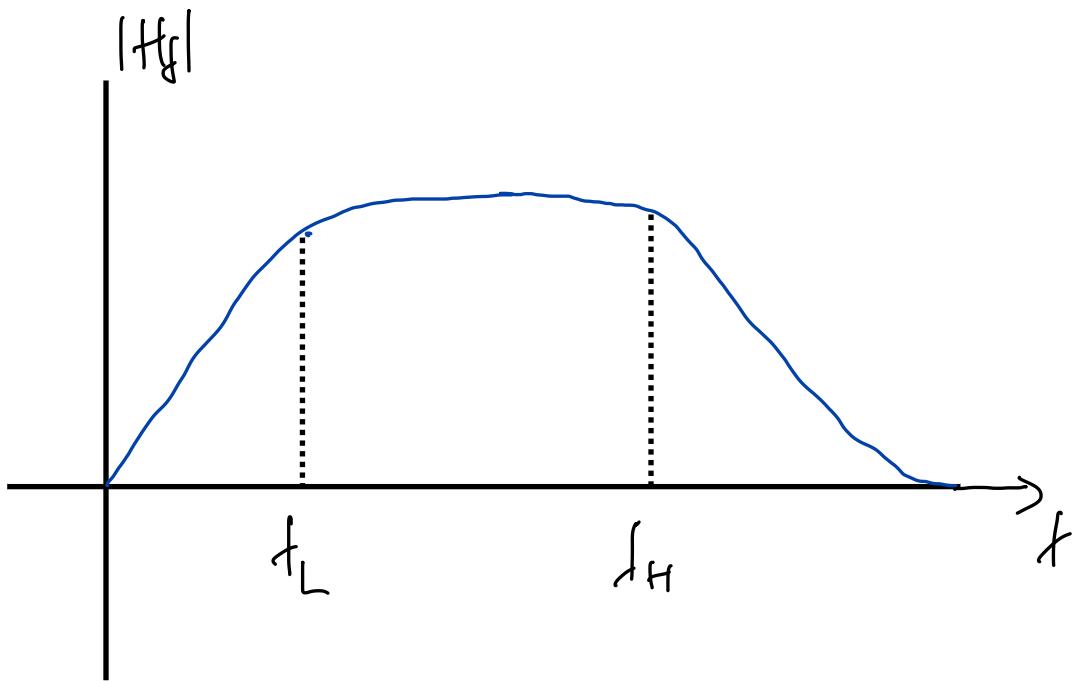
iii) band pass: Example expected frequency



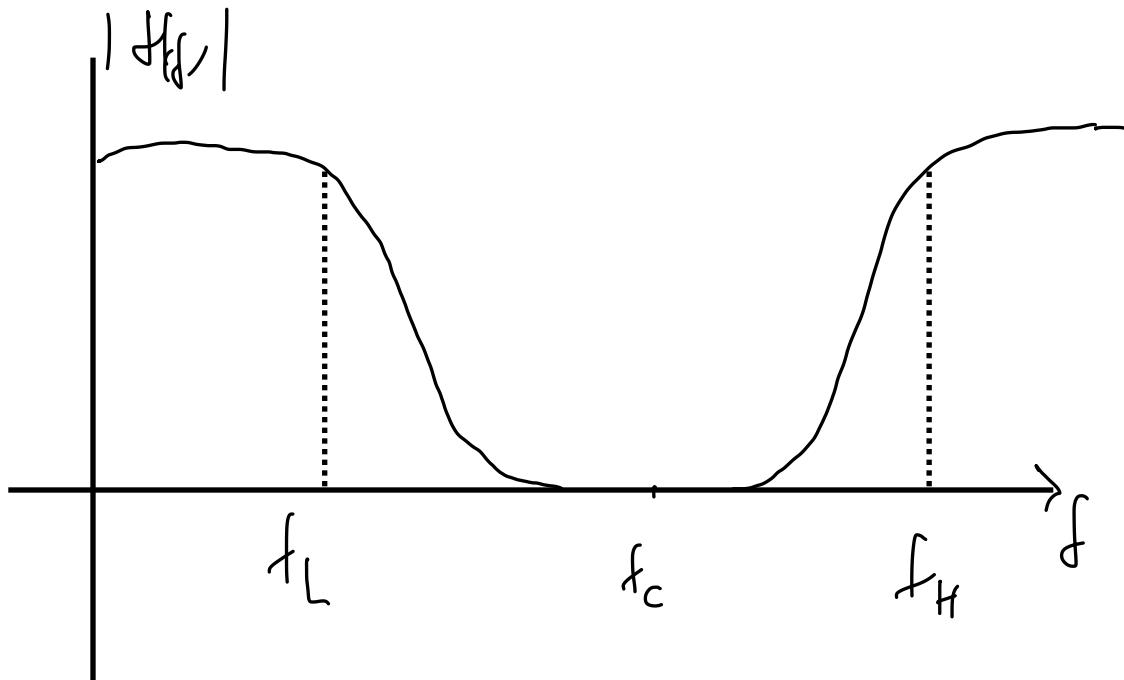iv) band Stop: Example expected frequency.



b) (Next page)

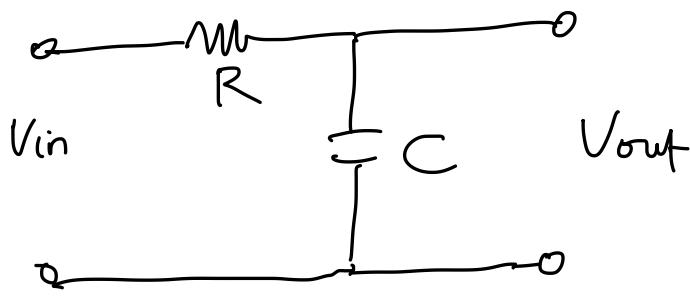

$$Z_C = \frac{1}{j\omega C}$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 + R_j\omega C} .$$

Since $\omega \rightarrow 0 \Rightarrow 1 + R_j\omega C \rightarrow 1 \Rightarrow \frac{V_{out}}{V_{in}} \sim 1$

While $\omega \rightarrow \infty \Rightarrow 1 + R_j\omega C \rightarrow \infty \Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 0$

\Rightarrow this circuit is PbW pass

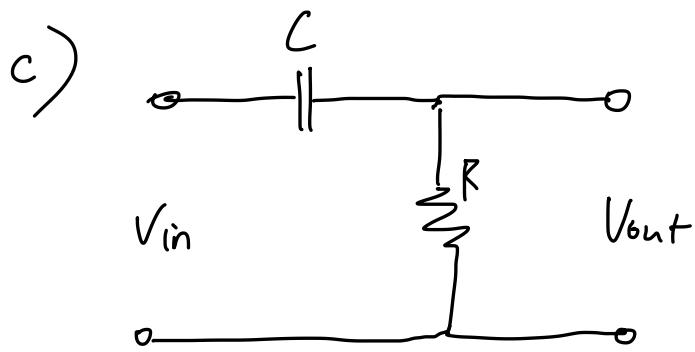


$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$= \frac{1}{1 + \frac{1}{j\omega RC}}$$

Since $\omega \rightarrow 0 \Rightarrow \frac{1}{j\omega RC} \rightarrow \infty$

$\Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 0$. While $\omega \rightarrow \infty \Rightarrow \frac{1}{j\omega RC} \rightarrow 0$

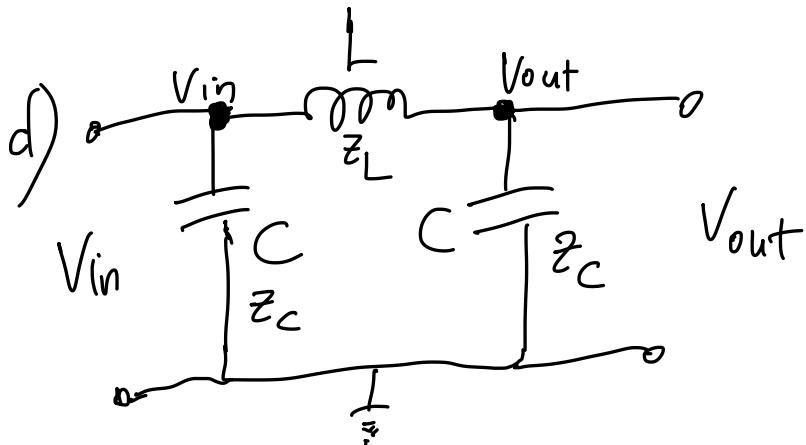$\Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 1 \Rightarrow$ this circuit is High-pass.



$$\left\{ \begin{array}{l} Z_L = j\omega L \\ Z_C = \frac{1}{j\omega C} \end{array} \right.$$

We have :

$$\frac{V_{out}}{V_{in}} = \frac{Z_C}{Z_C + Z_L} = \frac{1}{1 + \frac{Z_L}{Z_C}}$$

also :

$$\frac{Z_L}{Z_C} = \frac{j\omega L}{\frac{1}{j\omega C}} = j\omega L j\omega C = -\omega^2 LC$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 - \omega^2 LC}$$

When $\omega \rightarrow 0 \Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 1 \quad \} \Rightarrow$ this circuit

When $\omega \rightarrow \infty \Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 0 \quad \} \Rightarrow$ is low-pass

e)
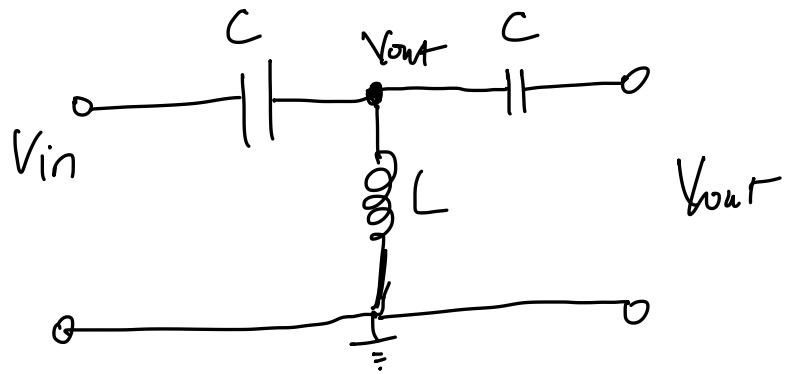
$$\text{Since } \frac{V_{out}}{V_{in}} = \frac{z_L}{z_C + z_L}$$




$$= \frac{1}{1 + \frac{z_C}{z_L}} \cdot \text{Also } \frac{z_C}{z_L} = \frac{\frac{1}{j\omega C}}{j\omega L} = \frac{1}{-\omega^2 CL}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 - \frac{1}{\omega^2 CL}}$$

When $\omega \rightarrow 0 \Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 0$

$\omega \rightarrow \infty \Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 1 \Rightarrow$ this circuit is high-pass

f)

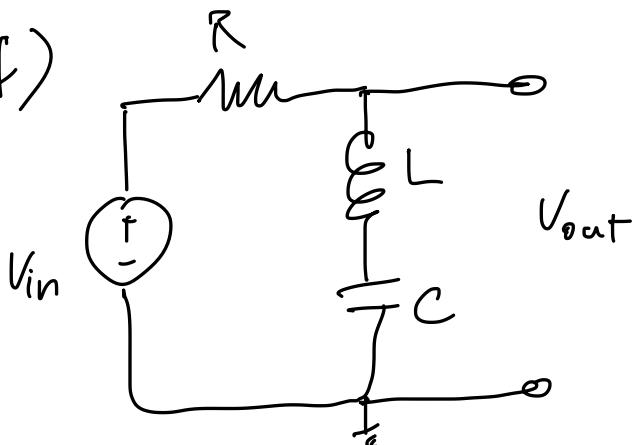

$$z_L + z_C = j\omega L - \frac{j}{\omega C}$$

$$= j \left(\omega L - \frac{1}{\omega C} \right)$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{z_L + z_C}{R + z_L + z_C} = \frac{1}{1 + \frac{R}{z_L + z_C}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{R}{j(\omega L - \frac{1}{\omega C})}}$$


When $\omega \rightarrow 0 \Rightarrow \begin{cases} \omega L \rightarrow 0 \\ \frac{1}{\omega C} \rightarrow \infty \end{cases} \Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 1$

When $\omega \rightarrow \infty \Rightarrow \begin{cases} \omega L \rightarrow 0 \\ \frac{1}{\omega C} \rightarrow 0 \end{cases} \Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 1$

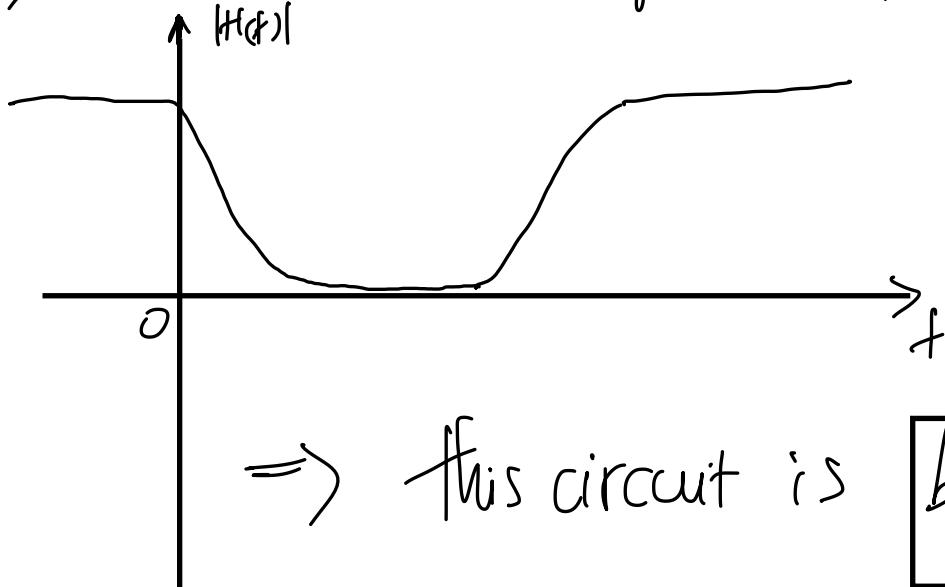\Rightarrow we can have the general diagram for this circuit:



\Rightarrow This circuit is band Stop.

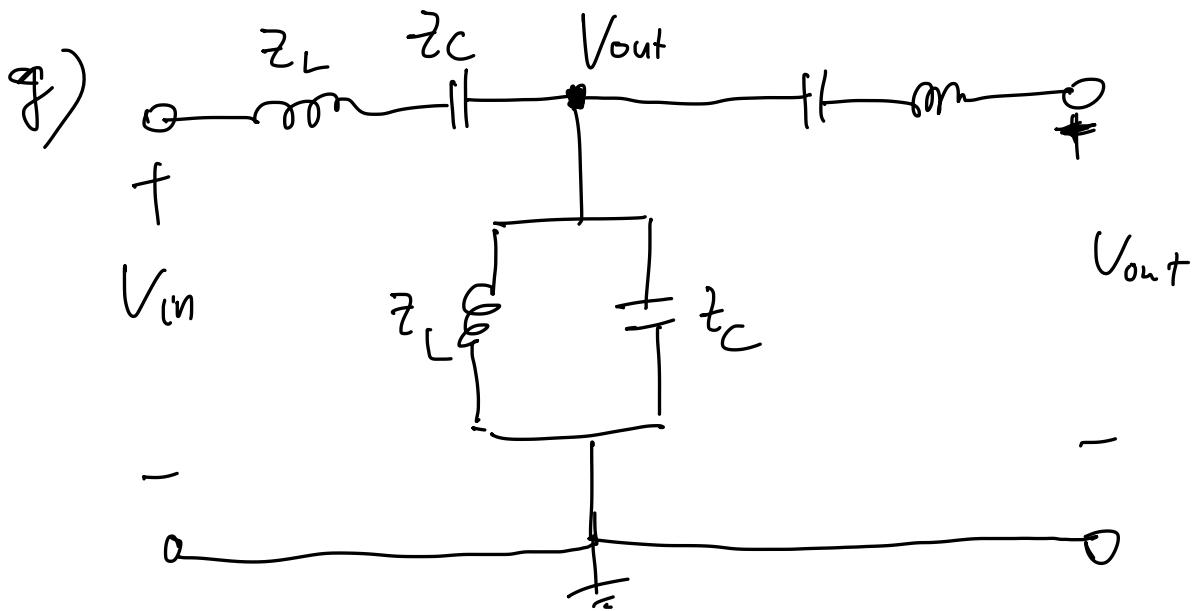

$$C \parallel L \Rightarrow z_{CL} = \frac{z_C \times z_L}{z_C + z_L}.$$

Also:

$$\begin{cases} z_C = \frac{1}{j\omega C} \\ z_L = j\omega L \end{cases} \Rightarrow \begin{cases} z_C \times z_L = \frac{j\omega L}{j\omega C} = \frac{L}{C} \\ z_C + z_L = \frac{1}{j\omega C} + j\omega L \\ = j\left(\omega L - \frac{1}{\omega C}\right) \end{cases}$$

Beside, we have: $\frac{V_{out}}{V_{in}} = \frac{z_{CL}}{z_L + z_C + z_{CL}}$

$$= \frac{1}{1 + \frac{z_L + z_C}{z_{CL}}} = \frac{1}{1 + \frac{(z_L + z_C)(z_C + z_L)}{z_C \times z_L}}$$

$$= \frac{1}{1 + \left(1 + \frac{z_L}{z_C}\right) \left(1 + \frac{z_C}{z_L}\right)}$$

$$\text{Since: } \frac{z_L}{z_C} = \frac{j\omega L}{\frac{1}{j\omega C}} = j\omega L j\omega C = -\omega^2 LC$$

$$\frac{z_C}{z_L} = \frac{\frac{1}{j\omega C}}{j\omega L} = \frac{1}{-\omega^2 CL}$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 + (1 - \omega^2 LC) \left(1 - \frac{1}{\omega^2 CL}\right)}$$

$$\text{So, checking: } \omega \rightarrow 0 \begin{cases} \omega^2 LC \rightarrow 0 \\ \frac{1}{\omega^2 LC} \rightarrow \infty \end{cases}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 0$$


$$\omega \rightarrow \infty \begin{cases} \omega^2 LC \rightarrow \infty \\ \frac{1}{\omega^2 LC} \rightarrow 0 \end{cases} \Rightarrow \frac{V_{out}}{V_{in}} \rightarrow 0$$

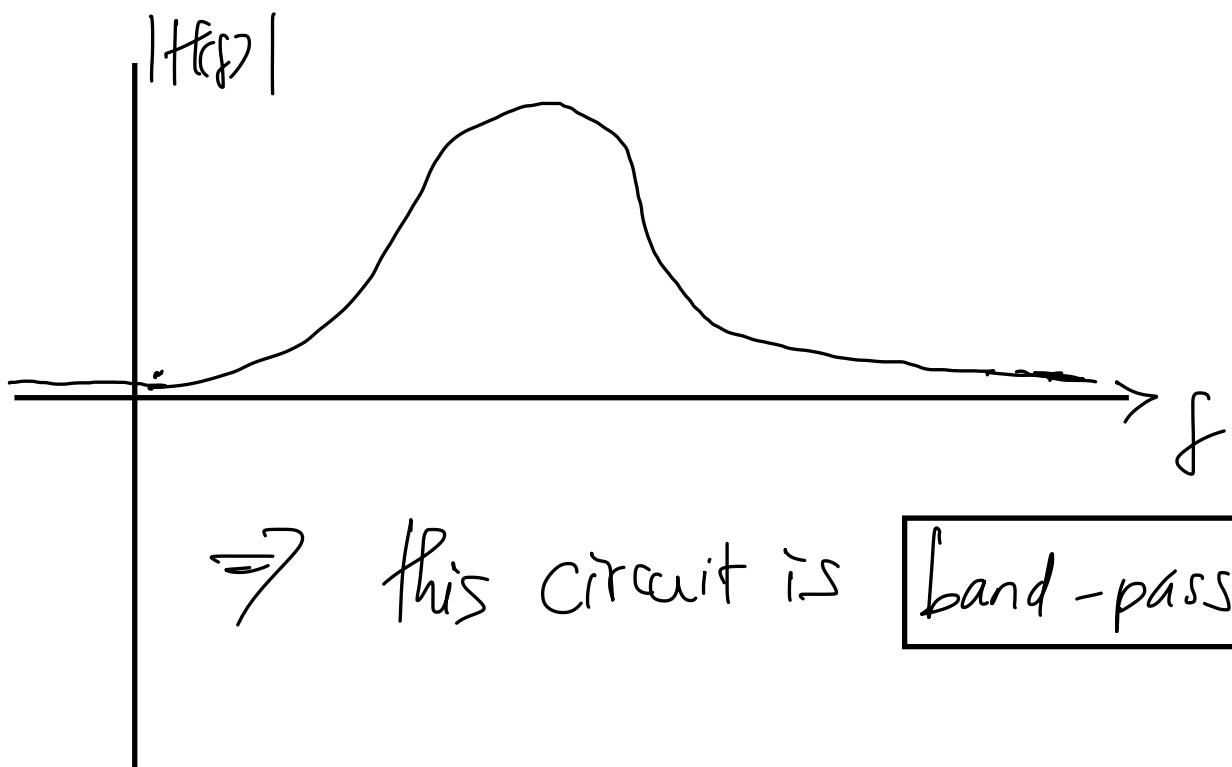\Rightarrow we can have the general diagram of this circuit:



\Rightarrow this circuit is band-pass

Problem 2:

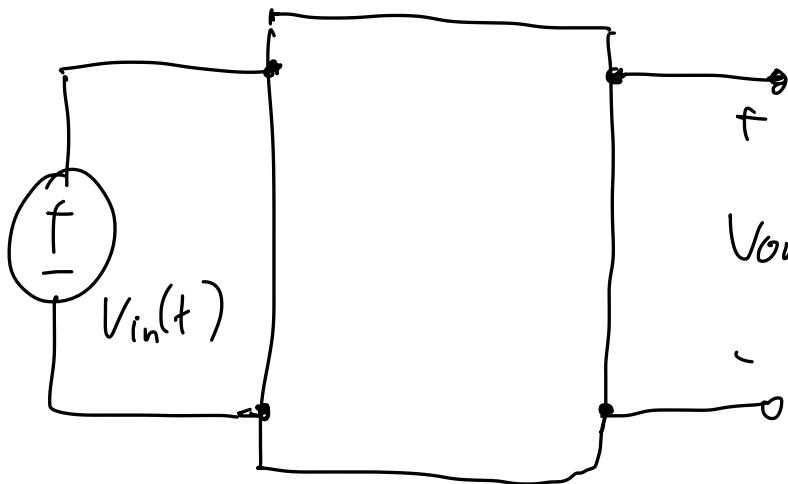

$$V_{out}(t) = \frac{dV_{in}(t)}{dt}$$

$$V_{in}(t) = V_{max} \cos(2\pi f t)$$

$$V_{out}(t) = \frac{dV_{in}(t)}{dt} = V_{max} [\cos(2\pi f t)]'$$

$$= -V_{max} \cdot 2\pi f \sin(2\pi f t)$$

$$\Rightarrow V_{out}(t) = -2\pi f V_{max} \sin(2\pi f t)$$

We have: $V_{in}(t) = V_{max} \cos(2\pi f t)$

$$\Rightarrow V_{in} = V_{max} \angle 0^\circ \quad (v)$$

$$V_{out}(t) = -2\pi f V_{max} \sin(2\pi f t)$$

$$= 2\pi f V_{max} \sin(-2\pi f t) = 2\pi f V_{max} \cos(2\pi f t + 90^\circ)$$


$$\Rightarrow V_{out} = 2\pi f V_{max} \angle 90^\circ \quad (V)$$

The transfer function:


$$H = \frac{V_{out}}{V_{in}} = \frac{2\pi f V_{max} \angle 90^\circ}{V_{max} \angle 0^\circ} = 2\pi f \angle 90^\circ$$

$$\Rightarrow H(f) = j2\pi f \quad . \quad \underline{\text{Plot:}}$$

Magnitude:

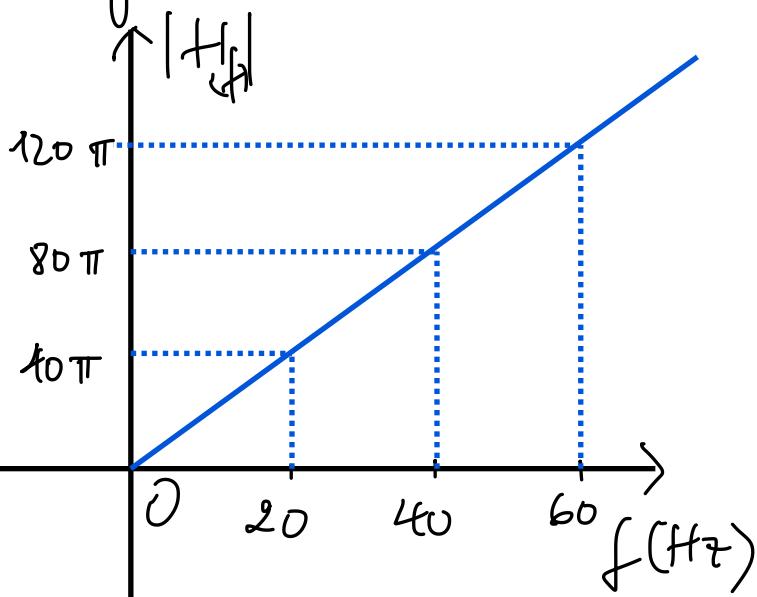

Phase:

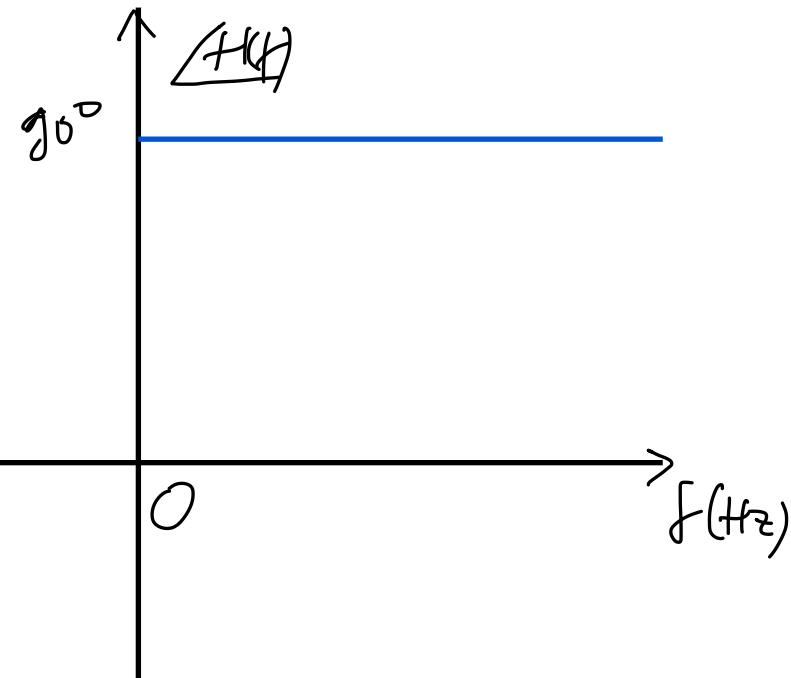


Problem 3:

$$V_{in}(+) = 5 \cos(500\pi t)$$

$$+ 5 \cos(1000\pi t)$$

$$+ 5 \cos(2000\pi t)$$

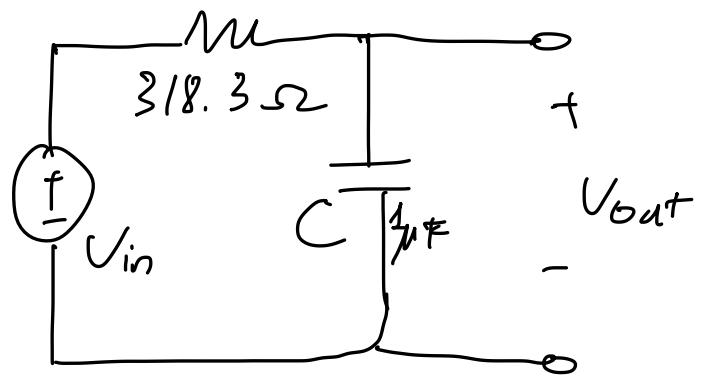

$$\begin{aligned} \text{We have: } \frac{V_{out}}{V_{in}} &= \frac{Z_C}{R + Z_C} = \frac{1}{1 + \frac{R}{Z_C}} \\ &= \frac{1}{1 + j\omega RC} \end{aligned}$$

$$\Rightarrow V_{out} = V_{in} \cdot \frac{1}{1 + j\omega RC}$$

$$\text{When } V_{in}(+) = 5 \cos(500\pi t) \Rightarrow \omega = 500\pi \text{ (rad/s)}$$

$$\Rightarrow j\omega RC = j \times 500\pi \times \frac{1000}{\pi} \times 10^{-6}$$

$$= 0.5j$$

$$\Rightarrow V_{out} = \frac{5 \cos(500\pi t)}{1 + 0.5j} = \frac{5 \angle 0^\circ}{1 + 0.5j}$$

$$= 4.472 \angle -26.565^\circ$$

$$\Rightarrow V_{\text{out}} = 4.472 \cos(500\pi t - 26.565^\circ) \quad (V) \quad (1)$$

⊕ When $V_{\text{in}}(t) = 5\cos(100\pi t) \Rightarrow \omega = 100\pi \text{ (rad/s)}$

$$\Rightarrow j\omega RC = j \times 100\pi \times \frac{100}{\pi} \times 10^{-6} = j$$

$$\Rightarrow V_{\text{out}} = \frac{5\cos(100\pi t)}{1+j} = \frac{5 \angle 0^\circ}{1+j} = 3.536 \angle -45^\circ$$

$$\Rightarrow V_{\text{out}}(t) = 3.536 \cos(100\pi t - 45^\circ) \quad (V) \quad (2)$$

⊕ When $V_{\text{in}}(t) = 5\cos(2000\pi t) \Rightarrow \omega = 2000\pi \text{ (rad/s)}$

$$\Rightarrow j\omega RC = j \times 2000\pi \times \frac{100}{\pi} \times 10^{-6} = 2j$$

$$\Rightarrow V_{\text{out}} = \frac{5\cos(2000\pi t)}{1+2j} = \frac{5 \angle 0^\circ}{1+2j}$$



$$= 2.236 \angle -63.435^\circ \quad (V) \quad (3)$$

$$\Rightarrow V_{\text{out}}(t) = 2.236 \cos(2000\pi t - 63.435^\circ) \quad (V) \quad (3)$$


From above analysis, we have:

$$V_{out}(t) = 4.472 \cos(500\pi t - 26.575^\circ)$$
$$+ 3.536 \cos(1000\pi t - 45^\circ)$$
$$+ 2.236 \cos(200\pi t - 63.435^\circ)$$

Problem 5:

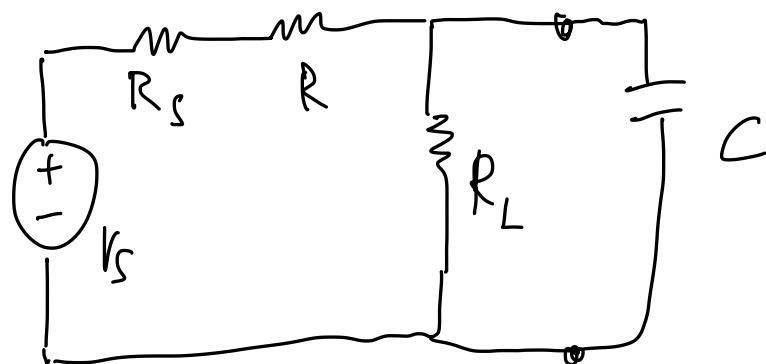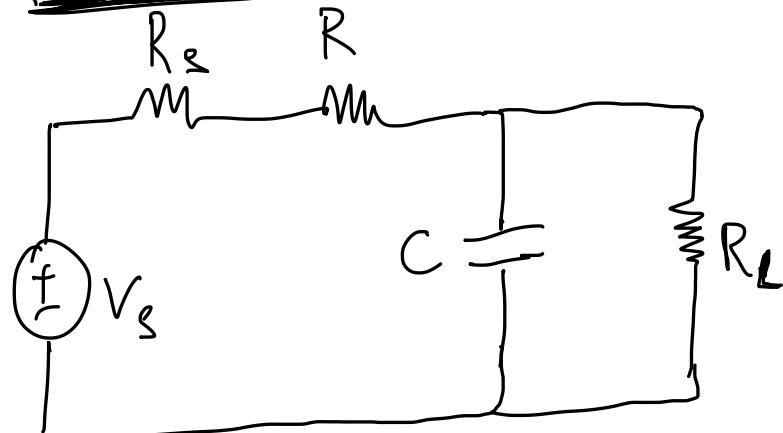


Need to find Thévenin equivalent for:

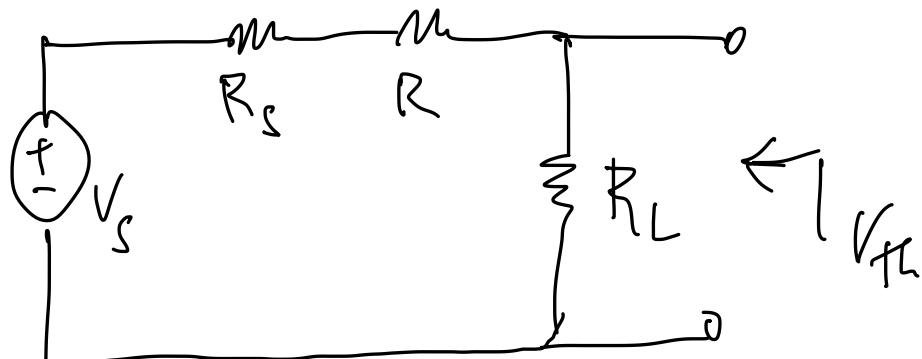

Using voltage divider, we have:

$$V_{th} = \frac{R_L}{R_s + R + R_L} V_s .$$

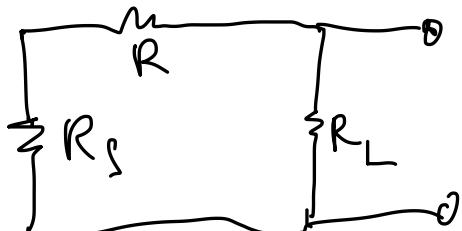Now, find r_{th} , short the voltage source:




Since $R_L \parallel (R \text{ series } R_s)$

$$\Rightarrow R_{th} = \frac{R_L \times (R + R_s)}{R_L + R + R_s}$$

$$\Rightarrow R_{th} = \frac{R_L(R + R_S)}{R_L + R + R_S}$$

\Rightarrow We have:-

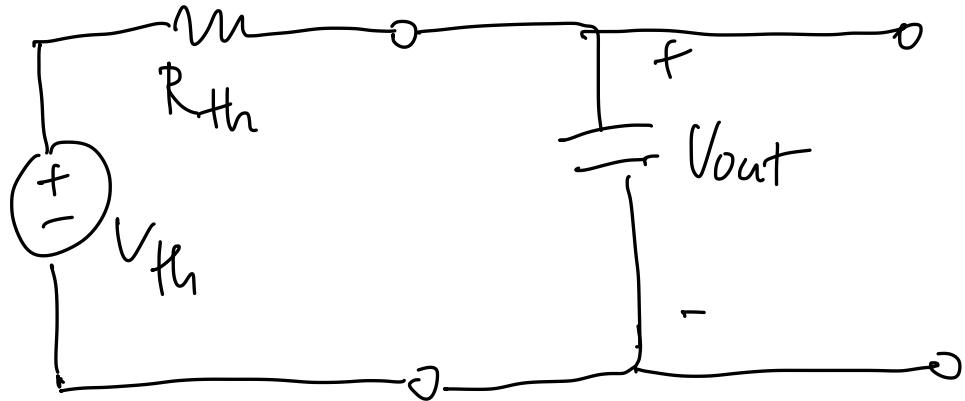

$$Z_C = \frac{1}{j\omega C}$$

$$\Rightarrow H(j) = \frac{V_{out}}{V_{th}} = \frac{Z_C}{R_{th} + Z_C} = \frac{1}{1 + \frac{R_{th}}{Z_C}}$$

$$\text{Since } V_{th} = \frac{R_L}{R_S + R + R_L} V_s$$

$$\Rightarrow \frac{V_{out}}{V_s} = \frac{1}{1 + \frac{R_{th}}{Z_C}} \cdot \frac{R_L}{R_S + R + R_L} = \frac{R_L}{R_S + R + R_L} \cdot \frac{1}{1 + \frac{R_{th}}{Z_C}}$$

$$= \frac{R_L}{R_S + R + R_L} \cdot \frac{1}{1 + j \frac{R_{th}}{Z_C} \omega C}$$

$$= \frac{R_L}{R_S + R + R_L} \cdot \frac{1}{1 + j \frac{f}{\frac{1}{2\pi R_{th} C}}} \quad \text{With } f_B = \frac{1}{2\pi R_{th} C}$$

$$\Rightarrow H(f) = \frac{R_L}{R_S + R + R_L} \cdot \frac{1}{1 + j \left(\frac{f}{f_B} \right)}$$

With $f_B = \frac{1}{2\pi R_{th} C}$ & $R_{th} = \frac{R_L(R + R_S)}{R_L + R + R_S}$

(G.E.D)

$$b) C = 0.2 \mu F, R_S = 2 k\Omega, R = 47 k\Omega$$

$$R_L = 1 k\Omega$$

$$\Rightarrow R_{th} = \frac{R_L(R + R_S)}{R_L + R + R_S} = \frac{1(2 + 47)}{1 + 2 + 47} = \frac{49}{50} \text{ (k}\Omega\text{)}$$


$$= 0.98 (\text{k}\Omega)$$

$$\Rightarrow f_B = \frac{1}{2\pi \times 0.98 \times 1000 \times 0.2 \times 10^{-6}} = 812 \text{ Hz}$$

Also: $\frac{R_L}{R_S + R + R_L} = \frac{1}{1+47+2} = \frac{1}{50}$


$$\Rightarrow H(j) = \frac{1}{50} \cdot \frac{1}{1 + j(\frac{f}{f_{812}})} = \frac{0.02}{1 + j(\frac{f}{f_{812}})}$$

$$\Rightarrow |H(j)| = \frac{0.02}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}$$

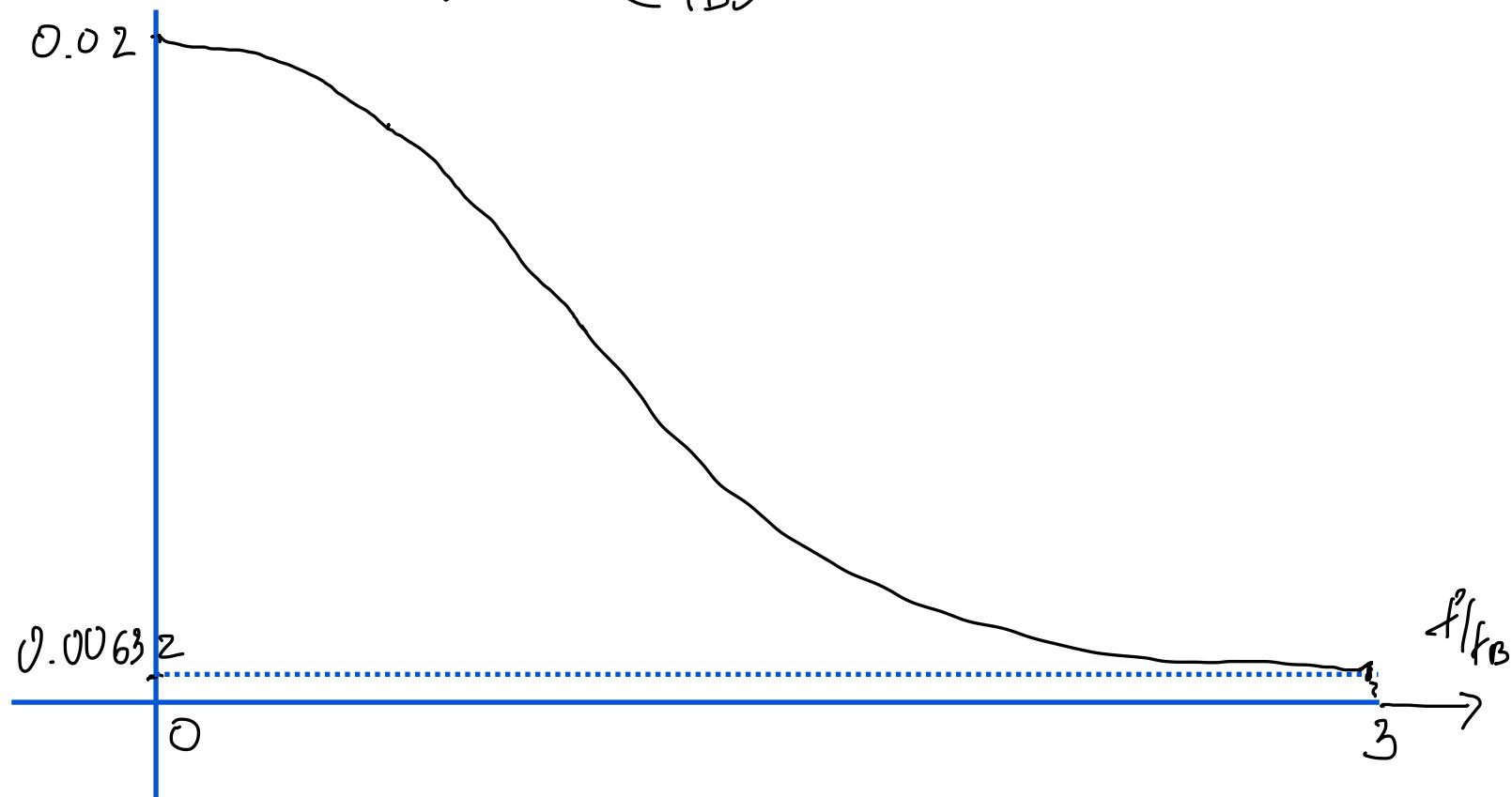


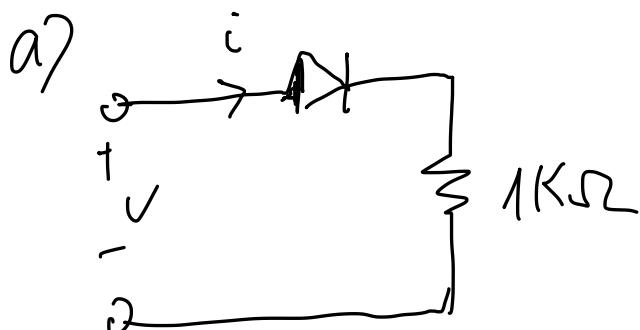Problem 10: Sketch i vs v .

Assume diode ideal & $\vartheta: -10 \rightarrow 10V$




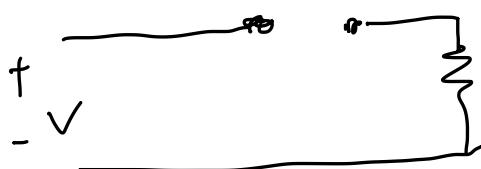⊕ When $V: -10 \rightarrow 0V$, diode is off, then we have :



$$\Rightarrow i = 0$$


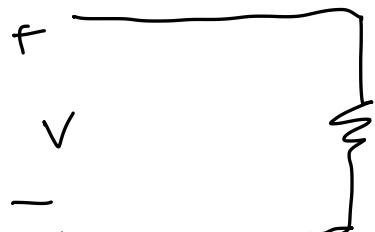
⊕ When $V: 0 \rightarrow 10V$, diode is on, then we have :



$$\Rightarrow i = \frac{v}{R} = \frac{v}{1000\Omega} \quad (\text{A})$$


Then, we have a diagram:

$V(V)$	≤ 0	2	4	6	8	10
$i(\text{mA})$	0	2	4	6	8	10

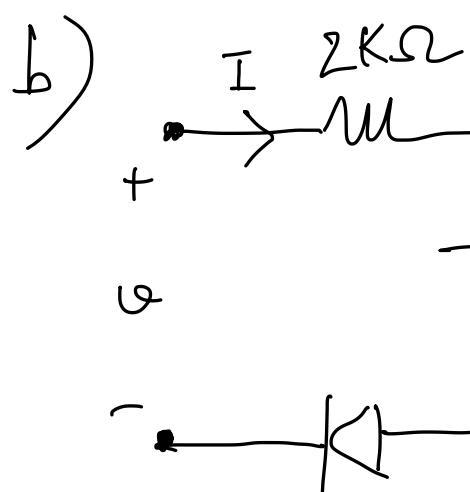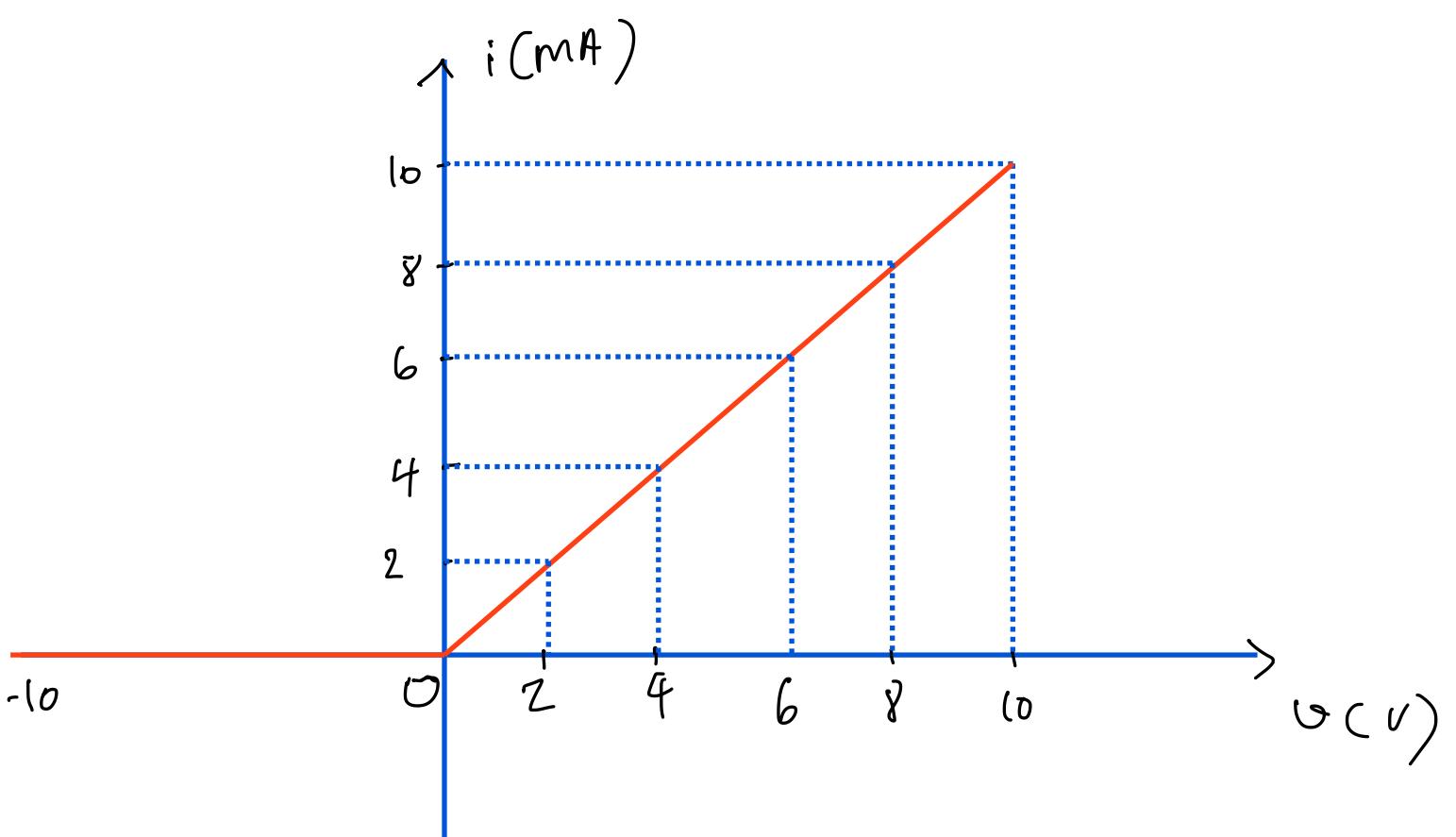

④ When the voltage u : $-10 \rightarrow 5V$
 the current $i < 0$
 \Rightarrow diode is off, then




We have:

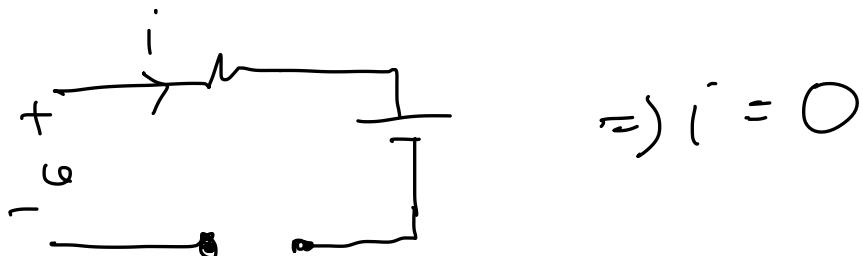


④ When voltage u : $5 \rightarrow 10V$, We have
 the diode is on .

$$-V + iR + \sqrt{V} = 0$$
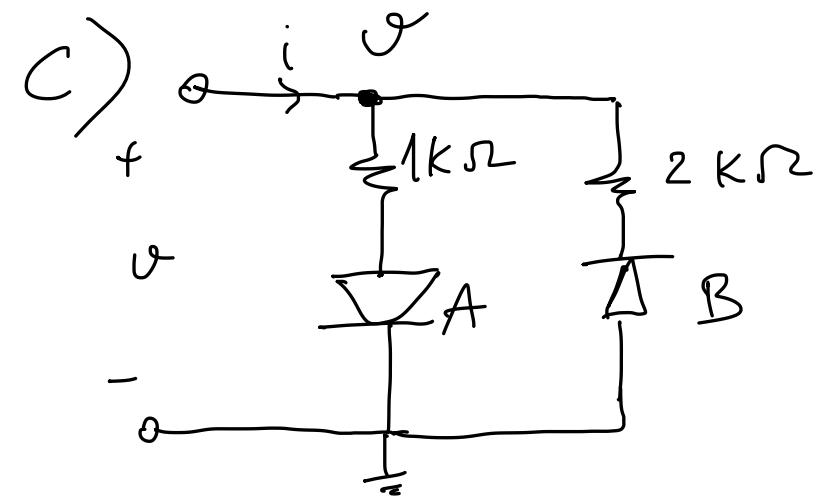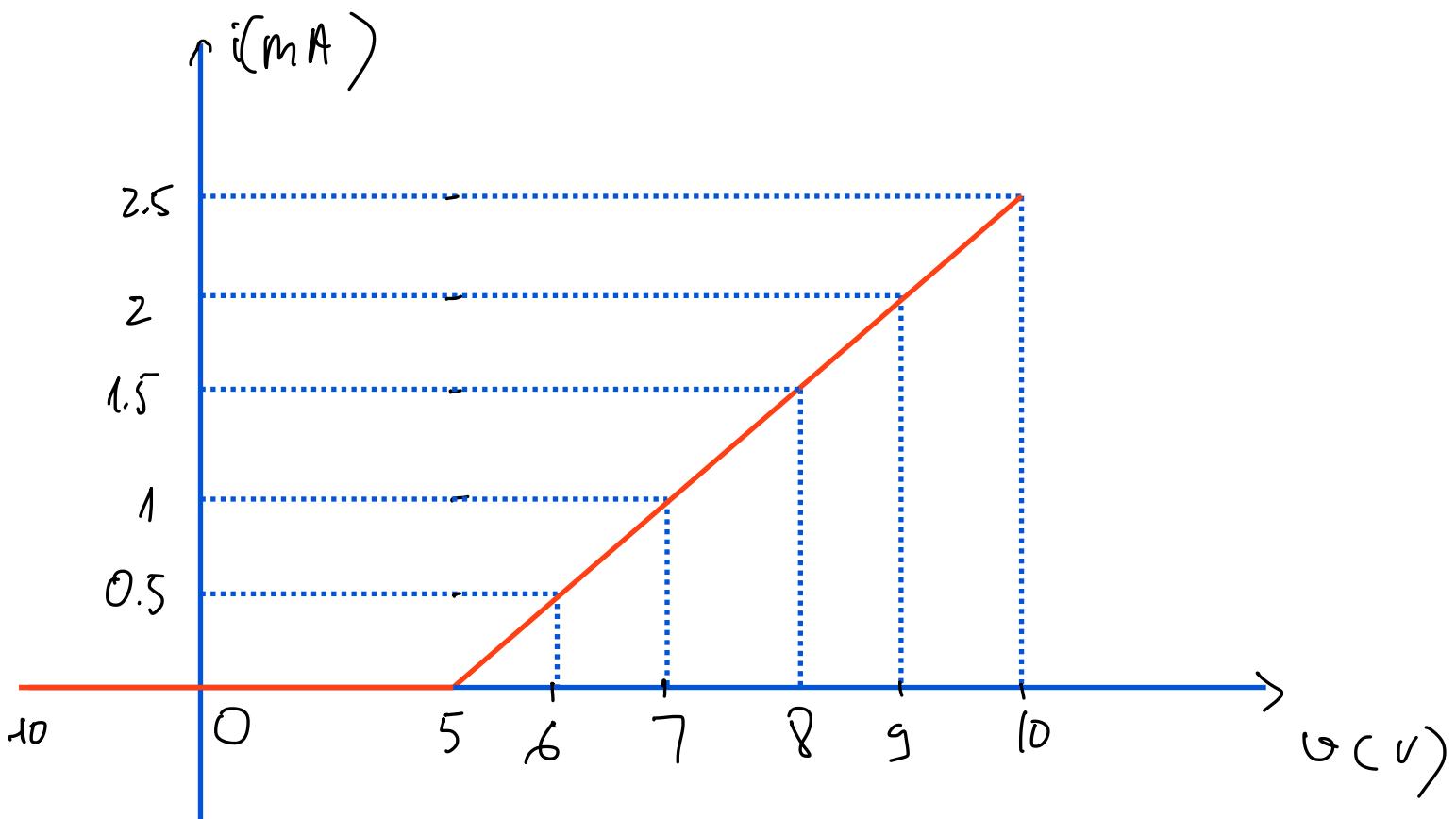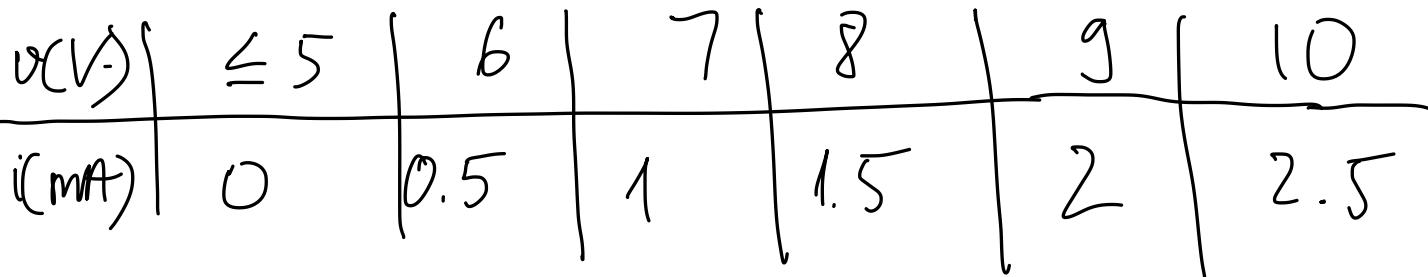
$$\Rightarrow i = \frac{V - 5}{2k\Omega} \geq 0 \text{ (mA)}$$



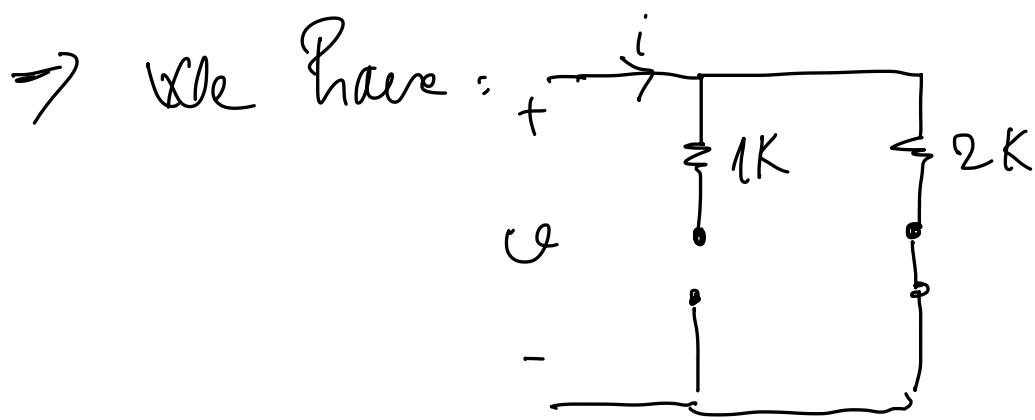When $v : -10 \rightarrow 0$
 \Rightarrow diode A is off
 diode B is on




$$\Rightarrow i = \frac{v}{2k} \text{ (mA)}$$

When voltage $v: 0 \rightarrow 10V$.



the diode A is on while diode B is off.

We have:

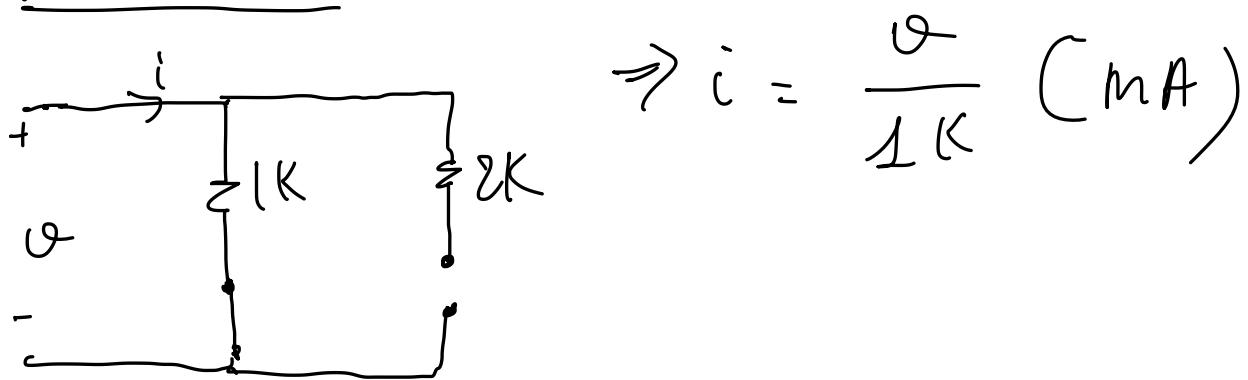


$v(V)$	-10	-8	-6	-4	-2	0
$i(mA)$	-5	-4	-3	-2	-1	0

$v(V)$	0	2	4	6	8	10
$i(mA)$	0	2	4	6	8	10

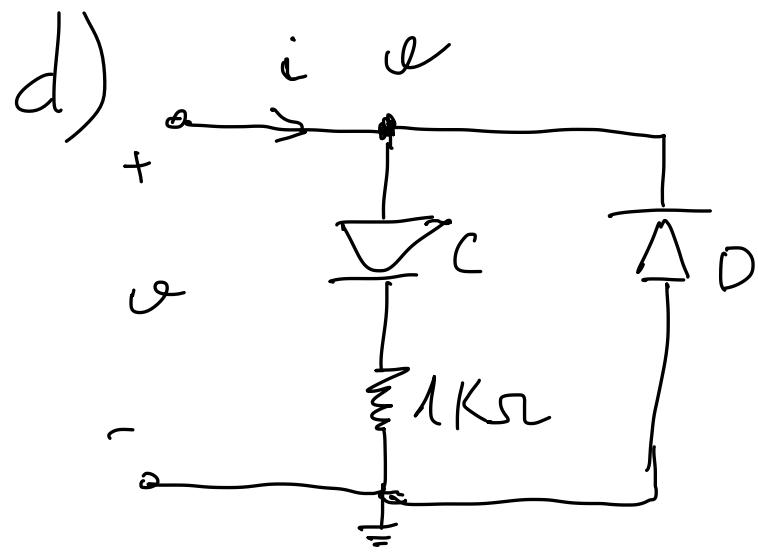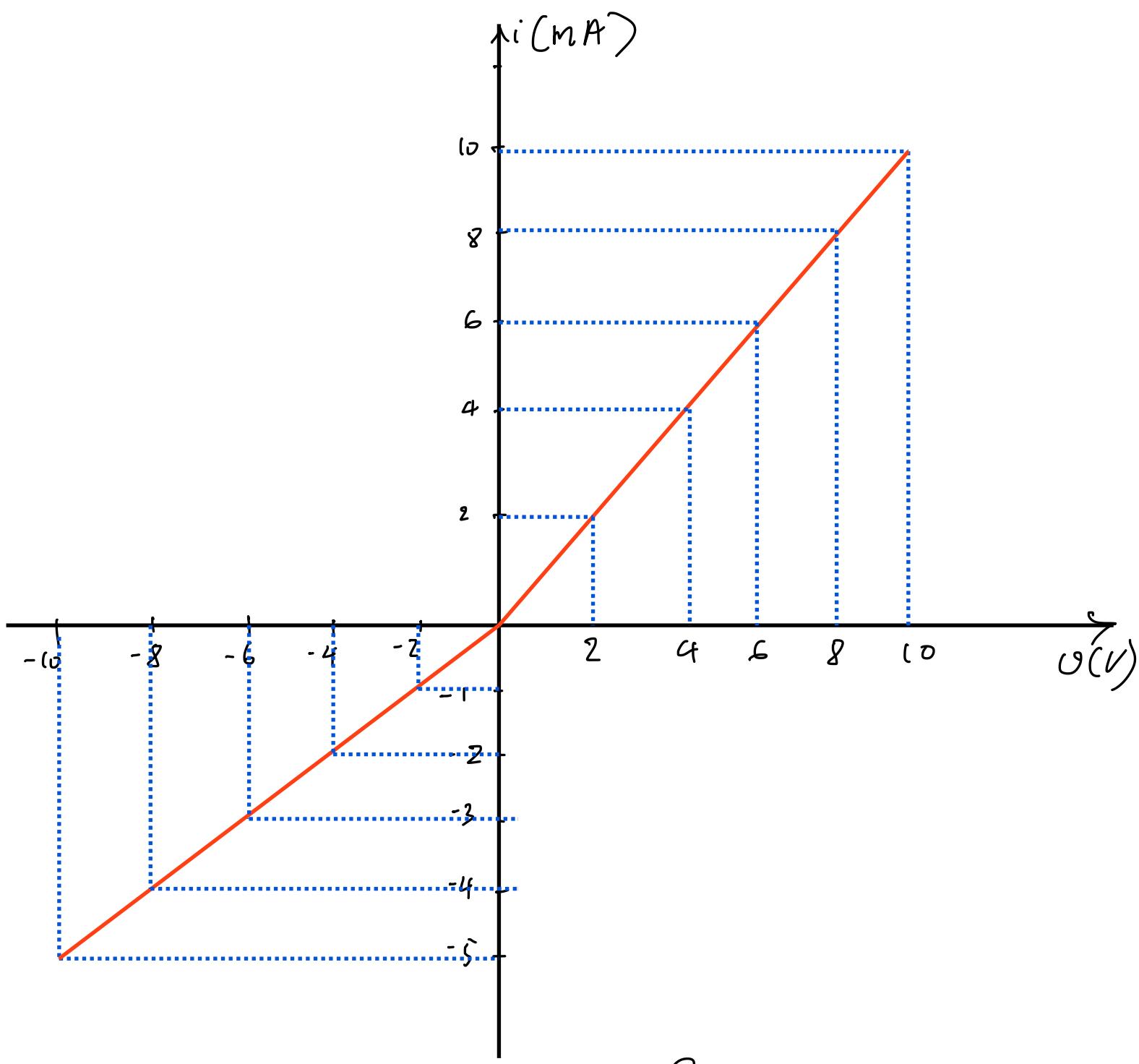


④ When voltage e :

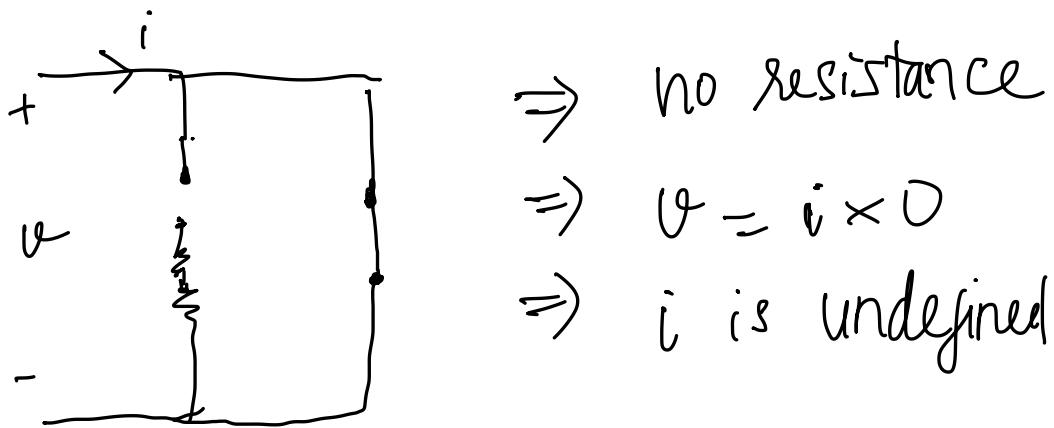$-10 \rightarrow 0 \text{ V}$, the diode
C is off & D is on
so we have:




④ When voltage $v : 0 \rightarrow 10 \text{ V}$, we have

diode C is on & D is off

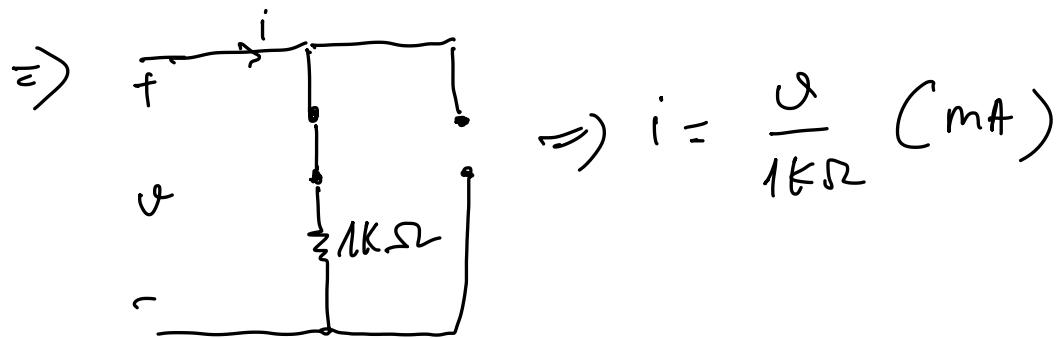

$v(\text{V})$	≤ 0	2	4	6	8	10
$i(\text{mA})$	undefined	2	4	6	8	10

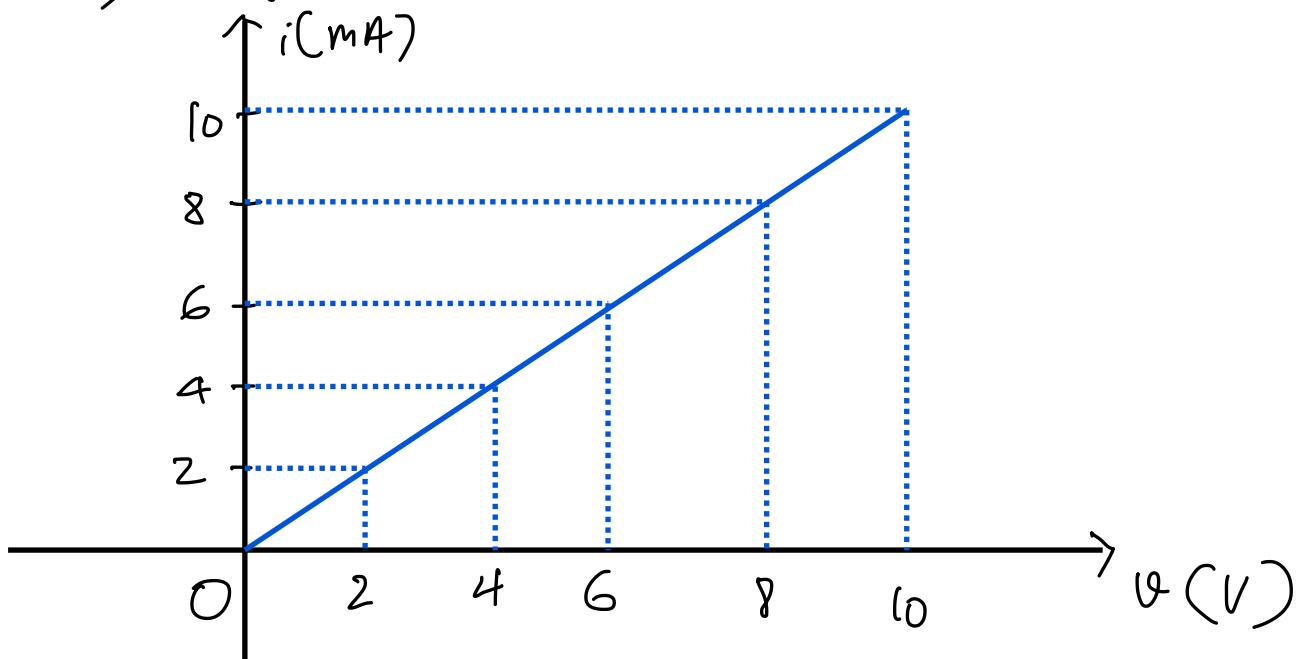

Problem 13:

a) Design a Half-Wave rectifier.

+ Average voltage gV with a peak-to-peak ripple at $2V$ to a load.

+ Current load 100mA

+ ideal diode & 60Hz, ac voltage

$$\Rightarrow V_L = gV, \quad V_R = 2V, \quad I_L = 100\text{mA} = 0.1\text{A}$$

$$f = 60\text{Hz} \Rightarrow T = \frac{1}{f} = \frac{1}{60} \text{ (s)}$$

$$\Rightarrow C = \frac{I_L T}{V_R} = \frac{0.1 \times 1/60}{2V} = \frac{0.1}{120} \text{ (F)}$$
$$= 833.33(\mu\text{F})$$


$$\text{And } \omega = 2\pi f = 120\pi$$

$$\text{Since } V_L = V_m - \frac{V_R}{2} \Rightarrow V_m = V_L + \frac{V_R}{2} = g + \frac{2}{2} = 10V$$

$$\Rightarrow v_S(t) = 10 \sin(120\pi t)$$

$$\text{Also } V_L = I_L R_L \Rightarrow R_L = \frac{V_L}{I_L} = \frac{9V}{0.1A} = 90\Omega$$

→ the fully circuit:

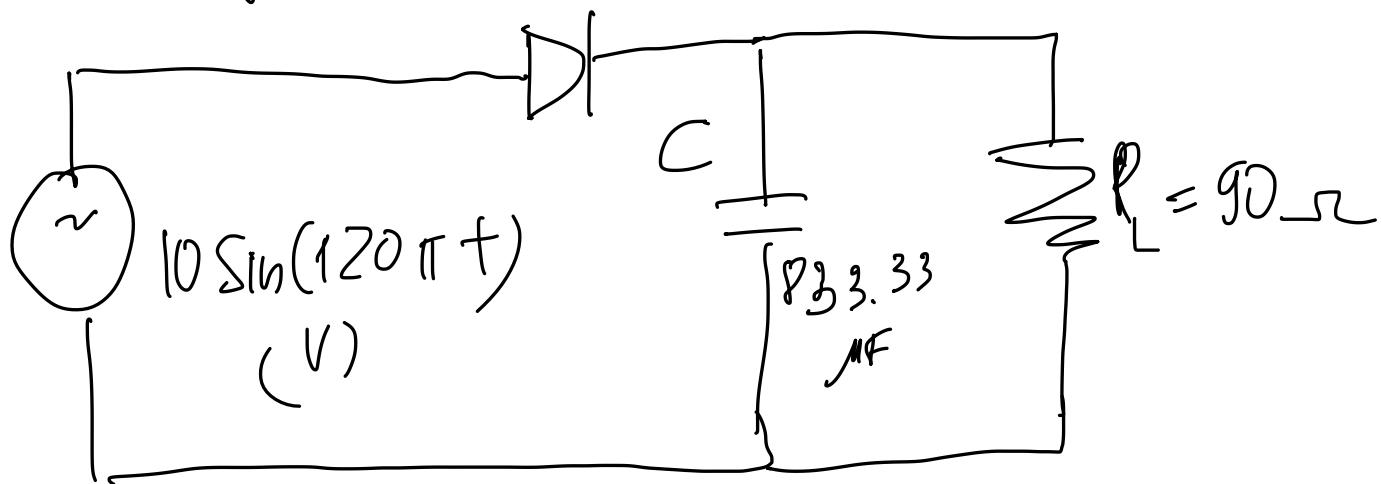

b) Repeated With full-Wave Bridge Rectifier.

We also have $V_L = 9V$, $V_R = 2V$, $I_L = 100mA$
 $f = 60Hz$, $\omega = 120\pi$


$$V_m = V_L + \frac{V_R}{2} = 9 + \frac{2}{2} = 10V$$

$$\text{But for } C, \text{ we have: } C = \frac{I_L T}{2 V_R} = \frac{0.1 \times 1/60}{2 \times 2}$$

$$\Rightarrow C = \frac{0.1}{240} = 416.67(\mu F)$$

$$R_L = \frac{V_L}{I_L} = \frac{9}{0.1 A} = 90 \Omega$$

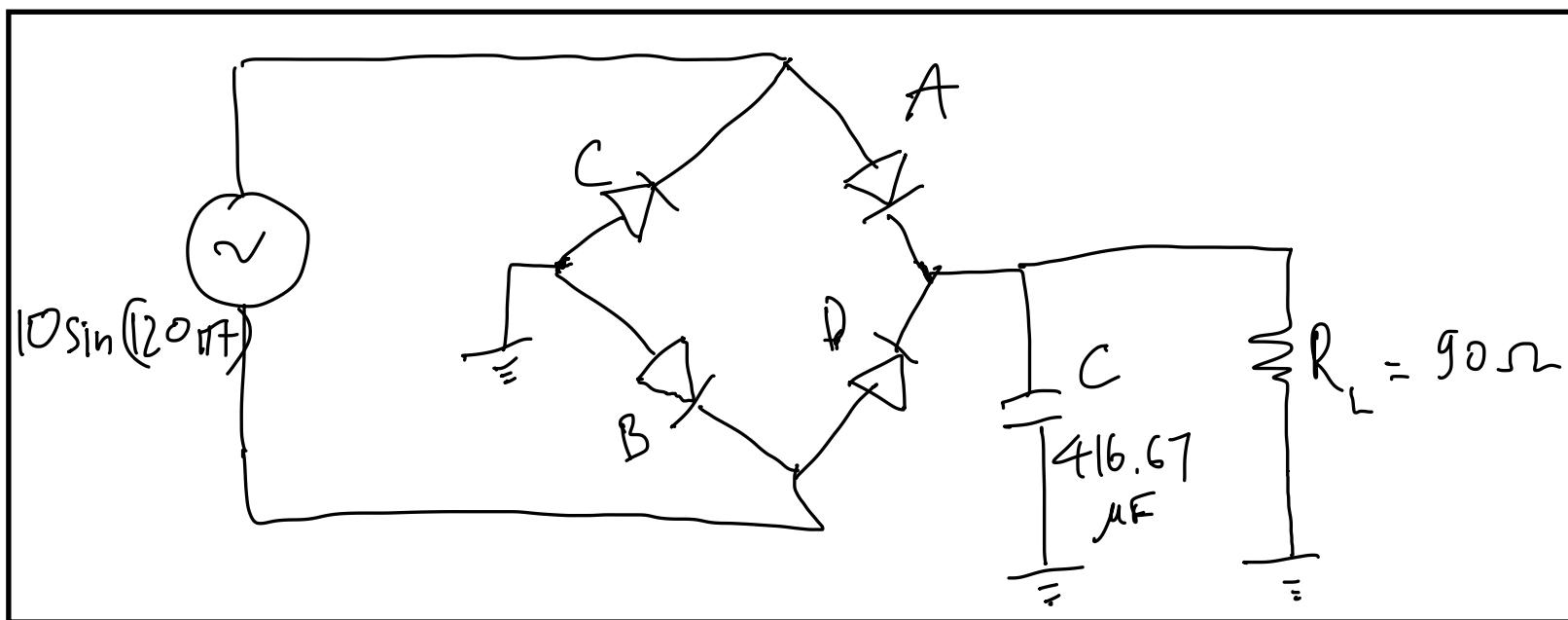So, we have the circuit diagram for full wave bridge rectifier:



c) Repeat with two diode & out of phase voltage to form a full Wave Rectifier.


Given: $V_L = 9 V$, $i_L = 100 mA$, $f = 60 Hz$

$$\Rightarrow \omega = 120\pi, V_d = 2 V, V_m = 10 V$$

$$C = \frac{I_L T}{V_d} = \frac{0.1 \times 1/60}{2 V} \Rightarrow C = 833.33 \mu F$$

$$R = \frac{V_L}{I_L} = \frac{9V}{0.1A} = 90\Omega$$

We have :

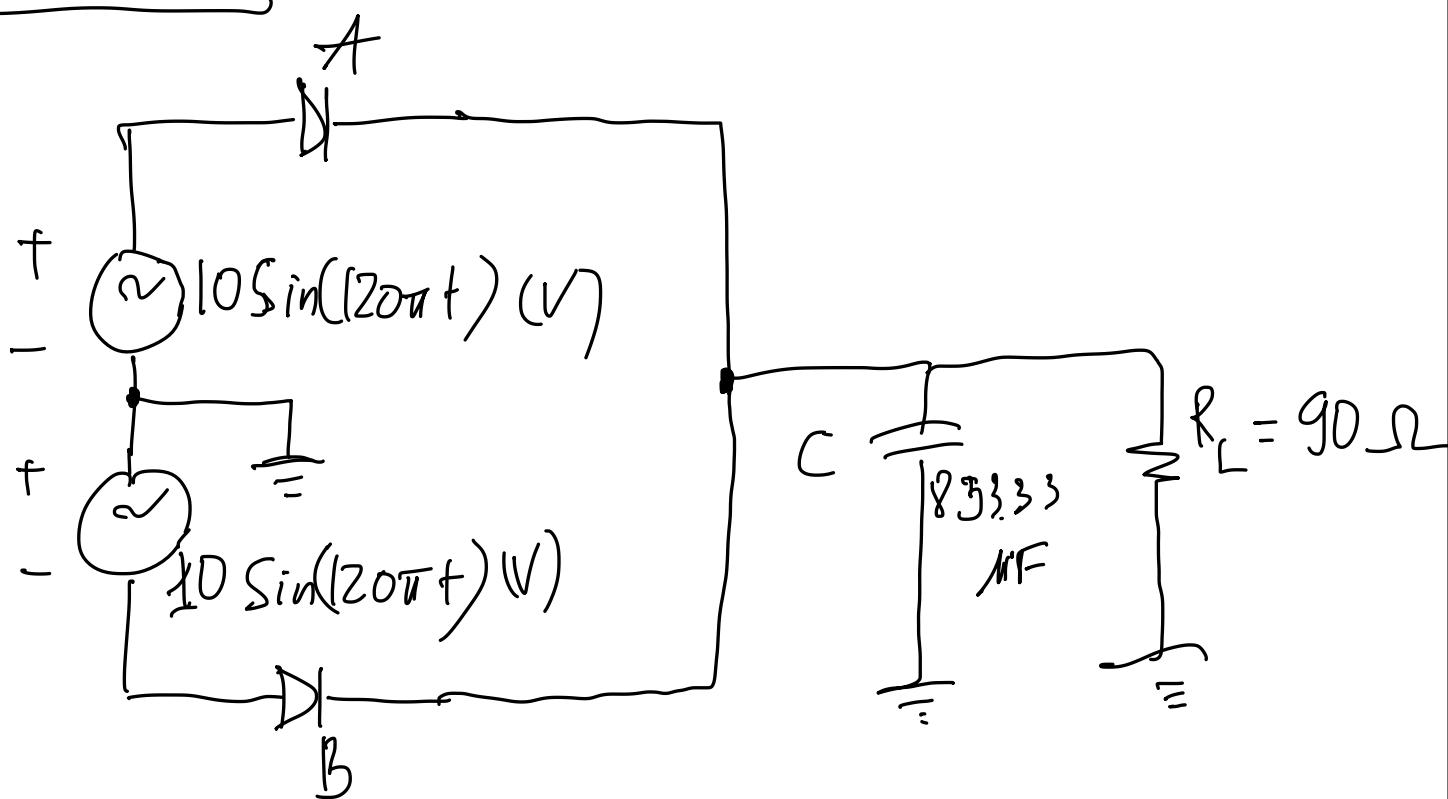

d) Repeat with assuming that the diodes have forward drop of 0.8V. (design a half wave rectifier).


As the a, we have already had :

$$V_L = 9V, V_f = 2V, \omega = 20\pi, C = 853.33 \mu F$$

$$R = 90 \Omega, \text{ and } V_m = 10V$$


Since in this case, diode is not ideal, & has forward drop of $0.8V \Rightarrow V_m = 10 + 0.8 = 10.8$ (V)

\Rightarrow We have a design:

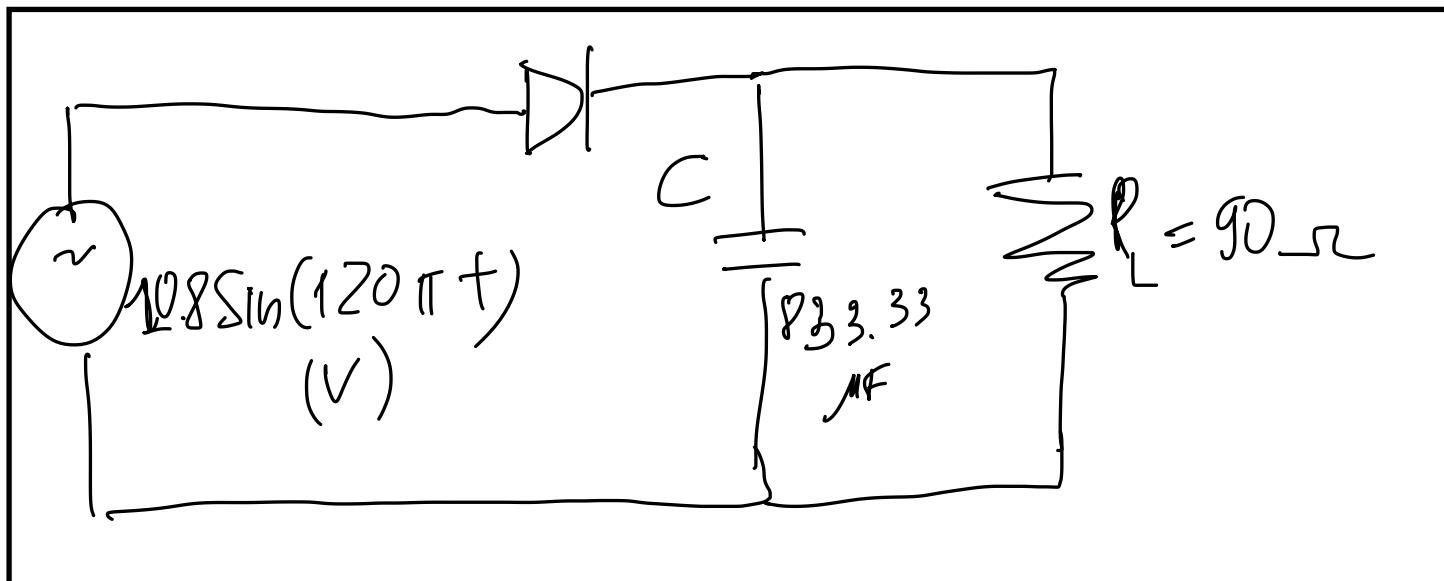


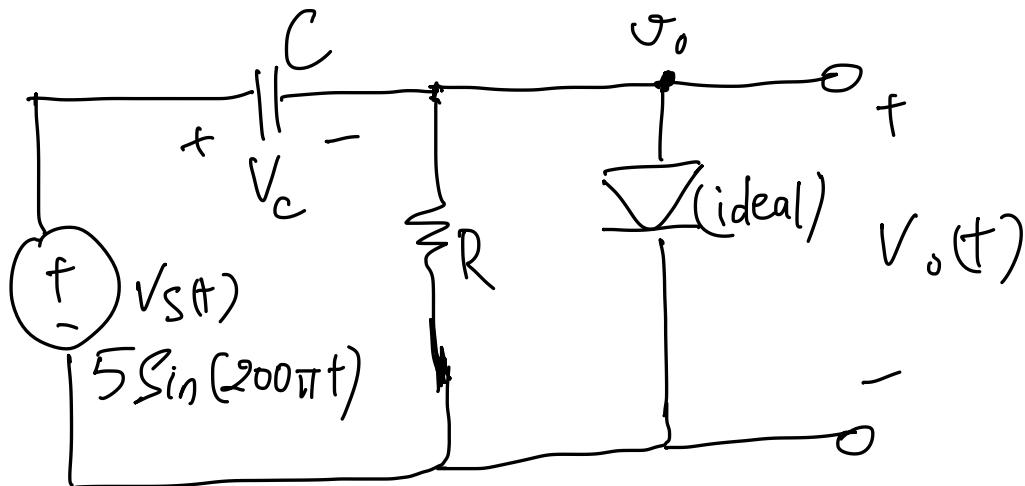Problem 14:

Given: the RC is very long compared with the period of input, diode is ideal.



* We have the wave form for V_{in} :

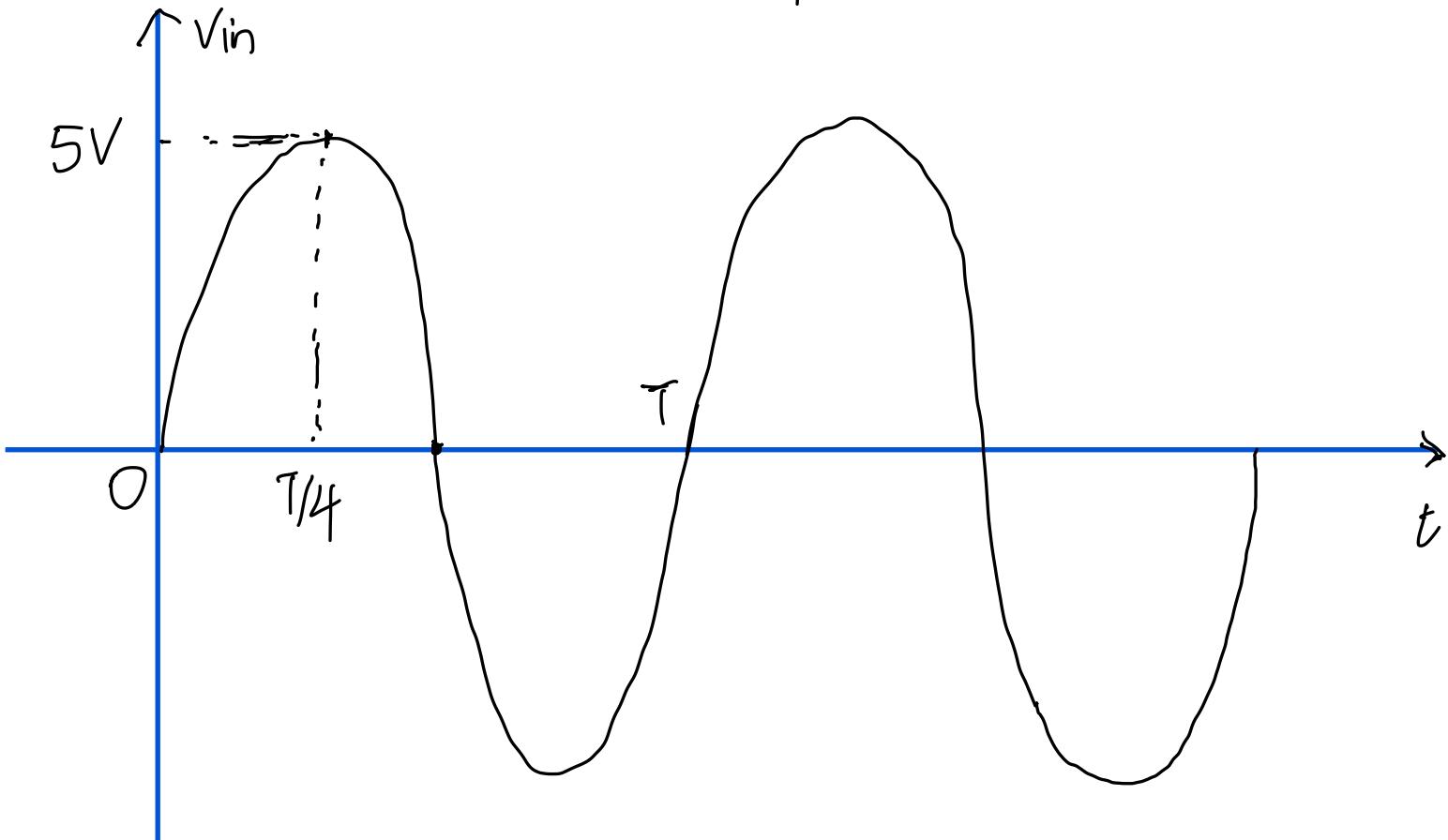

When $t : 0 \rightarrow T/4$, assume the capacitor has already in steady state, the $V_{in} \leq V_c$

Due to $RC \gg T \Rightarrow$ the capacitor will not discharged quickly, in this time $V_c = V_m \Rightarrow V_{out} = V_{in} - V_m$ and the diode will never go into forward.


at $t = T/4$, $V_{in} = V_{max} \Rightarrow V_o = 0V$

$t = 0 \Rightarrow V_{in} = 0 \Rightarrow V_o = -V_m$.

When $t : T/4 \rightarrow T$, $V_{out} = -V_m + V_{in}$

$$\Rightarrow V_{out} = -5 + 5\sin(200\pi t),$$

Finally, we have the negative clamped diagram:

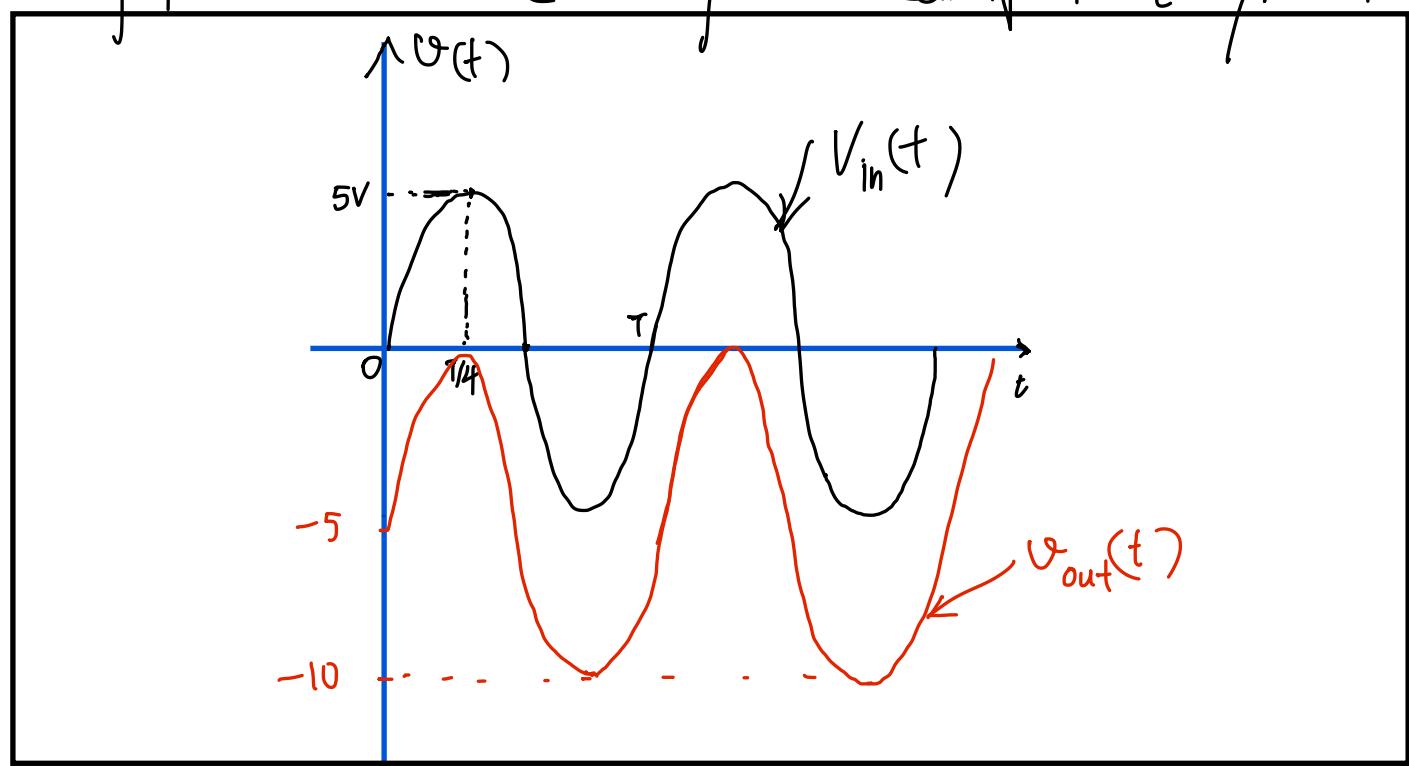


Problem 16: All device are NMOS mosfet. & $\theta_{th} = 0.7V$

So we have:

⊕ cut off region: $V_{G,S} \leq V_{th}$

⊕ Triode \Leftrightarrow resistor: $\begin{cases} V_{G,S} \geq V_{th} \\ 0 \leq V_{D,S} \leq V_{G,S} - V_{th} \end{cases}$

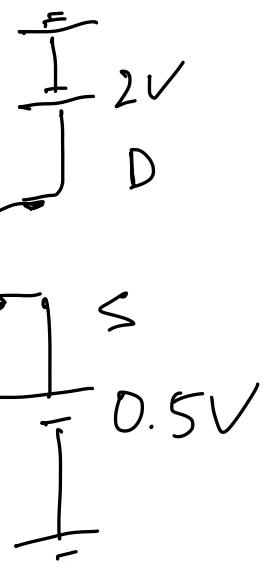⊕ saturation: $\begin{cases} V_{G,S} \geq V_{th} \\ V_{D,S} \geq V_{G,S} - V_{th} \end{cases}$




Since $V_{G,S} = 0.5 - 0.5 = 0(V) < V_{th}$

a)

\Rightarrow Cut off region

b)

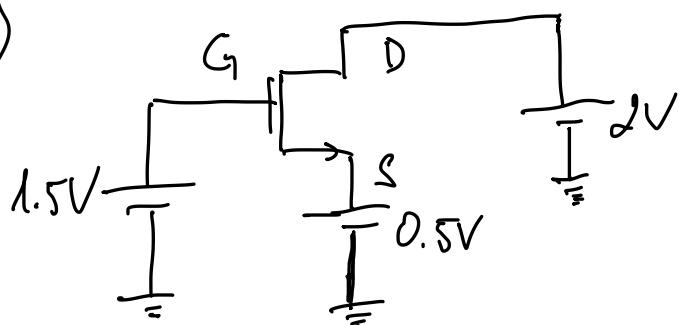


$$\begin{aligned} V_{G,S} &= 1.5 - 0.5 = 1V \\ &\geq V_{th} = 0.7V \end{aligned}$$

$$\begin{aligned} V_{D,S} &= 2 - 0.5 = 1.5V \\ &> V_{G,S} - V_{th} = 1 - 0.7 = 0.3V \end{aligned}$$


$$\Rightarrow \begin{cases} V_{G,S} \geq V_{th} \\ V_{D,S} \geq V_{G,S} - V_{th} \end{cases} \Rightarrow$$

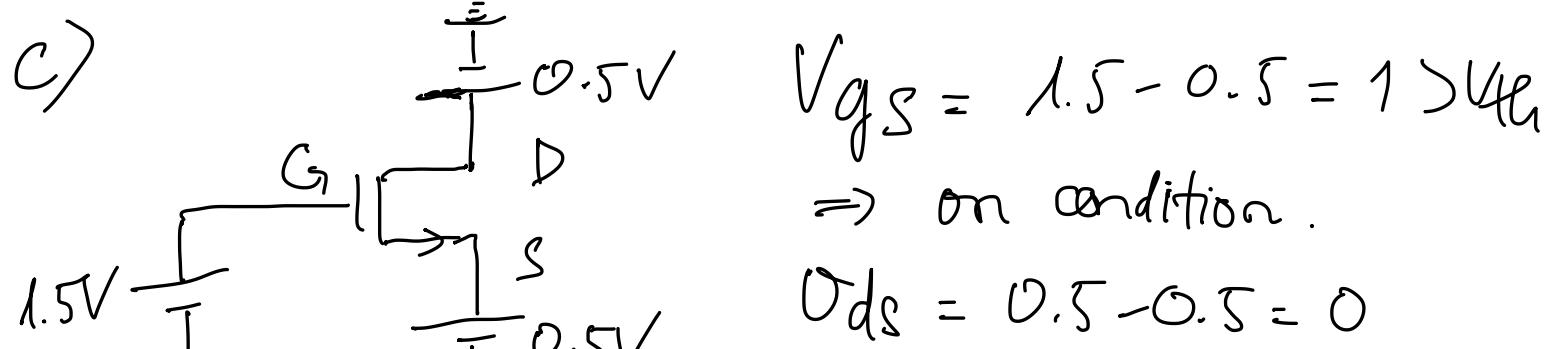Saturation region or
neither off nor resistor




Since $I_{DS} = 0 < I_{GS} - V_{th}$
 $= 1 - 0.7 = 0.3$

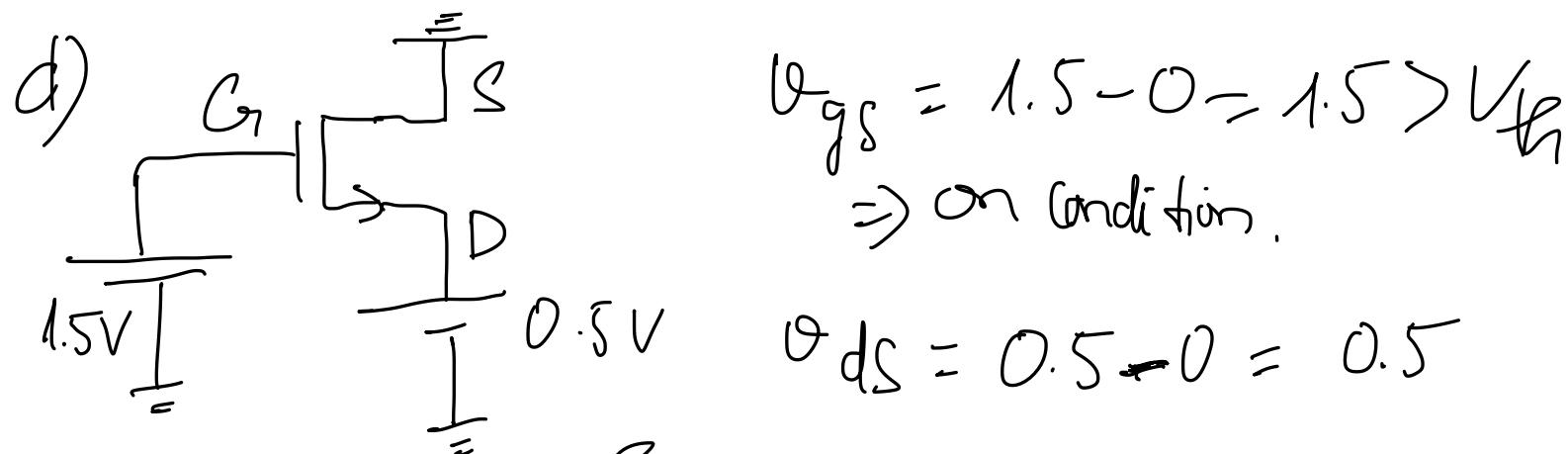$\Rightarrow I_{DS} < I_{GS} - V_{th} \Rightarrow$ act as resistor




Since $I_{DS} = 0.5 < I_{GS} - V_{th}$
 $= 1.5 - 0.7 = 0.8$

\Rightarrow act as resistor

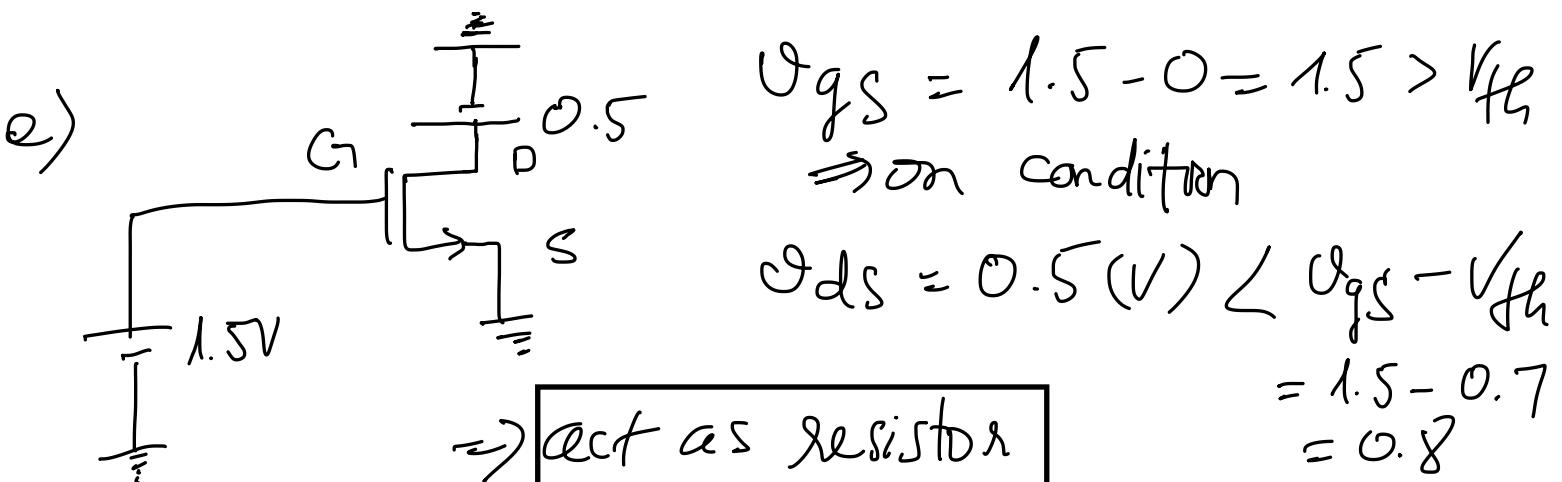

\Rightarrow act as resistor

f)

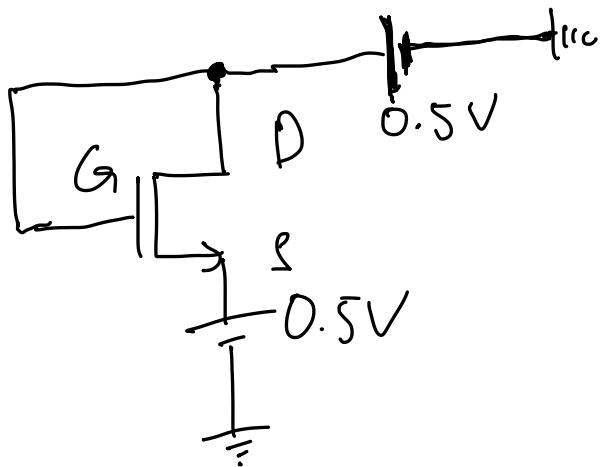


$$V_{GS} = 0.5 - 0.5 = 0$$

$\swarrow V_{th} = 0.7V$

⇒ Cut off region

g)

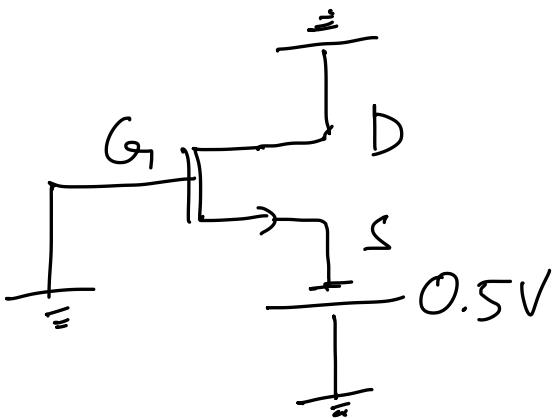


$$V_{GS} = 0 - (-0.5) = 0.5(V)$$

$\swarrow V_{th} = 0.7V$

⇒ Cut off region

h)

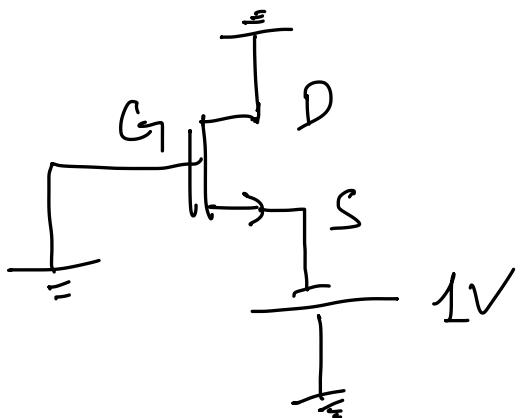

$$V_{GS} = 0 - (-1) = 1(V)$$


$\rightarrow V_{th} = 0.7(V)$

⇒ on condition.

$$V_{DS} = 0 - (-1) = 1V$$

$$\rightarrow V_{GS} - V_{th} = 1 - 0.7 = 0.3V$$

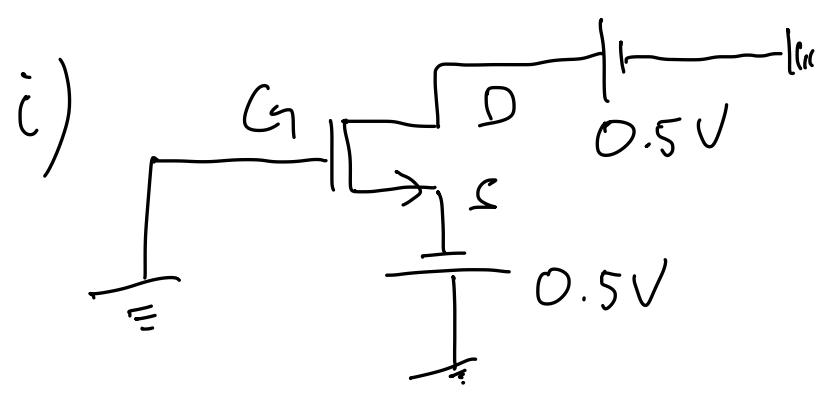
⇒ in saturation region
or neither cut off nor resistor




$$\begin{aligned}
 V_{GS} &= 0 - (-0.5) \\
 &= 0.5 < 0.7 \text{ V} \\
 &= V_{th}
 \end{aligned}$$

\Rightarrow off region

Problem (9)

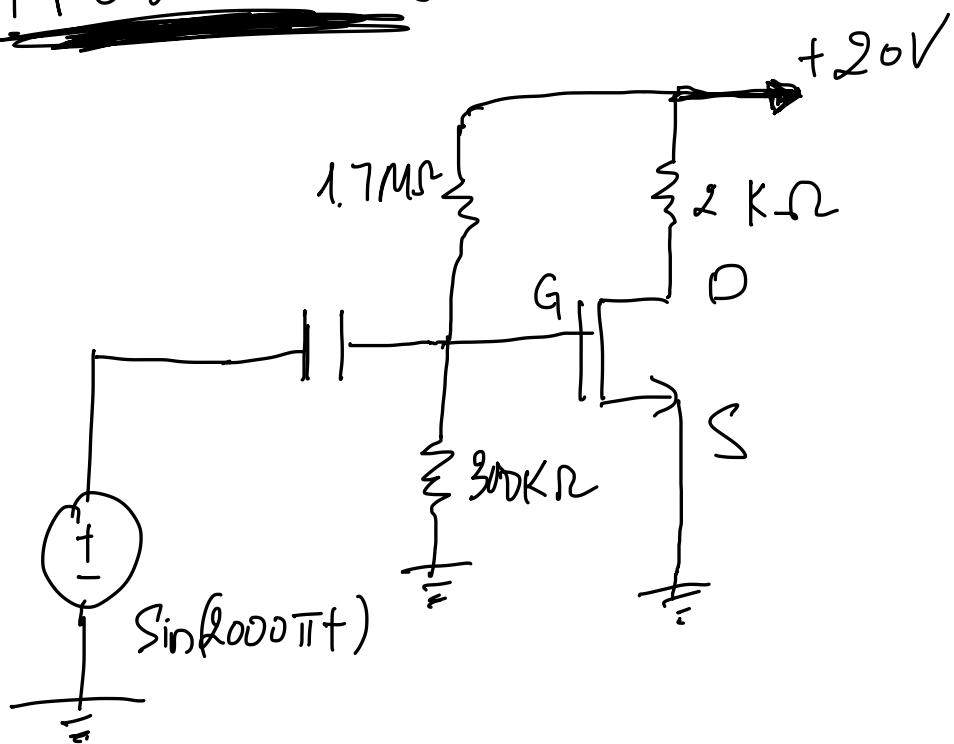

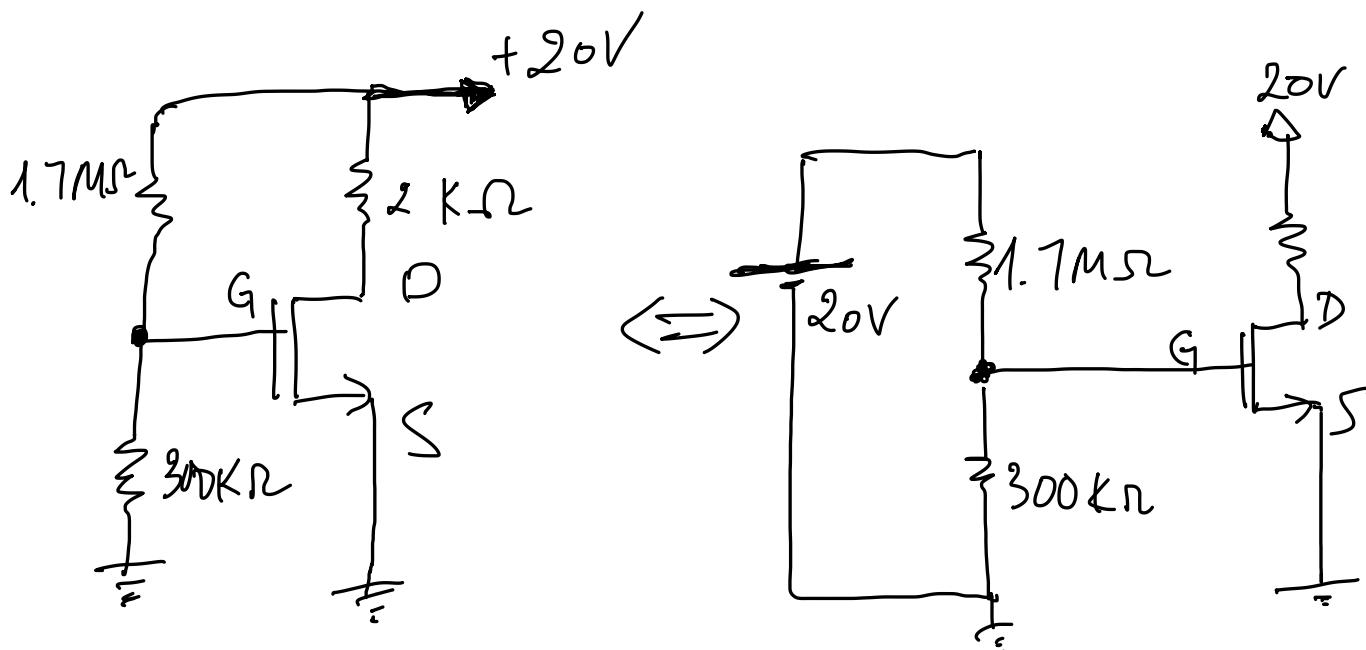
a) Apply the Superposition for DC Sources:
 (the coupling is open circuit for DC)



Apply the divide voltage :

$$V_G = V_{GSQ} = \frac{300 \times 10^3}{300 \times 10^3 + 1.7 \times 10^6} \times 20 = 3(V) \quad (1)$$

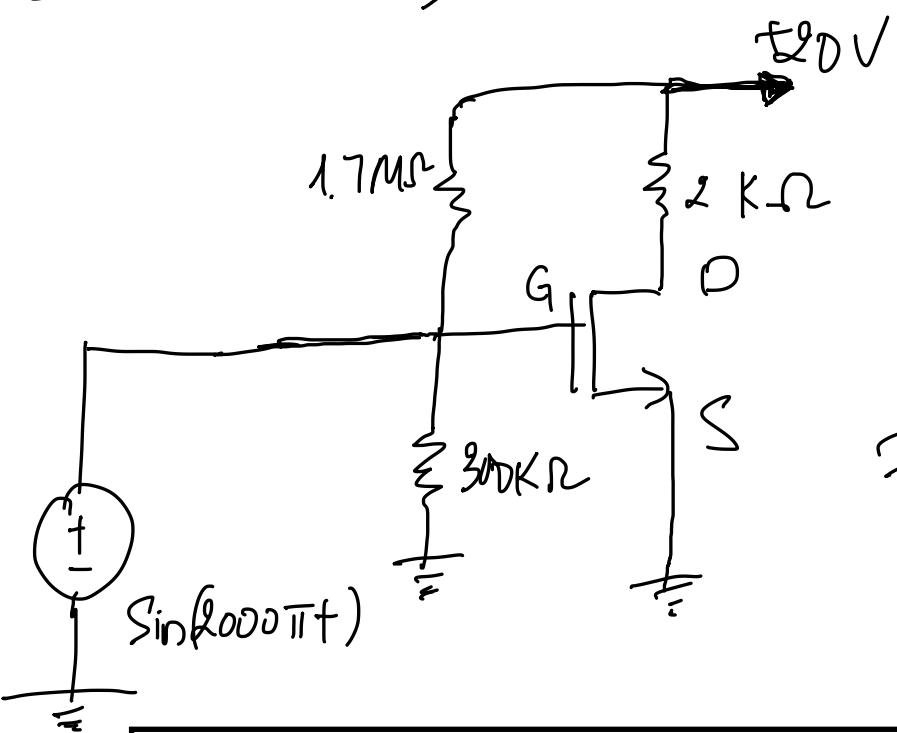For the ac circuit, the coupling capacitor is a short circuit, we have:



We can see,

$$\begin{aligned} \mathcal{O}_{GS}(t) &= \mathcal{O}_{in}(t) \\ &= \sin(2000\pi t) \end{aligned} \quad (2)$$

From (1) & (2), the voltage of $\mathcal{O}_{GS}(t)$.

$\mathcal{O}_{GS}(t) = 3 + \sin(2000\pi t) \text{ (V)}$

b) $V_{th} = 1V$ & $K = 0.5(\text{mA/V}^2)$

Need to sketch its drain characteristics to scale for $\mathcal{O}_{GS} = 1, 2, 3, \text{ & } 4V$.

With saturation region, we have:

$$i_D = k(V_{GS} - V_{th})^2 = 0.5(V_{GS} - 1)^2 \text{ (mA)}$$

⊕ $V_{GS} = 1 \text{ V}$

$$\Rightarrow i_D = 0 \text{ (mA)}$$

⊕ $V_{GS} = 2 \text{ V}$


$$\Rightarrow i_D = 0.5(2-1)^2 = 0.5 \text{ (mA)}$$

⊕ $V_{GS} = 3 \text{ V}$

$$\Rightarrow i_D = 0.5(3-1)^2 = 2 \text{ (mA)}$$

⊕ $V_{GS} = 4 \text{ V}$
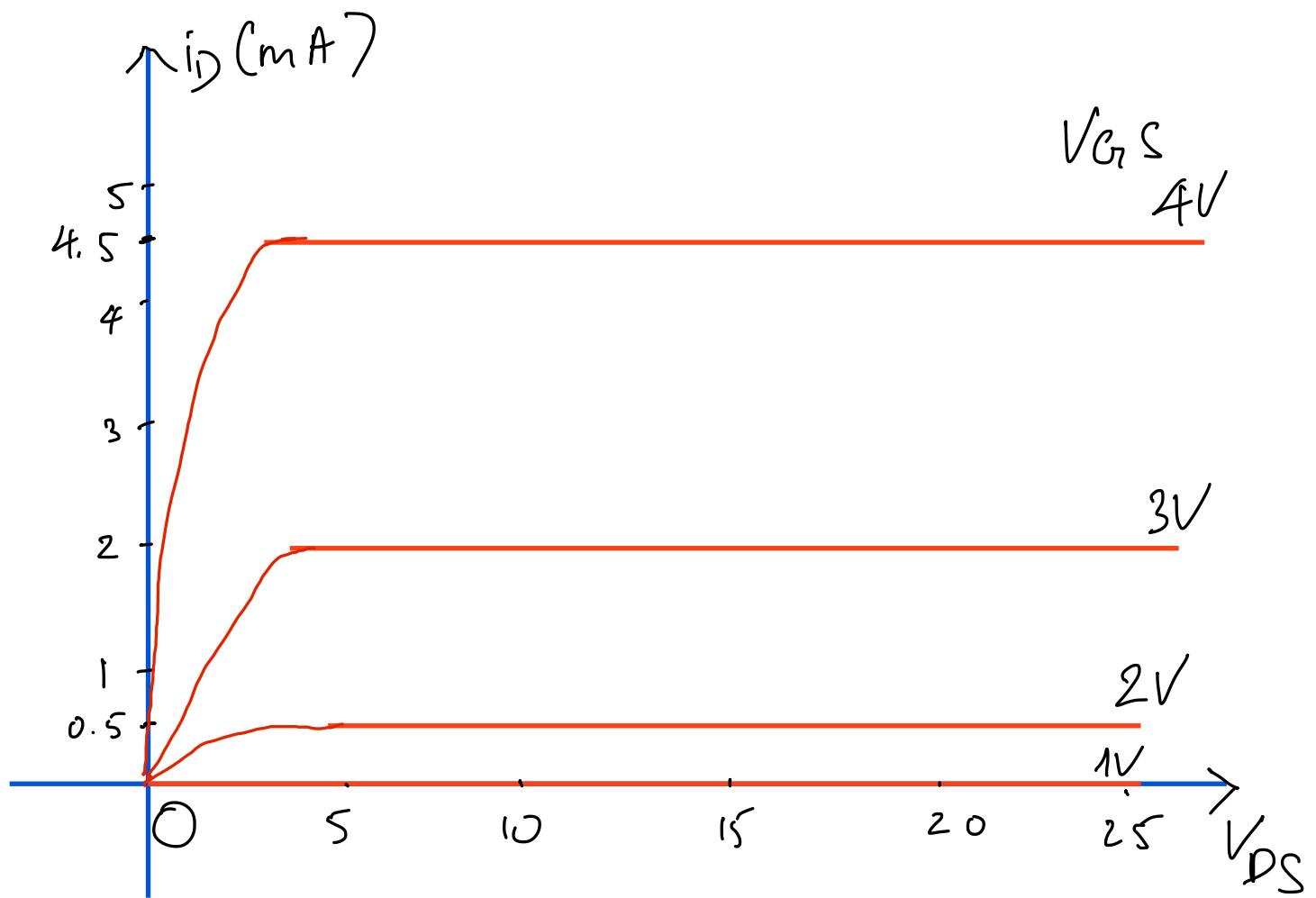
$$\Rightarrow i_D = 0.5(4-1)^2 = 4.5 \text{ (mA)}$$



c) Find the load line:


We have:

$$20 = i_D \times 2k\Omega + V_{DS}$$

① Assuming $i_D = 0 \Rightarrow V_{DS} = 20V$

② Assuming $V_{DS} = 0 \Rightarrow i_D = 10mA$

We have:

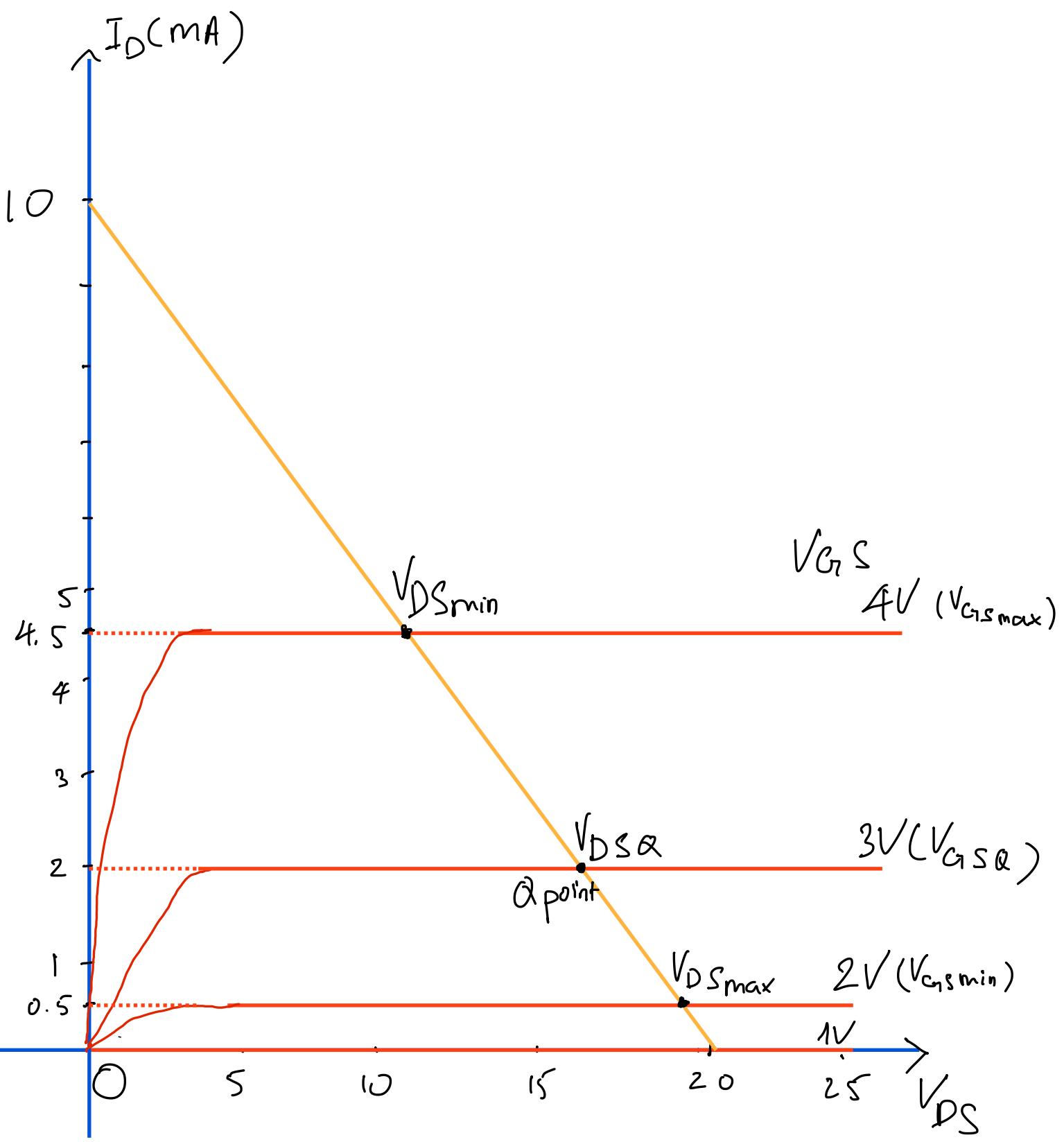

$$\text{Since } \mathcal{L}O = i_D \times 2K\Omega + V_{DS}$$

$$\textcircled{+} \text{ With } i_D = 4.5 \text{ mA} \Rightarrow V_{DS\text{min}} = \mathcal{L}O - 4.5 \times 2$$

$$\Rightarrow V_{DS_{min}} = 11(V)$$

⊕ With $i_D = 2mA \Rightarrow V_{DSQ} = 20 - 2 \times 2 = 16V$

$$\Rightarrow V_{DSQ} = 16(V)$$

⊕ With $i_D = 0.5mA \Rightarrow V_{DS_{max}} = 20 - 0.5 \times 2 = 19V$

$$\Rightarrow V_{DS_{max}} = 19(V)$$