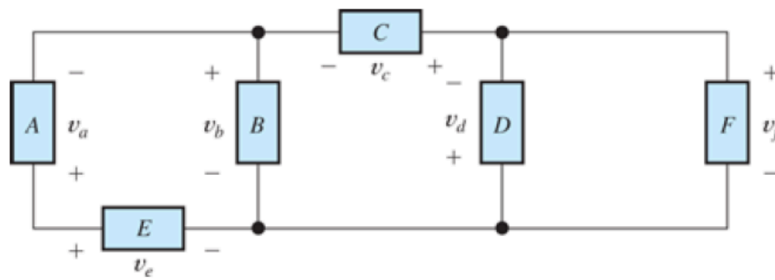


Consider the circuit in figure. Which elements are in parallel here?

2 points



☐ A,B,D, and F are in parallel

☒ D and F are in parallel



☐ B,C and F are in parallel

☐ B,C and D are in parallel

Which elements are in series?

2 points

☒ A and E are in series



☐ D and F are in series

☐ C and F are in series

☐ B and C are in series

What is the relationship between  $v_d$  and  $v_f$  (note the polarity defined in the figure)

2 points

☐  $v_d = v_f$

☒  $v_d = -v_f$



☐ can't be determined

Given that  $v_a=10$  V,  $v_c=15$  V, and  $v_e= 20$  V, determine values of  $v_b$  and  $v_f$ ?

4 points

Applying KVL in the loop containing A, B, E

$$\begin{aligned} v_a + v_b - v_e &= 0 \\ 10 + v_b - 20 &= 0 \\ \Rightarrow v_b &= 10 \end{aligned}$$

Applying KVL in the loop containing A, C, F and E

$$\begin{aligned} v_a - v_c + v_f - v_e &= 0 \\ 10 - 15 + v_f - 20 &= 0 \end{aligned}$$

$$\Rightarrow v_f = 25 \text{ V}$$

☒  $v_b = 10 \text{ V}$  and  $v_f = 25 \text{ V}$

