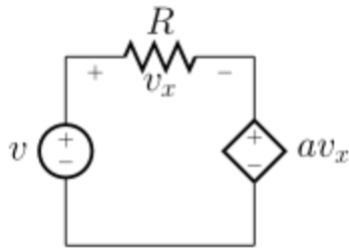


Today:

- Review Quiz #3 answers
- Ideal transformers
- Resistive networks
- Example Questions
- Magnetics review

(https://www.ieee.li/pdf/introduction_to_power_electronics/chapter_1_2.pdf)

Quiz 3 Answers:

solve by KVL:

$$\textcircled{1} \quad v = IR + av_x$$


$$\textcircled{2} \quad v_x = IR$$

$$\rightarrow v = IR + a(IR) = I(1+a)R$$

$$v = 100V, R = 20, I = 1A$$

$$100V = (1+a)20 \rightarrow 1+a = 5$$

$$\rightarrow \boxed{a = 4}$$

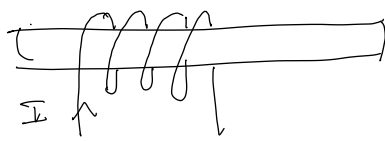
Inductance (Sections 3.4-3.7)

$$v(t) = L \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int v(t) dt$$

* when current changes in value, the resulting magnetic flux changes, Φ

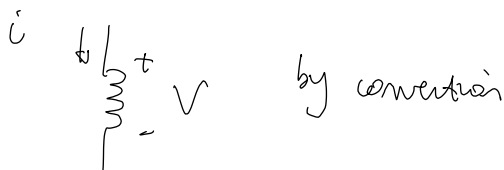* time-varying magnetic flux in a coil induces a voltage across a coil



Energy stored in a inductor:

$$E_{\text{cap}} = \frac{1}{2} C V^2 \quad (\text{this from lecture})$$

$$E_{\text{inductor}} = \int P_{\text{inductor}} dt$$



$$P(t) = I(t)V(t) = i(t) \times \left(L \frac{di(t)}{dt} \right)$$

$$E = \int P(t) dt = \int_0^t \left(L \frac{di}{dt} \times i(t) \right) dt$$

* assumption: $i(t=0^-) = 0$ (initial condition)

$$\rightarrow E_{\text{ind}} = \int_0^t L \times i(t) di = \boxed{\frac{1}{2} L i^2}$$

Example:

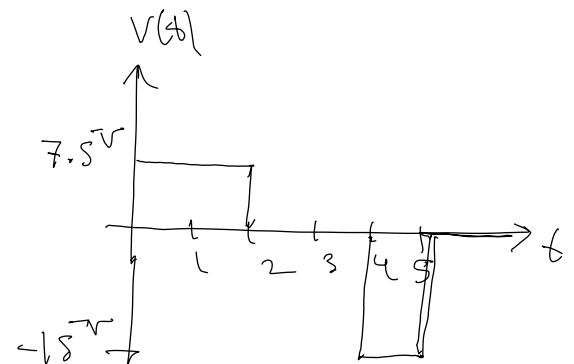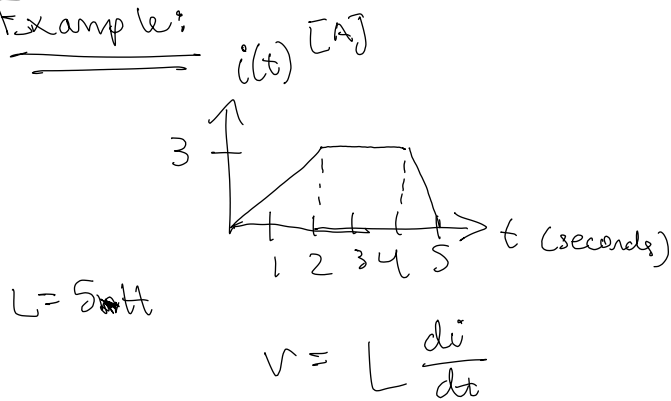

$$t=0 \rightarrow t=2: \quad \frac{di}{dt} = \frac{3}{2} = 1.5$$

$$V(t) = (5 \text{ mH}) \times 1.5 = 7.5 \text{ V}$$

$$t=2 \rightarrow t=4:$$


$$V = 0 \text{ V} \quad \text{b/c} \quad \frac{di}{dt} = 0$$

$$t=4 \rightarrow t=5:$$


$$\frac{di}{dt} = -3 \rightarrow V(t) = (5 \text{ mH}) (-3) = -15 \text{ V}$$

• what is $p(t)$?

$$p(t) = i(t) \times v(t)$$

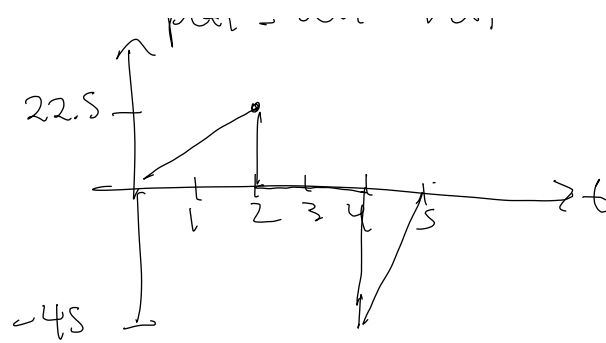

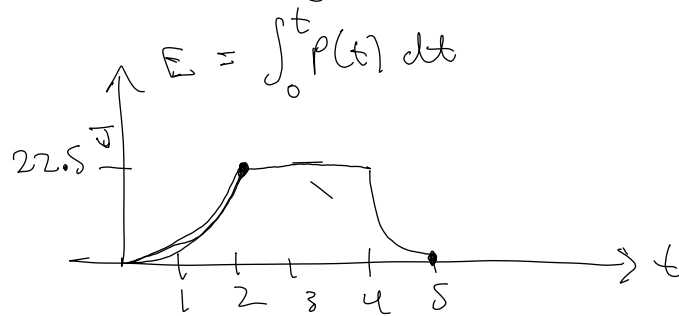
what is Energy stored across the inductor over time?



$$E(t=2) = \int_0^2 \left(\frac{22.5}{2} t \right) dt = \frac{22.5}{2} \times \frac{1}{2} t^2 \bigg|_0^2 = \boxed{22.5}$$

$$E = \int_4^5 (45t - 225) dt = \left(\frac{45t^2}{2} - 225t \right) \bigg|_4^5 = -22.5$$

Example #2 :

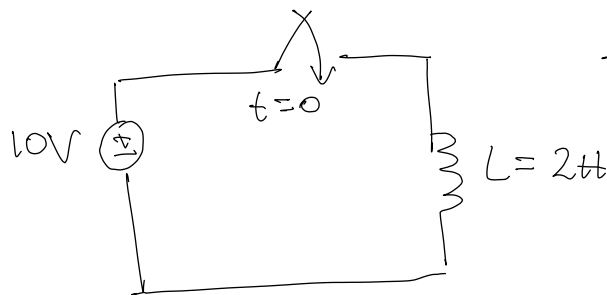




$$10V = 2t \times \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{10V}{2t} = 5$$



what happens as $t \rightarrow \infty$:

$$i \rightarrow \infty$$

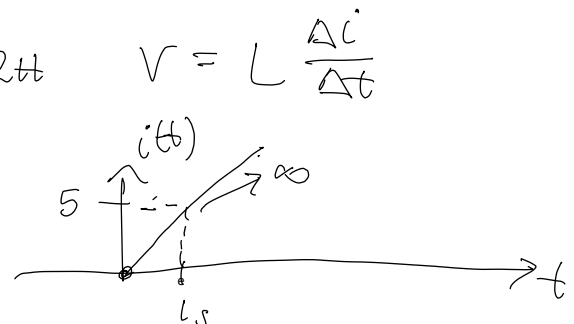

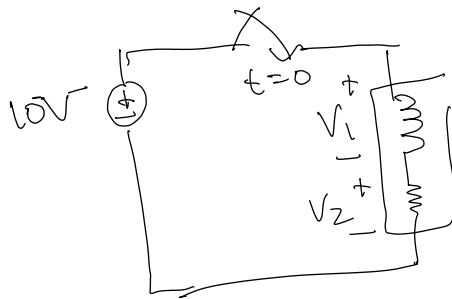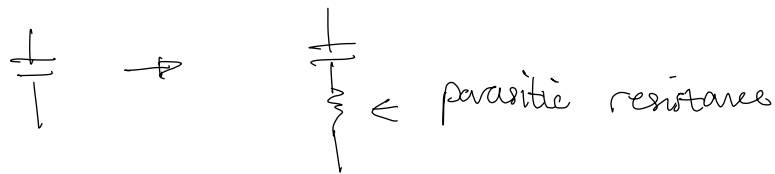

inductor

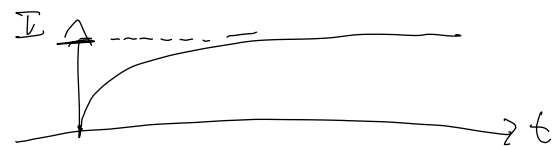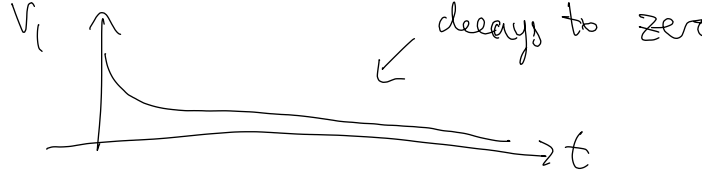

$$V(t) = IR + L \frac{di}{dt}$$


↳ differential equation

$$I(t) = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$\Rightarrow I(\infty) = \frac{V}{R}$$

* resistance-limited circuit

Series Inductance

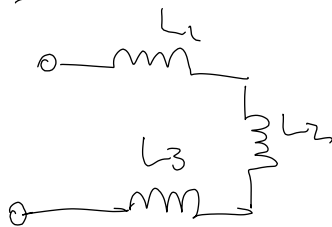


$$V(t) = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$

$$= L_{TOTAL} \frac{di}{dt}$$

$$\therefore L_{TOTAL} = L_1 + L_2 + L_3$$

Parallel Inductance

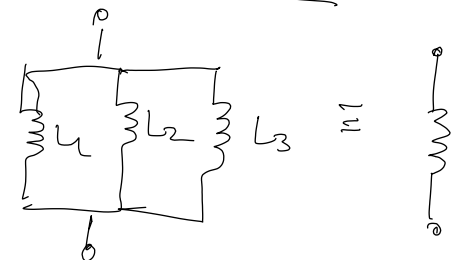

$$L_1 || L_2 || L_3$$

$$L_{TOTAL} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$$



Transformers:

Section 14.5 (ideal transformers)

very common

Section 14.1 - 14.4

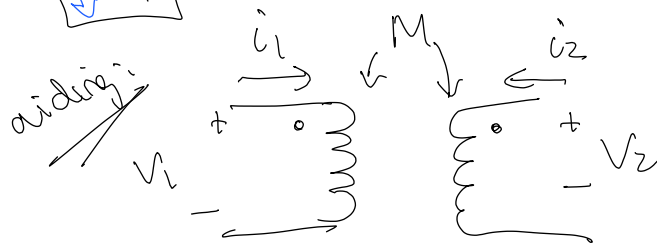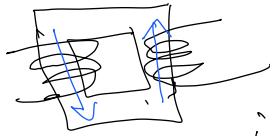cover useful background regarding electromagnetics




$$V_1 = L_1 \frac{di_1}{dt} + M_{21} \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M_{12} \frac{di_1}{dt}$$

note: $M_{12} = M_{21} = \underline{\underline{M}}$

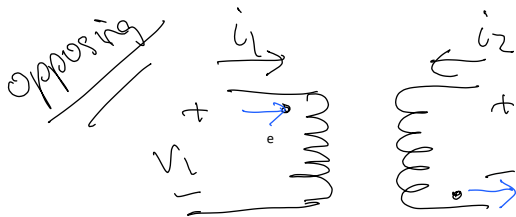* Magnetic flux produced by one coil can either aid or oppose the flux produced by the other coil




$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

Example:

$L_1 = 1H$ $L_2 = 2H$ $M = 1H$

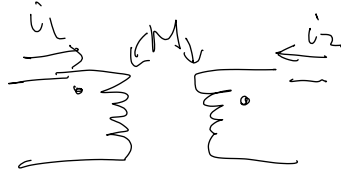

$i_1(t) = \sin(\omega t)$
 $i_2(t) = \frac{1}{2} \sin(\omega t)$

Solve on your own!

Find $V_1(t)$ & $V_2(t)$

answers:

$$V_1(t) = 15 \cos(\omega t) \text{ [V]}$$

$$V_2(t) = 20 \cos(\omega t) \text{ [V]}$$

sanity check:

$I_1 > I_2$

$\hookrightarrow V_1 < V_2$

$P = IV$

Ideal Transformers:

coupling coefficient:

$$k = \sqrt{L_1 L_2}$$

$$V_1(t) = N_1 \frac{d\Phi}{dt}$$

$$V_2 = N_2 \frac{d\Phi}{dt}$$

$k=1$: implies perfect coupling ^M

$$\Phi = \Phi_1 = \Phi_2$$

$$\rightarrow V_2 = \frac{N_2}{N_1} V_1$$


$$n = \frac{N_2}{N_1}$$

$\hookrightarrow n$: turns ratio

$$i_2(t) = \frac{-i_1(t)}{\left(\frac{N_2}{N_1}\right)} = \frac{-N_1}{N_2} i_1(t) = \frac{-1}{n} i_1(t)$$



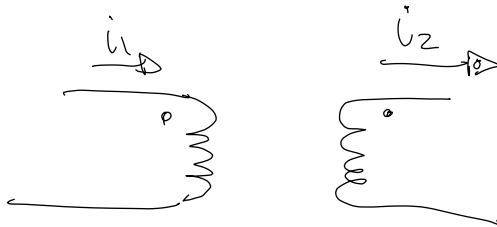book the book uses a slightly different convention:



$$\frac{i_2(t)}{i_1(t)} = \frac{N_1}{N_2} = \frac{1}{n}$$