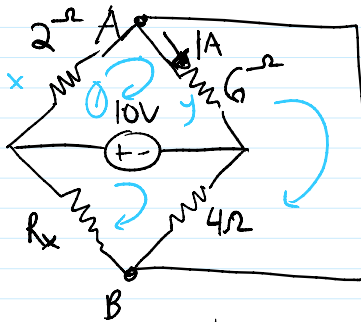



# Discussion 1A (Week #1)

Monday, March 29, 2021 3:17 PM
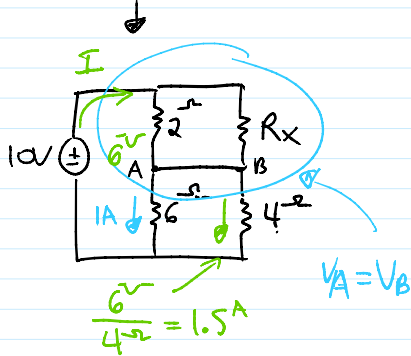
## Problem 1



$$10V - I_x 2\Omega - \frac{I_A}{I_y} 6\Omega = 0$$




in series:

$$\begin{array}{c} \text{---} \text{---} \\ R_A \quad R_B \end{array} \equiv \begin{array}{c} \text{---} \\ R' = R_A + R_B \end{array}$$

in parallel:
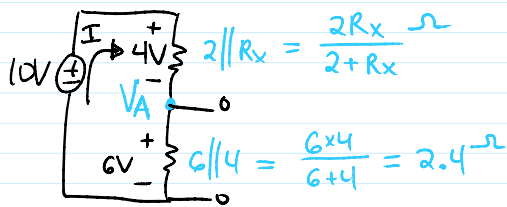
$$\begin{array}{c} R_C \\ \text{---} \\ A \quad B \\ \text{---} \\ R_D \end{array} \equiv \begin{array}{c} \text{---} \\ R' = R_C \parallel R_D = \frac{R_C R_D}{R_C + R_D} \end{array}$$



$$V_A = I_A \times 6\Omega = 6V$$

$$4V = I (2 \parallel R_x) = 1.6\Omega \times 2.5A = 4V$$


$$I = 2.5A$$

$$V_A = 6V = \frac{2.4\Omega}{2.4\Omega + 2 \parallel R_x} 10V$$

$$\frac{10}{6} \times 2.4 = 2.4 + \frac{2R_x}{2 + R_x}$$

$$\boxed{R_x = 8\Omega}$$

∴ Voltage Divider:

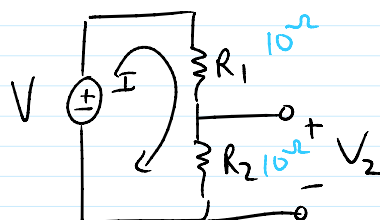


$$V_2 = \frac{R_2}{R_1 + R_2} V \rightarrow V_2 = \frac{10}{10+10} V = \frac{1}{2} V$$

$$V_2 = I R_2 \rightarrow I = \frac{V_2}{R_2}$$

$$V = I(R_1 + R_2) \rightarrow I = \frac{V}{R_1 + R_2}$$

$$\frac{V_2}{R_2} = \frac{V}{R_1 + R_2} \rightarrow \boxed{V_2 = \frac{R_2}{R_1 + R_2} V}$$

### Current Divider

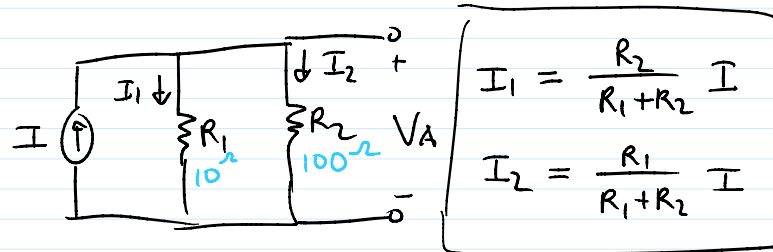

$$V_A = I_1 R_1 = I_2 R_2$$

$$I = I_1 + I_2$$


$$I_1 R_1 = I_2 R_2 \rightarrow I_2 = I_1 \frac{R_1}{R_2}$$

$$\text{solve for: } I_1 = I - I_2 = I - I_1 \frac{R_1}{R_2}$$

$$I_1 \left( 1 + \frac{R_1}{R_2} \right) = I$$

$$\rightarrow \boxed{I_1 = I \left( \frac{R_2}{R_1 + R_2} \right)}$$

### Problem 2 :

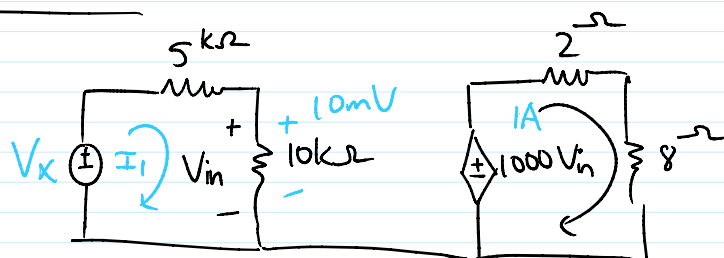

\* power delivered to the  $8\Omega$  resistor is  $8W$

$$P = I^2 R = IV$$

$$8W = I^2 (8\Omega) \rightarrow$$

$$\underline{\underline{I_2 = 1A}}$$


$$\textcircled{2} \quad 1000 V_{in} - (1A)(2+8) = 0$$

$$\hookrightarrow V_{in} = \frac{10}{1000} = 10mV$$

$$\textcircled{1} \quad V_x = I_1 (5k\Omega + 10k\Omega)$$

$$I_1 = \frac{V_{in}}{10k\Omega} = \frac{10mV}{10k\Omega} = 1\mu A$$

$$V_x = 1\mu A (15k\Omega) = 15mV$$

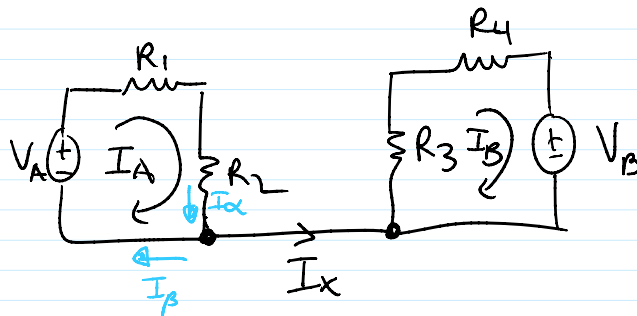

$$I_x = I_B + I_x$$

$$I_x = I_B$$

$$\hookrightarrow I_x = 0$$

