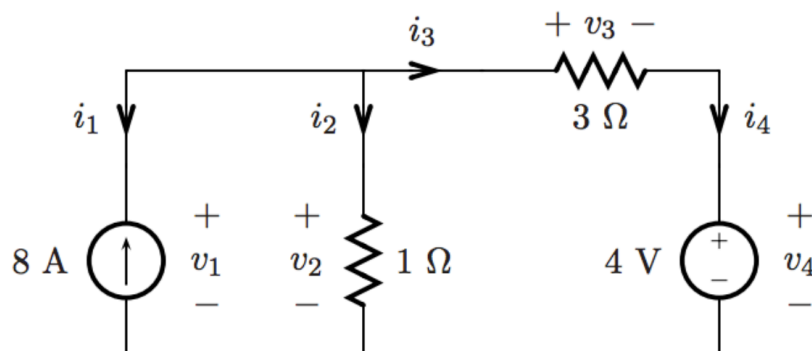


POP QUIZ-5 SOLUTIONS

For the circuit shown below how many nodes are there?

3 points



☐ 6


☐ 4

☒ 3



☐ 2

There are 3 nodes in the circuit.

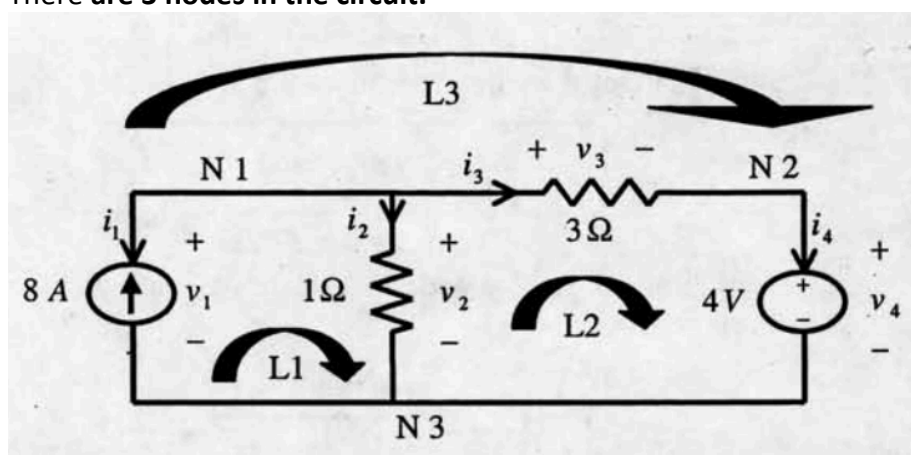

$$-i_1 - i_2 - i_3 = 0 \quad \text{For N1}$$

$$i_3 - i_4 = 0 \quad \text{For N2}$$

$$i_1 + i_2 + i_4 = 0 \quad \text{For N3}$$

But if the question is asking how many independent nodes, then there are only 2
Because $i_3 = i_4$

2. For the same circuit above how many independent loops are there?


The network has three loops. Only **two of the loops are independent** since v_1 and v_2 are the same voltage

The KVL for the three loops are

$$\begin{array}{ll} v_1 - v_2 = 0 & \text{For L1} \\ v_2 - v_3 - v_4 = 0 & \text{For L2} \\ v_1 - v_3 - v_4 = 0 & \text{For L3} \end{array}$$

If circuit in the left side below is to be transformed to a current source I_s with a resistor R_s in parallel, what is the value of I_s ?

2 points

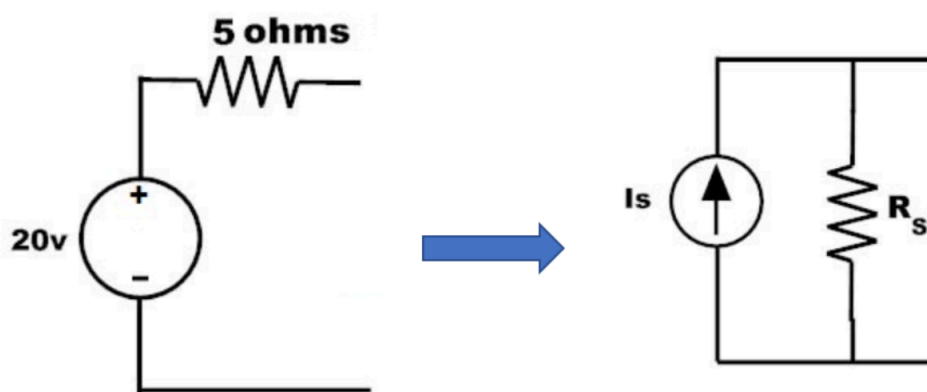

☒ 4 A



☐ 20 A

☐ 5 A

☐ None of the above

$$I_s = 20/5 = 4 \text{ A}$$

$$R_s = 5 \text{ ohms}$$

What is the value of R_s

2 points

☒ 5 ohms



☐ 4 ohms

☐ 20 ohms

☐ None of the above