

ECE100
Homework-4

Total Points: 100


Submit your work in a pdf file electronically in the CCLE website before May 9th 11:59 pm. Late homework will not get credit!

1. A current $i(t) = 10 \cos(2000\pi t)$ flows through a $100\ \Omega$ resistance. Sketch $i(t)$ and power $p(t)$ to scale versus time. Find the average power delivered to the resistance.


$$i(t) = 10 \cos(2000\pi t) \text{ A}$$

$$p(t) = Ri^2(t) = 10^4 \cos^2(2000\pi t) = 5000[1 + \cos(4000\pi t)] \text{ W}$$
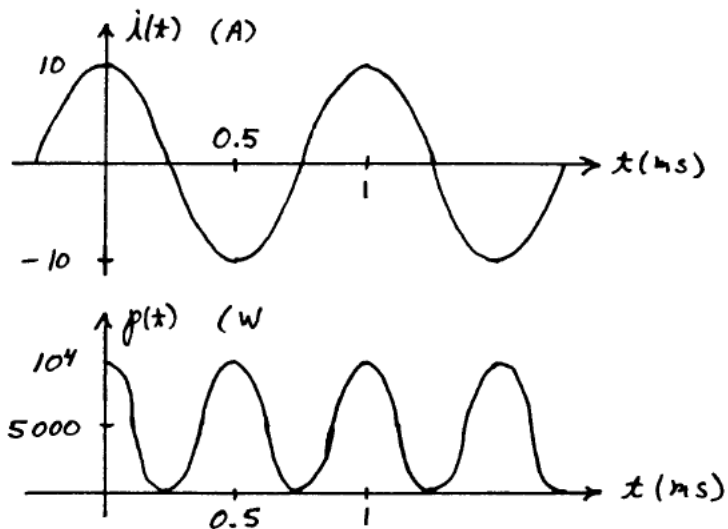
$$P_{avg} = R(I_{rms})^2 = 100(10/\sqrt{2})^2 = 5000 \text{ W}$$



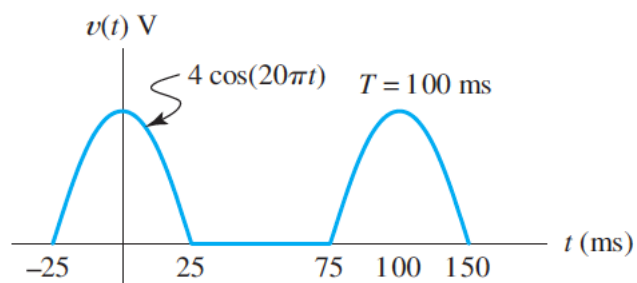2. Calculate the rms value of the half-wave rectified sinusoidal wave shown in Figure below




The limits on the integral don't matter as long as they cover one period

$$V_{rms} = \sqrt{\frac{1}{T} \int_{-T/2}^{T/2} v^2(t) dt} = \sqrt{10 \int_{-0.025}^{0.025} [4 \cos(20\pi t)]^2 dt} = \sqrt{10 \int_{-0.025}^{0.025} [8 + 8 \cos(40\pi t)] dt}$$

$$V_{rms} = \sqrt{\left(80t + \frac{80}{40\pi} \sin(40\pi t) \right) \Big|_{t=-0.025}^{t=0.025}} = \sqrt{4} = 2 \text{ V}$$

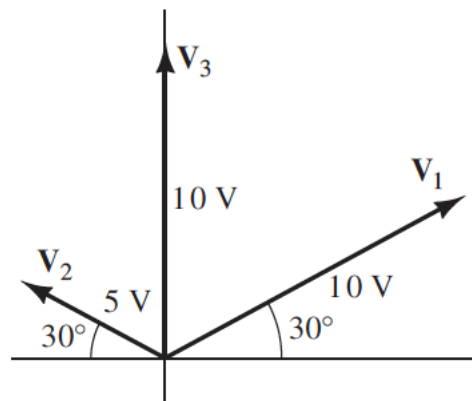3. Consider the phasors shown in Figure below. The frequency of each signal is $f = 200\text{Hz}$. Write a time-domain expression for each voltage in the form $V_m \cos(\omega t + \theta)$. State the phase relationships between pairs of these phasors



$$\omega = 2\pi f = 400\pi$$

$$v_1(t) = 10 \cos(400\pi t + 30^\circ)$$

$$v_2(t) = 5 \cos(400\pi t + 150^\circ)$$

$$v_3(t) = 10 \cos(400\pi t + 90^\circ)$$

$$v_1(t) \text{ lags } v_2(t) \text{ by } 120^\circ$$

$$v_1(t) \text{ lags } v_3(t) \text{ by } 60^\circ$$

$$v_2(t) \text{ leads } v_3(t) \text{ by } 60^\circ$$

4. (a) The current and voltage for a certain circuit element is shown in Figure - A. Determine the nature and value of the element.
- (b) Repeat for Figure B

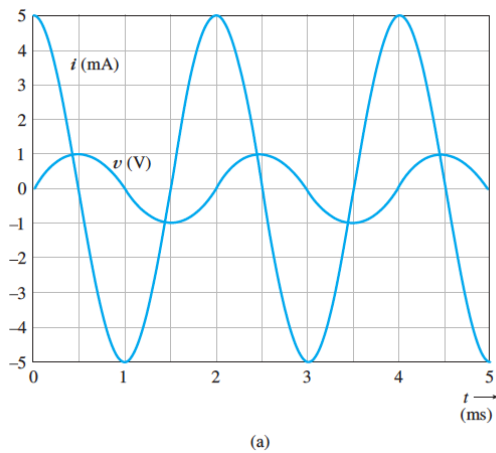


Figure- A


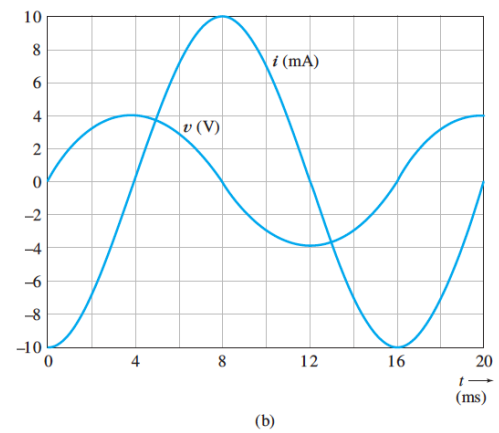


Figure- B

(a) From the plot, we see that $T = 2 \text{ ms}$, so we have $f = 1/T = 500 \text{ Hz}$ and $\omega = 1000\pi$. Also, we see that the current leads the voltage by 0.5 ms or 90° , so we have a capacitance. Finally, $1/\omega C = V_m / I_m = 200 \Omega$, from which we find that $C = 1.592 \mu\text{F}$.

(b) From the plot, we see that $T = 16 \text{ ms}$, so we have $f = 1/T = 62.5 \text{ Hz}$ and $\omega = 125\pi$. Also, we see that the current lags the voltage by 4 ms or 90° , so we have an inductance. Finally, $\omega L = V_m / I_m = 400 \Omega$, from which we find that $L = 1.018 \text{ H}$.

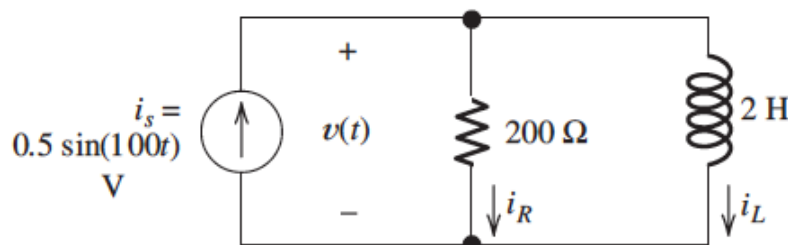5. Find the phasors for the voltage and the currents of the circuit shown in Figure below. Construct a phasor diagram showing I_s , V , I_R , and I_L . What is the phase relationship between V and I_s ?



$$\mathbf{I}_s = 0.5 \angle -90^\circ \text{ A}$$


$$\mathbf{V} = \mathbf{I}_s \frac{1}{1/200 + 1/j200}$$

$$= 70.71 \angle -45^\circ \text{ V}$$


$$\mathbf{I}_R = \mathbf{V}/R = 0.3536 \angle -45^\circ \text{ A}$$

$$\mathbf{I}_L = \mathbf{V}/j\omega L = 0.3536 \angle -135^\circ \text{ A}$$

\mathbf{V} leads \mathbf{I}_s by 45°

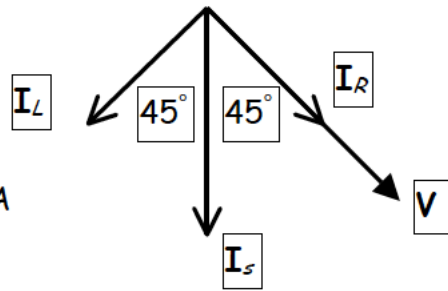

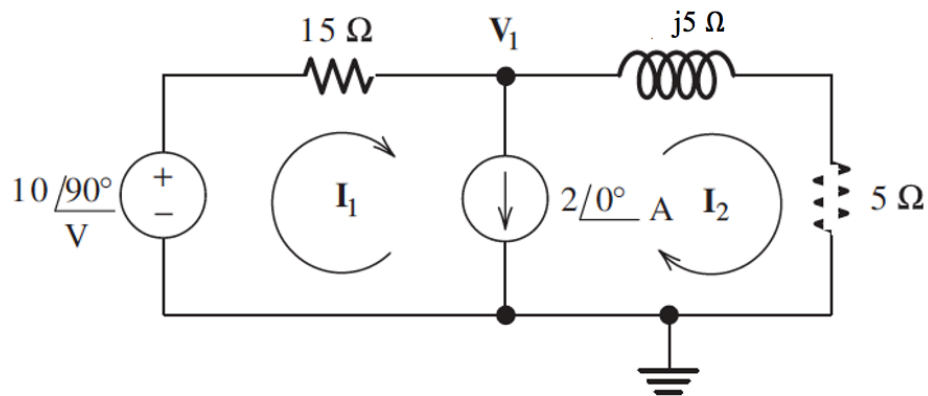
6. Solve for the node voltage shown in Figure



The KCL equation is $\frac{\mathbf{V}_1 - j10}{15} + \frac{\mathbf{V}_1}{5 + j5} + 2 = 0$. Solving, we find

$$\mathbf{V}_1 = -10.58 - j2.35 = 10.84 \angle -167.47^\circ \text{ V}.$$

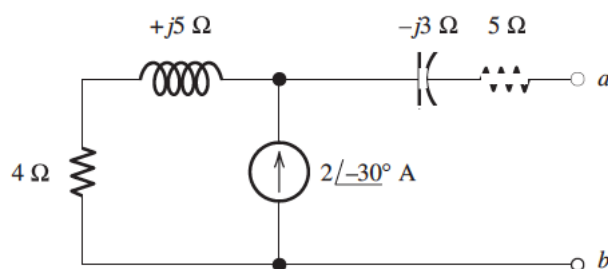7. Find the Thevenin voltage, Thevenin impedance, and Norton current for the two terminal circuit shown in Figure



Under open-circuit conditions, we have

$$\mathbf{V}_t = \mathbf{V}_{ab-oc} = (4 + j5)2\angle -30^\circ = 11.92 + j4.66 = 12.80\angle 21.34^\circ \text{ V}$$

With the source zeroed, we look back into the terminals and see

$$\mathbf{Z}_t = 5 - j3 + j5 + 4 = 9 + j2 \Omega$$

Next, the Norton current is

$$\mathbf{I}_n = \frac{\mathbf{V}_t}{\mathbf{Z}_t} = 1.389\angle 8.81^\circ \text{ A}$$


8. A balanced wye-connected three-phase source has line-to-neutral voltages of 440V rms. Find the rms line-to-line voltage magnitude. If this source is applied to a wye-connected load composed of three 30 Ω resistances, find the rms line-current magnitude and the total power delivered.

$$V_L = \sqrt{3} \times V_Y = \sqrt{3} \times 440 = 762.1 \text{ V rms}$$

$$I_L = \frac{V_Y}{R} = \frac{440}{30} = 14.67 \text{ A rms}$$

$$P = 3V_Y I_L \cos(\theta) = 3 \times 440 \times 14.67 \times \cos(0) \\ = 19.36 \text{ kW}$$

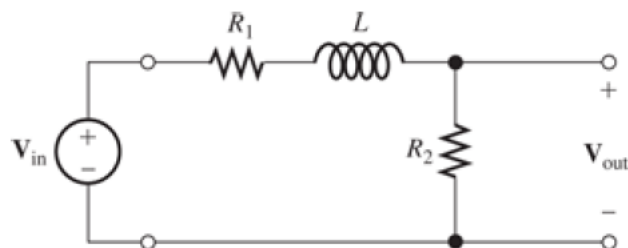9. (a) Derive an expression for the transfer function $H(f) = V_{out}/V_{in}$ for the circuit shown in Figure. Find an expression for the half-power frequency.
- (b) Given $R_1 = 50 \Omega$, $R_2 = 50 \Omega$, and $L = 15 \mu\text{H}$, sketch the magnitude of the transfer function versus frequency



(a) Applying the voltage-division principle, we have:

$$H(f) = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2 + j2\pi fL} = \frac{R_2/(R_1 + R_2)}{1 + j2\pi fL/(R_1 + R_2)} = \frac{R_2/(R_1 + R_2)}{1 + j(f/f_B)}$$


where $f_B = (R_1 + R_2)/(2\pi L)$

(b) Evaluating for the component values given, we have:

$$f_B = 1.061 \text{ MHz}$$


$$H(f) = \frac{0.5}{1 + j(f/f_B)}$$

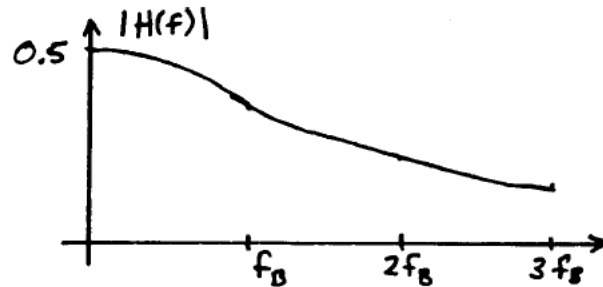A sketch of the transfer function magnitude is:



10. (a) A parallel resonant circuit has $R = 5 \text{ k}\Omega$, $L = 50 \text{ }\mu\text{H}$, and $C = 200 \text{ pF}$. Determine the resonant frequency, quality factor, and bandwidth.

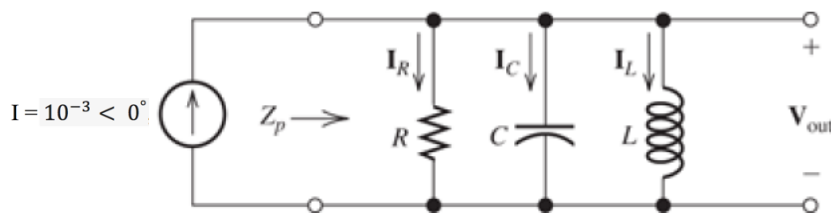(b) Consider the parallel resonant circuit shown in Figure below. Determine the L and C values, given $R = 1 \text{ k}\Omega$, $f_0 = 10 \text{ MHz}$, and bandwidth $B = 500 \text{ kHz}$. If the source current $I = 10^{-3} \angle 0^\circ$, draw a phasor diagram showing the currents through each of the elements in the circuit at resonance.



(a)
$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 1.592 \text{ MHz}$$

$$Q_p = \frac{R}{2\pi f_0 L} = 10.00$$


$$B = \frac{f_0}{Q_p} = 159.2 \text{ kHz}$$

(b)

$$Q_p = \frac{f_0}{B} = 20$$

$$C = \frac{Q_p}{2\pi f_0 R} = 318.3 \text{ pF}$$
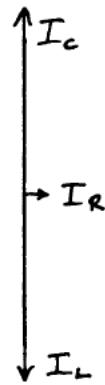
$$L = \frac{R}{2\pi f_0 Q_p} = 0.7958 \text{ } \mu\text{H}$$



$$\mathbf{I} = \mathbf{I}_R = 1 \angle 0^\circ \text{ mA}$$

$$\mathbf{I}_L = \frac{\mathbf{V}}{j2\pi f_0 L} = \frac{R\mathbf{I}}{j2\pi f_0 L} = 20 \angle -90^\circ \text{ mA}$$

$$\mathbf{I}_C = \frac{\mathbf{V}}{1/(j2\pi f_0 C)} = \frac{R\mathbf{I}}{1/(j2\pi f_0 C)} = 20 \angle +90^\circ \text{ mA}$$