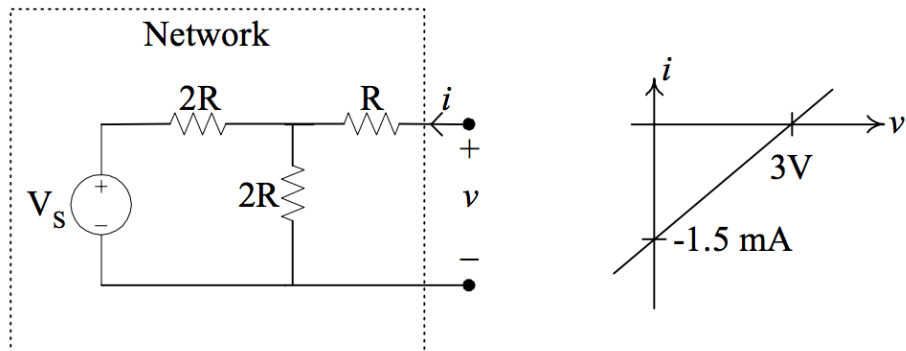


ECE100
Homework-4


Total Points: 100

Submit your work in a pdf file electronically in the CCLE website before April 25th 11:59 pm. Late homework will not get credit!


1. A network that is implemented with three resistors and a voltage source as shown below. Its terminal characteristics are also given graphically below. (3 x 4 = 12 points)



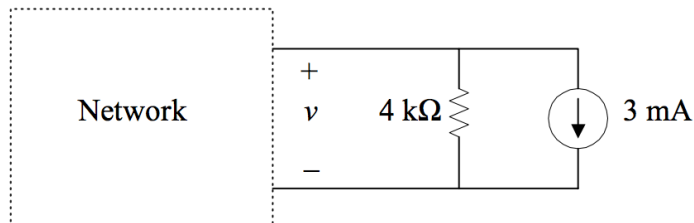
- (a) From the graphical data given above, determine numerical values for the parameters of the Thevenin equivalent of the network.
- (b) Determine numerical values for the parameters V_s and R that characterize the implementation of the network shown above.
- (c) The network is connected to an external current source and resistor as shown below. Determine the value of its terminal voltage v given the external connection.



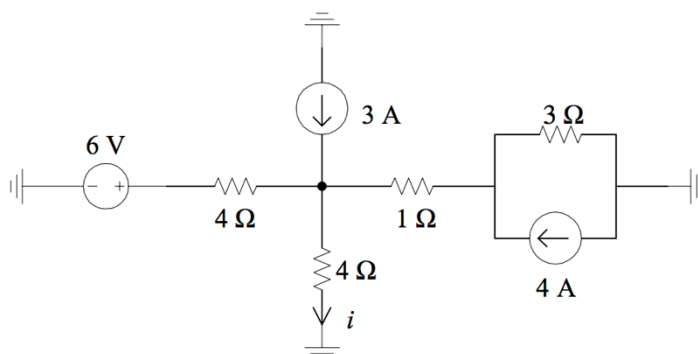
2. Determine the current i in the network below. (8 points)



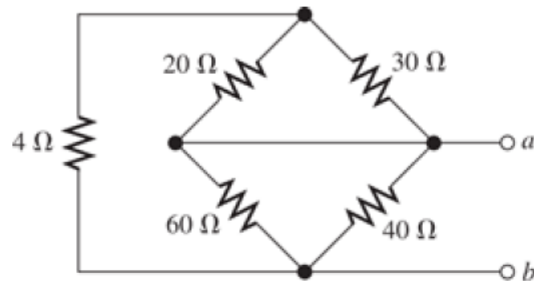
3. Find the equivalent resistance between terminals a and b in Figure below (5 points)



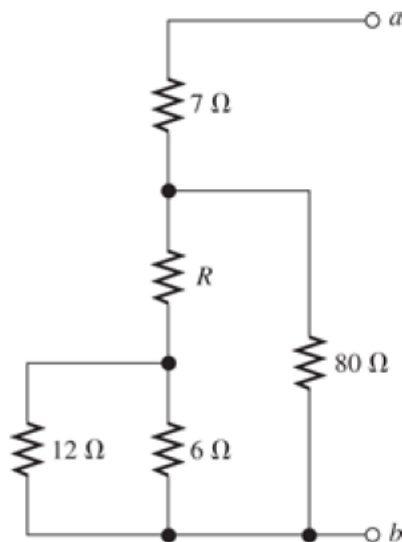
4. The equivalent resistance between terminals a and b in Figure below is 23 ohms. Determine the value of R. (5 points)



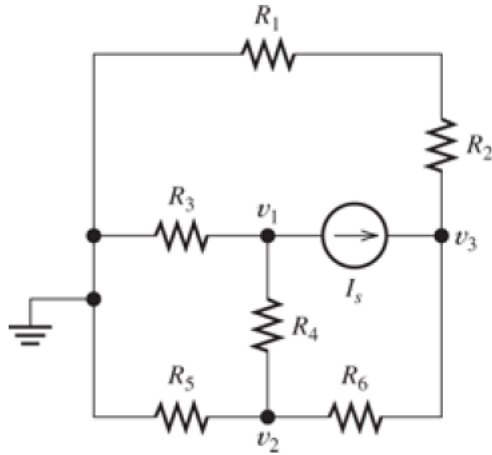
5. Given $R_1=15\ \Omega$, $R_2=5\ \Omega$, $R_3=20\ \Omega$, $R_4=10\ \Omega$, $R_5=8\ \Omega$, $R_6=4\ \Omega$ and $I_s=5\text{ A}$, solve for the node voltages shown in Figure. (10 points)



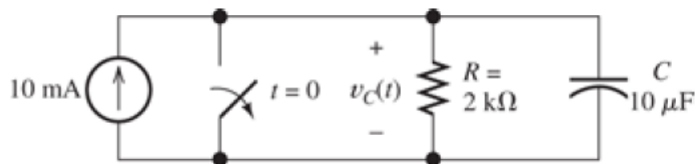6. Starting from the Norton equivalent circuit (current source I_n in parallel with R_t) with a resistive load attached (R_L), find an expression for the power delivered to the load in terms of I_n , R_t and R_L . Assuming that I_n , R_t are fixed values and that R_L is variable, show that maximum power is delivered for $R_L = R_t$. Find an expression for maximum power delivered to the load in terms of I_n , R_t . (10 points)
7. A $100\ \mu\text{F}$ capacitance is initially charged to $1000\ \text{V}$. At $t=0$ it is connected to a $1\text{-k}\Omega$ resistance. At what time t_2 has 50 percent of the initial energy stored in the capacitance been dissipated in the resistance? (10 points)
8. Derive an expression for $v_c(t)$ in the circuit below and sketch $v_c(t)$ to scale versus time. (Note that switch was closed before $t=0$ and becomes an open after $t=0$) (15 points)



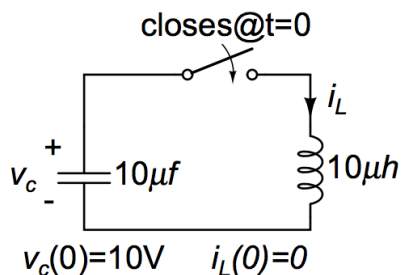9. Determine the maximum value of I_L (10 points)



10. The circuit shown in Figure has been set up for a long time prior to $t=0$ with the switch closed. Find the value of v_C prior to $t=0$. Find the steady-state value of v_C after the switch has been opened for a long time. (15 points)

