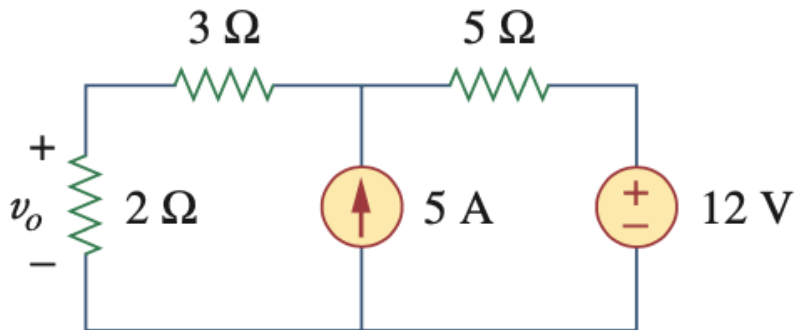


ECE 100 (Spring 2021) - Homework #5 (not graded)

This will serve as Midterm Exam preparation questions.

Due Date: Not graded


Problem 1: Solve following circuit 3 different ways



- (a) Solve using KCL/KVL
- (b) Solve using Source Transformations
- (c) Solve using Superposition


Problem 2: Superposition

Use superposition to find node voltage, v_x .

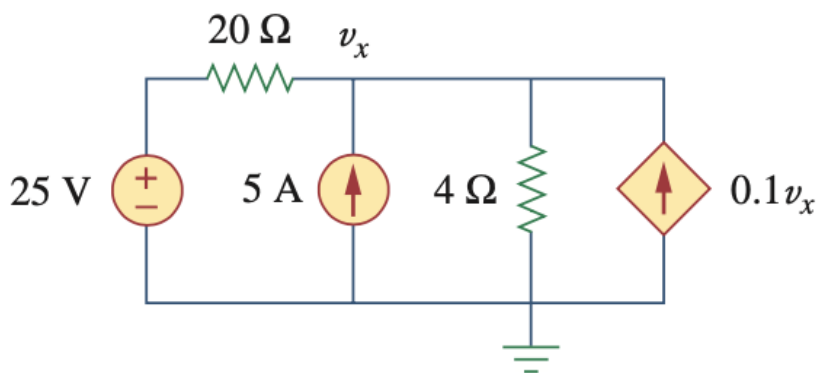


Problem 3: Superposition

Use superposition to find current, i_o .

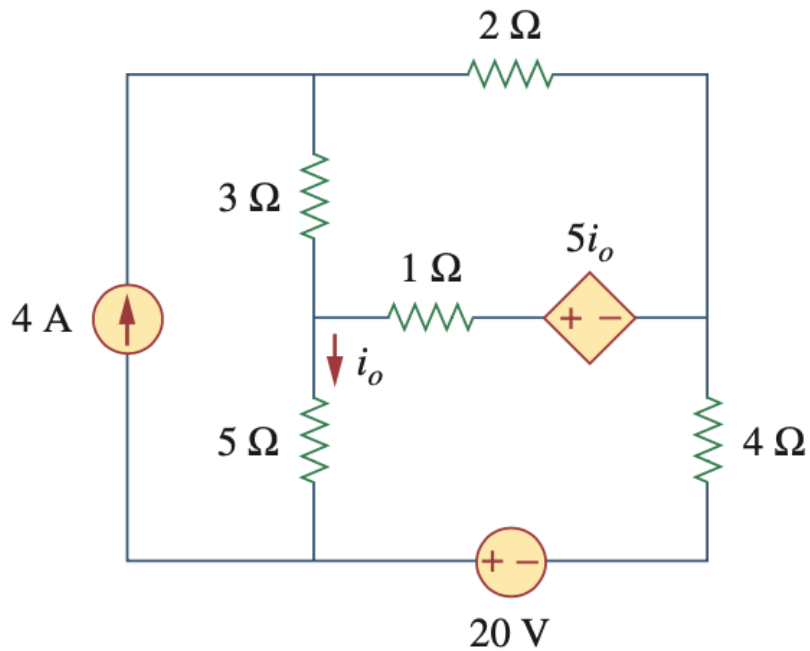


Problem 4: Superposition

Use superposition to find current, i .

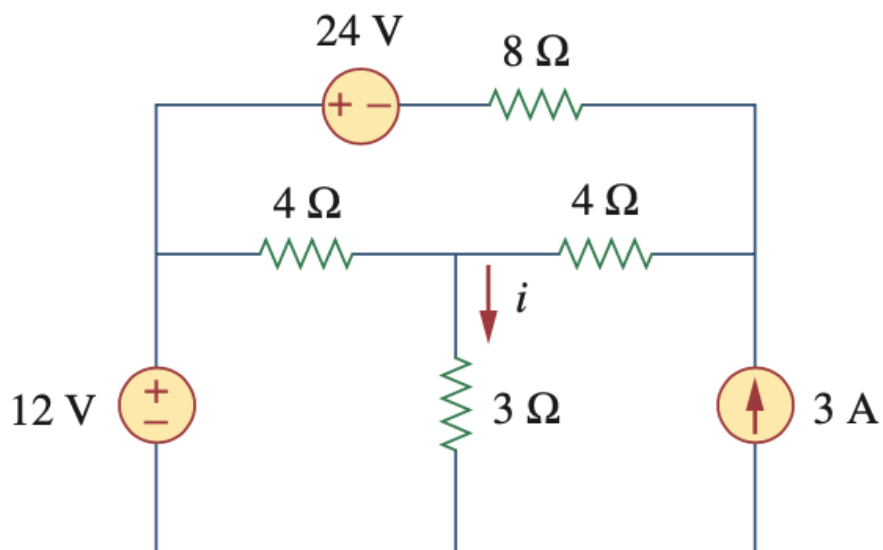

Problem 5: Mutual Inductance

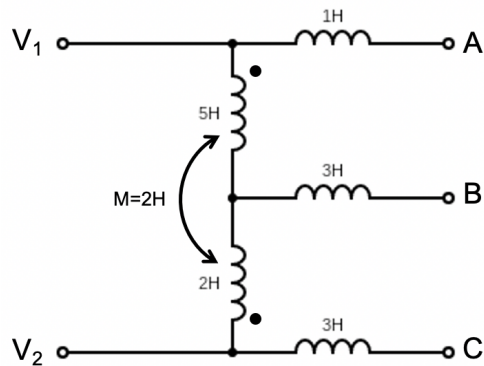


Hint: Coupling, with mutual inductance $M=2\text{H}$, is shown between 5H & 2H inductors. There is no coupling to any of the other branches.

- Find the equivalent inductance, L_{eq} , seen between terminals V_1 and V_2 .
- Find the equivalent inductance, L_{eq} , seen between terminals V_1 and V_2 if nodes B & C are connected together.

Problem 6

P4.13. Derive an expression for $v_C(t)$ in the circuit of [Figure P4.13](#) and sketch $v_C(t)$ to scale versus time.

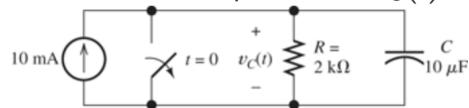

Problem 7

P4.18. Consider the circuit shown in [Figure P4.18](#). Prior to $t = 0$, $v_1 = 100\text{ V}$, and $v_2 = 0$.

- Immediately after the switch is closed, what is the value of the current [i.e., what is the value of $i(0+)$]?
- Write the KVL equation for the circuit in terms of the current and initial voltages. Take the derivative to obtain a differential equation.
- What is the value of the time constant in this circuit?
- Find an expression for the current as a function of time.
- Find the value that v_2 approaches as t becomes very large.


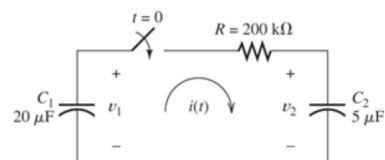


Figure P4.18


Problem 8

P4.24. The circuit shown in [Figure P4.24](#) has been set up for a long time prior to $t = 0$ with the switch closed. Find the value of v_C prior to $t = 0$. Find the steady-state value of v_C after the switch has been opened for a long time.

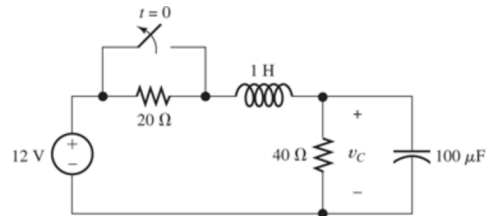


Problem 9

P4.38. For the circuit shown in [Figure P4.38](#), find an expression for the current $i_L(t)$ and sketch it to scale versus time. Also, find an expression for $v_L(t)$ and sketch it to scale versus time.

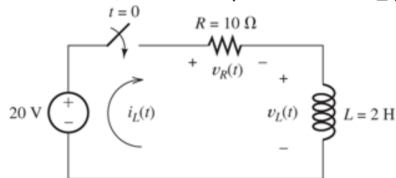

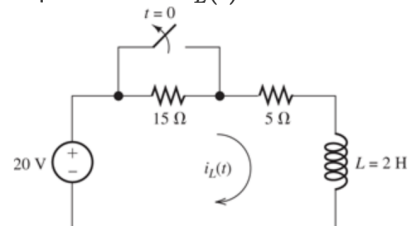Problem 10

P4.39. The circuit shown in [Figure P4.39](#) is operating in steady state with the switch closed prior to $t = 0$. Find expressions for $i_L(t)$ for $t < 0$ and for $t \geq 0$. Sketch $i_L(t)$ to scale versus time.



Problem 11 (Note: includes Problems 4.61-4.63)

Hint: See provided notes on 2nd order differential equations

***P4.61.** A dc source is connected to a series RLC circuit by a switch that closes at $t = 0$, as shown in **Figure P4.61**. The initial conditions are $i(0+) = 0$ and $v_C(0+) = 0$. Write the differential equation for $v_C(t)$. Solve for $v_C(t)$, if $R = 80 \Omega$.

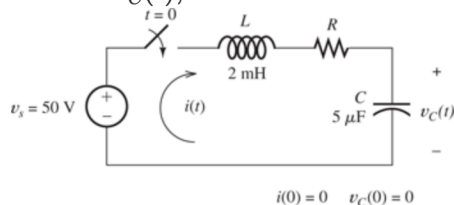


Figure P4.61

***P4.62.** Repeat **Problem P4.61** for $R = 40 \Omega$.

***P4.63.** Repeat **Problem P4.61** for $R = 20 \Omega$.

Problem 12

P4.64. Consider the circuit shown in **Figure P4.64** in which the switch has been open for a long time prior to $t = 0$ and we are given $R = 25 \Omega$.

- Compute the undamped resonant frequency, the damping coefficient, and the damping ratio of the circuit after the switch closes.
- Assume that the capacitor is initially charged by a 25-V dc source not shown in the figure, so we have $v(0+) = 25 \text{ V}$. Determine the values of $i_L(0+)$ and $v'(0+)$.
- Find the particular solution for $v(t)$.
- Find the general solution for $v(t)$, including the numerical values of all parameters.

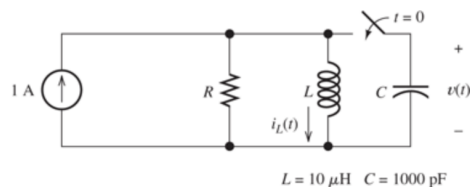


Figure P4.64

Problem 13

Refer to Figure 1 below. The inductor has no initial energy (Hint: $i_L(0^+) = 0 \text{ A}$)

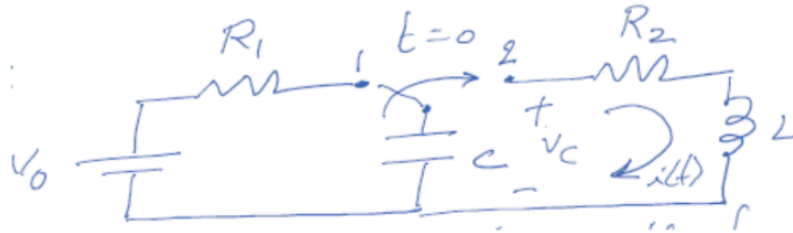


Figure 1.

- Derive the differential equation that governs the current $i(t)$ for time $t \geq 0$.
- What is the characteristic equation that governs the behavior of this circuit?
For the following assume $R_1 = 5 \text{ k}\Omega$, $R_2 = 16 \Omega$, $L = 400 \text{ nH}$, $C = 4 \text{ nF}$, and $V_0 = 10 \text{ Volts}$.
- Derive an expression for the voltage across the capacitor, $V_C(t)$ for $t \geq 0$. Assume that the circuit achieved steady state before $t = 0$ i.e. assume that the circuit came into being at $t = -\infty$.
- Draw a rough sketch of the waveform.

Problem 14

Refer to Figure 2 below. Both switches changed from their position 1 \rightarrow 2, respectively, at time $t=0$, after the circuits having already achieved steady state.

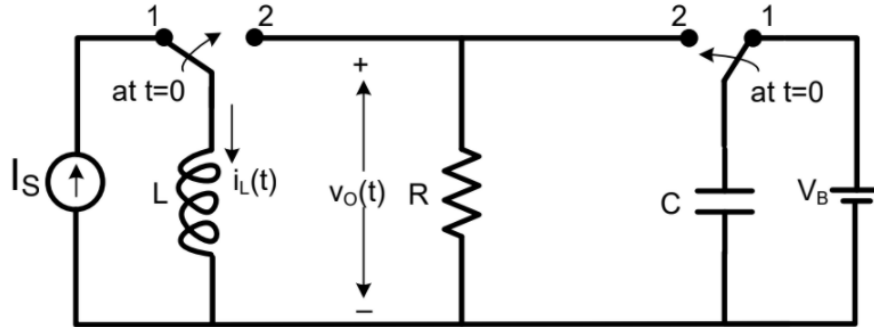


Figure 2.

For parts (a) through (d), express your answers in terms of V_B , I_S , R , L , and C .

- a. Derive a differential equation in terms of $v_O(t)$ that characterizes circuit behavior for $t \geq 0$.
- b. What is the characteristic equation of this circuit for time $t \geq 0$?
- c. Determine the value of $v_O(t)$ just after $t = 0$.
- d. Determine the value of $\left. \frac{dv_O(t)}{dt} \right|_{t=0+}$.

For the rest, use $V_B = 2\text{V}$, $I_S = 0.6\text{mA}$, $C = 1\text{nF}$, $L = 64\text{nH}$, and $R = 5\text{ Ohms}$.

- e. Calculate the damping factor of the circuit. What kind of damping is this?
- f. Derive an expression for the complete solution of $v_O(t)$ in this circuit.
- g. Derive an expression for the current, $i_L(t)$ in this circuit.
- h. Draw a rough sketch of the solution, $v_O(t)$. Do not forget to show the initial and final values of $v_O(t)$. If $v_O(t)$ shows some ringing, mark the period and the time constant of the envelope as well.
- i. What will happen if R were infinitely large? Derive an expression for $v_O(t)$ and sketch it.