

**Problem 1:** Refer to Figure 1 for this problem. The switch changes from position 1 to position 2 at time  $t = 0$ , after the circuit having already achieved steady state before  $t = 0$ .

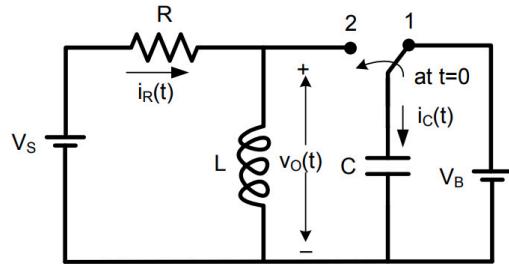


Figure 1.

For parts (a) through (d), express your answers symbolically, in terms of  $V_s$ ,  $V_B$ ,  $R$ ,  $L$  and  $C$ .

- Derive a differential equation in terms of  $v_o(t)$  that characterizes circuit behavior for  $t \geq 0$ .  
**Hint:** Apply KCL at the node that is the junction of  $R$ ,  $L$ , and  $C$ .
- Determine the values of  $v_o(t)$  and  $i_R(t)$  just after  $t = 0$ .
- Determine the value of  $\frac{dv_o(t)}{dt} \Big|_{t=0+}$ . **Hint:** Note that  $C \frac{dv_o(t)}{dt} \Big|_{t=0+}$  equals  $i_C(0+)$ .


For the rest, use numerical values,  $V_s = 10V$ ,  $V_B = 5V$ ,  $C = 4nF$ ,  $L = 400nH$ , and  $R = 5$  Ohms.

- Determine the resonant frequency and the damping factor of the circuit. What kind of damping does this circuit exhibit?
- Derive an expression for the complete solution of  $v_o(t)$  in this circuit.
- Draw a rough sketch of the solution,  $v_o(t)$ . Do not forget to show the initial and final values of  $v_o(t)$ . If  $v_o(t)$  shows any ringing, mark the period and the time constant of the envelope as well.

**Note:** For parts (e) and (f), you may need various boundary conditions i.e. answers from parts (b), and/or (c). If you are unsure of your answers, proceed symbolically i.e. derive your answers in terms of symbols such as  $v_o(0+)$  etc., for partial credit. You will be penalized a maximum of 5 points for this.

**(8 + 4 + 4 + 4 + 8 + 4 = 32 points)**

**Solution:**

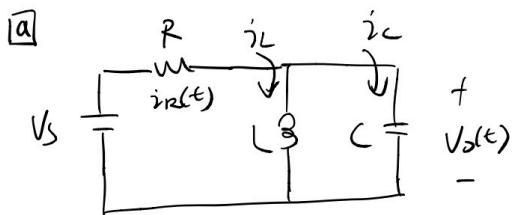

$$KCL: i_R = i_L + i_C$$

$$i_R = \frac{V_s - V_B}{R}$$

$$V_L = L \frac{di_L}{dt} = V_B \rightarrow i_L = \frac{1}{L} \int_{-\infty}^t V_B dt$$

$$i_C = C \frac{dV_B}{dt}$$


$$\therefore KCL: \frac{V_s - V_B(t)}{R} = \frac{1}{L} \int_{-\infty}^t V_B(t) dt + C \frac{dV_B(t)}{dt}$$

$$(diff) \Rightarrow C \frac{d^2 V_B(t)}{dt^2} + \frac{1}{R} \frac{dV_B(t)}{dt} + \frac{1}{L} V_B(t) = 0$$

$$\Rightarrow \boxed{\frac{d^2 V_B(t)}{dt^2} + \frac{1}{RC} \frac{dV_B(t)}{dt} + \frac{1}{LC} V_B(t) = 0}$$

[b]  $|V_s(t=0^+) = V_B$

$$|i_R(t=0^+) = \frac{V_s - V_B}{R}$$

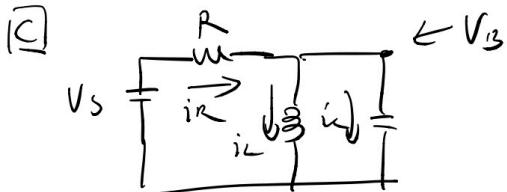

$$KCL @ t=0^+: i_R = i_L + i_C$$

$$\Rightarrow \frac{V_s - V_B}{R} = \frac{V_s}{R} + i_C$$

$$\Rightarrow i_C = -\frac{V_B}{R} = C \frac{dV_B}{dt} \Big|_{t=0^+} \Rightarrow \boxed{\frac{dV_B}{dt} \Big|_{t=0^+} = -\frac{V_B}{RC}}$$

d

$$\left\{ \begin{array}{l} s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \\ \frac{1}{RC} = \frac{10^9}{5 \times 4} = 5 \times 10^7 \\ \frac{1}{LC} = \frac{(10^9)^2}{400 \times 4} = (2.5 \times 10^7)^2 \end{array} \right.$$

$$\therefore s^2 + 5 \times 10^7 s + (2.5 \times 10^7)^2 = 0$$

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$\therefore \left\{ \begin{array}{l} \omega_n = 2.5 \times 10^7 \\ \zeta = 1 \end{array} \right. \rightarrow \text{critical damp}$$

Q  $V_s(t) = k_1 e^{s_1 t} + t k_2 e^{s_2 t}$

$$\textcircled{1} V_s(t=0) = V_B = \boxed{k_1 = 5}$$

$$\textcircled{2} \frac{dV_s}{dt} \Big|_{t=0} = - \frac{V_B}{RC} = - \frac{5}{5 \times 4} \times 10^9 = - 2.5 \times 10^8 = s_1 k_1 + k_2$$

$$\Rightarrow -2.5 \times 10^8 = 5 \times (-2.5 \times 10^7) + k_2$$

$$\Rightarrow \boxed{k_2 = 1.25 \times 10^8 - 2.5 \times 10^8 = -1.25 \times 10^8}$$

$$\therefore \boxed{V_s(t) = 5 e^{-2.5 \times 10^7 t} - t \cdot (1.25 \times 10^8) e^{-2.5 \times 10^7 t}}$$

$$= (5 - 1.25 \times 10^8 t) e^{-2.5 \times 10^7 t}$$

田

$$V_o(t) = (5 - 1.25 \times 10^8 t) e^{-2.5 \times 10^7 t}$$

To find its minimum value, take derivative:

$$V'_o(t) = (-1.25 \times 10^8) e^{-2.5 \times 10^7 t} - 2.5 \times 10^7 (5 - 1.25 \times 10^8 t) e^{-2.5 \times 10^7 t}$$

$$V'_o(t) = 0, \text{ get:}$$

$$-1.25 \times 10^8 = 2.5 \times 10^7 (5 - 1.25 \times 10^8 t)$$

$$\Rightarrow 1.25 \times 10^8 = 2.5 \times 1.25 \times 10^{15} t - 1.25 \times 10^8$$

$$\Rightarrow 2.5 \times 10^8 = 2.5 \times 1.25 \times 10^{15} t$$


$$\Rightarrow t = \frac{1}{1.25 \times 10^7} = 8 \times 10^{-8}$$

∴ Minimum of  $V_o(t)$  is at  $t = 8 \times 10^{-8}$ .

$$\therefore V_{o,\min} = V_o(t=8 \times 10^{-8}) = \left. \frac{(5 - 1.25 \times 10^8 t)}{e^{-2.5 \times 10^7 t}} \right|_{t=8 \times 10^{-8}}$$

$$= \frac{5 - 1.25 \times 8}{e^{2.5 \times 8 \times 10^{-7}}} = \frac{-5}{e^2} \approx -0.677 \ll 5.$$

∴ plot

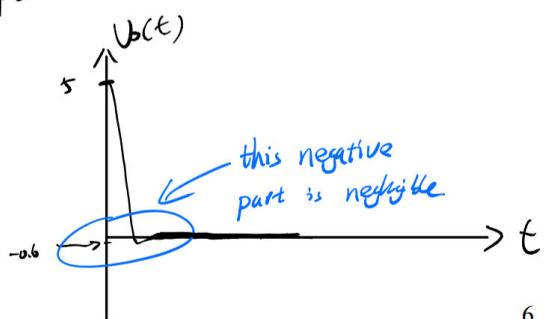

**Problem 2:**

- (a) Determine the Thevenin's equivalent of the circuit shown in Figure 2, looking into 1-1'.
- (b) If a 10 Ohm resistance is connected between the terminals 1 and 1', how much current will flow through it, and in which direction? **Hint:** Use the Thevenin's equivalent.


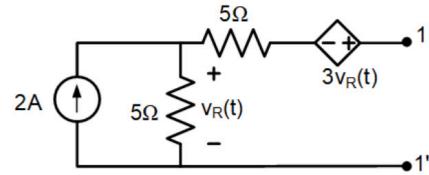
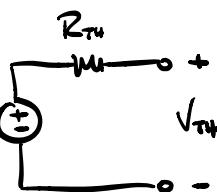
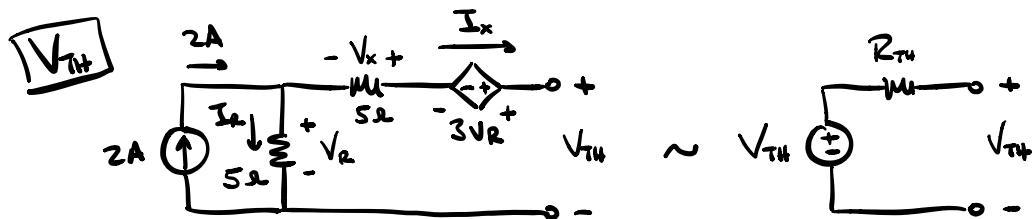
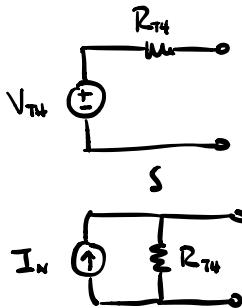


Figure 2

(12 + 6 = 18 points)

**Solution:**

(a) Compute the Thevenin Equivalent.

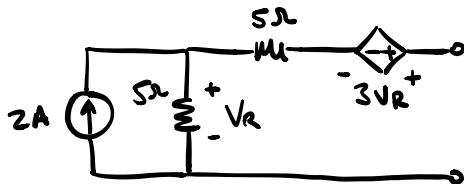

$I_x = 0 \text{ A}$  because no current flows

through an open circuit.

Via Ohm's Law,  $V_x = -5I_x = 0$ .

Applying KVL, it follows that:


$$V_{TH} = 3V_R + V_x + V_R = 4V_R$$

Applying KCL, it follows that:

$$2 \text{ A} = I_x + I_R = I_R$$

$$V_R = 5I_R = 10 \text{ V}$$
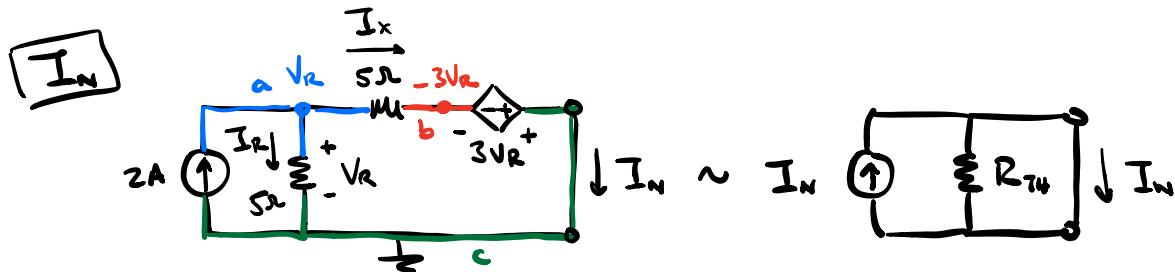
$$\text{Hence, } V_{TH} = 40 \text{ V.}$$



Apply KVL. (Definition of voltage difference.)

$$V_{cb} = V_c - V_b = 3V_R \rightarrow V_b = -3V_R$$

Apply KCL.  $V_a - 0 = V_R$      $V_b - 0 = -3V_R$



$$\begin{aligned} 2 &= I_R + I_x \\ &= \frac{V_R}{5} + \frac{V_R - (-3V_R)}{5} = V_R \end{aligned}$$

and  $I_x = I_N$  implies that:

$$I_N = \frac{V_R - (-3V_R)}{5} = \frac{8}{5} A$$

$$R_{T4} = \frac{V_{ta}}{I_N} = \frac{40V}{8/5A} = 25 \Omega$$

$R_{Th}$

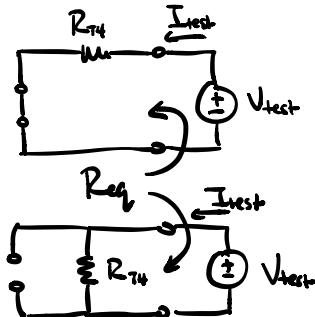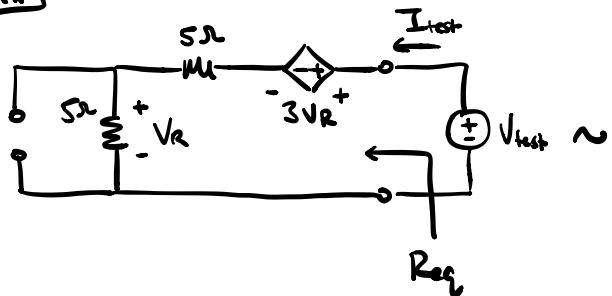

Via Thevenin's Theorem and Ohm's Law,

$$R_{Th} = R_{eq} = \frac{V_{test}}{I_{test}}$$


Apply KVL (and Ohm's Law).

$$\begin{aligned} V_{test} &= 3V_R + 5I_{test} + 5I_{test} \\ &= 3(5I_{test}) + 5I_{test} + 5I_{test} \\ &= 25I_{test} \end{aligned}$$

$$\downarrow$$


$$R_{Th} = 25\Omega = \frac{V_{Th}}{I_{in}}$$

Alternatively, apply a source transform.

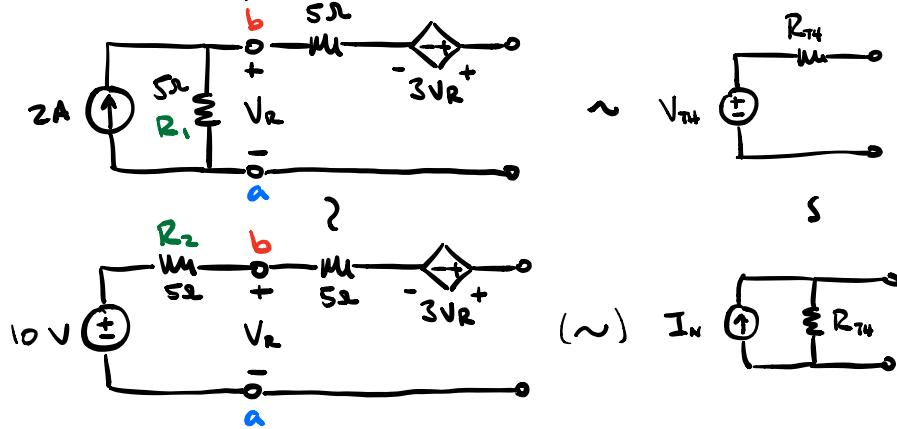

Note.  $V_R = V_{ba}$  does not change. The original resistance ceases to exist just as the current source ceases to exist under Thévenin's transform.

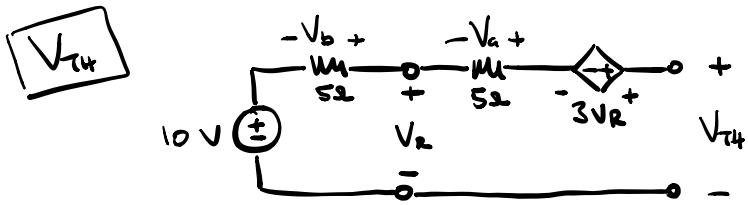Via the transitive property of the equivalence relation ( $\sim$ ), the source-transformed circuit can be represented by the same Thévenin / Norton equivalent.




No current flows in the open circuit.

Apply KVL, we have:

$$V_R = 10 + V_b = 10 \text{ V}$$
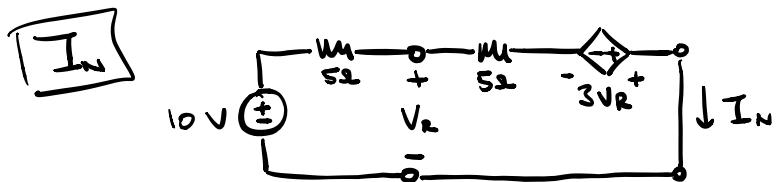
$$\begin{aligned} V_{Th4} &= 3V_R + \cancel{V_a} + \cancel{V_b} + 10 \\ &= 40 \text{ V} \end{aligned}$$



Applying KVL, it follows that:

$$V_R = 10 - 5I_N$$


$$10 = 5I_N + 5I_N - 3V_R$$

$$= 10I_N - 3(10 - 5I_N)$$

$$= 25I_N - 30$$

$$I_N = \frac{40}{25} = \frac{8}{5} \text{ A}$$

$R_{Th}$

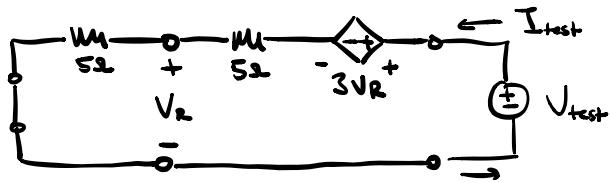

Apply KVL (and Ohm's Law).

$$V_R = 5 I_{test}$$

$$\begin{aligned} V_{test} &= 3V_R + 5I_{test} + 5I_{test} \\ &= 25 I_{test} \end{aligned}$$

$$R_{Th} = 25 \Omega = \frac{V_{Th}}{I_n}$$