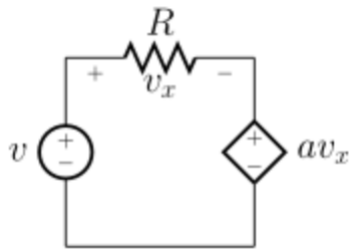


Today:

- Review Quiz #3 answers
- Ideal transformers
- Resistive networks
- Example Questions
- Magnetism review

(https://www.ieee.li/pdf/introduction_to_power_electronics/chapter_12.pdf)

Quiz #3 Review:



Q2b.) not solvable

if $I = 1A$ was provided?

$$\text{KVL: } V = IR + aV_x$$


$$V_x = IR$$

$$\rightarrow V = IR + aIR = (1+a)IR$$

$$V = 100V, \quad R = 20\Omega, \quad \underline{I = 1A}$$

$$100 = (1+a)20 \rightarrow \boxed{a=4} \star$$

Inductance (Sections 3.4-3.7)

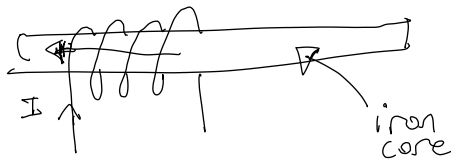

magnetic field direction
determined by the
"right-hand rule"

$$\boxed{V = L \frac{di}{dt}}$$

• when current changes ($\frac{di}{dt} \neq 0$)
the resulting magnetic flux, Φ , changes

• time-varying magnetic flux in a coil induces a voltage across the coil

What happens if $I = 1A$ (constant), what is the voltage across the inductor?

$$\underline{V = 0}$$

$$C = \frac{\epsilon A}{d}$$

② Energy stored in an inductor

$$E_{\text{capacitor}} = \frac{1}{2} CV^2$$

$$P = IV$$

$$E_{\text{inductor}} = \int P \cdot dt$$

* provide: $i(t=0^-) = 0$ (initial condition)


$$E_{\text{inductor}} = \int_0^t P \cdot dt$$

$$P = IV = i(t) \times \left(L \frac{di}{dt} \right)$$

$$E_{\text{inductor}} = \int_0^t i(t) \times L \frac{di}{dt} dt = \int_0^t i(t) \times L di$$

$$= \frac{1}{2} L i^2$$

Example #1: $V = L \frac{di}{dt}$

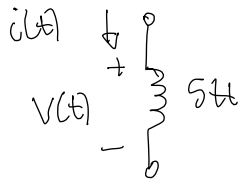

① $t=0 \rightarrow t=2$:

$$\frac{di}{dt} = \frac{3}{2} \rightarrow$$



$$V = L \frac{di}{dt} = (5H) \times \frac{3}{2} = 7.5$$

② $t=2 \rightarrow t=4$:


$$\frac{di}{dt} = 0 \Rightarrow V = 0$$

③ $t=4 \rightarrow t=5$:
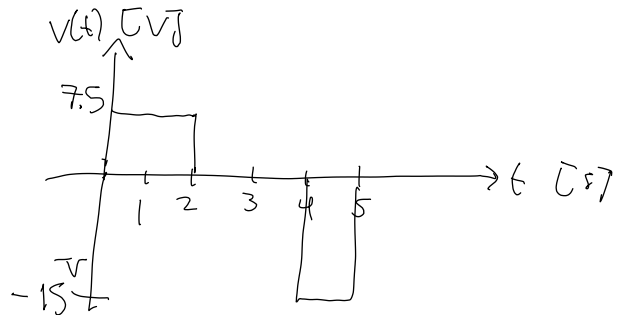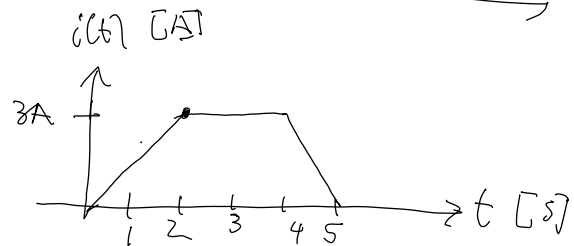
$$\frac{di}{dt} = -3 \rightarrow V = 5 \times (-3) = -15V$$




$$P(t) = i(t) \times V(t) \text{ [W]}$$

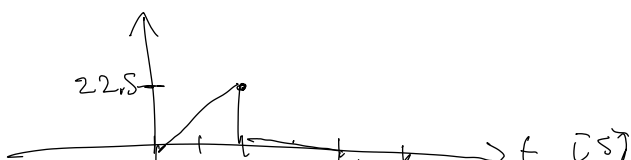

$$-45 \frac{W}{s} \quad 2 \quad 4 \quad 5$$

$$E(t) = \int P \cdot dt$$


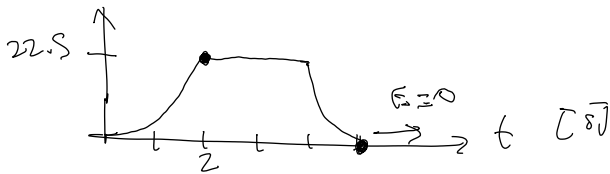


$$t=2: E_1 = \int_0^2 P(t) dt = \int_0^2 \left(\frac{22.5}{2} t \right) dt = \frac{22.5}{2} \times \frac{1}{2} t^2 \Big|_0^2 = \underline{\underline{22.5 J}}$$


$$t=4 \rightarrow t=5:$$

$$E_2 = \int_4^5 (45t - 22.5) dt = \left[\frac{45t^2}{2} - 22.5t \right] \Big|_4^5 = \boxed{-22.5 J}$$

Example #2

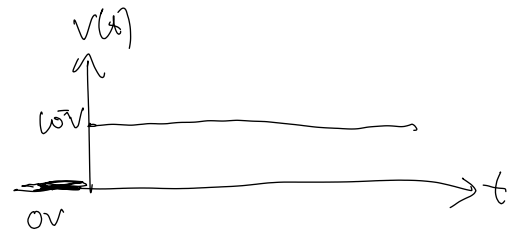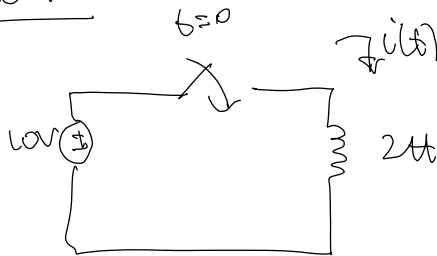
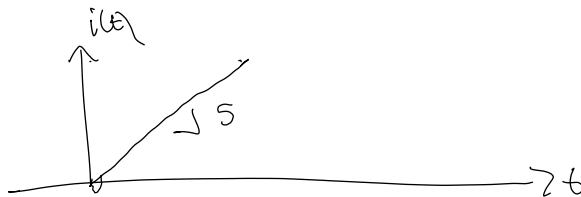
$$V = L \frac{di}{dt} \rightarrow \frac{di}{dt} = \frac{V}{L} = \frac{10V}{2H} = 5$$




What happens as $t \rightarrow \infty$?


$$i(t) \rightarrow \infty$$

not realistic.

↳ circuit break, i cannot ∞

Example #3:

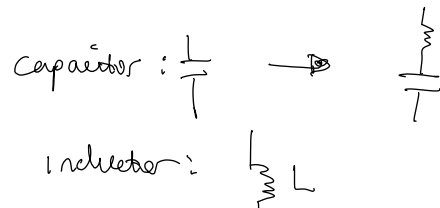

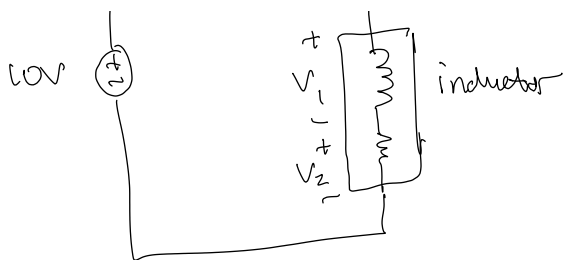


R_{par} parasitic resistance


$$V(t) = iR_{par} + L \frac{di}{dt}$$

outside of scope of class
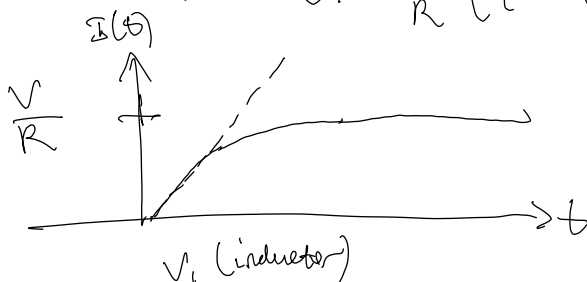
$$I(t) = \frac{V}{R} \left(1 - e^{-\frac{R_{par}}{L}t} \right)$$



$$I(\infty) = \frac{V}{R}$$

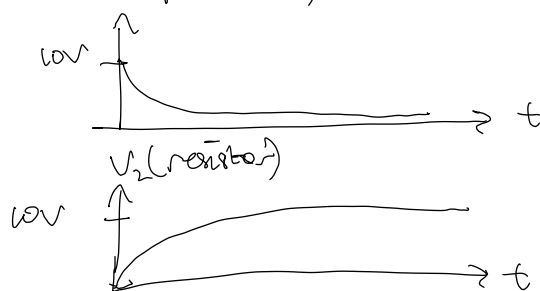


* called:

resistance-limited circuit

Transformers

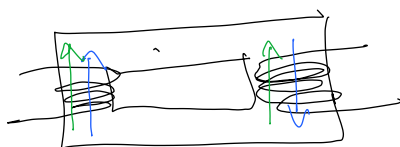
(Ideal transformer: 14.5
↳ for EM review: 14.1-14.4)



* aids
* opposing

(direction of \vec{B} determined by right hand rule)

① aids:

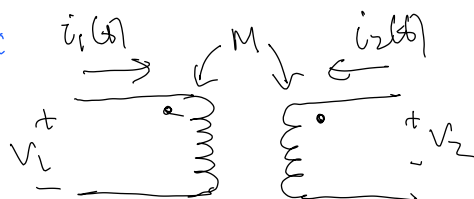


$$V_1 = L_1 \frac{di_1}{dt} + M_{21} \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M_{12} \frac{di_1}{dt}$$

$$Note: M_{12} = M_{21} = M$$

② opposing:

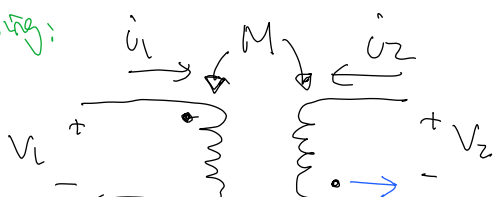


" i_2 flowing out of the dot "

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

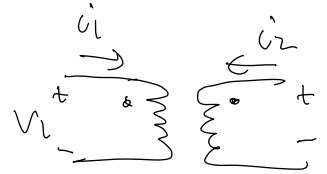Example #4:

$$L_1 = 1H, \quad L_2 = 2H, \quad M = 1H$$



$$i_1(t) = \sin(10t) [A] \quad i_2(t) = \frac{1}{2} \sin(10t) [A]$$

What is $V_1(t)$ & $V_2(t)$?

$$\begin{aligned} V_1(t) &= 15 \cos(10t) [V] \\ V_2(t) &= 20 \cos(10t) [V] \end{aligned}$$

note: $H \equiv \Omega \cdot s$
(for units)

Ideal Transformers (Section 14.5)

* coupling coefficient

$$k = \frac{\sqrt{L_1 L_2}}{M} \quad (0 \leq k \leq 1)$$

$k=1$: perfect coupling

* ideal transformer we assume perfect coupling

$$V_1(t) = N_1 \frac{d\Phi_1}{dt} \quad V_2(t) = N_2 \frac{d\Phi_2}{dt}$$

$$\Phi_1 = \Phi_2 = \Phi$$

$$V_2(t) = N_2 \frac{d\Phi}{dt} = N_2 \left(\frac{V_1}{N_1} \right) = \frac{N_2}{N_1} V_1$$

$$\frac{N_s}{N_p} \quad (\text{secondary})$$

$$\frac{N_p}{N_p} \quad (\text{primary})$$


$$n = \frac{N_2}{N_1} \quad (\text{turns ratio})$$

$$i_2 = \frac{-i_1}{\left(\frac{N_2}{N_1} \right)} = \frac{-N_1}{N_2} i_1 = \frac{-1}{n} i_1$$

convention:



textbook:

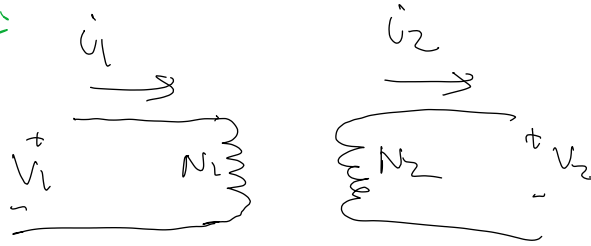

$$i_2 = \frac{1}{n} i_1 = \frac{N_1}{N_2} i_1$$

Office hours today:

Thursday (4/8) 1-2pm PDT (weekly)

4:30-5pm PDT (today only)

using same zoom links as
discussion