

1-

$$(a) \quad v_1 = 5 - 3 = 2$$

$$v_2 = -1 + v_1 = 1$$

$$v_3 = 1 + 3 = 4$$

$$(b) \quad v_1 = -2 - 3 = -5$$


$$v_2 = v_1 = -5$$

$$v_3 = v_2 + 5 = 0$$

$$i_2 = 2 - 1 - (-1) = 2$$

$$i_3 = -1$$


2.

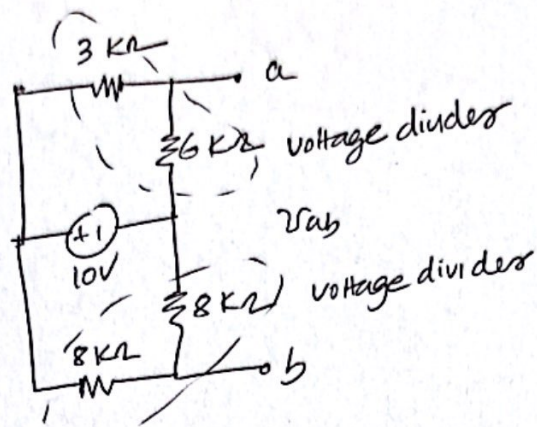

Determining $V_{oc} = V_{ab}$

$$V_{ab} = +10 \times \frac{6}{3+6} - \frac{10 \times 8}{8+8} = \frac{20}{3} - 5 = +\frac{5}{3} \text{ volts}$$

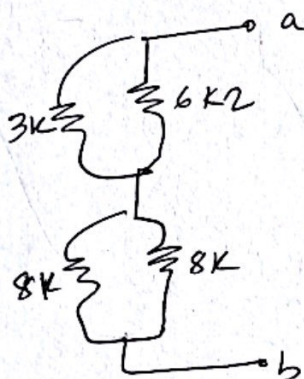
With the 10V source replaced by a short circuit, the circuit reduces to




$$R_{th} = 3 \parallel 6 + 8 \parallel 8 = 2 + 4 = 6 \text{ k}\Omega$$

$$I_{sc} = \frac{V_{oc}}{R_{th}} = \frac{5/3}{6 \text{ k}} = \frac{5}{18} \text{ mA}$$

Thevenin Equivalent

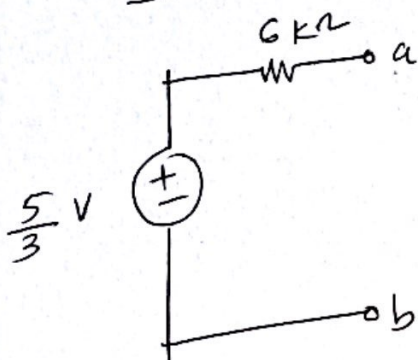


Norton Equivalent

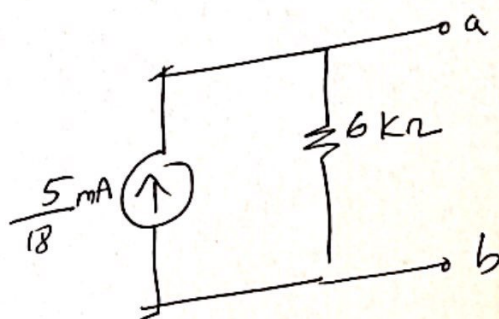

Problem 3

Solution to mid term problem

Subm Mid Term problem 1

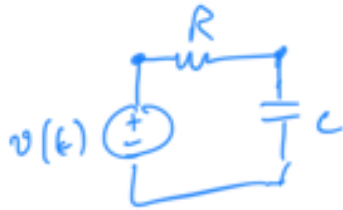

apply KVL

$$\frac{v_c(t) - v(t)}{R} + C \frac{dv_c(t)}{dt} = 0$$

rearrange the eqn. and write $v(t) = t$

$$RC \frac{dv_c(t)}{dt} + v_c(t) = t \quad \dots \dots \textcircled{1}$$

We try a particular solution of

$$\text{the form } v_{cp}(t) = A + Bt \quad \dots \dots \textcircled{2}$$

where A, B are constants to be determined

Substtuting $\textcircled{2}$ in $\textcircled{1}$ we get

$$RCB + A + Bt = t$$

$$\therefore B = 1$$

$$A = -RC$$

Hence the particular solution is

$$v_{cp}(t) = -RC + t$$

The homogenous eqn has a solution

$$V_{ch}(t) = K_1 \exp[-t/RC]$$

[we use the complementary soln. as we know that without the forcing fn the capacitor voltage must decay]

The complete solution is

$$\begin{aligned} V_c(t) &= V_{ch}(t) + V_{cp}(t) \\ &= -RC + t + K_1 \exp(-t/RC) \end{aligned}$$


The initial condition at $t=0$ is

$$V_c(0) = 0 \quad \text{[given]}$$

$$\therefore 0 = -RC + K_1 \quad \therefore K_1 = RC$$

$$\begin{aligned} \therefore V_c(t) &= V_{cp}(t) + V_{ch}(t) = -RC + t + RC \exp[-t/RC] \\ &= t - RC [1 - \exp[-t/RC]] \quad \text{--- (3)} \end{aligned}$$

(b) sketch this fn

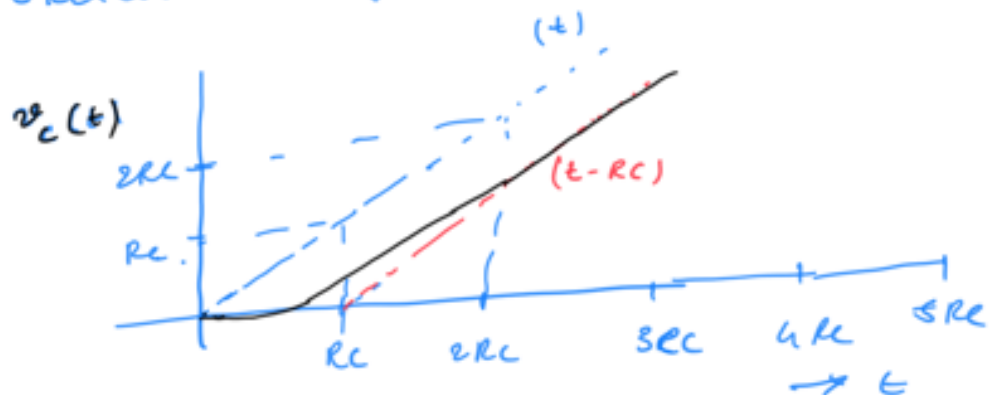

(c) as can be seen in (b), about 3.5 time constants is a sufficiently long time (sec)
 at long enough time, the capacitor voltage is

$$v_c(t) \approx t - RC = 5RC - RC \\ = 4RC = 4 \text{ volts.}$$

(d) the current flowing thru the capacitor must be supplied by the battery

$$i_c(t) = C \frac{dv_c(t)}{dt} \\ i_c(t) \Big|_{t=5RC} = C \frac{d}{dt} \left\{ -RC + t + R \exp\left(-\frac{t}{RC}\right) \right\} \\ = C \frac{d}{dt} \left[-RC + t \right] = C \\ = C \\ \approx 1 \text{ mA.}$$

(e) $P_{\text{battery}} = V_{\text{battery}} \times i_{\text{battery}}$

$$= t \times C \frac{d}{dt} \left[-RC + t + R \exp\left(-\frac{t}{RC}\right) \right] \\ = \left[0 + 1 - t \exp\left(-\frac{t}{RC}\right) \right]$$


$$= t \times C \left[1 - \frac{t}{10^{-3}} \exp(-t) \right] \quad \text{--- (4)}$$

(f): this power does two things

(a) heats up the resistor r
that power is $I_c^2 R$

(b) Stores energy in the Capacitor
that power is
 $P_{\text{batt}} = I_c^2 R$
↳ from eq (4)

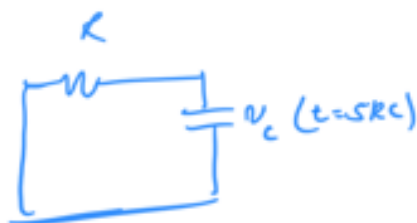(g) if the battery runs out the
battery is represented by a short
circuit




(h) at 10s

$$v_c \approx t - RC = 10 - 1 = 9$$

We now have a decaying voltage

$$v_c(t) = v_c(10) \cdot e^{-\frac{(t-10)}{RC}}$$

: ~~20~~ 9 e

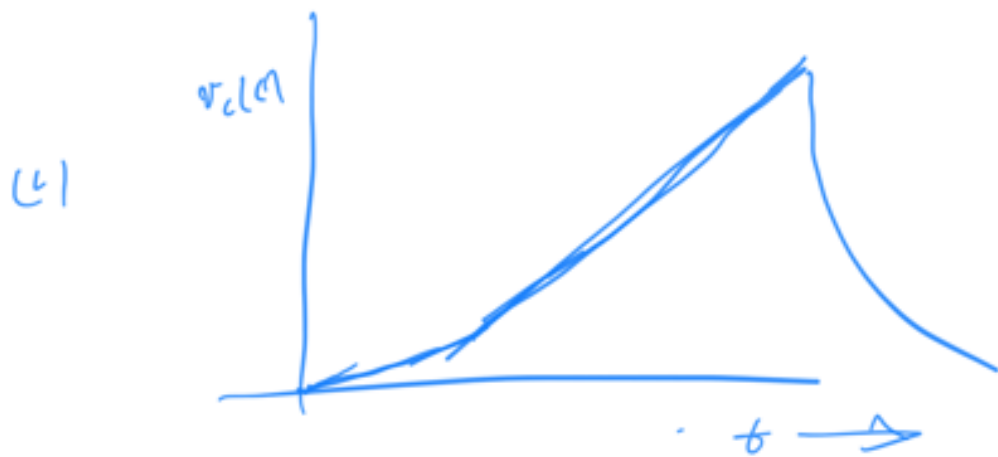

Problem 4


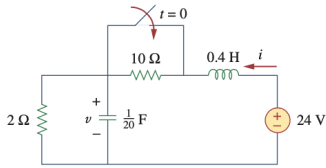



Figure 8.4
For Practice Prob. 8.1.

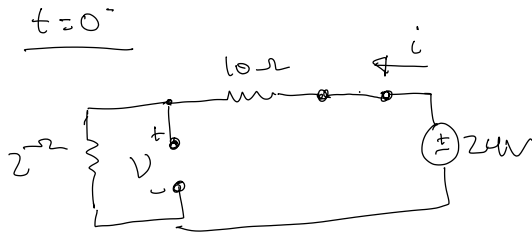Answer: (a) 2 A, 4 V, (b) 50 A/s, 0 V/s, (c) 12 A, 24 V.



$$i(0^+) = i(0^-) = \frac{24V}{(10\Omega + 2\Omega)} = \boxed{2A}$$
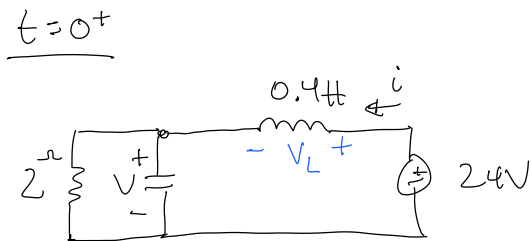
$$v(0^+) = v(0^-) = \frac{2\Omega}{2\Omega + 10\Omega} \times 24V = \boxed{4V}$$



$$i(0^+) = i(0^-) =$$

$$v_L = L \frac{di}{dt}$$

$$v(0^+) = v(0^-) = 4V$$


$$\Rightarrow v_L(0^+) = 20V \rightarrow$$

$$\frac{di(0^+)}{dt} = \frac{1}{L} v_L(0^+) = \left(\frac{1}{0.4H}\right) \times 20V$$

$$\boxed{\frac{di(0^+)}{dt} = 50 \frac{A}{s}}$$

$$\boxed{\frac{dv(0^+)}{dt} = 0}$$


$(t = \infty):$

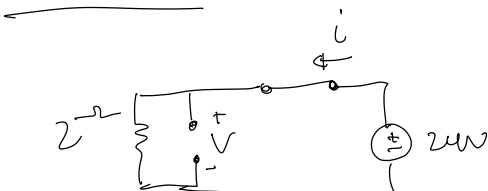


$$\boxed{i(\infty) = \frac{24V}{2\Omega} = 12A}$$

$$\boxed{v(\infty) = 24V}$$


Problem 5

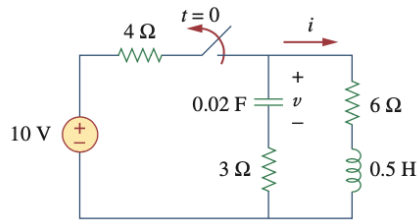

(a) $t \geq 0$:

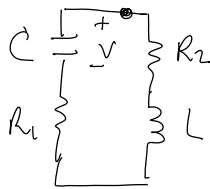

OR

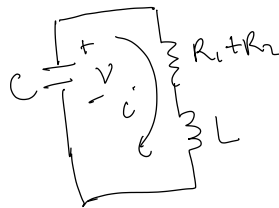

$$V = i(R_1 + R_2) + L \frac{di(t)}{dt}$$

$$\text{note: } i = -C \frac{dV}{dt}$$


$$\Rightarrow V = -C \frac{dV}{dt} (R_1 + R_2) - LC \frac{d^2 V(t)}{dt^2}$$

$$\boxed{\frac{d^2 V(t)}{dt^2} + \frac{R_1 + R_2}{L} \frac{dV(t)}{dt} + \frac{1}{LC} V(t) = 0}$$

$\frac{9}{0.5} = 18$

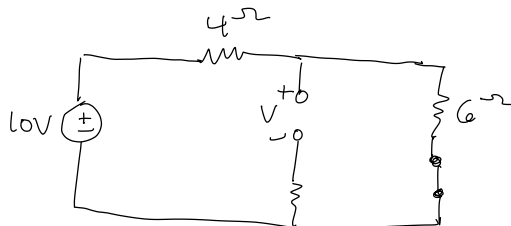(b) $V(0^+)$:


$$V(0^+) = V(0^-) = \frac{6\Omega}{4\Omega + 6\Omega} 10V = \boxed{6V} = \frac{R_2}{R_2 + R_3} V_s$$



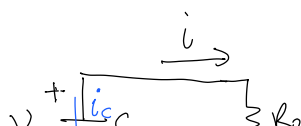
(c) $\frac{dV(0^+)}{dt}$:

$$\text{note: } i_c = C \frac{dV(0^+)}{dt}$$

$$i(0^+) = i(0^-) = \frac{10V}{4\Omega + 6\Omega} = 1A$$



note: $i_c = -i$

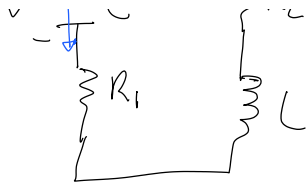

$$\frac{dV(0^+)}{dt} = -\frac{1}{C} i(t=0^+) \\ = \frac{-1}{0.02F} \times 1A = \boxed{-50 \frac{V}{s}}$$

(d) $t = \infty$

$$V(t \rightarrow \infty) \rightarrow 0$$

$$\boxed{V(\infty) \approx 0V}$$

(e)

$$\zeta = \frac{1}{2} \frac{R_{tot}}{\sqrt{L/C}} = \frac{1}{2} \frac{(3+6 \Omega)}{\sqrt{\frac{0.8H}{0.02F}}}$$

$$\boxed{\zeta = 0.9} \quad \text{underdamped}$$

(f)

resonant frequency : $\omega_0 = \frac{1}{\sqrt{LC}} = \boxed{10} \frac{\text{rad}}{s}$

natural

frequency : $\omega_n = \sqrt{1 - \zeta^2} \omega_0$
 $= 0.436 \times 10 = \boxed{4.36 \frac{\text{rad}}{s}}$

(g) roots :

$$s = -\sigma \pm j\omega_n$$

$$\sigma = \zeta \omega_0 = 0.9 \times 10 = 9 \frac{\text{rad}}{s}$$

$$\boxed{s_1, s_2 = -9 \pm j4.36}$$

(h)

$$V(t) = K_1 e^{-\sigma t} \cos(\omega_n t) + K_2 e^{-\sigma t} \sin(\omega_n t) + K_3$$

(i)

(1) $V(\infty) = 0 = K_3 \rightarrow \boxed{K_3 = 0}$

(2) $V(0^+) = 6V$

(3) $\frac{dV(0^+)}{dt} = -50 \frac{V}{s}$

$$\rightarrow (2) \quad V(0^+) = 6V = K_1 + K_2 \cdot 0 = K_1$$

$$\Rightarrow \boxed{K_1 = 6V}$$

$$\rightarrow (3) \quad \frac{dV(0^+)}{dt} = -50 \frac{V}{s} = \left[-\sigma K_1 e^{-\sigma t} \cos(\omega_n t) - K_1 e^{-\sigma t} (\omega_n \sin(\omega_n t)) \right] \Big|_{t=0} \\ + \left[-\sigma K_2 e^{-\sigma t} \sin(\omega_n t) + K_2 e^{-\sigma t} (\omega_n \cos(\omega_n t)) \right] \Big|_{t=0}$$

$$-50 \frac{V}{s} = -\sigma K_1 + K_2 \omega_n$$


$$\Rightarrow K_2 = \frac{-50 + \sigma K_1}{\omega_n} = \frac{-50 + (9)(6)}{4.36} = \\ = \frac{4}{4.36} \approx \boxed{0.92}$$

$$\Rightarrow V(t) \approx 6e^{-\sigma t} \cos(\omega_n t) + 0.92e^{-\sigma t} \sin(\omega_n t)$$

$$\sigma = 9$$

$$\omega_n = 4.36$$

(j)

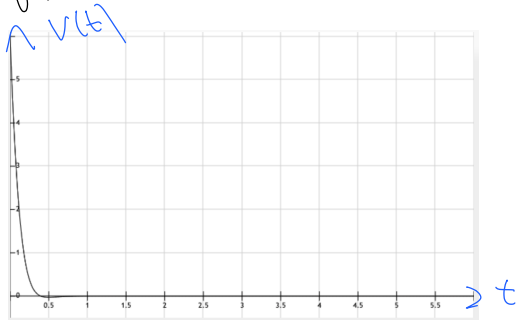

↑ minor overshoot

Zoomed-in:

