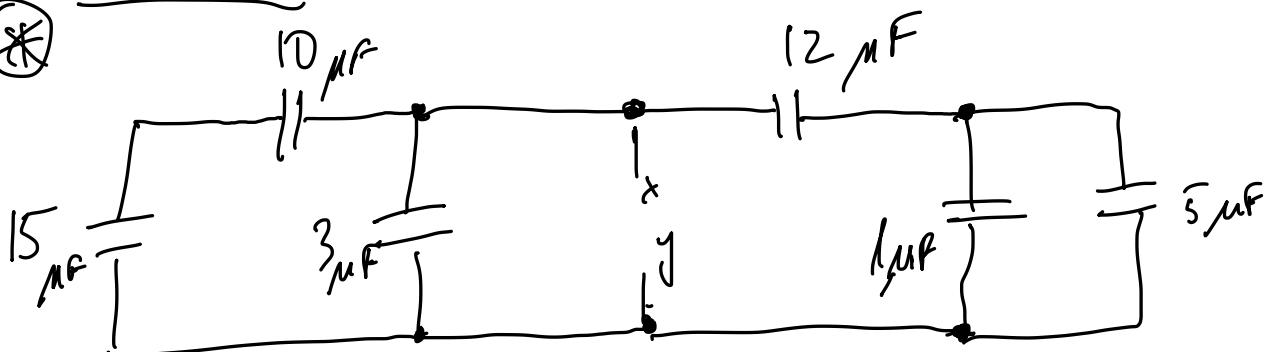


# Home Work 3:

What to


## Problem 1:



We have:  $(1\mu F \parallel 5\mu F) \Rightarrow C_{15} = 1\mu F + 5\mu F = 6\mu F$

$$(15\mu F \text{ series } 10\mu F) \Rightarrow C_{1510} = \frac{15 \times 10}{15+10} = 6\mu F \quad \left( \frac{1}{C_{1510}} = \frac{1}{15} + \frac{1}{10} \right)$$


We have a new circuit:

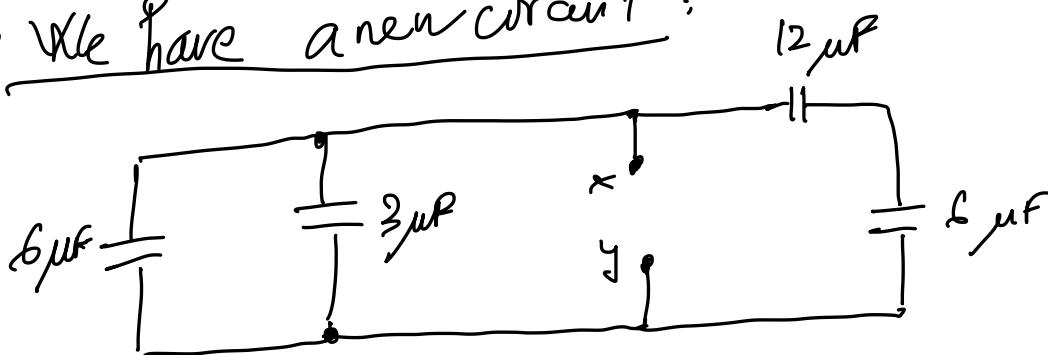

$$\text{Also, } (6\mu F \parallel 3\mu F) \Rightarrow C_{63} = 6 + 3 = 9\mu F$$



For the last part,  $(12\mu F \text{ series } 6\mu F)$
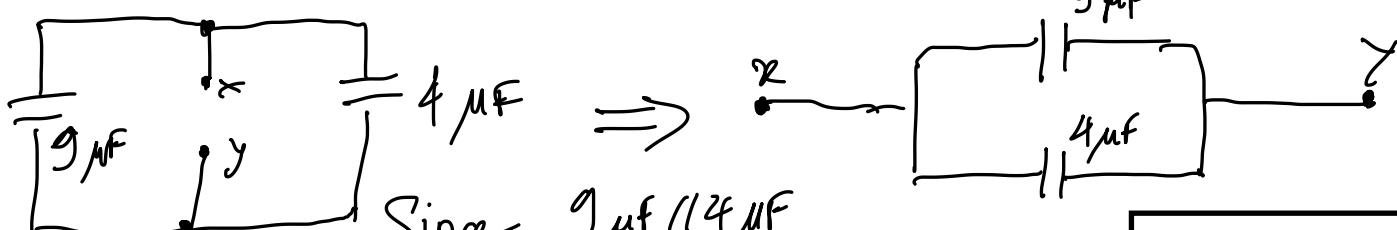
$$\Rightarrow C_{126} = \frac{12 \times 6}{12+6} = 4\mu F \Rightarrow \text{Continue having:}$$



Since  $9\mu F \parallel 4\mu F$
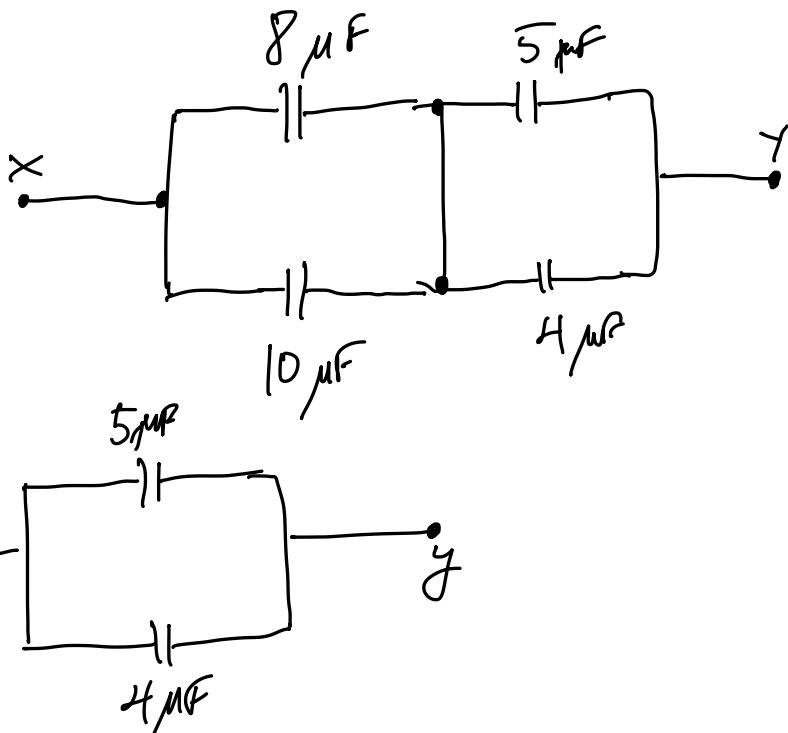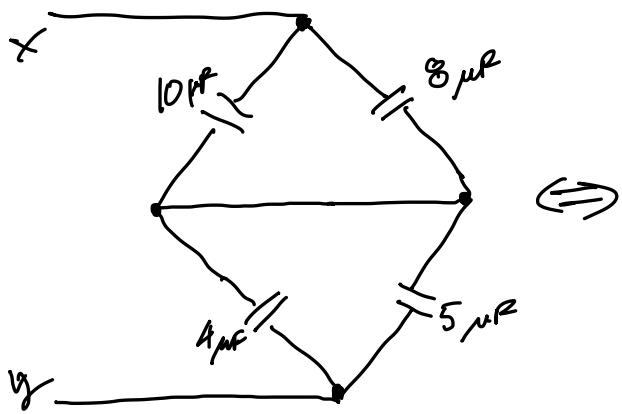
$$\Rightarrow C_{xy} = 9 + 4 = 13\mu F \Rightarrow C_{xy} = 13\mu F$$



$$\text{Since } (8 \mu\text{F} // 10 \mu\text{F}) \Rightarrow C_{810} = 8 + 10 = 18 \mu\text{F}$$

$$(5 \mu\text{F} // 4 \mu\text{F}) \Rightarrow C_{54} = 5 + 4 = 9 \mu\text{F}.$$

$$\Rightarrow \begin{array}{c} x \\ | \\ 18 \mu\text{F} \\ | \\ y \end{array} \quad \text{Since } 18 \mu\text{F} \text{ series } 9 \mu\text{F}$$

$$\Rightarrow C_{xy} = \frac{18 \times 9}{18 + 9} = 6 \mu\text{F} \quad \left( \frac{1}{C_{xy}} = \frac{1}{18} + \frac{1}{9} \right)$$


$$\boxed{\Rightarrow C_{xy} = 6 \mu\text{F}}$$

Problem 2: Given  $i_L(t=0) = -100mA = -0.1A$

a) What time  $t_x$  if

$$i = +100mA = 0.1A$$

We have:

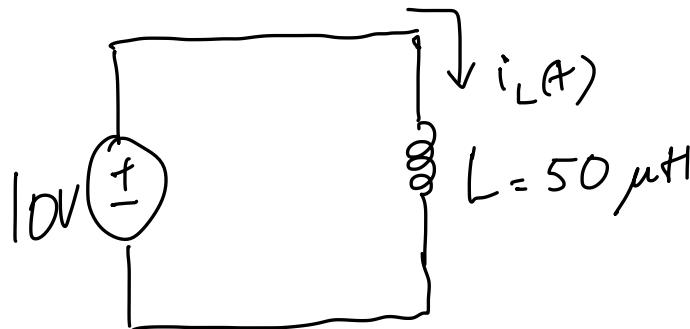

$$i_L(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i_L(t_0)$$

$\left\{ \begin{array}{l} \text{Since } v(t) = 10V \\ i_L(t_0 = 0) = -0.1A \end{array} \right.$

$$\Rightarrow i_L(t) = \frac{1}{L} \int_0^t 10 dt - 0.1 \quad (\text{A})$$

When  $i_L(t) = 0.1A$



$$\Rightarrow 0.1 + 0.1 = \frac{1}{50 \cdot 10^{-6}} \int_0^t 10 dt = 2 \times 10^4 \cdot 10t \Big|_0^t \quad (\text{A})$$

$$\Rightarrow 0.2A = 2 \times 10^5 t \Rightarrow t = \frac{0.2A}{2 \times 10^5} = 0.1 \times 10^{-5} \text{ (S)}$$


$$\Rightarrow t = 1 \times 10^{-6} \text{ (S)} \Leftrightarrow t = 1 \mu\text{s}$$

b) Because in this circuit, it only has 1 inductor that does not dissipate the energy. So the process of dissipation will not occur and the oscillation will happen for infinite time. This is not realistic in the real life. Practically, this circuit should have a series of resistance that absorb and dissipate energy to become a realistic model.

### Problem 3:

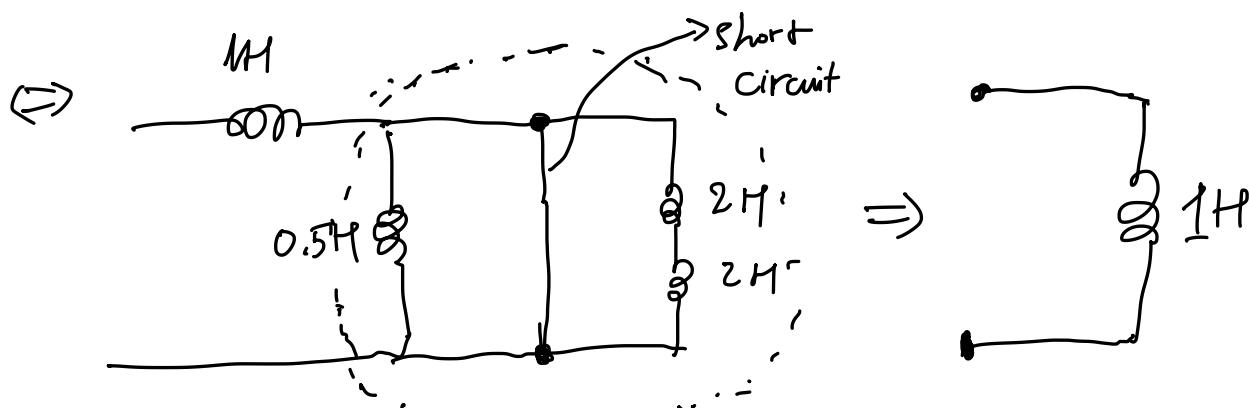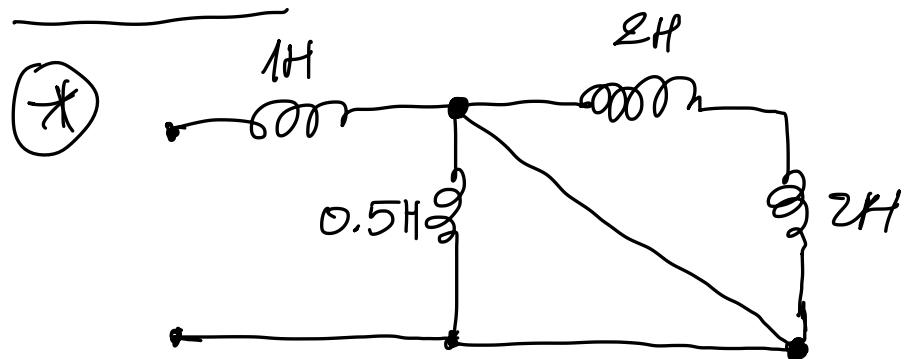


$$\Rightarrow L_{eq} = 1\text{H}$$

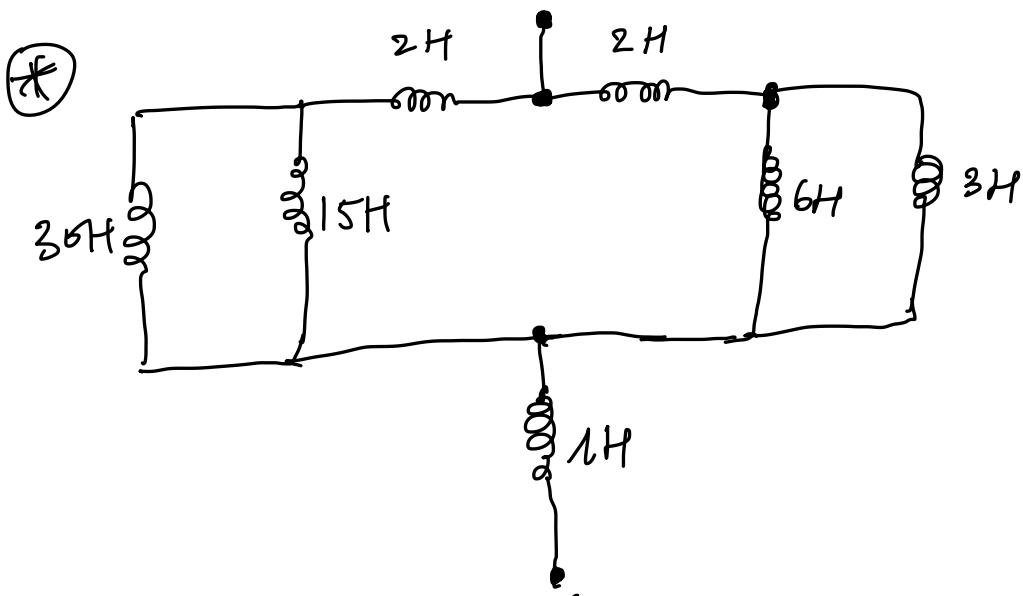

$$\text{Because } 30\text{H} \parallel 15\text{H} \Rightarrow \frac{1}{30+15} = \frac{1}{30} + \frac{1}{15} \Rightarrow L_{30+15} = \frac{30 \times 15}{30+15} = 10\text{H}$$

$$(6\text{H} \parallel 3\text{H}) \Rightarrow \frac{1}{L_{6+3}} = \frac{1}{6} + \frac{1}{3} \Rightarrow L_{6+3} = \frac{6 \times 3}{6+3} = 2\text{H}$$

$\Rightarrow$  We have a new circuit:

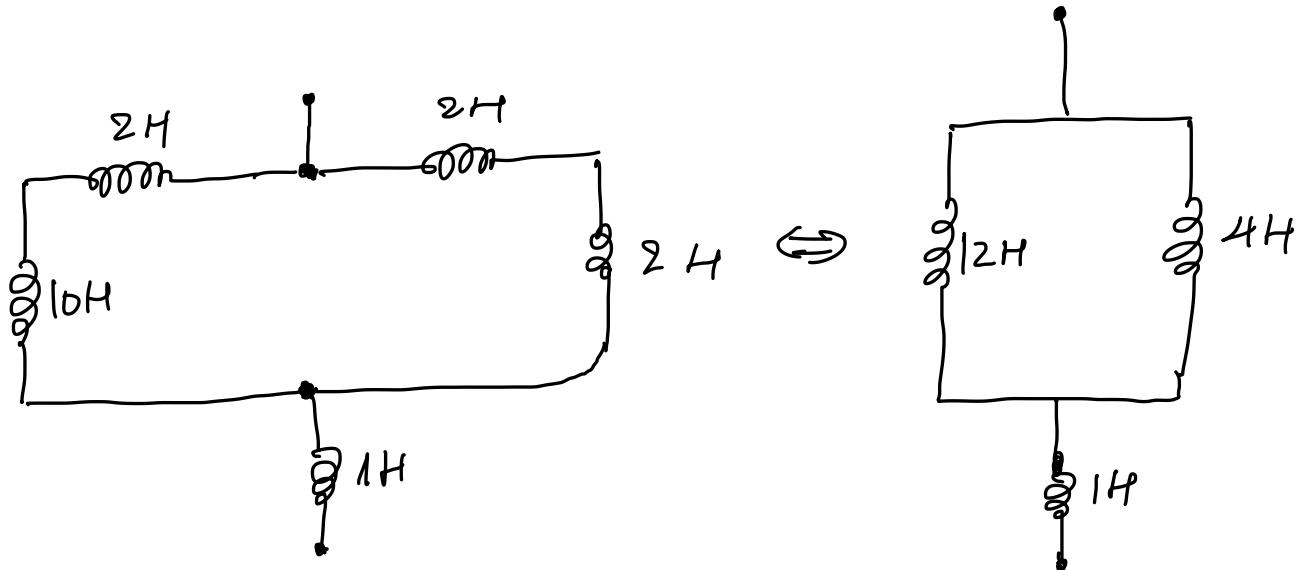


$$12H \parallel 4H \Rightarrow L_{124} = \frac{12 \times 4}{12 + 4} = 3H$$

$\Rightarrow$

$\Rightarrow L_{eq} = 3 + 1 = 4H$

The diagram shows a simplified circuit consisting of a vertical branch with an inductor labeled 3H in series with a resistor labeled 1H. To the right of this branch is an equation box containing the calculation  $L_{eq} = 3 + 1 = 4H$ .

Problem 4:

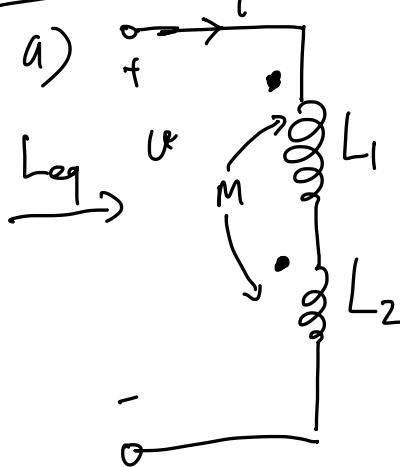

$$\text{Von Phasen: } \vartheta = L \frac{di}{dt}$$

$$U_1 = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt}$$

$$= L_1 \frac{di(t)}{dt} + M \frac{di(t)}{dt}$$


$$U_2 = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt}$$

$$= L_2 \frac{di(t)}{dt} + M \frac{di(t)}{dt}$$

$$\Rightarrow \vartheta = L_1 \frac{di(t)}{dt} + M \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + M \frac{di(t)}{dt}$$

$$= (L_1 + L_2 + 2M) \frac{di(t)}{dt} = L_{eq} \frac{di(t)}{dt}$$

$$\Rightarrow L_{eq} = L_1 + L_2 + 2M$$

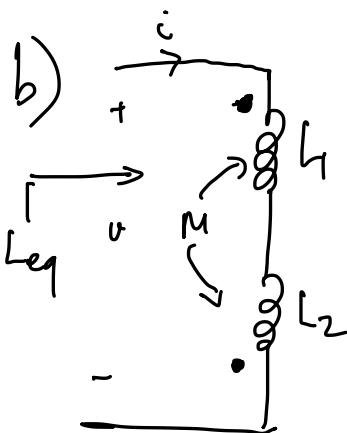

$$\text{Von Phasen: } U_1 = L_1 \frac{di_1(t)}{dt} - M \frac{di_2(t)}{dt}$$

$$= L_1 \frac{di(t)}{dt} - M \frac{di(t)}{dt}$$

$$U_2 = L_2 \frac{di_2(t)}{dt} - M \frac{di_1(t)}{dt}$$

$$= L_2 \frac{di(t)}{dt} - M \frac{di(t)}{dt}$$

$$\Rightarrow \vartheta = U_1 + U_2 = L_1 \frac{di(t)}{dt} - M \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} - M \frac{di(t)}{dt}$$

$$= (L_1 + L_2 - 2M) \frac{di(t)}{dt} = L_{eq} \frac{di}{dt} \Rightarrow L_{eq} = L_1 + L_2 - 2M$$

Problem 5: Ideal transformer with two coils.

$$R = 4 \Omega, \quad \phi = \phi_0 \sin \omega t \Rightarrow d\phi/dt = \phi_0 \omega \cos \omega t$$



We Have  $V_1 = N_1 \frac{d\phi}{dt} = N_1 \phi_0 \omega \cos \omega t$

$$\Rightarrow \boxed{\mathcal{E}_1(t) = N_1 \phi_0 \omega \cos(\omega t)} \quad (V) ; \text{ since } \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\text{since } \mathcal{E}_2(t) = \frac{N_2}{N_1} \mathcal{E}_1(t) = N_2 \phi_0 \omega \cos(\omega t) \quad (V)$$

$$\text{Because } \mathcal{E}_1(t) = L \frac{di_1}{dt} \Rightarrow \frac{di_1}{dt} = \frac{\mathcal{E}_1(t)}{L}$$

$$\Rightarrow \frac{di_1}{dt} = \frac{N_1 \phi_0 \omega \cos(\omega t)}{L}$$

$$\Rightarrow i_1(t) = \frac{N_1 \phi_0}{L} \cdot \sin(\omega t) \quad (A) \Rightarrow i_2(t) = \frac{N_1}{N_2} i_1(t)$$

$$\Rightarrow i_2(t) = \frac{N_1^2}{N_2} \frac{\phi_0}{L} \sin(\omega t) \quad (A)$$

We also have  $V_2(t) = i_2(t) \cdot R = 4i_2(t)$

$$\Rightarrow N_2 \phi w \cos wt = 4 \cdot \frac{N_1^2}{N_2} \cdot \frac{\phi_0}{L} \sin(wt)$$

$$\Rightarrow N_2^2 L \phi w \cos wt = 4 N_1^2 \phi_0 \sin wt$$

$$\Rightarrow L = \frac{4 N_1^2 \phi_0 \sin wt}{N_2^2 \phi_0 w \cos wt} = \frac{4 N_1^2}{w \cdot N_2^2} \operatorname{tg}(wt)$$

$$\Rightarrow i_1(t) = \frac{N_1 \phi_0}{L} \sin wt = \frac{N_1 \phi_0 \sin wt}{4 N_1^2 \operatorname{tg}(wt)} \cdot \frac{w N_2^2}{w N_2^2}$$

$$\Rightarrow i_1(t) = \boxed{\frac{\phi_0 w N_2^2 \cos wt}{4 N_1}}$$

Therefore:

$$\frac{\vartheta_1(t)}{i_1(t)} = \frac{N_1 \phi_0 w \cos(wt)}{N_2^2 \phi_0 w \cos(wt)} \times 4 N_1 = \frac{4 N_1^2}{N_2^2}$$


$$\Rightarrow \boxed{\frac{\vartheta_1(t)}{i_1(t)} = \frac{4 N_1^2}{N_2^2}}$$

$$\text{or } \operatorname{Req} = 4 \left( \frac{N_1}{N_2} \right)^2$$

↔ technique "reflection"

## Problem 6:

a)

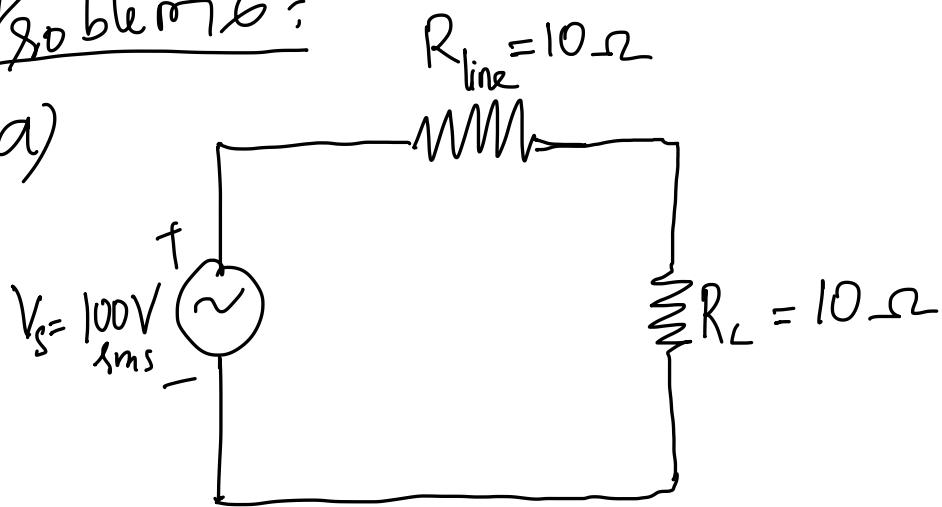

$$\text{We have: } I_L = \frac{V_s}{R_{\text{line}} + R_L} = \frac{100\text{V}}{(10 + 10)\Omega} = 5\text{A}$$

\* Power delivered by the source:

$$P_S = V_s I_L = 100 \times 5 = \boxed{500\text{ W}}$$

\* Power dissipated in the line resistance:


$$P_{\text{line}} = I_L^2 R_{\text{line}} = 5^2 \times 10 = \boxed{250\text{ W}}$$

\* Power delivered to the load:

$$P_L = I_L^2 R_L = 5^2 \cdot 10 = \boxed{250\text{ W}}$$

$\Rightarrow$  the efficiency is
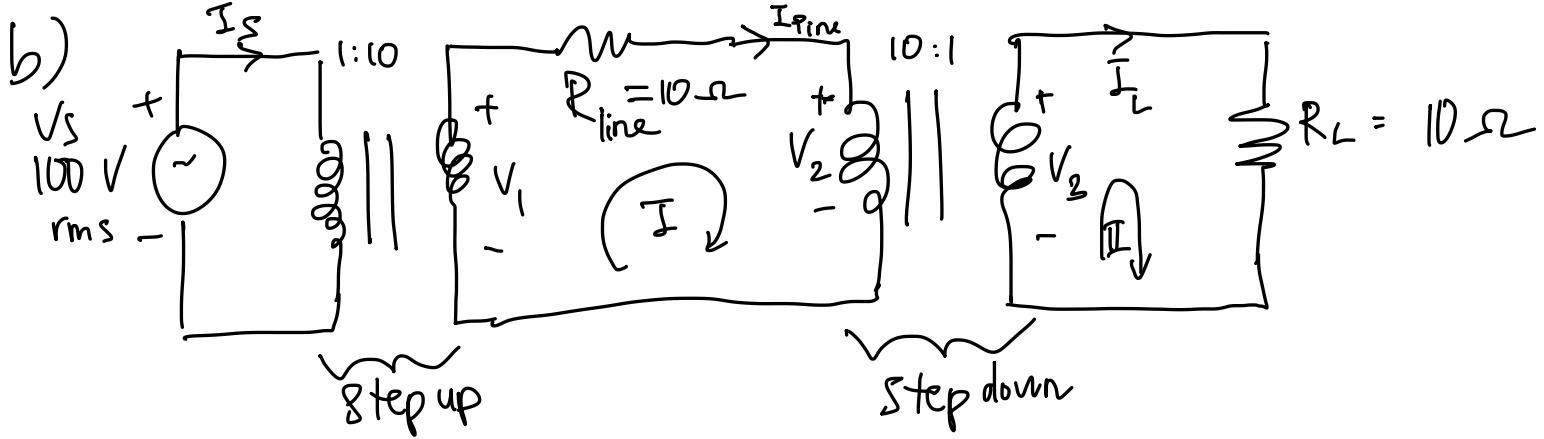
$$\eta = \frac{P_L}{P_S} \times 100 = \frac{250}{500} \times 100 = \boxed{50\%}$$



We have:

$$\frac{V_S}{V_1} = \frac{1}{10} \Rightarrow V_1 = 10V_S \quad (1)$$

also,  $\frac{I_S}{I_{\text{line}}} = \frac{10}{1} \Rightarrow I_S = 10I_{\text{line}} \Leftrightarrow I_{\text{line}} = \frac{I_S}{10} \quad (2)$

Apply KVC for I,  $V_1 = I_{\text{line}} \cdot R_{\text{line}} + V_2$

$$\text{From } (1) \text{ & } (2), \Rightarrow 10V_S = \frac{I_S}{10} \cdot R_{\text{line}} + V_2$$

$$\Rightarrow V_2 = 10V_S - \frac{I_S}{10} R_{\text{line}} \quad (3)$$

Besides,  $\frac{V_2}{V_3} = \frac{10}{1} \Rightarrow V_2 = 10V_3 ; \quad \frac{I_{\text{line}}}{I_L} = \frac{1}{10} \quad (4)$

$$\Rightarrow I_L = 10I_{\text{line}} . \text{ From } (2) I_{\text{line}} = \frac{I_S}{10} \Rightarrow I_S = 10I_{\text{line}}$$

$$\Rightarrow I_S = I_L \quad (5)$$

Apply KVL for II, We have:  $V_3 = I_L R_L$

$$\Rightarrow 10V_3 = 10I_L R_L . \text{ Since } V_2 = 10V_3 \text{ (from 4)}$$

$$I_S = I_L \text{ (from 5)} \quad (6)$$

$$\Rightarrow V_2 = 10 I_S R_L \text{. Since } V_2 = 10V_S - \frac{I_S}{10} R_{\text{line}} \text{ from (2)}$$

$$\Rightarrow 10V_S - \frac{I_S}{10} R_{\text{line}} = 10 I_S R_L$$

Plug  $V_S = 100V$ ,  $R_{\text{line}} = 10 \Omega = R_L$

$$\Rightarrow 10 \times 100 - \frac{I_S}{10} \cdot 10 = 10 \cdot I_S \cdot 10$$

$$\Rightarrow 1000 - I_S = 100 I_S \Rightarrow I_S = \frac{1000}{101} = 9.901 A$$

$\Rightarrow$  \* Power delivered by the source:

$$P_S = V_S \cdot I_S = 100V \times 9.901A = 990.1(W)$$

Also,  $I_S = I_L$  (from (6))

$\Rightarrow$  \* Power delivered to the load:

$$P_L = I_L^2 R_L = 9.901^2 A \times 10 = 980.3(W)$$

From (4),  $I_{\text{line}} = \frac{I_L}{10} = \frac{9.901}{10} = 0.9901(A)$


$\Rightarrow$  power dissipated in the line resistance:

$$P = I_{\text{line}}^2 R_{\text{line}} = (0.9901)^2 \times 10 \Omega = 9.803(W)$$

$\Rightarrow$  the efficiency:  $\eta = \frac{P_L \times 100}{P_S} = \frac{980.3}{990.1} \times 100 = 99.01\%$

$\Rightarrow \eta = 99.01\%$   $\Rightarrow$  the efficiency of delivering power to the load is increasing by using transformer.

## Problem 7:

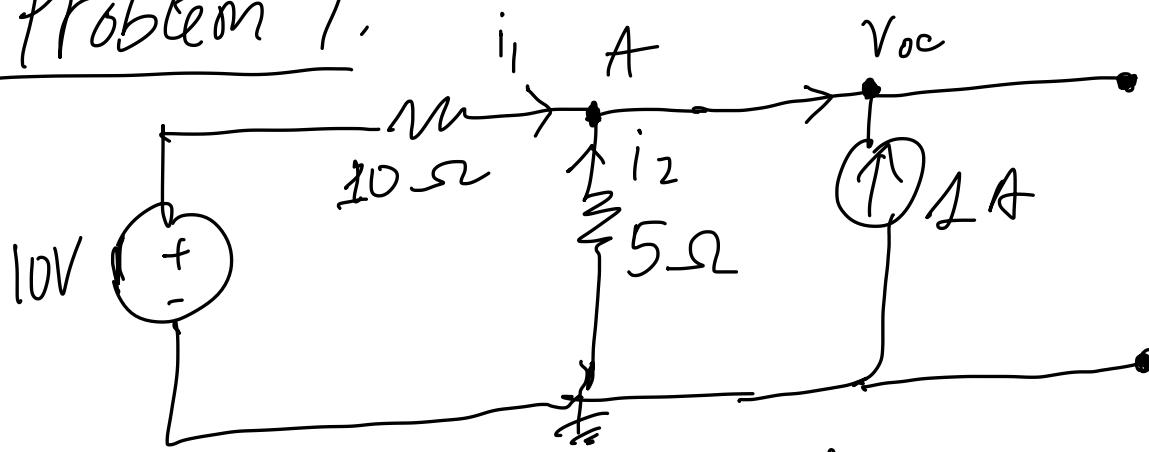

Apply KCL at A, we have:

$$i_1 + i_2 + 1 = 0$$

$$\frac{10 - V_{oc}}{10} + \frac{0 - V_{oc}}{5} + 1 = 0$$


$$\Rightarrow 10 - V_{oc} + 2(0 - V_{oc}) + 10 = 0$$

$$\Rightarrow 10 - V_{oc} - 2V_{oc} + 10 = 0$$

$$\Rightarrow 20 = 3V_{oc} \Rightarrow V_{oc} = \frac{20}{3}(V) = V_{th}$$

\* Finding the equivalent resistance:


We have the new circuit:

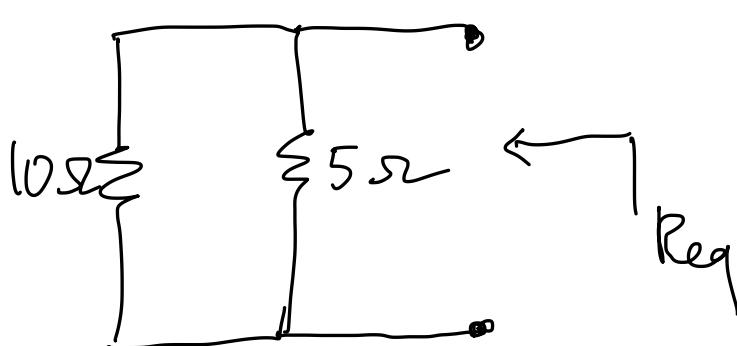

$$10\Omega // 5\Omega$$


$$\Rightarrow R_{eq} = \frac{5 \times 10}{5 + 10} = \frac{10}{3}(\Omega)$$

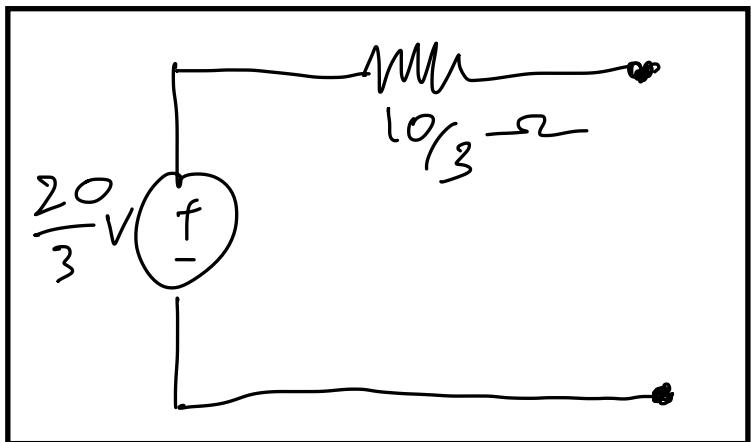⇒ We have the Thevenin's equivalent circuit:




$$\Rightarrow I_N = \frac{20}{3} \cdot \frac{3}{10} = 2A$$

⇒ The Norton's equivalent circuit is:

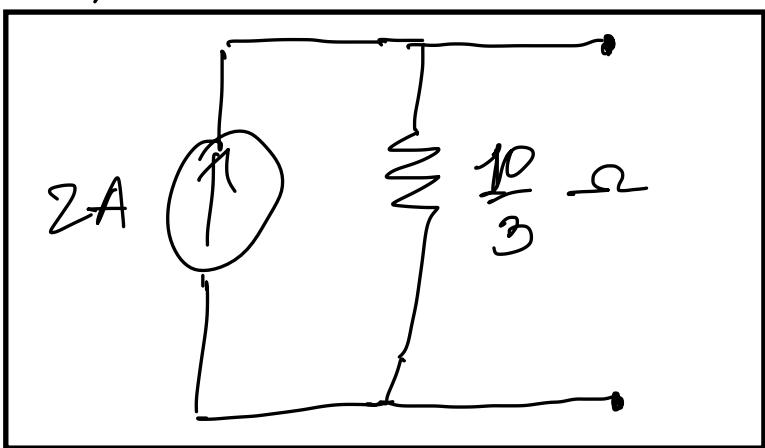

### Problem 8 :

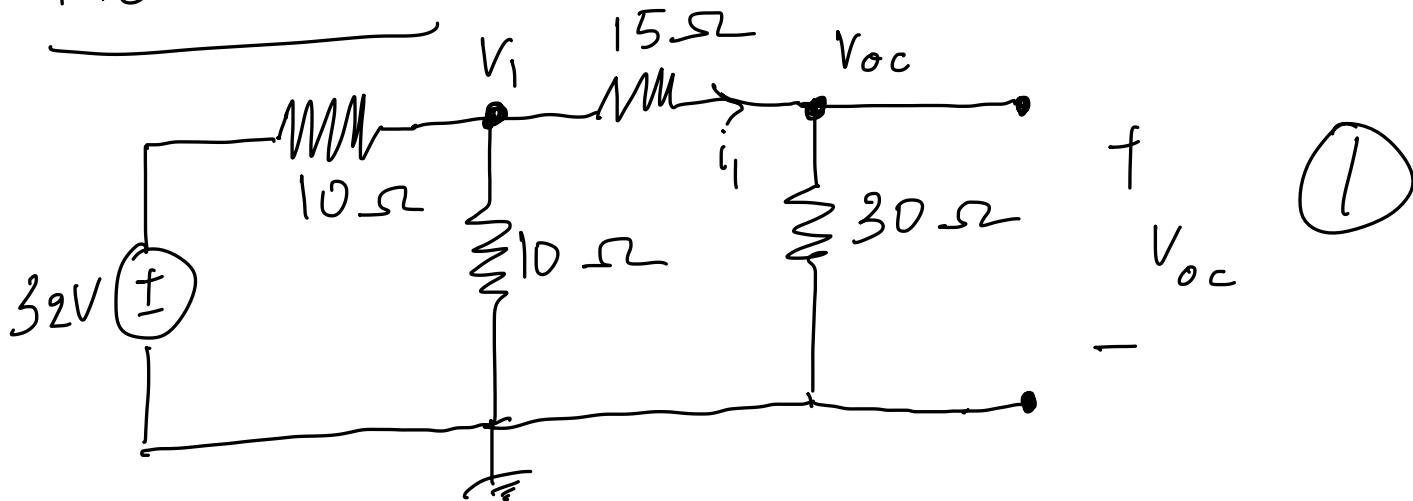


We have  $(15\Omega \text{ series } 30\Omega) \parallel 10\Omega$

$$\Rightarrow R_{15-30} = 15 + 30 = 45\Omega$$

$$\Rightarrow R_{15-30-10} = \frac{45 \times 10}{45 + 10} = \frac{90}{11} (\Omega)$$

We have the new circuit :

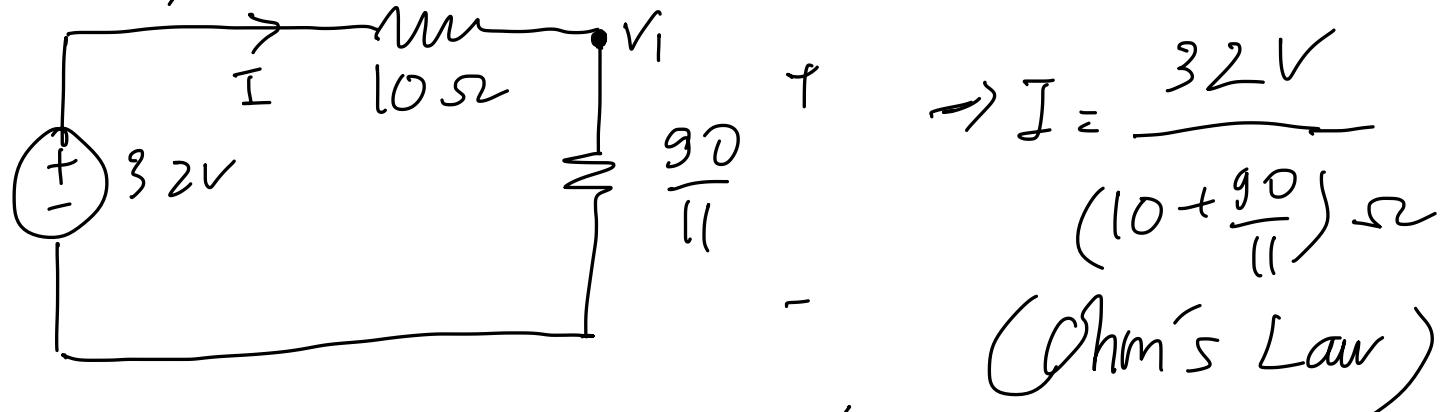

$$\Rightarrow V_1 = I \cdot \frac{90}{11} = \frac{32V}{(10 + \frac{90}{11})} \cdot \frac{90}{11} = 14.4(V)$$


Go back to circuit ①, We have  $V_1 = (15 + 30)i_1$

$$\Rightarrow i_1 = \frac{V_1}{45} (A) \text{ . Also } V_{oc} = i_1 \times 30\Omega$$


$$\Rightarrow V_{bc} = \frac{V_1}{45} \times 30 = \frac{2}{3} \times 14.4 = 9.6(V)$$
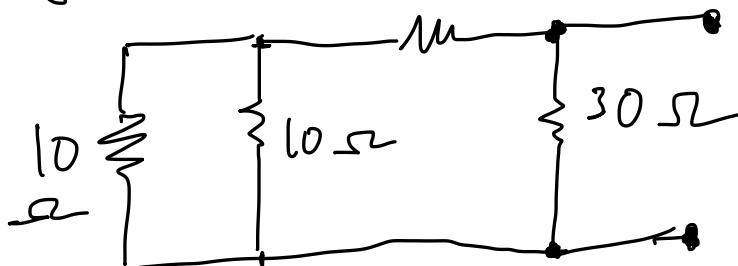
# Find the equivalent resistance:


We have a new circuit by shorting the voltage source:  $15\Omega$



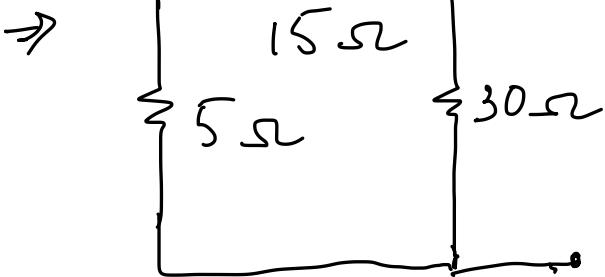Since  $10\Omega \parallel 10\Omega$   
 $\Rightarrow R_{10-10} = \frac{10 \times 10}{10+10} = 5\Omega$




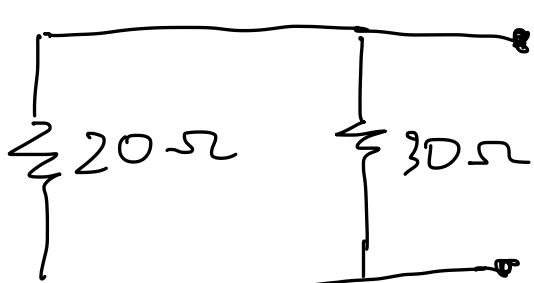Since  $15\Omega$  series to  $5\Omega$   
 $\Rightarrow R_{15-5} = 15 + 5 = 20\Omega$




$20\Omega \parallel 30\Omega$   
 $\Rightarrow R_{20-30} = \frac{20 \times 30}{20+30} = 12\Omega$

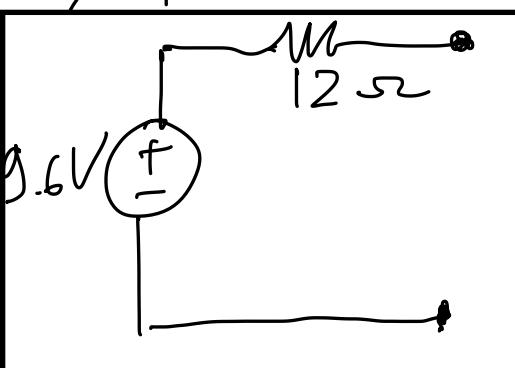$\Rightarrow$  The Thevenin equivalent circuit:




$$\Rightarrow I_N = \frac{9.6V}{12\Omega} = 0.8A$$

The Norton equivalent circuit:

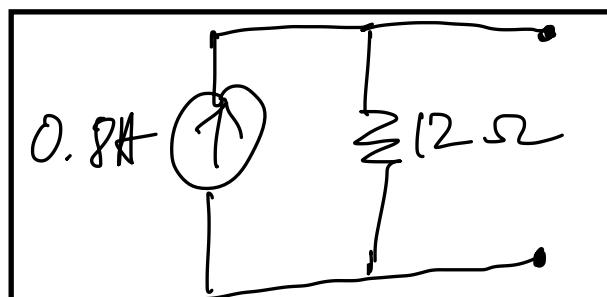

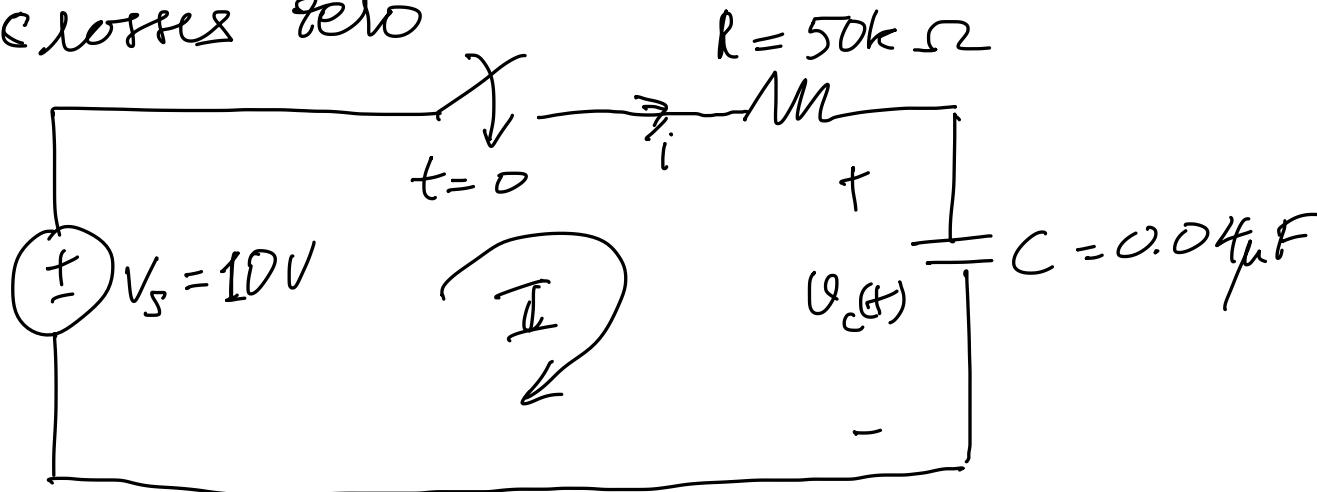Problem 9:  $v_c(0^+) = -10V$ . Find  $v_c(t)$ .

Determine the time  $t_0$  at which the voltage crosses zero



Apply KVC for loop I, we have: (at  $t=0^+$ )

$$-V_S + R i_c + v_c(t) = 0 \quad . \text{ Also } i_c = C \frac{dv_c}{dt}$$

$$\Rightarrow -V_S + RC \frac{dv_c(t)}{dt} + v_c(t) = 0$$

$$\Rightarrow RC \frac{dv_c(t)}{dt} + v_c(t) = V_S \quad ①$$

We can use the solution form of this linear first order differential equation, we have the form of  $v_c(t) = k_1 + k_2 e^{st}$  with  $k_1$  &  $k_2$  are constant (4.13 in text book)

$$\Rightarrow \frac{dv_c(t)}{dt} = k_2 s e^{st}, \text{ then plug it into } ①, \text{ we have:}$$

$$\frac{RC}{s} K_2 s e^{st} + K_1 + \frac{K_2}{s} e^{st} = V_S$$

$$\Leftrightarrow K_2 e^{st} (RCs + 1) + K_1 = V_S$$

For equality, the coefficient of  $e^{st}$  must be 0

$$\Rightarrow \left\{ \begin{array}{l} K_1 = V_S = 10 \\ \end{array} \right.$$

$$s = \frac{-1}{RC} = \frac{-1}{50 \times 10^3 \times 0.04 \times 10^{-6}} = -500$$

$$\Rightarrow v_c(t) = K_1 + K_2 e^{-st} = 10 + K_2 e^{-500t}$$

$$\text{as given, } v_c(0^+) = -10V$$

$$\Rightarrow -10 = 10 + K_2 \Rightarrow K_2 = -20$$

$\Rightarrow$  the expression for the voltage across the capacitor by the time:

$$v_c(t) = 10 - 20e^{-500t} \quad (V)$$

$$\text{When } v_c(t) = 0 \Rightarrow 20e^{-500t} = 10$$

$$\Rightarrow e^{-500t} = 0.5 \Rightarrow -500t = \ln 0.5$$

$$\Rightarrow t = \frac{-\ln 0.5}{500} = 0.0013863 \text{ (s)}$$

$$\Leftrightarrow t = 1.3863 \text{ (ms)}$$