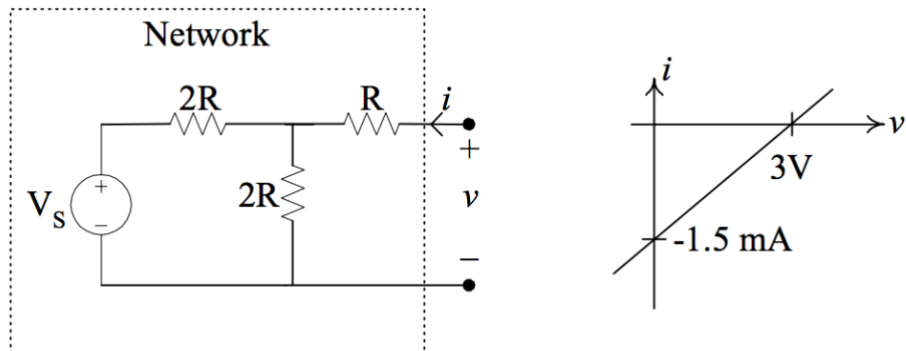


ECE100
Homework-4


Total Points: 100

Submit your work in a pdf file electronically in the CCLE website before April 25th 11:59 pm. Late homework will not get credit!

1. A network that is implemented with three resistors and a voltage source as shown below. Its terminal characteristics are also given graphically below.



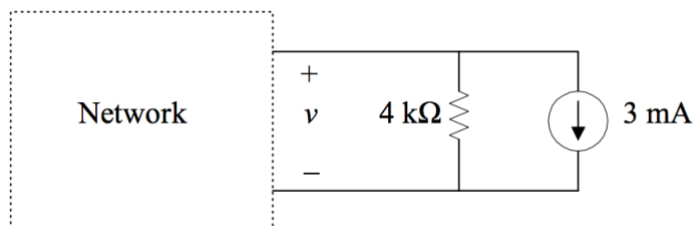
- (a) From the graphical data given above, determine numerical values for the parameters of the Thevenin equivalent of the network.
- (b) Determine numerical values for the parameters V_s and R that characterize the implementation of the network shown above.
- (c) The network is connected to an external current source and resistor as shown below. Determine the value of its terminal voltage v given the external connection.



$$V_{TH} = \text{Open-circuit } (i=0) \text{ voltage} = 3V$$

$$R_{TH} = - \frac{\text{Open-circuit voltage}}{\text{Short-circuit } (v=0) \text{ Current}} = \frac{3V}{1.5 \text{ mA}} = 2 \text{ k}\Omega$$

Open circuit voltage \Rightarrow

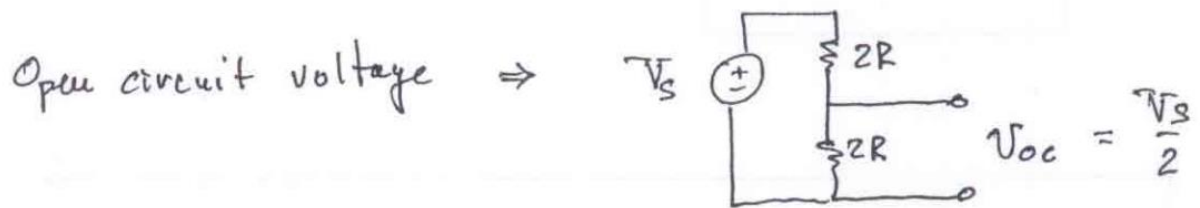


$$\Rightarrow V_s = 2 V_{TH} = 6 \text{ V}$$

$$R_{TH} = \begin{array}{c} \text{Circuit diagram showing two } 2R \text{ resistors in parallel, followed by a resistor } R \text{ in series with the output terminals.} \end{array} = 2R = 2 \text{ k}\Omega$$


$$\Rightarrow R = 1 \text{ k}\Omega$$

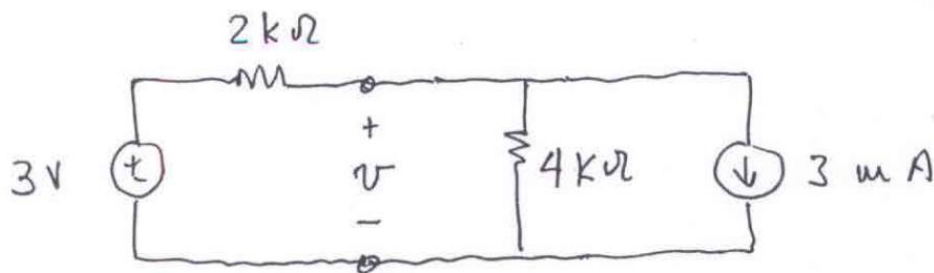Use the Thevenin equivalent and Superposition.



$$v = \frac{2}{3} \cdot 3 \text{ V} - \frac{4 \text{ k}\Omega \cdot 2 \text{ k}\Omega}{6 \text{ k}\Omega} \cdot 3 \text{ mA} = -2 \text{ V}$$

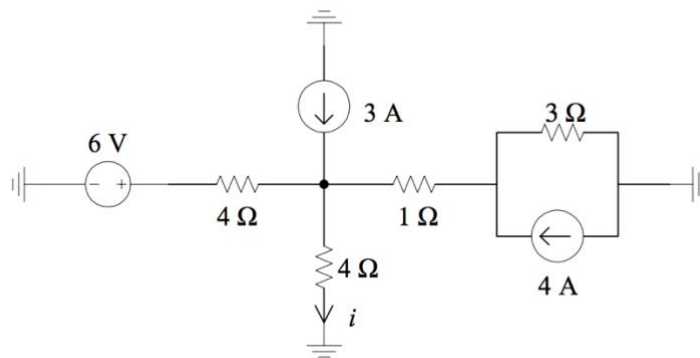2. Determine the current i in the network below.



Use superposition.


$$6V \text{ Source} \Rightarrow i = \frac{1}{2} \cdot \frac{6V}{6\Omega} = \frac{1}{2} A$$

$$3A \text{ Source} \Rightarrow i = \frac{1}{3} \cdot 3A = 1 A$$

$$4A \text{ Source} \Rightarrow i = \frac{1}{2} \cdot \frac{1}{2} \cdot 4A = 1 A$$

$$\text{Total } i = 2 \frac{1}{2} A$$

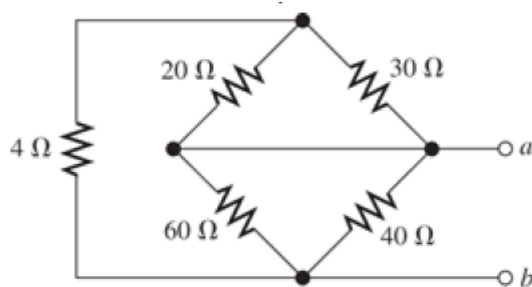
3. Find the equivalent resistance between terminals a and b in Figure below



The $20\text{-}\Omega$ and $30\text{-}\Omega$ resistances are in parallel and have an equivalent resistance of $R_{eq1} = 12\text{ }\Omega$. Also the $40\text{-}\Omega$ and $60\text{-}\Omega$ resistances are in parallel with an equivalent resistance of $R_{eq2} = 24\text{ }\Omega$. Next we see that R_{eq1} and the $4\text{-}\Omega$ resistor are in series and have an equivalent resistance of $R_{eq3} = 4 + R_{eq1} = 16\text{ }\Omega$. Finally R_{eq3} and R_{eq2} are in parallel and the overall equivalent resistance is

$$R_{ab} = \frac{1}{1/R_{eq1} + 1/R_{eq2}} = 9.6\text{ }\Omega$$

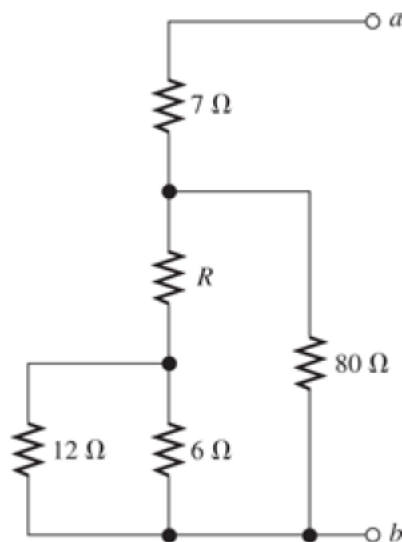4. The equivalent resistance between terminals a and b in Figure below is 23 ohms.
Determine the value of R.




$$R + (6 \parallel 12) = R + 4$$

$$(R + 4) \parallel 80 = 23 - 7 = 16$$

$$\Rightarrow R + 4 = 20$$

$$\Rightarrow R = 16\text{ ohms}$$

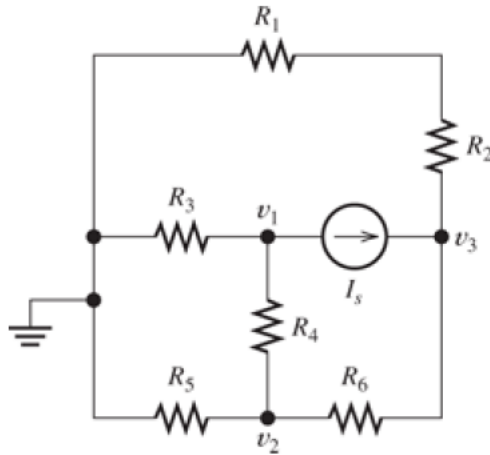5. Given $R_1=15\ \Omega$, $R_2=5\ \Omega$, $R_3=20\ \Omega$, $R_4=10\ \Omega$, $R_5=8\ \Omega$, $R_6=4\ \Omega$ and $I_s=5\ \text{A}$, solve for the node voltages shown in Figure.



Writing KCL equations at nodes 1, 2, and 3, we have

$$\frac{v_1}{R_3} + \frac{v_1 - v_2}{R_4} + I_s = 0$$

$$\frac{v_2 - v_1}{R_4} + \frac{v_2 - v_3}{R_6} + \frac{v_2}{R_5} = 0$$

$$\frac{v_3}{R_1 + R_2} + \frac{v_3 - v_2}{R_6} = I_s$$

In standard form, we have:


$$0.15v_1 - 0.10v_2 = -5$$

$$-0.10v_1 + 0.475v_2 - 0.25v_3 = 0$$

$$-0.25v_2 + 0.30v_3 = 5$$

$$v_1 = -30.56\ \text{V} \quad v_2 = 4.167\ \text{V} \quad v_3 = 20.14\ \text{V}$$

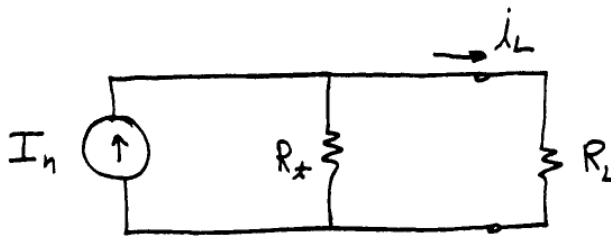6. Starting from the Norton equivalent circuit (current source I_n in parallel with R_t) with a resistive load attached (R_L), find an expression for the power delivered to the load in terms of I_n , R_t and R_L . Assuming that I_n , R_t are fixed values and that R_L is variable, show that maximum power is delivered for $R_L = R_t$. Find an expression for maximum power delivered to the load in terms of I_n , R_t .



By the current division principle:

$$i_L = I_n \frac{R_r}{R_L + R_r}$$

The power delivered to the load is

$$P_L = (i_L)^2 R_L = (I_n)^2 \frac{(R_r)^2 R_L}{(R_L + R_r)^2}$$

Taking the derivative and setting it equal to zero, we have

$$\frac{dP_L}{dR_L} = 0 = (I_n)^2 \frac{(R_r)^2 (R_r + R_L)^2 - 2(R_r)^2 R_L (R_r + R_L)}{(R_r + R_L)^4}$$

which yields $R_L = R_r$.

The maximum power is $P_{L\max} = (I_n)^2 R_r / 4$.

7. A $100 \mu F$ capacitance is initially charged to $1000 V$. At $t=0$ it is connected to a $1\text{-k}\Omega$ resistance. At what time t_2 has 50 percent of the initial energy stored in the capacitance been dissipated in the resistance?

The initial energy is

$$W_1 = \frac{1}{2} C (V_i)^2 = \frac{1}{2} 100 \times 10^{-6} \times 1000^2 = 50 \text{ J}$$

At $t = t_2$, half of the energy remains, and we have $25 = \frac{1}{2} C [v(t_2)]^2$, which

yields $v(t_2) = 707.1 V$. The voltage across the capacitance is given by


$$v_C(t) = V_i \exp(-t/RC) = 1000 \exp(-10t) \text{ for } t > 0$$

Substituting, we have $707.1 = 1000 \exp(-10t_2)$. Solving, we obtain

$$\ln(0.7071) = -10t_2$$

$$t_2 = 0.03466 \text{ seconds}$$

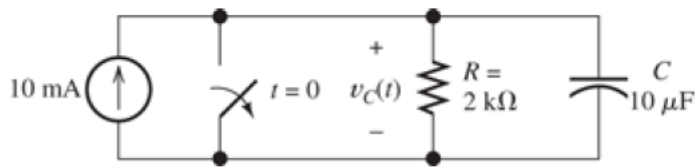8. Derive an expression for $v_c(t)$ in the circuit below and sketch $v_c(t)$ to scale versus time. (Note that switch was closed before $t=0$ and becomes an open after $t=0$)



Prior to $t = 0$, we have $v_C(t) = 0$ because the switch is closed. After $t = 0$, we can write the following KCL equation at the top node of the circuit:

$$\frac{v_C(t)}{R} + C \frac{dv_C(t)}{dt} = 10 \text{ mA}$$

Multiplying both sides by R and substituting values, we have

$$0.02 \frac{dv_C(t)}{dt} + v_C(t) = 20 \quad (1)$$

The solution is of the form

$$v_C(t) = K_1 + K_2 \exp(-t/RC) = K_1 + K_2 \exp(-50t) \quad (2)$$

Using Equation (2) to substitute into Equation (1), we eventually obtain $K_1 = 20$


The voltage across the capacitance cannot change instantaneously, so we have

$$\begin{aligned} v_C(0+) &= v_C(0-) = 0 \\ v_C(0+) &= 0 = K_1 + K_2 \end{aligned}$$


Thus, $K_2 = -K_1 = -20$, and the solution is

$$v_C(t) = 20 - 20 \exp(-50t) \text{ for } t > 0$$

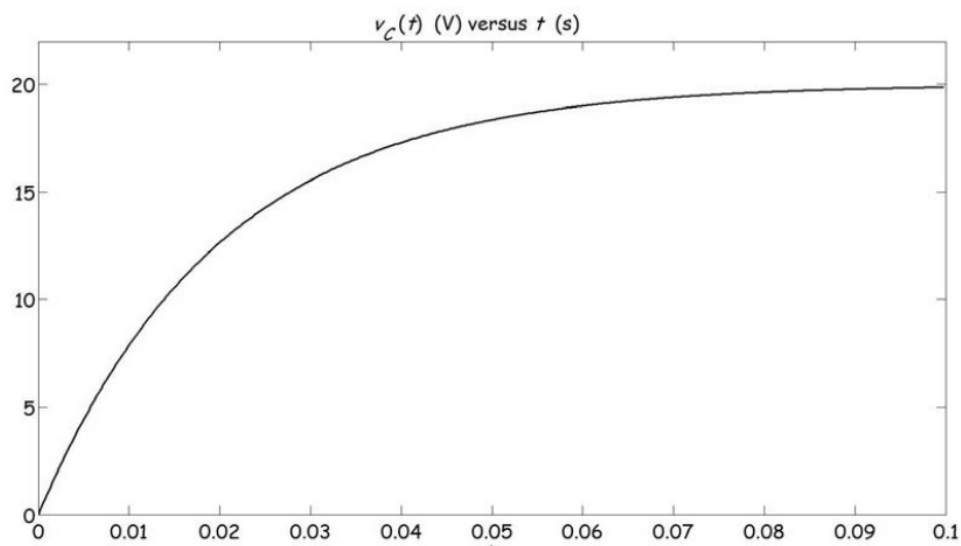The sketch should resemble the following plot:



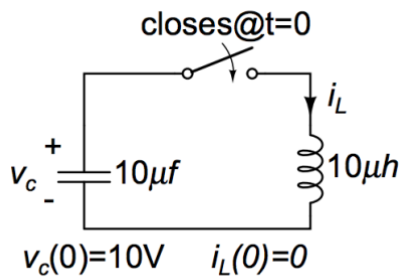9. Determine the maximum value of I_L (10 points)




Energy oscillates between L and C.


$$0.5 C V^2 = 0.5 L I^2$$

Plugging in values, $I = 10 A$

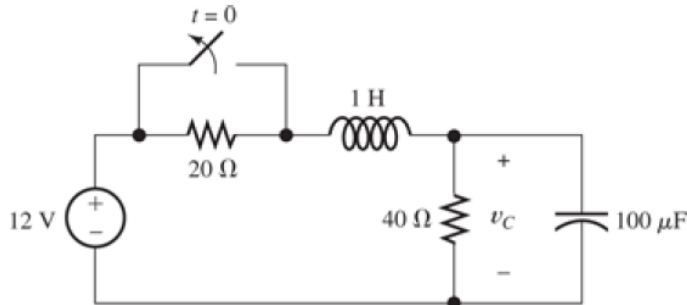10. The circuit shown in Figure has been set up for a long time prior to $t=0$ with the switch closed. Find the value of v_C prior to $t=0$. Find the steady-state value of v_C after the switch has been opened for a long time. (15 points)




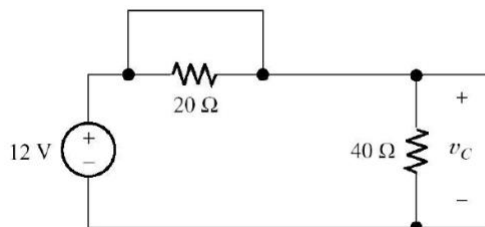Prior to $t = 0$, the steady-state equivalent circuit is:



and we see that $v_c = 12V$.

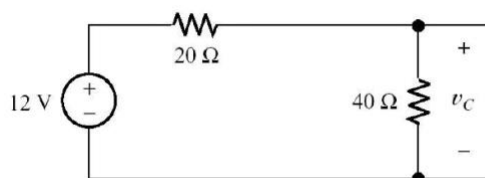A long time after $t = 0$, the steady-state equivalent circuit is:



$$\text{and we have } v_c = 12 \frac{40}{40 + 20} = 8V.$$