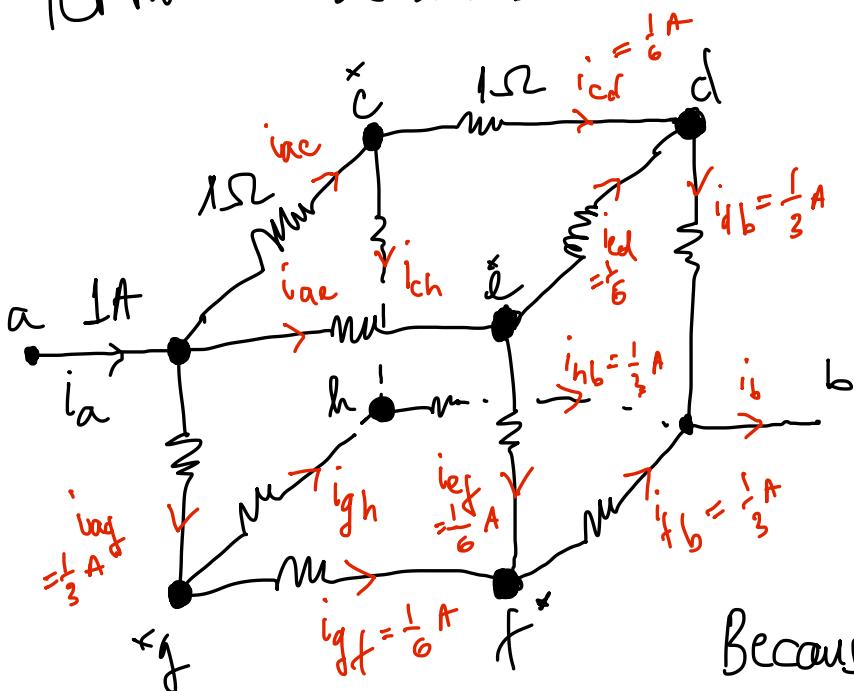


Home Work 2:

What No
105355311

1) Find the ΣR between the terminal a & b.



Because we assume there has $i = 1A$ go through $a \rightarrow b$, $i_a = 1A$.

Apply KCL at a,
we have:

$$i_a = i_{act} + i_{ae} + i_{ag}$$

Because all resistor has the

same value 1 R and use symmetric consideration,

$$i_{act} = i_{ae} = i_{ag} = \frac{i_a}{3} = \frac{1}{3}(A)$$

Based on the symmetric consideration,
+ apply KCL at c, we have:

$$i_{ac} = i_{cd} + i_{ch} = \frac{1}{3} \quad \& \quad i_{cd} = i_{ch} \Rightarrow i_{cd} = i_{ch} = \frac{i_{ac}}{2} = \frac{1}{6}(A)$$

$$+ \text{apply KCL at } \underline{g}, \text{ also have } i_{gh} = i_{gt} = \frac{i_{ag}}{2} = \frac{1}{6}(A)$$

$$+ \text{apply KCL at } \underline{e}, \text{ also have } i_{ed} = i_{ef} = \frac{i_{ae}}{2} = \frac{1}{6}(A)$$


$$+ \text{apply KCL at } \underline{f}, \quad i_{fb} = i_{ef} + i_{gf} = \frac{1}{6} + \frac{1}{6} = \frac{1}{3}(A)$$

+ Apply KCL at d, $i_{db} = i_{cd} + i_{ed} = \frac{1}{6} + \frac{1}{6} = \frac{1}{3} (A)$

+ Apply KCL at h, $i_{hb} = i_{ch} + i_{gh} = \frac{1}{6} + \frac{1}{6} = \frac{1}{3} (A)$

+ Apply KCL at b, $i_b = i_{db} + i_{hb} + i_{fb} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3} = 1 (A)$
 (matching with the assumption)

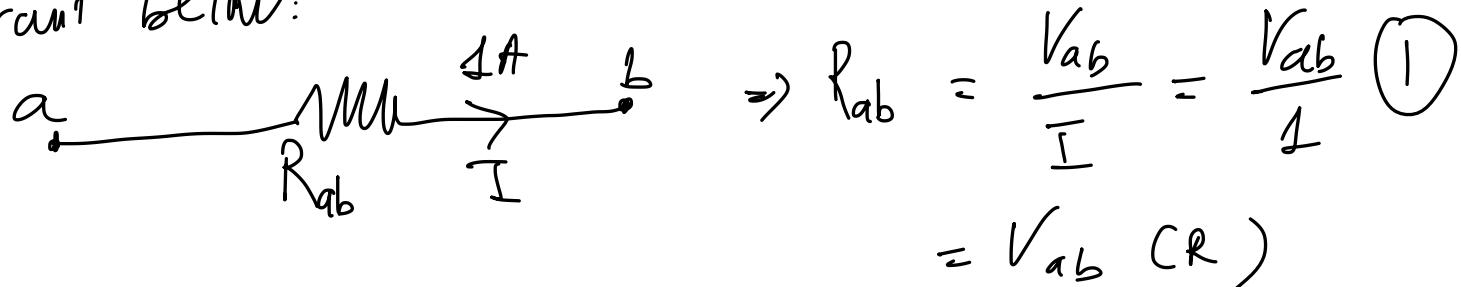We can represent the original circuit to the equivalent circuit below:



→ the voltage between a & b is equal to the unknown resistance. Then apply KVL from $a \rightarrow g \rightarrow f \rightarrow b$, we have:

$$V_a - V_b = i_{ag} R + i_{gf} R + i_{fb} R = R(i_{ag} + i_{gf} + i_{fb})$$

$$\Rightarrow V_{ab} = \left(\frac{1}{3} + \frac{1}{6} + \frac{1}{3} \right) A \cdot 1 R = \left(\frac{2}{3} + \frac{1}{6} \right) V$$



$$\Rightarrow V_{ab} = \frac{5}{6} V$$

. From (1), we have

$$R_{ab} = \frac{V_{ab}}{1 \Omega} = \frac{5}{6} (\Omega)$$

⇒ The resistance between a & b:

$$R = \frac{5}{6} (\Omega)$$

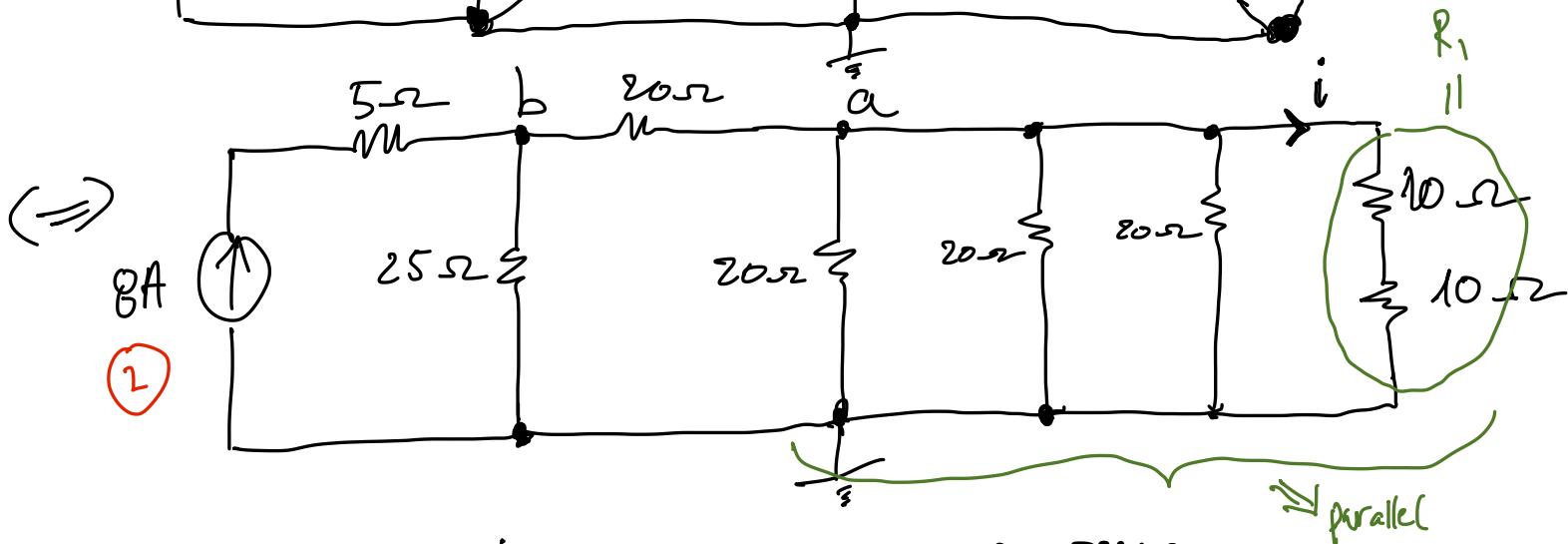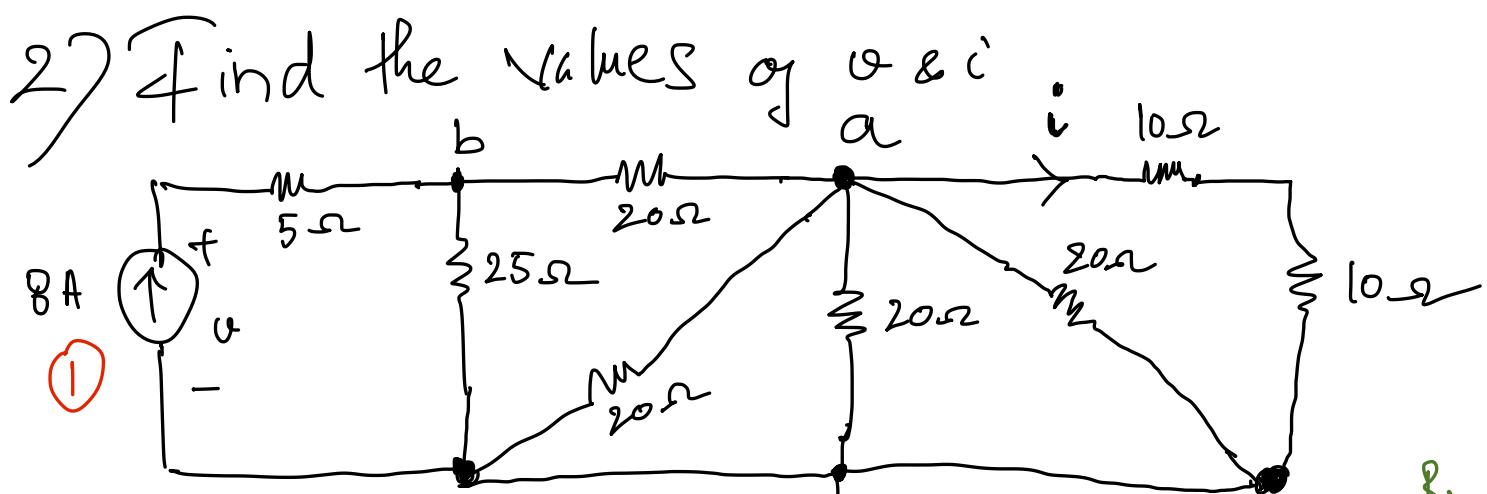



As we can see, two resistor 10Ω are series

$$\Rightarrow R_1 = 10 + 10 = 20(\Omega)$$


Then the last 3 resistor 20Ω are parallel and also parallel with $R_1 = 20\Omega$

$$\Rightarrow \text{we have: } \frac{1}{R_2} = \frac{1}{20} + \frac{1}{20} + \frac{1}{20} + \frac{1}{20} = \frac{4}{20}$$

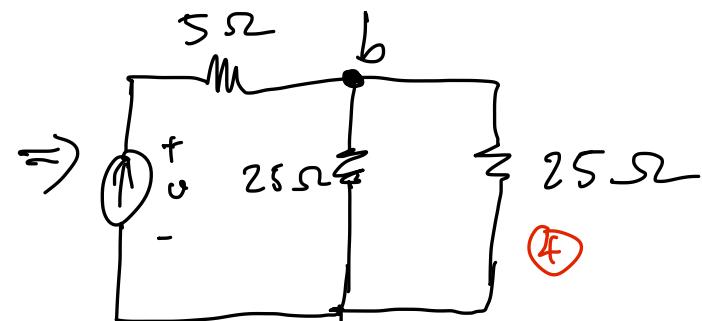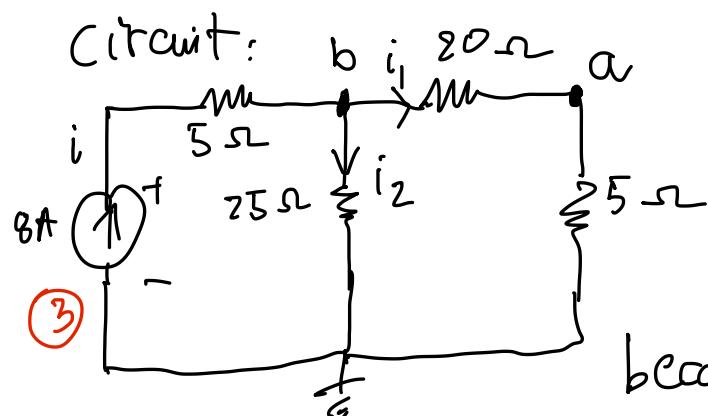$\Rightarrow R_2 = \frac{20}{4} = 5(\Omega)$, we can have the new reduced



because 20Ω series with 5Ω

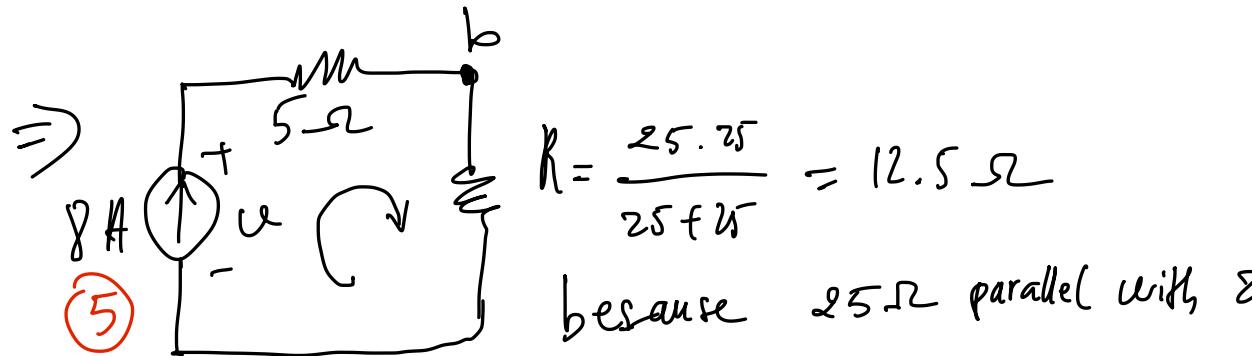

Based on circuit (5), apply KVL, we have:

$$-\vartheta + iR = 0 \Rightarrow \vartheta = iR = 8A \times (5 + 12.5)\Omega$$

$$\Rightarrow \vartheta = 8 \times 17.5 = \boxed{140V}$$

$$\text{Also, } -\vartheta + i \cdot 5 \Omega + V_b \Rightarrow V_b = \vartheta - 5i$$

$$\Rightarrow V_b = 140V - 5 \times 8 = 100V$$

Apply KCL at b for circuit (3), we have:

$$i = i_1 + i_2 \Rightarrow i = \frac{V_b - V_a}{20\Omega} + \frac{V_b - 0}{25\Omega}$$


$$\Rightarrow \vartheta = \frac{100 - V_a}{20} + \frac{100V}{25\Omega} = \frac{100 - V_a}{20} + 4$$

$$\Rightarrow \frac{100 - V_a}{20} = \vartheta - 4 = 4 \Rightarrow V_a = 100 - 80 = 20V$$


Go back to the circuit (2), we have:

$$\frac{V_a}{10\Omega + 10\Omega} = i \Rightarrow i = \frac{20V}{20\Omega} = \boxed{1A}$$

3) Find the equivalent resistance:

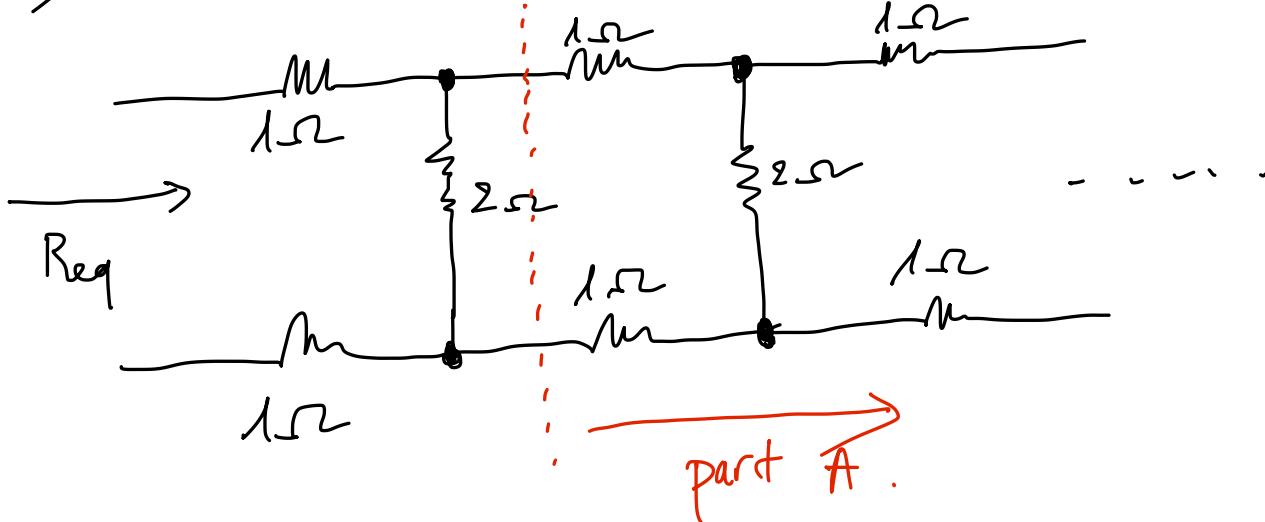

We divide the original circuit as the above picture.
Called part A is the circuit has n resistors which has value 2Ω . \Rightarrow the original circuit has $(n+1)$ resistors 2Ω . Because the original circuit is the infinite network $\Rightarrow n \rightarrow \infty$ means $n \approx n+1$. In the other words, the total resistance of part A $\approx R_{eq}$. Based on this idea we can redraw the circuit:

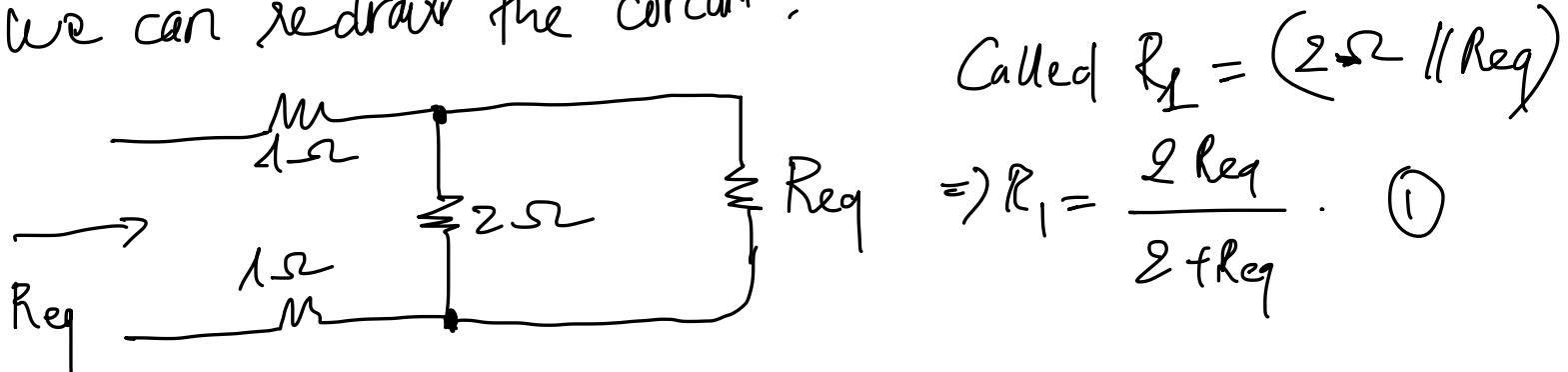

$$\Leftrightarrow \frac{1}{Req} = \frac{1}{1\Omega} + \frac{1}{2\Omega} + R_1 \Rightarrow Req = 1\Omega + 1\Omega + R_1$$

$$\Rightarrow Req = 2 + \frac{2 * Req}{2 + Req} = \frac{2(2 + Req) + 2 * Req}{2 + Req} = \frac{4 * Req + 4}{2 + Req}$$

For easier calculation, called $R_{eq} = \frac{R}{2}$ ($\alpha > 0$)

$$\Rightarrow R = \frac{4x + 4}{2 + x} \Rightarrow x^2 + 2x = 4x + 4$$


$$\Rightarrow x^2 - 2x - 4 = 0 \Leftrightarrow \begin{cases} x = \frac{2 + \sqrt{4+16}}{2} \\ x = \frac{2 - \sqrt{4+16}}{2} \end{cases}$$

$$\Leftrightarrow \begin{cases} x = \frac{2 + \sqrt{20}}{2} = \frac{2 + 2\sqrt{5}}{2} = 1 + \sqrt{5} \end{cases}$$

$$\begin{cases} x = \frac{2 - \sqrt{20}}{2} = \frac{2 - 2\sqrt{5}}{2} = 1 - \sqrt{5} < 0 \Rightarrow \text{rejection} \\ (\text{value of resistor can not be negative}) \end{cases}$$

$$\Rightarrow R_{eq} = R = \boxed{1 + \sqrt{5} \approx 3.236 \Omega}$$

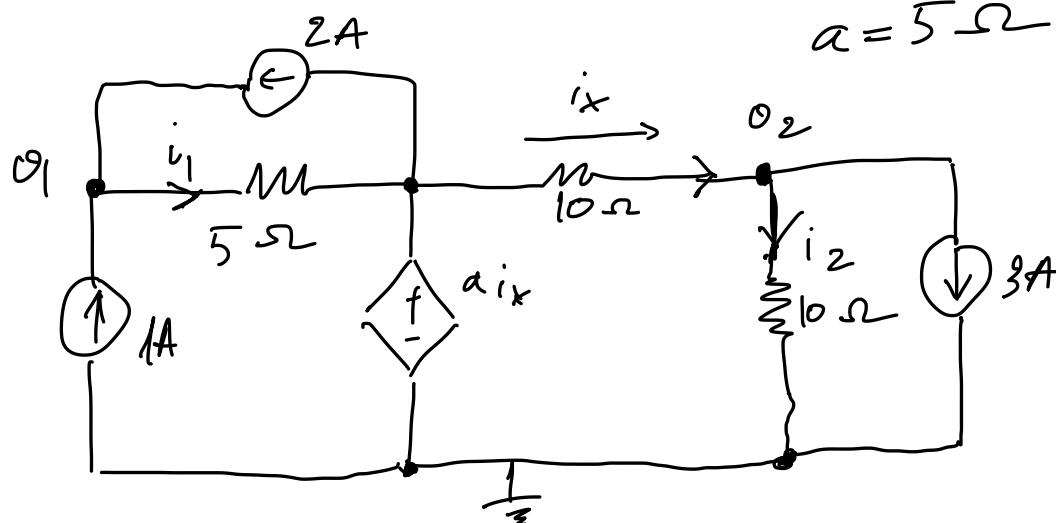4) Solve for the node voltage ϑ_1 & ϑ_2 .



Apply KCL at ϑ_1 , we have: $i_1 = 2 + 1 = 3A$.

$$(\Rightarrow) \frac{\vartheta_1 - a i_x}{5\Omega} = 3A \Rightarrow \vartheta_1 - a i_x = 15V$$

$$\Rightarrow \vartheta_1 - 5i_x = 15 \quad (1)$$

Apply KCL at ϑ_2 , we have: $i_x = i_2 + 3A$.

$$(\Rightarrow) \frac{a i_x - \vartheta_2}{10\Omega} = \frac{\vartheta_2 - 0}{10\Omega} + 3A$$

$$\Rightarrow 5i_x - \vartheta_2 = \vartheta_2 + 30V \Rightarrow 5i_x - 2\vartheta_2 = 30V \quad (2)$$

$$\text{Also } \frac{a i_x - \vartheta_2}{10} = i_x \Rightarrow 5i_x - \vartheta_2 = 10i_x \text{ (Ohm's Law)}$$

$$\Rightarrow \vartheta_2 = -5i_x \quad (3)$$


Plug (3) into (2), we have: $-\vartheta_2 - 2\vartheta_2 = 30V$

$$\Rightarrow \boxed{\vartheta_2 = -10V} \Rightarrow i_x = \frac{\vartheta_2}{-5} = \frac{-10}{-5} = 2A$$


Plug i_x into (1) $\Rightarrow \vartheta_1 = 15 + 5i_x = 15 + 10 = \boxed{25V}$

5) Find R_1, R_2, R_3 .

* First experiment:

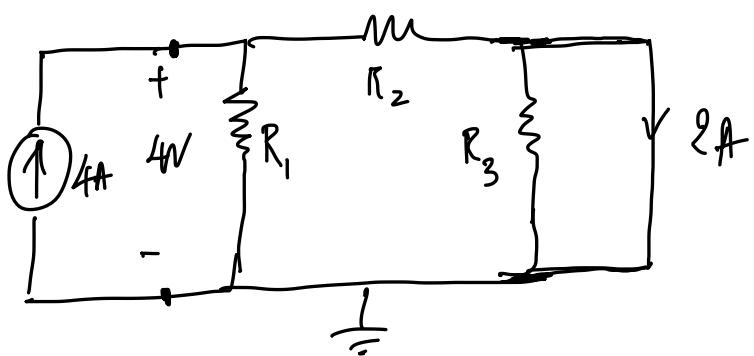

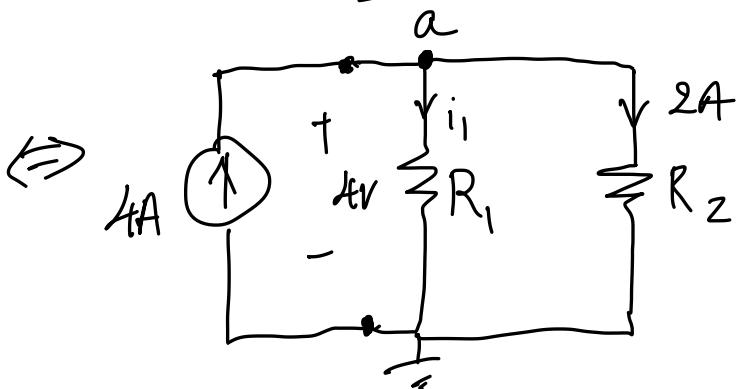Because R_3 is shorted, so there is no current go through it, we can have a new circuit.



Apply KCL at a , we have:

$$4 = i_1 + 2A$$

$$\Rightarrow i_1 = 2A$$

$$\text{Also, } i_1 R_1 = V_a - 0 = 4V$$

(Ohm's Law)


$$\Rightarrow 2R_1 = 4V \Rightarrow R_1 = \frac{4}{2} = 2(\Omega)$$

$$\text{Beside: } V_a - 0 = 2A \cdot R_2 \Rightarrow 2R_2 = 4 \Rightarrow R_2 = 2(\Omega)$$

(Ohm's Law)

$$\boxed{\begin{aligned} R_1 &= 2(\Omega) \\ R_2 &= 2(\Omega) \end{aligned}}$$

* Second Experiment:

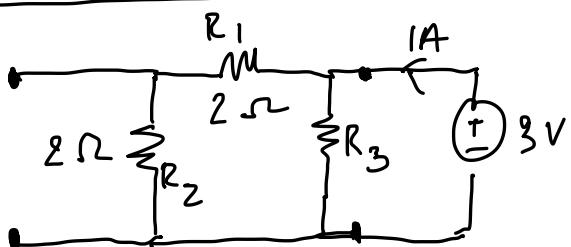

In this case, we have R_1 series to R_2 , called $R = R_1 + R_2$
 $\Rightarrow R = 4\Omega$.

So we can have the new circuit.: Let $R_{eq} = (R \parallel R_3)$

$$\text{Circuit Diagram: } R \parallel 4\Omega \parallel R_3 \text{ with current } 1A \text{ entering the top node. A } 3V \text{ DC voltage source is connected across the parallel combination.}$$
$$(R \parallel R_3) \Rightarrow R_{eq} = \frac{R \cdot R_3}{R + R_3} = \frac{4R_3}{4 + R_3} \quad (*)$$

Applying Ohm's Law:


$$\text{Circuit Diagram: } R_{eq} \parallel 3V \text{ DC voltage source with current } 1A \text{ entering the top node.}$$
$$R_{eq} \parallel 3V \Rightarrow R_{eq} \cdot I = V$$
$$\Rightarrow R_{eq} \cdot 1A = 3V \Rightarrow R_{eq} = 3\Omega$$

\Rightarrow Plug $R_{eq} = 3\Omega$ into $(*)$, we have:

$$\frac{4R_3}{4 + R_3} = 3\Omega \Rightarrow 4R_3 = 3(4 + R_3)$$

$$\Rightarrow 4R_3 = 12 + 3R_3 \Rightarrow R_3 = 12\Omega$$

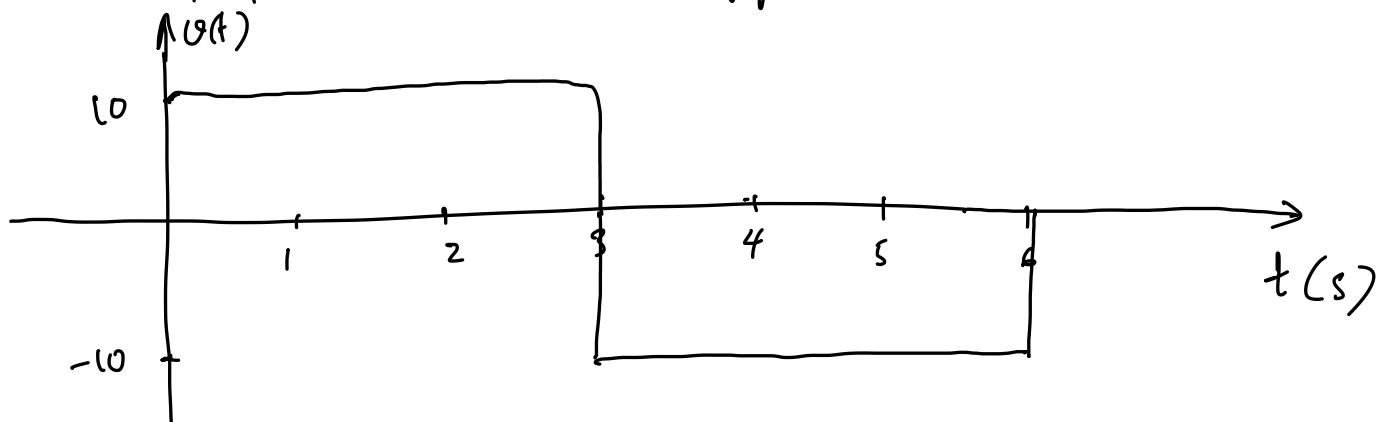⑥ Given $L = 2H$, $i_L(0) = 0$. Need to sketch the current, power, & stored energy to scale versus time.



Based on the Figure, we have:

$$v(t) = 10V, \quad t = 0 \rightarrow 3s$$

$$v(t) = -10V, \quad t = 3 \rightarrow 6s$$

$$\text{Also, } i_L(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i_L(t_0) = \frac{1}{2} \int_{t_0}^t v(t) dt + i_L(t_0)$$

* For $t = 0 \rightarrow 3s$, $v(t) = 10V$, and $i_L(0) = 0$

$$\Rightarrow i_L(t) = \frac{1}{2} \int_0^t 10 dt = 5 \int_0^t dt = 5t \quad (A)$$

* For $t = 3 \rightarrow 6s$, $v(t) = -10V$, and at $t = 3s$, $i_L(3s) = 5 \times 3 = 15A$


$$\Rightarrow i_L(t) = \frac{1}{2} \int_3^t (-10) dt + 15 \quad (A)$$

$$\Rightarrow i_L(t) = -5 \int_3^t dt + 15 = -5(t - 3) + 15 = -5t + 30 \quad (A)$$

\Rightarrow We have:

$$i_L(t) = \begin{cases} 5t(A), & t=0 \rightarrow 3s \\ -5t + 30(A), & t=3s \rightarrow 6s \end{cases}$$

⇒ the figure of current:

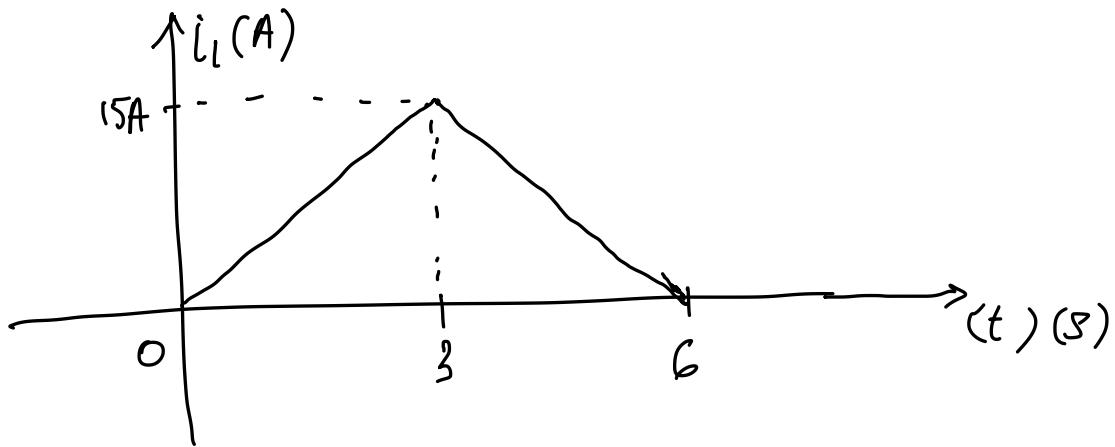


Also, $p(t) = \vartheta(t)i(t)$

④ For $t=0 \rightarrow 3s$, $\begin{cases} \vartheta(t)=10(V) \\ i(t)=5t(A) \end{cases} \Rightarrow p(t)=50t(W)$

⑤ For $t=3s \rightarrow 6s$, $\begin{cases} \vartheta(t)=-10V \\ i(t)=-5t+30(A) \end{cases}$

$$\Rightarrow p(t) = -10(-5t + 30) = 50t - 300(W)$$

⇒ the figure of power:

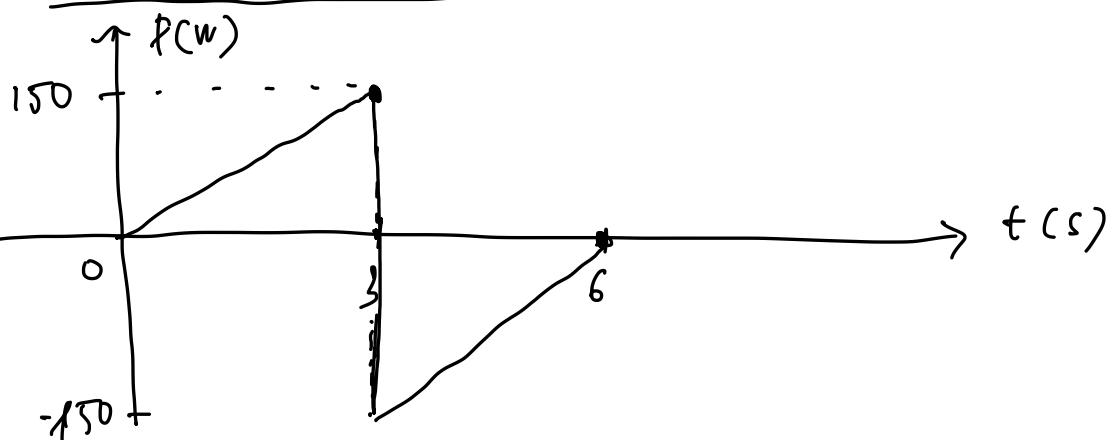

$$\text{We Have: } W(t) = \frac{1}{2} L i^2(t) = \frac{1}{2} \times 2 i(t)^2 = i_L^2(t)$$

Since:

$$i_L(t) = \begin{cases} 5t \text{ (A), } t = 0 \rightarrow 3s \\ -5t + 30 \text{ (A), } t = 3s \rightarrow 6s \end{cases}$$

\Rightarrow For $t = 0 \rightarrow t = 3s$:

$$W(t) = i_L^2(t) = (5t)^2 = 25t^2 \text{ (J)}$$

For $t = 3s \rightarrow 6s$,

$$W(t) = i_L^2(t) = (-5t + 30)^2 = 25t^2 - 300t + 900 \text{ (J)}$$

Then the figure of stored energy:

