

Problem 1

$$(a) \quad i_T(t) = i_1(t) + i_2(t)$$

$$i_1(t) = 4 \cos(\omega t + 30^\circ)$$

$$i_2(t) = 5 \sin(\omega t - 20^\circ) = 5 \cos(\omega t - 0^\circ - 90^\circ) = 5 \cos(\omega t - 110^\circ)$$

$$\underline{I}_1 = 4 \angle 30^\circ = 4 \cos(30^\circ) + j4 \sin(30^\circ) = \frac{4\sqrt{3}}{2} + j\frac{4}{2}(4)$$

$$\underline{I}_2 = 5 \angle 110^\circ = 5 \cos(110^\circ) + j5 \sin(110^\circ) \approx -4.7 - j1.7$$

$$\underline{I}_T = \underline{I}_1 + \underline{I}_2 \approx (2\sqrt{3} + j2) + (-4.7 - j1.7) = 1.75 - j2.7$$

$$\underline{I}_T = \sqrt{1.75^2 + 2.7^2} \angle \tan^{-1}\left(\frac{-2.7}{1.75}\right)$$

$$\rightarrow \boxed{\begin{aligned} \underline{I}_T &= 3.218 \angle -57^\circ \\ i_T(t) &= 3.218 \cos(\omega t - 57^\circ) \end{aligned}}$$

(b) (b) Using the phasor approach, determine the current $i(t)$ in a circuit described by the following 2nd order differential equation. (5 points)

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

Let's recall:

for an inductor:

$$V = L \frac{di}{dt} \rightarrow \underline{V}_L = j\omega L \underline{I}_L$$

for a capacitor:

$$V = \frac{1}{C} \int i dt \quad \underline{V}_C = \frac{1}{j\omega C} \underline{I}_C$$

transform eq. into phasor domain:

$$4i(t) + 8 \int i(t) dt - 3 \frac{di(t)}{dt} = 50 \cos(2t + 75^\circ)$$

$$\rightarrow 4\mathbf{I} + 8 \frac{1}{j\omega} \mathbf{I} - 3j\omega \mathbf{I} = 50 \angle 75^\circ$$

\uparrow note: $8 = \frac{1}{C_{eq}}$ \nwarrow $L_{eq} = 3H$

$$\Rightarrow C_{eq} = \frac{1}{8} = 0.25H$$

given $\omega = 2$:


$$\mathbf{I}(4 - j\frac{8}{2} - j3(2)) = 50 \angle 75^\circ$$

$$\begin{aligned} \mathbf{I} &= \frac{50 \angle 75^\circ}{4 - j10} = \frac{50 \angle 75^\circ}{\sqrt{4^2 + 10^2} \angle \tan^{-1}(\frac{-10}{4})} \\ &= \frac{50 \angle 75^\circ}{10.77 \angle -68.2^\circ} = \boxed{4.64 \angle 143.2^\circ} \end{aligned}$$

$$\rightarrow \boxed{i(t) = 4.64 \cos(2t + 143.2^\circ)}$$

Note: this is known as the particular solution
 OR steady-state solution
 (does not require knowledge of initial conditions)

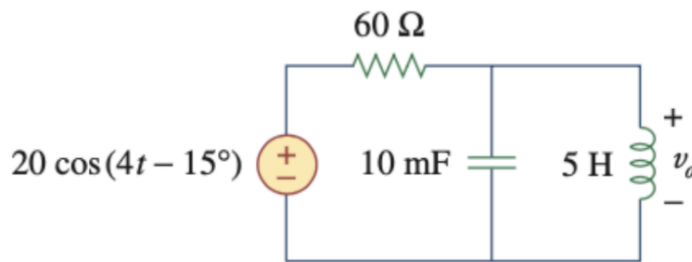(c) (c) Determine $v_o(t)$ in the following circuit. (5 points)



* solve using voltage divider

$$v_o(t) = \frac{\left(\frac{1}{j\omega C}\right) \parallel j\omega L}{60\Omega + \left(\frac{1}{j\omega C}\right) \parallel j\omega L} \cdot 20 \angle -15^\circ$$

* $\omega = 4$:

$$\frac{1}{j\omega C} = \frac{1}{j(4)(0.01F)} = -j25$$

$$j\omega L = j(4)(5H) = j20$$

$$\frac{1}{j\omega C} \parallel j\omega L = \frac{(-j25)(j20)}{-j25 + j20} = \frac{500}{-j5} = j100$$

$$\rightarrow V_o(t) = \left(\frac{j100}{60\Omega + j100} \right) 20 \angle -15^\circ$$


$$\equiv \left(\frac{100 \angle 90^\circ}{\sqrt{60^2 + 100^2} \angle \tan^{-1}\left(\frac{100}{60}\right)} \right) 20 \angle -15^\circ$$

$$= \left(\frac{100 \angle 90^\circ}{116.62 \angle 59^\circ} \right) 20 \angle -15^\circ$$

$$= (0.857 \angle 31^\circ)(20 \angle -15^\circ) = \boxed{17.15 \angle 16^\circ}$$

$$\Rightarrow \boxed{V_o(t) = 17.15 \cos(4t + 16^\circ) [V]}$$

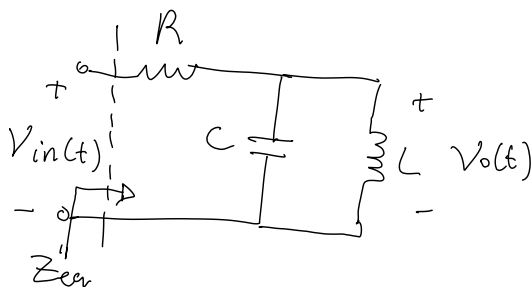(d) (d) What type of filter can be constructed using the circuit topology shown in part (c)? (1 point)



$$\textcircled{1} \quad Z_{eq} = R + j\omega L \parallel \frac{1}{j\omega C} = R + \frac{\frac{L}{C}}{j\omega L - j\frac{1}{\omega C}}$$

$$Z_{eq} = R + j\frac{L}{C} \left(\frac{1}{\frac{1}{\omega C} - \omega L} \right)$$

$$\textcircled{a} \quad \omega = \omega_0 = \frac{1}{\sqrt{LC}} \text{ (resonance):}$$


$$Z_{eq} = R + jX \quad \text{where} \quad X \rightarrow \infty$$

→ ...

$$Z_{eq} \approx j\omega$$

$$|V_{out}| = |V_{in}|$$


② $\omega = 0$:

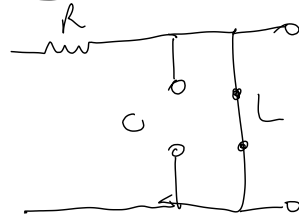

inductor acts as a short

$$V_{out} \approx 0$$

③ $\omega = \infty$:

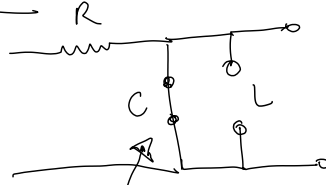

capacitor acts as a short

$$V_{out} \approx 0$$



\therefore bandpass filter

$$(a) \quad V_s = V_R + V_L + V_C$$

$$R i + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_s$$

$$\Rightarrow L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = \frac{dV_s}{dt}$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = V_m \cos(\omega t) \cdot \omega$$

$$\boxed{i_p = a e^{j\omega t}} \quad (1)$$

$$\Rightarrow L i'' + R i' + \frac{i}{C} = V_m \omega e^{j\omega t} \quad (4)$$

$$i_p' = a e^{j\omega t} j\omega \quad (2)$$

$$i_p'' = -a \omega^2 e^{j\omega t} \quad (3)$$

Substituting (1), (2), (3) in (4)

$$\Rightarrow -L a \omega^2 e^{j\omega t} + j\omega R a e^{j\omega t} + \frac{a e^{j\omega t}}{C} = V_m \omega e^{j\omega t}$$

$$\Rightarrow a (-L\omega^2 + j\omega R + \frac{1}{C}) = V_m \omega$$


$$a (-L\omega + jR + \frac{1}{\omega C}) = V_m$$

$$a (R + j(L\omega - \frac{1}{\omega C})) = -jV_m$$

$$\boxed{a = \frac{V_m \angle -90^\circ}{R + j(L\omega - \frac{1}{\omega C})}}$$

$$\therefore \boxed{V_R = aR = \frac{V_m R \angle -90^\circ}{R + j(L\omega - \frac{1}{\omega C})}}$$

(b)

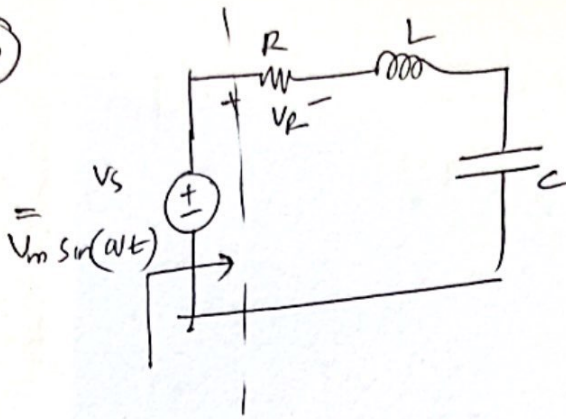

$$v_m \sin(\omega t) = V_m \cos(\omega t - 90^\circ)$$

$$I = \frac{V_s}{R + j\omega L + \frac{-j}{\omega C}} = \frac{V_m \angle -90^\circ}{(R + j(\omega L - \frac{1}{\omega C}))}$$

$$V_R = I \cdot R = \frac{(V_m \angle -90^\circ) \cdot R}{(R + j(\omega L - \frac{1}{\omega C}))} = \frac{V_m R \angle -90^\circ}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} \angle \tan^{-1}(\frac{\omega L - \frac{1}{\omega C}}{R})}$$

$$V_R = \frac{V_m R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \angle -90^\circ - \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$$

$$V_R(t) = \frac{V_m R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \cos(\omega t - 90^\circ - \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right))$$

$$V_R(t) = \frac{V_m R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \sin(\omega t + \phi)$$

$$\text{where } \phi = -\tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$$

$$(c) \quad Z_s = R + j\omega L + \frac{-j}{\omega C}$$

$$(d) \quad H(j\omega) = \frac{V_R(j\omega)}{V_s(j\omega)} = \frac{I \cdot R}{V_s} = \frac{V_s}{(R + j\omega L - \frac{j}{\omega C})} \cdot \frac{R}{V_s}$$


$$H(j\omega) = \frac{R}{(R + j\omega L - \frac{j}{\omega C})}$$

$$(e) \quad |H(j\omega)| = \frac{R}{\sqrt{R^2 + \left(L\omega - \frac{1}{\omega C}\right)^2}}$$


$$\angle H(j\omega) = \angle 0^\circ - \tan^{-1}\left(\frac{L\omega - \frac{1}{\omega C}}{R}\right)$$

$$\text{in dB} = 20 \log\left(\frac{R}{\sqrt{R^2 + \left(L\omega - \frac{1}{\omega C}\right)^2}}\right)$$
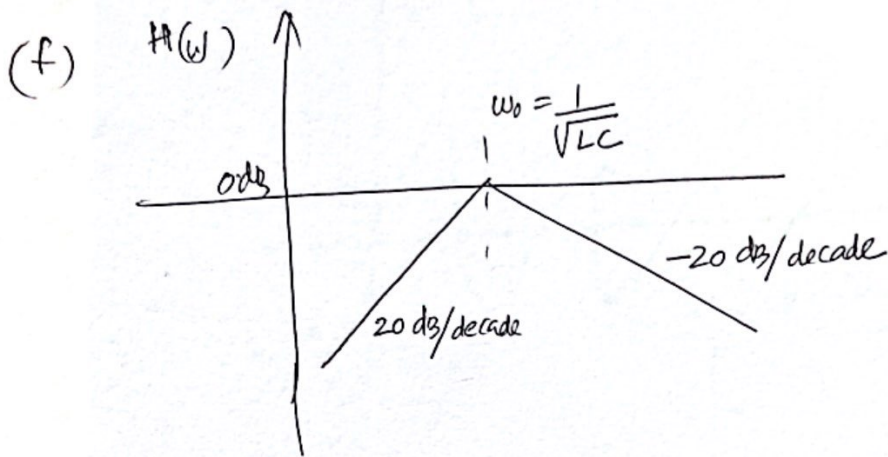
$$= -\tan^{-1}\left(\frac{L\omega - \frac{1}{\omega C}}{R}\right)$$


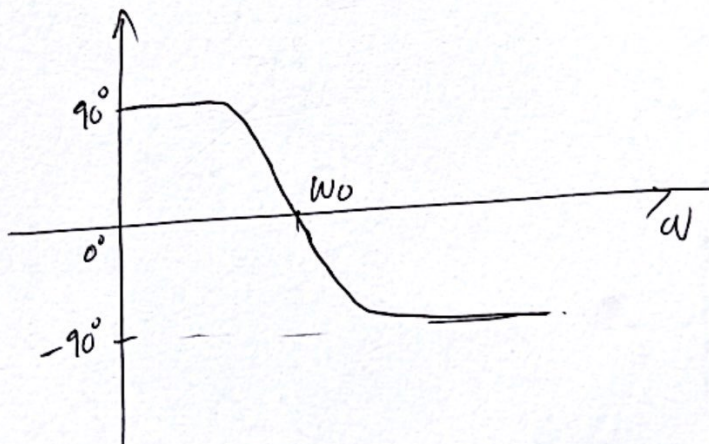
$$\angle H(\omega) = 0^\circ - \tan^{-1}\left(\frac{L\omega - \frac{1}{\omega C}}{R}\right)$$



(g) At $\omega_0 = L\omega_0 = \frac{1}{\omega_0 C}$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

(h) phase ~~is~~ o/p phase w.r.t to input at resonance = 0°

$$(1) Q = \frac{L\omega}{R} = \frac{2\pi f L}{R}$$

$$(2) B = \frac{f_0}{Q} = \frac{1}{2\pi\sqrt{LC}} \cdot \frac{1}{Q} = \frac{1}{2\pi\sqrt{LC}} \frac{R}{2\pi \frac{1}{2\pi\sqrt{LC}}}$$


$$\Rightarrow B = \frac{R}{2\pi L}$$

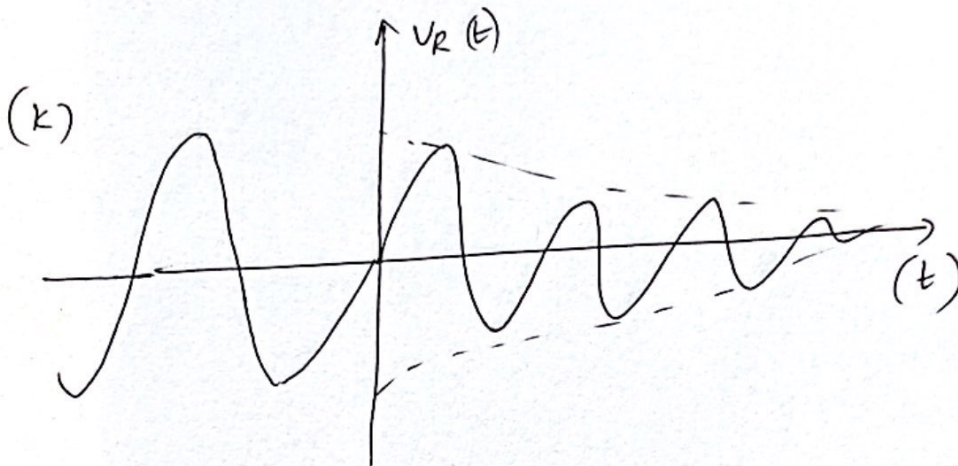

$$(l) \text{ Energy } E_1 = \int_{\text{first cycle}} L i dt = \int_{\text{first cycle}} L \frac{V_R}{R} di$$

$$E_1 = \frac{L}{R} \int_{\text{first cycle}} V_R$$
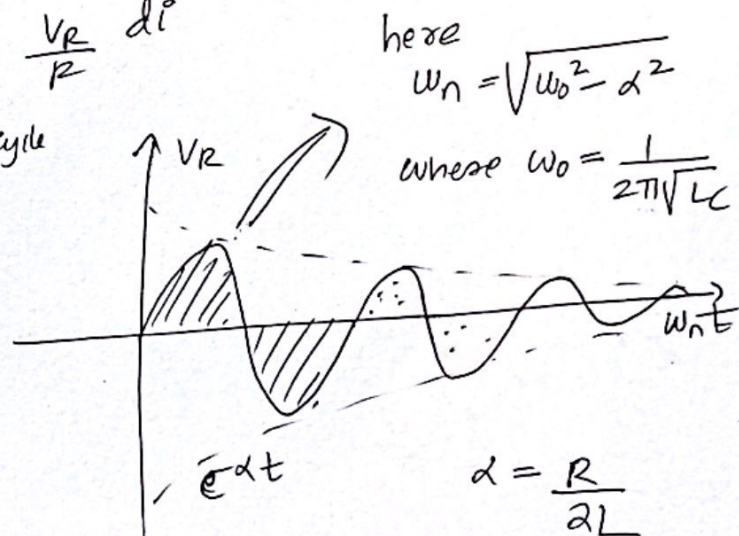
$$E_2 = \frac{L}{R} \int_{\text{second cycle}} V_R$$



$$(m) Q = \frac{2\pi \cdot \text{Energy stored per cycle}}{\text{Energy lost}} = \frac{2\pi E_1}{(E_1 - E_2)} \quad \left(\text{Note } Q = \frac{L\omega}{R} = \frac{2\pi f L}{R} \right)$$

$$\left[E_2 = E_1 - \Delta E \right. \\ \left. \text{where } \Delta E \text{ is the energy lost in first cycle} \right]$$