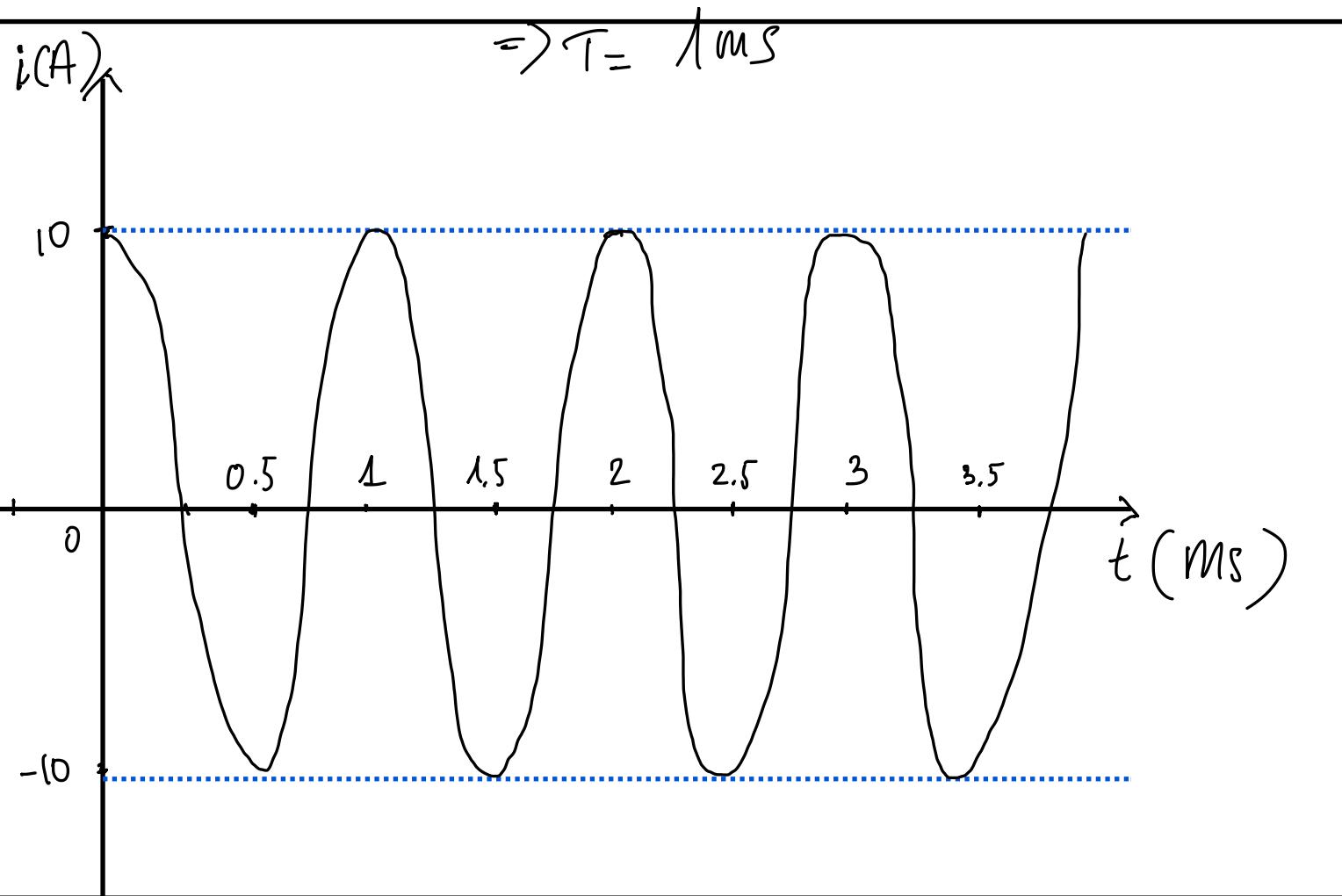


Home Work 6:

What to

Problem 1: Given $i(t) = 10 \cos(2000\pi t)$ flow through a 100Ω resistance

* Sketch $i(t)$. $\omega = 2000\pi = 2\pi f \Rightarrow f = 1000 \text{ Hz}$



⊕ We have :

$$\begin{aligned}
 p(t) &= i^2(t) \cdot R = [10 \cos(2000\pi t)]^2 \times 100 \text{ (W)} \\
 &= 10000 \cos^2(2000\pi t) \text{ (W)}
 \end{aligned}$$


Sketch p(t):

$$\text{Since } \cos^2(2000\pi t) = \frac{1 + \cos(4000\pi t)}{2}$$

$$\Rightarrow 10000 \cos^2(2000\pi t) = 5000(1 + \cos(4000\pi t))$$

$$\Rightarrow \omega = 4000\pi = 2\pi f \Rightarrow f = 2000 \text{ Hz}$$


$$\Rightarrow T = 0.5 \text{ ms}$$

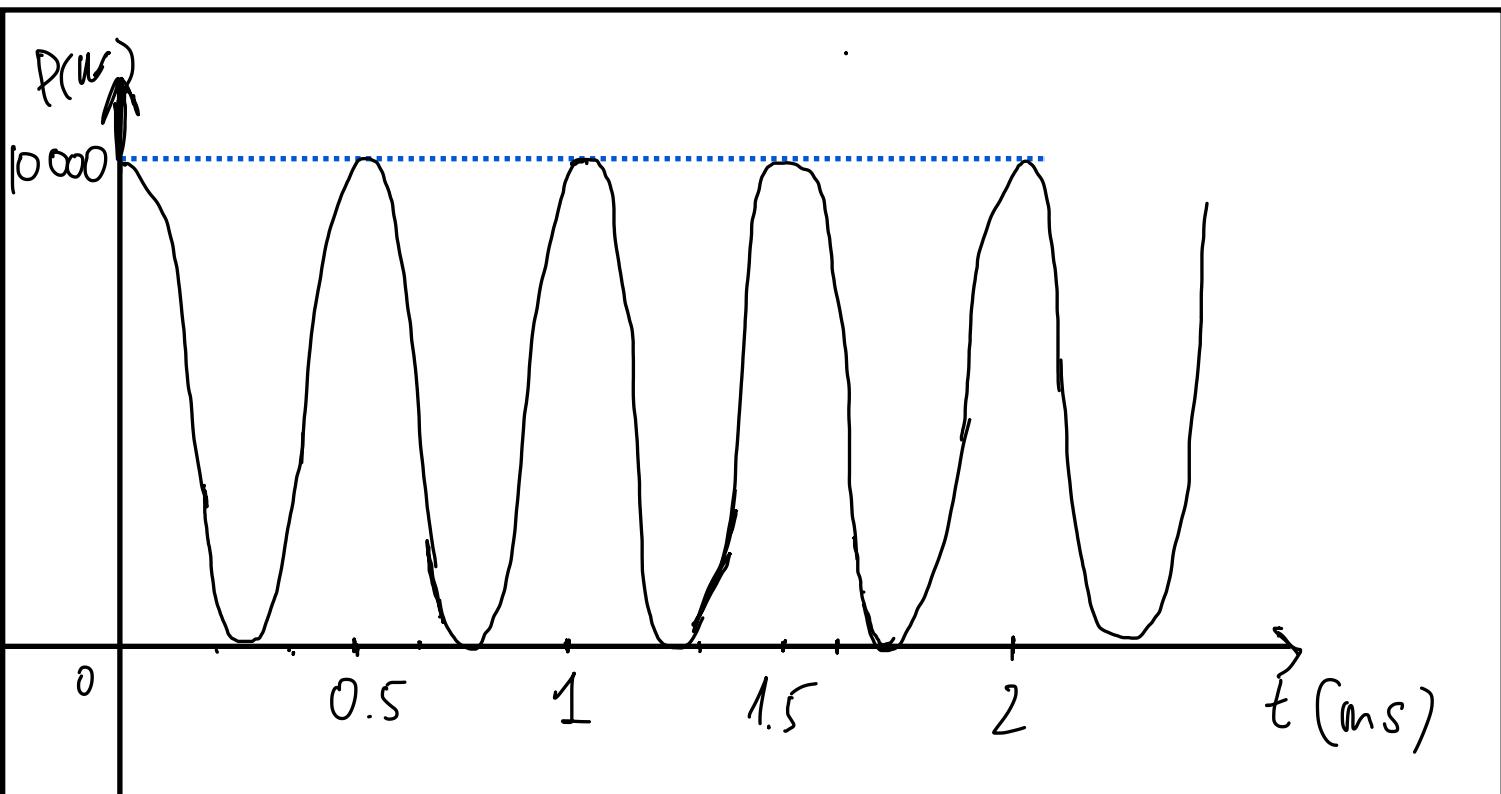

* Average power: We have $I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} \text{ (A)}$

$$\Rightarrow P_{avg} = I_{rms}^2 \times R = \frac{10^2}{2} \times 100 = \boxed{5000 \text{ (W)}}$$

Problem 2:

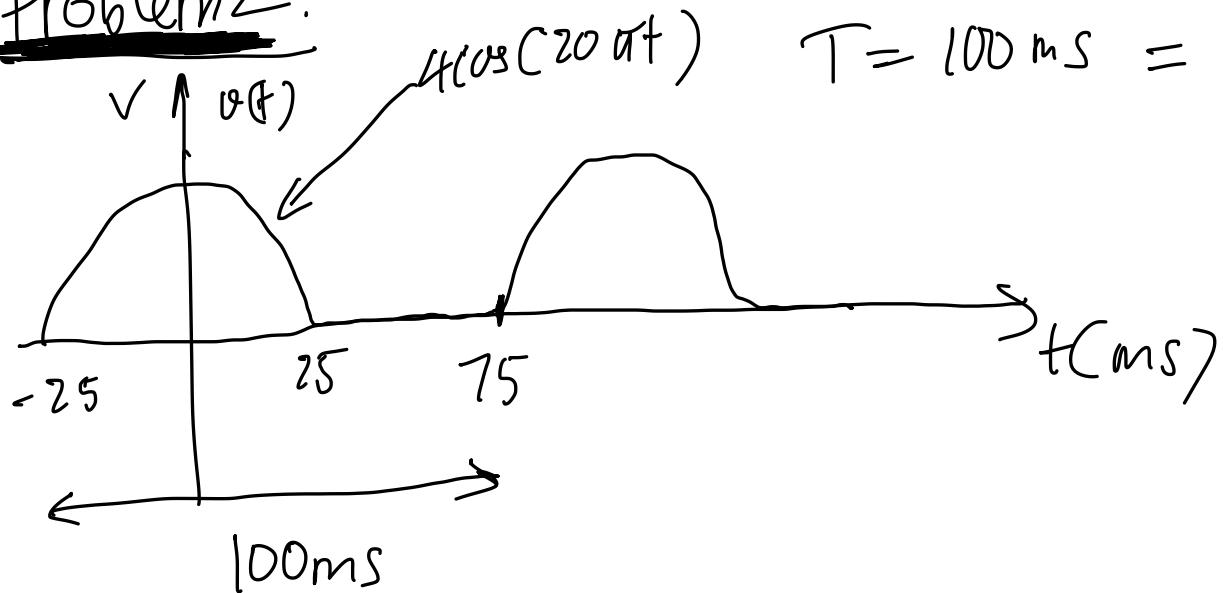

$$\text{We have: } V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$\Rightarrow V_{\text{rms}}^2 = \frac{1}{T} \int_0^T v^2(t) dt$$

Check the period from $-25 \rightarrow 75$, we have:

$$v(t) = \begin{cases} 4 \cos(20\pi t), & -25 \leq t \leq 25 \text{ (ms)} \\ 0, & 25 \leq t \leq 75 \text{ (ms)} \end{cases}$$

$$\Rightarrow V_{\text{rms}}^2 = \frac{1}{0.1} \left[\int_{-0.025}^{0.025} [4 \cos(20\pi t)]^2 dt \right]$$

$$= 160 \int_{0.025}^{0.025} \cos^2(20\pi t) dt .$$

$$\text{Also, } \int_{-0.025}^{0.025} \cos^2(20\pi t) dt = \int_{-0.025}^{0.025} \frac{1 + \cos(40\pi t)}{2} dt$$

$$= \int_{-0.025}^{0.025} \frac{1}{2} dt + \int_{-0.025}^{0.025} \cos(40\pi t) dt$$

$$= \frac{1}{2} (0.025 + 0.025) + \frac{1}{2} \cdot \frac{1}{40\pi} \sin(40\pi t) \Big|_{-0.025}^{0.025}$$

$$= 0.025 + \frac{1}{80\pi} [\sin 0 + \sin 0]$$


$$= 0.025 .$$

$$\Rightarrow V_{\text{rms}}^2 = 160 \times 0.025 = 4$$

$$\Rightarrow V_{\text{rms}} = \sqrt{4} = 2(V)$$

Problem 3: Given:

$$f = 200 \text{ Hz}$$

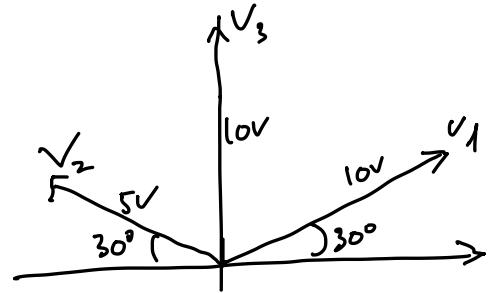

$$\text{Since } \omega = 2\pi f \Rightarrow \omega = 2\pi \times 200 = 400\pi \text{ (rad/s)}$$

From the diagram, we see that the V_1 is 30° leading with the reference line & has $V_m = 10V$
 $\Rightarrow V_1 = V_m \cos(\omega t + \theta) \Leftrightarrow$

$$V_1 = 10 \cos(400\pi t + 30^\circ) \quad (\text{V})$$

For the V_3 , it has $V_m = 10V$ & $\theta = 90^\circ$ from the diagram

$$\Rightarrow V_3 = 10 \cos(400\pi t + 90^\circ) \quad (\text{V})$$

For the V_2 , it has $V_m = 5V$ & the degree of it will be equal $180^\circ - 30^\circ = 150^\circ$ lead the reference line

$$\Rightarrow V_2 = 5 \cos(400\pi t + 150^\circ) \quad (\text{V})$$

- Also, from the diagram, we have:

V_1 lags V_3 by 60°

V_1 lags V_2 by 120°

V_3 lags V_2 by 60°

Problem 4:

a) The current and voltage for a certain circuit element is shown in Figure A of the figure.

Determine the nature and value of the element

From the figure A, we know the period of current & voltage wave form is

$$T = 2 \text{ ms} \Rightarrow f = \frac{1}{T} = \frac{1}{2 \times 10^{-3}} = 500 \text{ Hz}$$

$$\Rightarrow \omega = 2\pi f = 2 \times \pi \times 500 = 1000\pi \text{ (rad/s)}$$

Also we have the peak value of current

$$I_m = 5(\text{mA}) = 5 \times 10^{-3}(\text{A})$$

$$\Rightarrow i(t) = I_m \cos(\omega t + \theta) (\text{A})$$

$$\Rightarrow i(t) = 5 \times 10^{-3} \cos(1000\pi t + \theta) (\text{A})$$

Since the current gets maximum value at $t=0$ (from the figure) $\Rightarrow 5 \times 10^{-3} \cos(\theta) = I_m$

\Rightarrow the phase angle of current is $\theta = 0^\circ$

$$\Rightarrow i(t) = 5 \times 10^{-3} \cos(1000\pi t) \text{ (A)}$$

$$\Leftrightarrow I = 5 \times 10^{-3} \angle 0^\circ \text{ (A)} \quad ①$$

* Also, the maximum of voltage at 0.5 ms

\Rightarrow the different time between the current & voltage is 0.5 ms . From the figure we can have $\theta_i - \theta_v = \theta = \omega t$ with $t = 0.5 \text{ ms}$ as their different time.

$$\Rightarrow 0 - \theta_v = 1000\pi \times 0.5 \times 10^{-3} = \frac{\pi}{2}$$

$$\Rightarrow \theta_v = -\frac{\pi}{2} = -90^\circ$$

Also, the peak value of voltage $V_m = 1 \text{ V}$

$$\Rightarrow v(t) = V_m \cos(\omega t + \theta) = 1 \cos(1000\pi t - 90^\circ) \quad (V)$$

$$\Rightarrow V = 1 \angle -90^\circ \text{ (V)} \quad ②$$

From ① & ②, we have:

$$V = 1 \angle -90^\circ \quad (\checkmark)$$

$$I = 5 \times 10^{-3} \angle 0^\circ \quad (A)$$

\Rightarrow Voltage lags the current by 90°

\Rightarrow the component is pure capacitance

$$\Rightarrow Z_C = \frac{V_C}{I_C} \Rightarrow \frac{1}{\omega C} \angle -90^\circ = \frac{1 \angle -90^\circ}{5 \times 10^{-3} \angle 0^\circ} = 200 \angle -90^\circ$$

$$\Rightarrow \frac{1}{\omega C} = 200 \Rightarrow C = \frac{1}{\omega \times 200}$$

$$\Rightarrow C = \frac{1}{1000\pi \times 200} = 1.59 \times 10^{-6} F$$

$$\Leftrightarrow C = 1.59 \mu F$$

b) Repeat for b.

From the figure B of HomeWork, we have
the period time of both current and voltage
is $16 \text{ ms} \Rightarrow T = 16 \text{ ms} \Rightarrow f = \frac{1}{16 \times 10^{-3}}$
 $\Rightarrow f = 62.5 \text{ Hz} \Rightarrow \omega = 2\pi f = 2 \times 62.5\pi$
 $\Rightarrow \omega = 125\pi \text{ (rad/s)}$.

Also we have the peak value of voltage.

$$V_m = 4V \Rightarrow v(t) = V_m \cos(\omega t + \theta) \quad (V)$$

$$\Rightarrow v(t) = 4 \cos(125\pi t + \theta) \quad (V)$$

Since $v(t)$ gets maximum value V_m at $t = 4 \text{ ms}$

$$\Rightarrow \cos(125\pi \times 4 \times 10^{-3} + \theta) = 1$$

$$\Rightarrow \cos(0.5\pi + \theta) = 1$$

$$\Rightarrow \theta = -\frac{\pi}{2}$$

$$\Rightarrow v(t) = 4 \cos(125\pi t - \frac{\pi}{2}) \quad V$$

$$\Leftrightarrow V = 4 \angle -90^\circ \text{ (V)} \quad (1)$$

⊕ From the figure 3, we know the voltage gets maximum value at $t = 4 \text{ ms}$ while the current gets maximum value at $t = 8 \text{ ms}$

\Rightarrow the different time between them $\Delta t = 4 \text{ ms}$

$\Rightarrow \theta_r - \theta_i = \theta = \omega \cdot \Delta t$

$\Rightarrow -90^\circ - \theta_i = 125\pi \times 4 \times 10^{-3} = \frac{\pi}{2}$

$\Rightarrow \theta_i = -\frac{\pi}{2} - \frac{\pi}{2} = -\pi.$

Also $I_m = 10 \text{ mA}$

$\Rightarrow i(t) = I_m \cos(\omega t + \theta)$

$\Leftrightarrow i(t) = 10 \times 10^{-3} \cos(125\pi t - \pi) \text{ (A)}$

$\Rightarrow I = 10^{-2} \angle -\pi \text{ (A)} \quad (2)$

From ① & ②, we have:

$$V = 4 \angle -90^\circ \text{ (V)} \quad | \Rightarrow \text{voltage leads current by } 90^\circ$$

$$I = 10^{-2} \angle -180^\circ \text{ (A)} \quad | \Rightarrow \text{current by } 90^\circ$$

\Rightarrow the component is pure inductance


$$\Rightarrow Z_L = \frac{V_L}{I_L} = \frac{4 \angle -90^\circ}{10^{-2} \angle -180^\circ} = j\omega L$$

$$\Rightarrow j\omega L = 400 \angle 90^\circ \Rightarrow \omega L = 400$$

$$\Rightarrow L = \frac{400}{\omega} = \frac{400}{125\pi} = 1.02 \text{ H}$$

$$\Rightarrow L \approx 1.02 \text{ H}$$

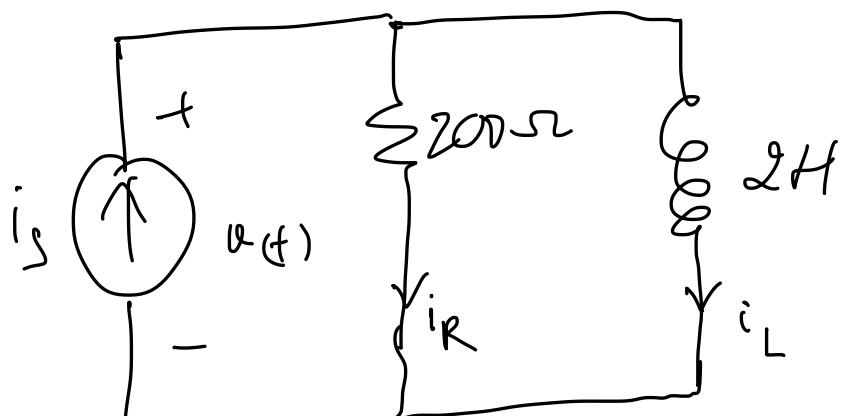Problem 5: Given $i_s = 0.5 \sin(100t)$ (A)



We have:

$$w = 100 \text{ rad/s}$$

$$\Rightarrow Z_L = jwL$$


$$= j100 \times 2$$

$$= 200j$$

$$\text{Since } (R \parallel L) \Rightarrow Z_{eq} = \frac{R \times Z_L}{R + Z_L} = \frac{200 \times 200j}{200 + 200j}$$

$$= \frac{200j}{1+j} = 100 + 100j \text{ (}\Omega\text{)}$$

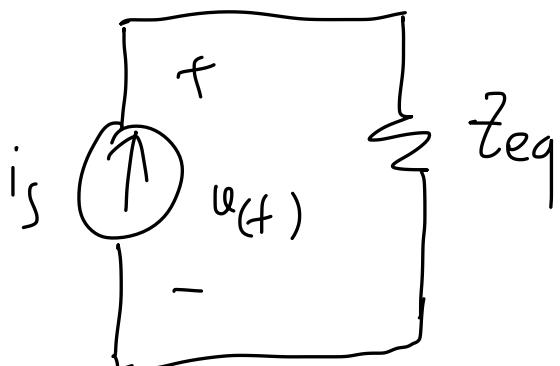\Rightarrow new circuit: $i_s(t) = 0.5 \sin(100t)$ (A)



$$= 0.5 \cos(100t - \pi/2)$$

$$= 0.5 \angle -90^\circ \text{ (A)}$$


$$\Rightarrow v(t) = i_s(t) \times Z_{eq} = (100 + 100j) 0.5 \angle -90^\circ$$

$$v_{(A)} = 50 - 50j = \boxed{70.7 \angle -45^\circ} \quad (V)$$

$$\Rightarrow i_R = \frac{v_{(A)}}{R} = \frac{70.7 \angle -45^\circ}{200}$$

$$\Rightarrow i_R = \boxed{0.3535 \angle -45^\circ} \quad (A)$$

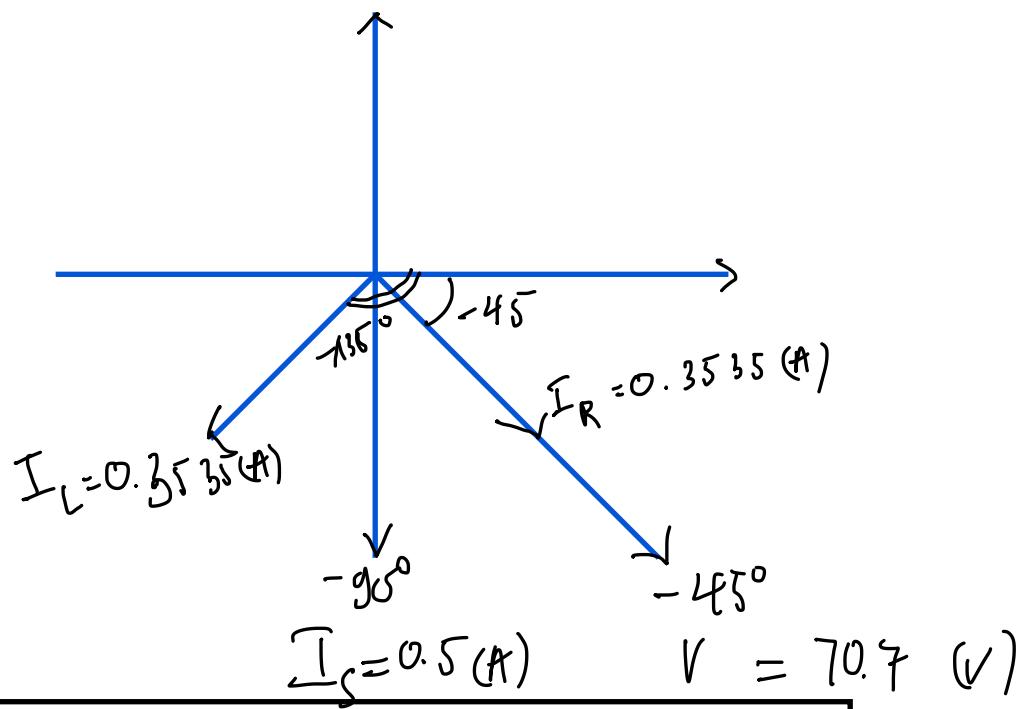
$$i_L = \frac{v_{(A)}}{Z_L} = \frac{70.7 \angle -45^\circ}{200j} = \boxed{0.3535 \angle -135^\circ} \quad (A)$$



Relationship between V & I_S :

Voltage V leads the current I_S by 45° .

Problem 6:

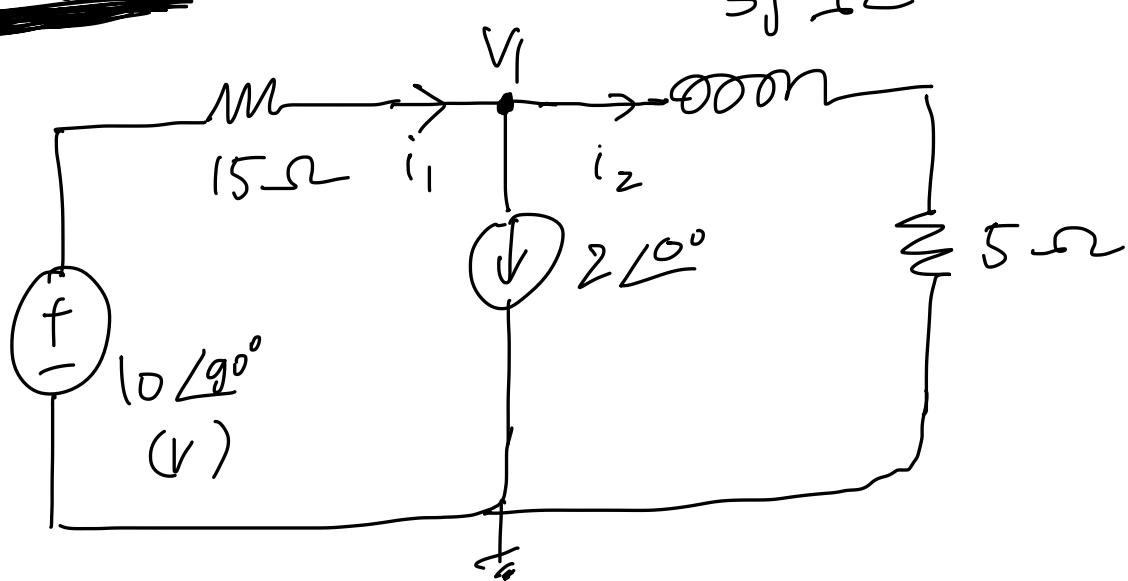

Apply KCL at V_1 : $i = 2\angle 0^\circ + i_2$

$$\Rightarrow \frac{10\angle 90^\circ - V_1}{15\Omega} = 2\angle 0^\circ + \frac{V_1}{5j + 5}$$


$$\Rightarrow \frac{10\angle 90^\circ}{15} - 2\angle 0^\circ = \frac{V_1}{5j + 5} + \frac{V_1}{15}$$

$$\Rightarrow -2 + \frac{2}{3}j = \left(\frac{1}{5j + 5} + \frac{1}{15} \right) V_1 =$$

$$\Rightarrow V_1 = -10.588 - 2.353j \quad (V)$$

$$\text{or } V_1 = 10.847 \angle -167.47^\circ \quad (V)$$

Problem 7 :

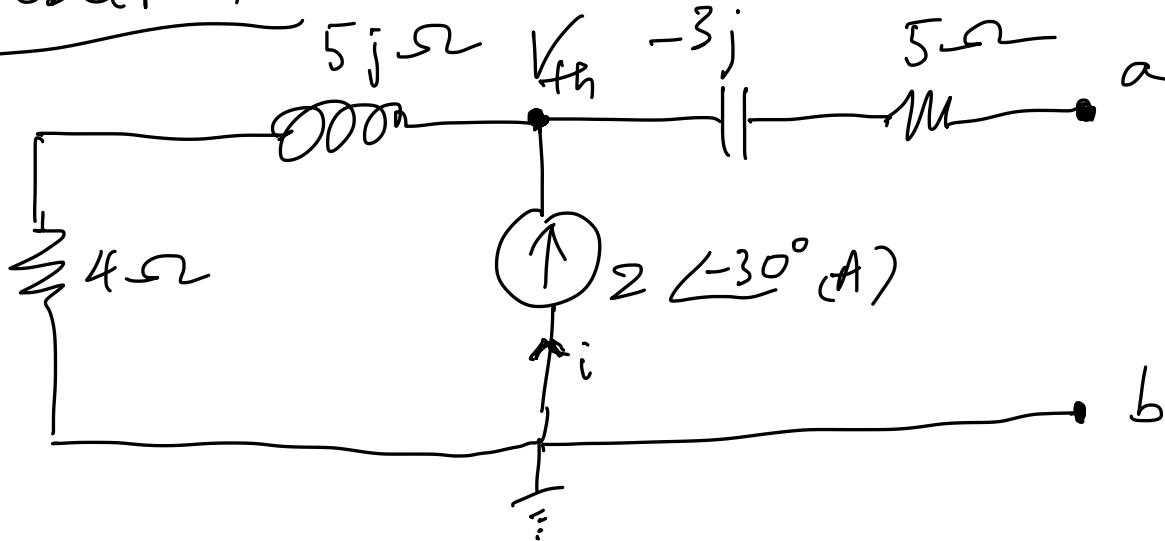


Find V_{th} : We have $V_{th} = i \times (5j + 4)\Omega$

$$\Rightarrow V_{th} = 2 \angle -30^\circ \times (4 + 5j)$$

$$\Rightarrow V_{th} = 12.806 \angle 21.34^\circ (V)$$

Find Z_{th} : We have new circuit

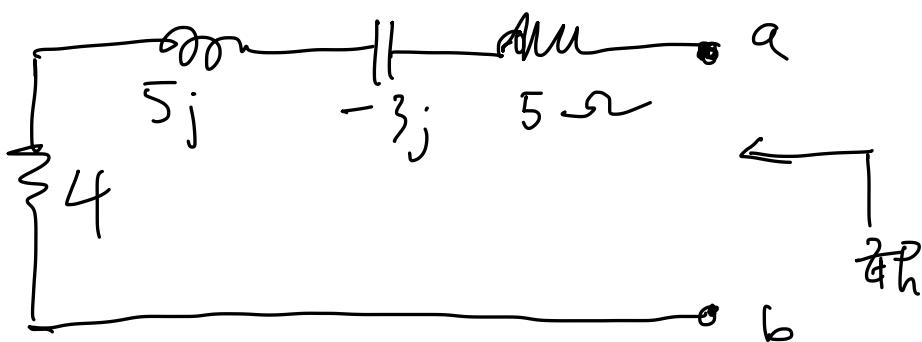


$$\Rightarrow Z_{th} = 4 + 5j - 3j + 5 = 9 + 2j (\Omega)$$

$$\Rightarrow I_{N_{\text{Notn}}} = \frac{V_{th}}{Z_{th}} = \frac{12.806 \angle 21.34^\circ}{j + z_j}$$


$$\Rightarrow I_N = 1.389 \angle 8.81^\circ \text{ (A)}$$

We have:

Thevenin:

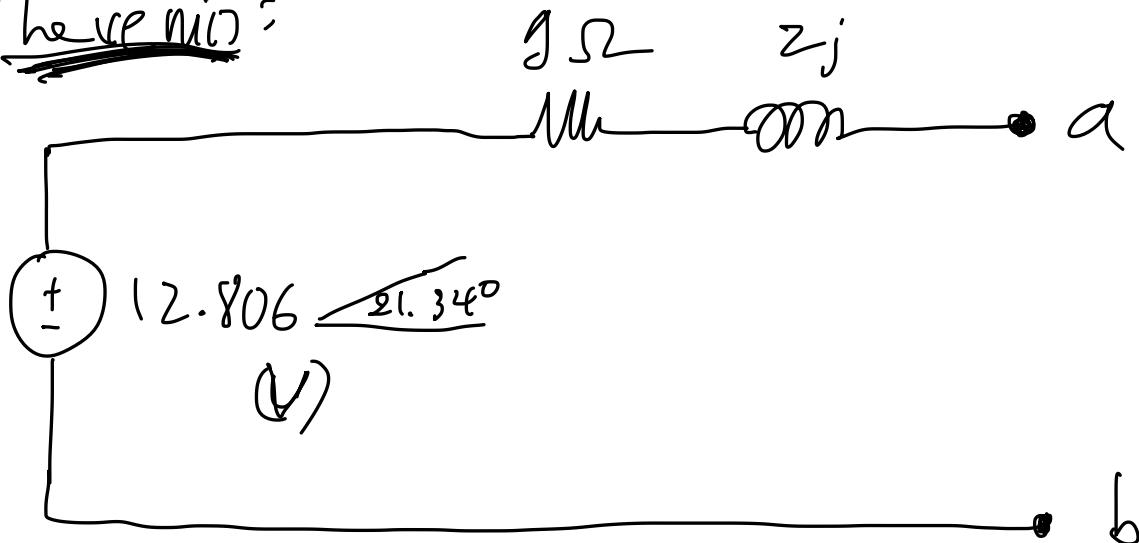


Norton:

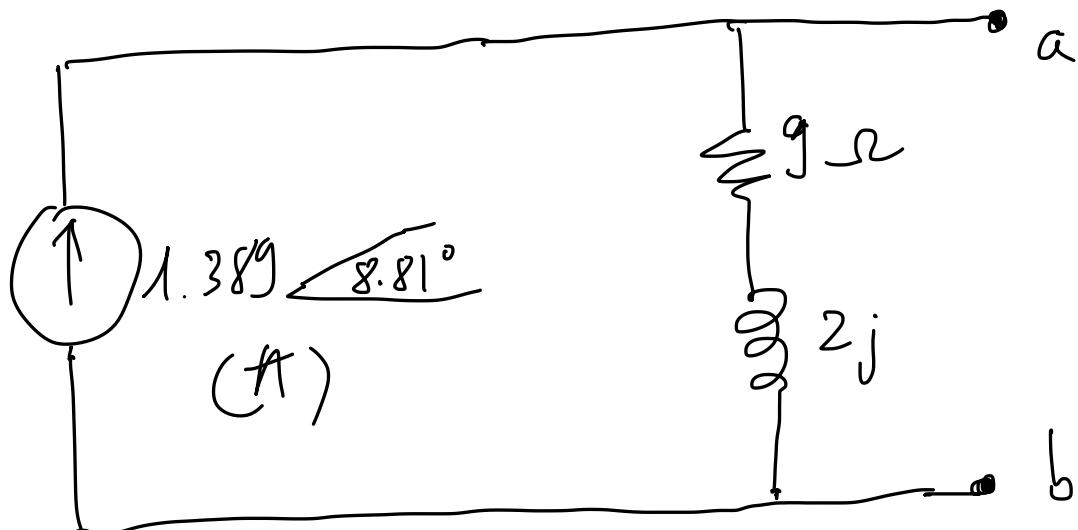

Problem 8 :

We have the circuit :-

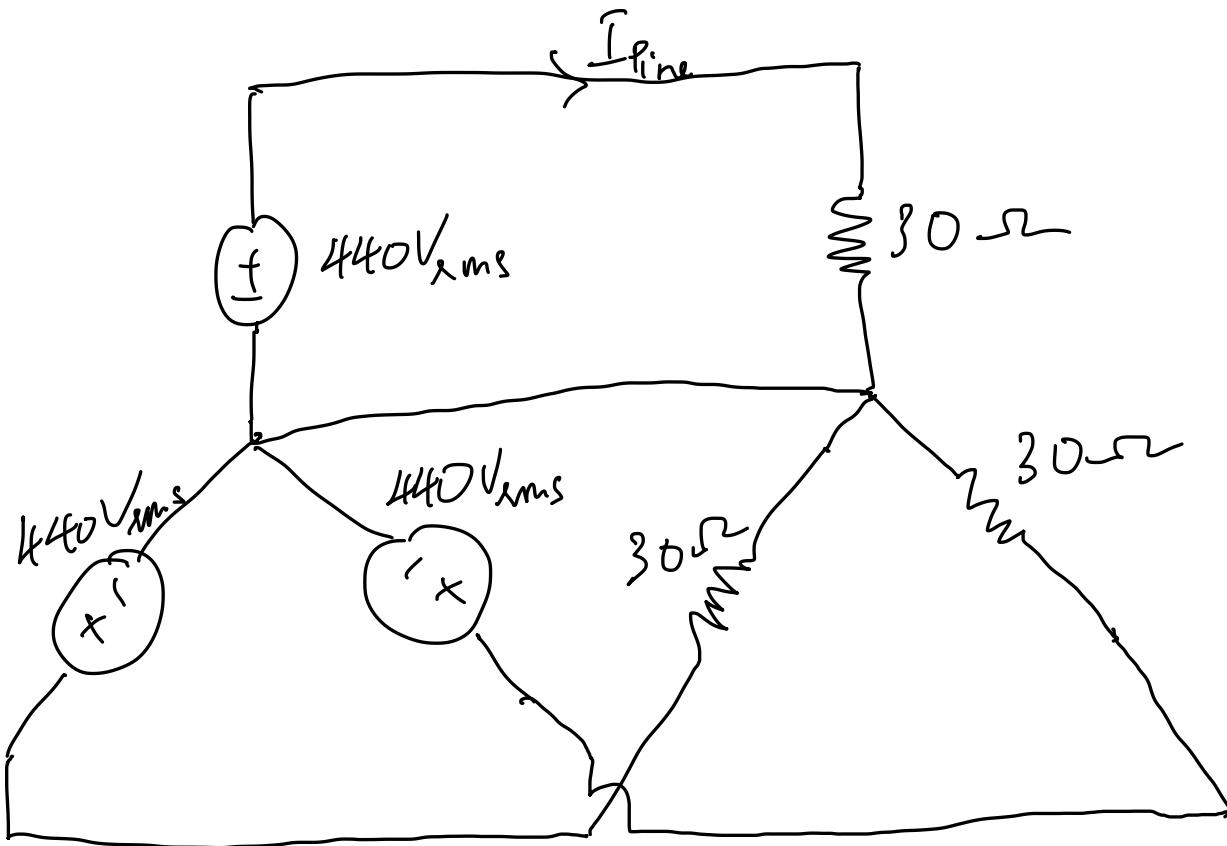

$$\text{Given } V_{\text{an}} = 440 \text{ V}_{\text{rms}}$$

$$\text{In connected star, } V_{\text{line-line}} = \sqrt{3} V_{\text{line-neutral}} = \sqrt{3} V_{\text{an}}$$

$$\Rightarrow V_{\text{line-line}} = \sqrt{3} \times 440 \text{ V}_{\text{rms}} = 726.1 \text{ V}_{\text{rms}}$$

$$\text{Also } I_{\text{line}} = \frac{V_{\text{line-neutral}}}{R} = \frac{440 \text{ V}_{\text{rms}}}{30 \Omega} = 14.67 \text{ A}_{\text{rms}}$$

$$\Rightarrow I_{\text{line}} = 14.67 \text{ A}_{\text{rms}}$$

The power from one voltage source :

$$P_1 = \frac{V_{rms}^2}{R} = \frac{440^2}{30\Omega} = 6453.33(W)$$

$$\Rightarrow P_1 = 6.453 (kW)$$


Since this is an balanced Wye - connected 3 phases

$$\Rightarrow P_{total} = P_1 + P_2 + P_3 = 3P_1 = \boxed{19.36(kW)}$$

Problem 9:

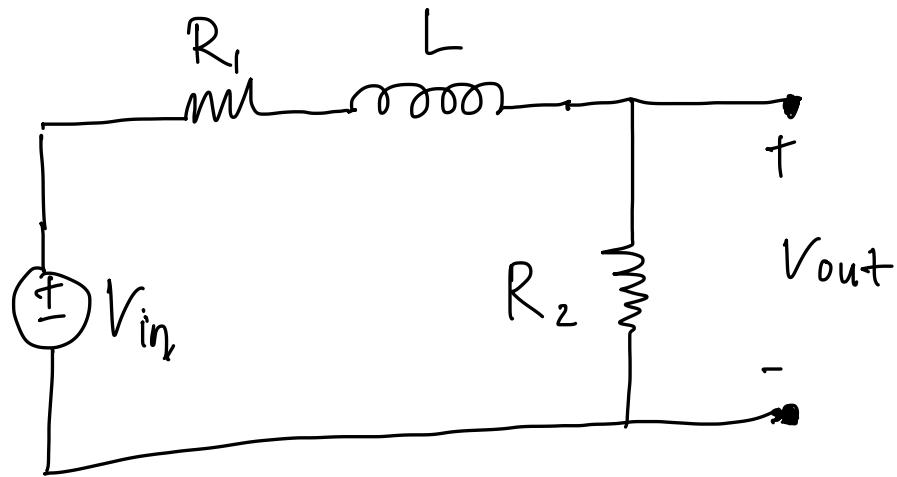a) Derive an expression for the transfer function

$H(f) = \frac{V_{out}}{V_{in}}$. Find an expression for the half power frequency



$$\text{We have : } Z_L = j\omega L$$

$$\text{Using Voltage divider, } V_{out} = \frac{R_2}{R_1 + R_2 + j\omega L} V_{in}$$

$$\Rightarrow H(f) = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2 + j\omega L} = \frac{R_2}{(R_1 + R_2) \left(1 + \frac{j\omega L}{R_1 + R_2} \right)}$$

$$= \frac{R_2}{R_1 + R_2} \times \frac{1}{1 + j \frac{\omega L}{R_1 + R_2}}$$

$$\text{Check for: } \frac{WL}{R_1+R_2} = \frac{2\pi f L}{R_1+R_2} = \frac{f}{\frac{R_1+R_2}{2\pi L}}$$

$$\Rightarrow H(f) = \frac{R_2}{R_1+R_2} \times \frac{1}{1+j \frac{f}{\left(\frac{R_1+R_2}{2\pi L}\right)}}$$

$$\Rightarrow f_B = \frac{R_1+R_2}{2\pi L} \quad \textcircled{1}$$

then, we have:

$$H(f) = \frac{R_2}{R_1+R_2} \times \frac{1}{1+j\left(\frac{f}{f_B}\right)}$$


b) Given $R_1 = 50 \Omega$, $R_2 = 50 \Omega$, $L = 15 \mu H$
 Sketch the magnitude of the transfer functions
 versus frequency

We use these values to plug into ①, then

$$f_B = \frac{50+50}{2\pi \times 15 \times 10^{-6}} = 1.06 \times 10^6 \text{ Hz}$$

$$= 1.06 \text{ MHz}$$

$$\Rightarrow H(f) = \frac{1}{1+j\frac{f}{1.06 \times 10^6}} \times \frac{50}{50+50} = \frac{0.5}{1+j\frac{f}{1.06 \times 10^6}}$$

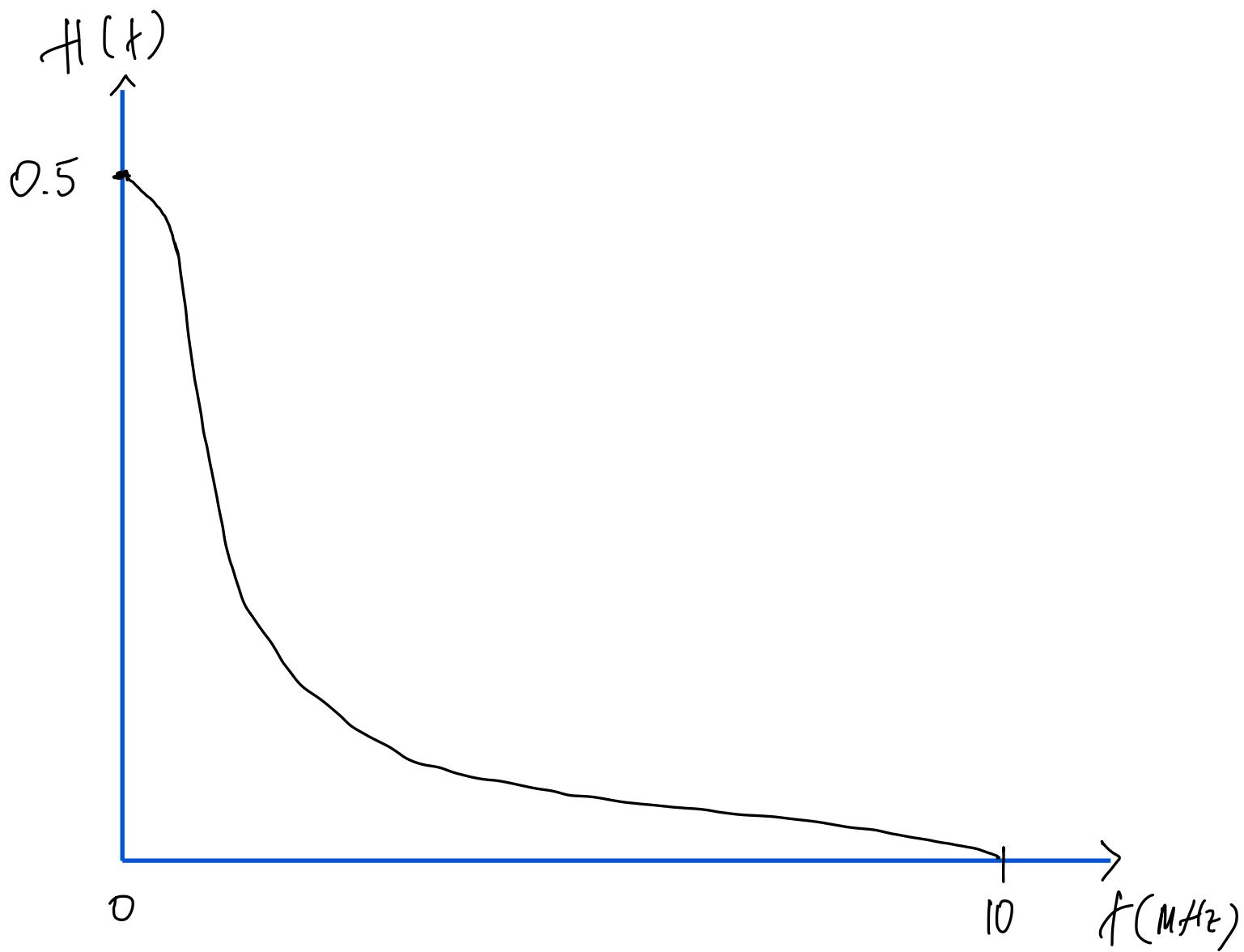

Problem 10:

a) Given $R = 5\text{ k}\Omega$, $L = 50\mu\text{H}$, $C = 200\text{ pF}$

$$\Rightarrow \text{Resonant frequency: } f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{50 \times 10^{-6} \times 200 \times 10^{-12}}} = 1.592 \times 10^6 \text{ Hz}$$

$$\Rightarrow f_0 = 1.592 \text{ MHz}$$

* Quality factor:

$$Q_p = 2\pi f_0 CR = 2\pi \times 1.592 \times 10^6 \times 200 \times 10^{-12} \times 5 \times 10^3$$

$$\Rightarrow Q_p = 10$$

$$\Rightarrow \text{the bandwidth: } B = \frac{f_0}{Q_p} = \frac{1.592 \times 10^6}{10}$$

$$= 159.2 \times 10^5 \text{ Hz} \Rightarrow B = 159.2 \text{ KHz}$$

b) Determine L & C , given $R = 1\text{ k}\Omega$, $f_0 = 10\text{ MHz}$

$$B = 500\text{ kHz}$$

We have: $\beta = \frac{f_0}{Q_p} \Rightarrow Q_p = \frac{f_0}{B} = \frac{10 \times 10^6}{500 \times 10^3}$

$$\Rightarrow Q_p = 20.$$

Also, $Q_p = 2\pi f_0 CR \Rightarrow C = \frac{Q_p}{2\pi f_0 R}$

$$= \frac{20}{2\pi \times 10 \times 10^6 \times 1000} = 3.183 \times 10^{-10} (\text{F})$$


$$\Rightarrow C = 0.3183 (\text{nF})$$

Besides, $Q_p = \frac{R}{2\pi f_0 L} \Rightarrow L = \frac{R}{2\pi f_0 Q_p}$

$$= \frac{1000}{2\pi \times 10^7 \times 20} = 0.796 \times 10^{-6} (\text{H})$$

$$\Rightarrow L = 0.796 (\mu\text{H})$$

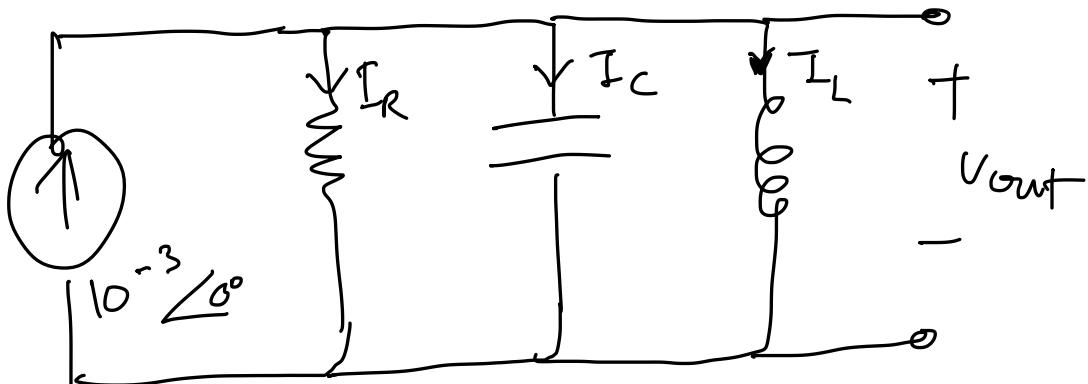We have: $I = 10^{-3} = 10^{-3} \angle 0^\circ$



At resonance, $V_{out} = IR = 10^{-3} \angle 0^\circ \times 1000$

$$\Rightarrow V_{out} = 1 \angle 0^\circ \text{ (V)}$$

$$\Rightarrow I_R = \frac{V_{out}}{R} = \frac{1 \angle 0^\circ}{1000} = 10^{-3} \angle 0^\circ \text{ (A)}$$

$$\Rightarrow I_R = 1 \angle 0^\circ \text{ (mA)}$$

$$\oplus I_C = \frac{V_{out}}{Z_C} = \frac{V_{out}}{\frac{-j}{2\pi f_0 C}} = \frac{j V_{out}}{\frac{1}{2\pi f_0 C}}$$

$$= j V_{out} 2\pi f_0 C = j \cdot 1 \angle 0^\circ \times 2\pi \times 10^7 \times 0.3183 \times 10^{-9}$$

$$\approx 0.02 \angle 90^\circ \text{ (A)}$$

$$\Rightarrow I_C = 20 \angle 90^\circ (\text{mA})$$

$$\oplus I_L = \frac{V_{out}}{Z_L} = \frac{V_{out}}{j2\pi f_0 L} = \frac{1 \angle 0^\circ}{j2\pi \times 10^7 \times 0.796 \times 10^{-6}}$$

$$= 0.02 \angle -90^\circ (\text{A})$$

$$\Rightarrow I_L = 20 \angle -90^\circ (\text{mA})$$

The phasor diagram :

