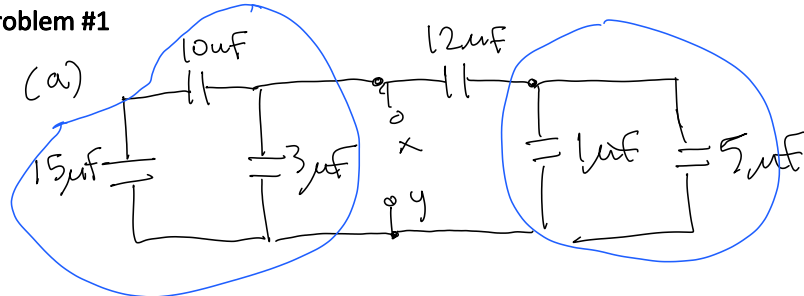


Homework #3 Solutions


Sunday, April 11, 2021 10:11 PM

Problem #1





① $\frac{10 \times 15}{10 + 15} \parallel 3 = \frac{1}{\frac{1}{\frac{150}{25}} + 3} = 9 \mu F$

② $1 \parallel 5 = 6 \mu F$

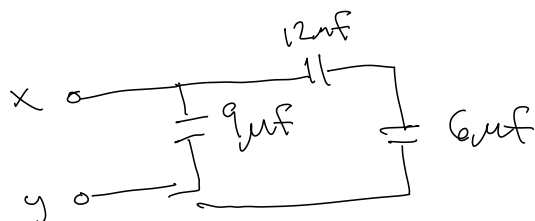

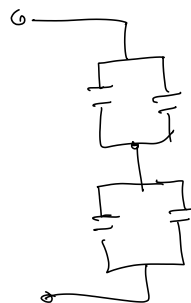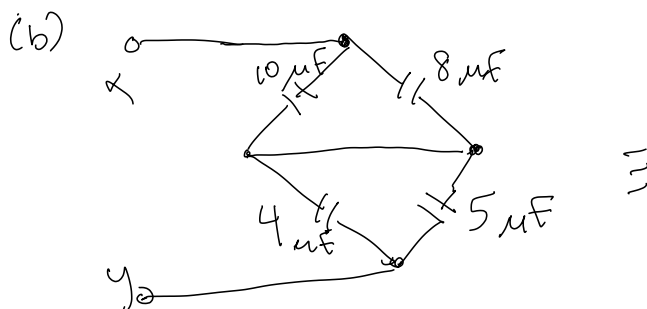
$$C_{eq} = 9 \mu F + \frac{6 \times 12}{6 + 12} = 13 \mu F$$



$$C_{eq} = 18 \parallel 9 = 6 \mu F$$

Problem #2

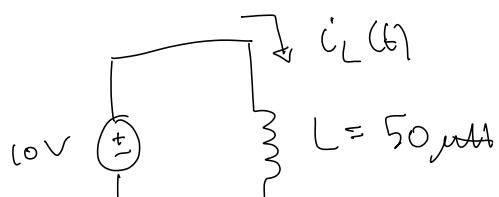

$$i_L(t=0) = -100 \text{ mA}$$

$$V_L(t) = 50 \mu H \times \frac{di_L(t)}{dt} = 10 \text{ V}$$

$$\rightarrow \frac{di_L}{dt} = 2 \times 10^5 \frac{A}{s}$$

(a) $i_L(t = t_x) = +100 \text{ mA}$


$$\frac{\Delta i}{\Delta t} = \frac{+100 \text{ mA} - (-100 \text{ mA})}{\Delta t} = 2 \times 10^5 \frac{A}{s}$$

$$\rightarrow t_x = \Delta t = 1 \mu s$$


(b) why is this circuit unrealistic?

Because if $\frac{di_L}{dt}$ is always > 0 , then it implies that $i_L(t) \rightarrow \infty$ (as $t \rightarrow \infty$). The circuit would stop working well before that point as it would either (1) burn up or (2) parasitic resistances would limit the current that can flow through the inductor ("resistance-limited circuit")

Problem #3

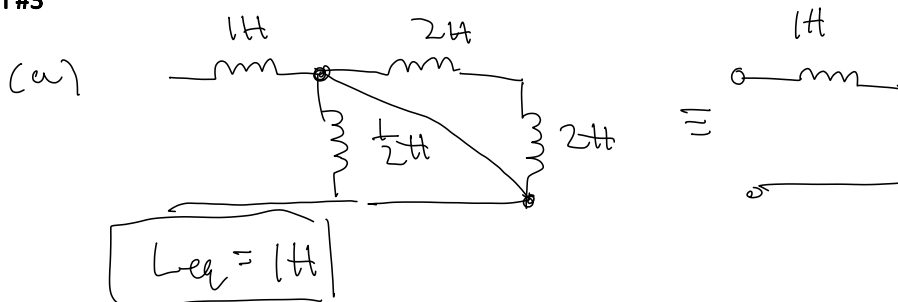

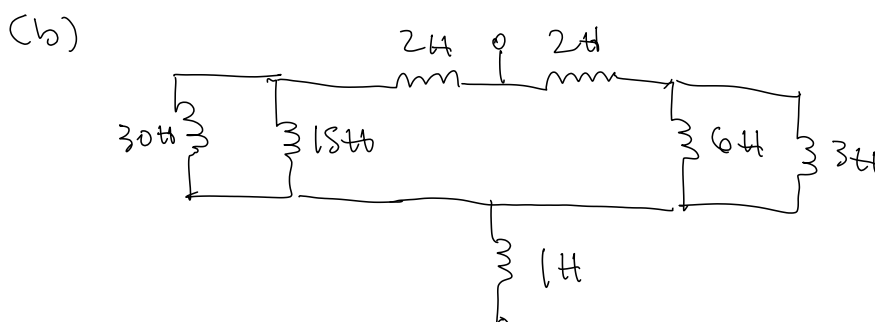
* $\frac{1}{2}H$ and $4H$ ($2+2$) inductors have no effect as they are in parallel w/ a short circuit



$$L_{eq} = 1H + [(30 \parallel 15) + 2] \parallel [(6 \parallel 3) + 2]$$

$$= 1H + 12H \parallel 4H = 1H + 3H = \boxed{4H}$$

Problem #4

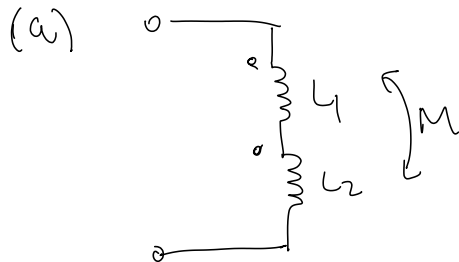


$$V(t) = V_1(t) + V_2(t)$$

$$V_1(t) = L_1 \frac{di}{dt} + M \frac{di}{dt}$$

$$V_2(t) = L_2 \frac{di}{dt} + M \frac{di}{dt}$$

$$V(t) = [L_1 + L_2 + 2M] \frac{di}{dt}$$

$$\therefore L_{eq} = L_1 + L_2 + 2M$$

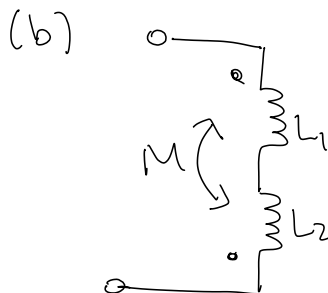


$$V_1(t) = L_1 \frac{di}{dt} - M \frac{di}{dt}$$

$$V_2(t) = L_2 \frac{di}{dt} - M \frac{di}{dt}$$

$$\rightarrow L_{eq} = L_1 + L_2 - 2M$$

Problem #5

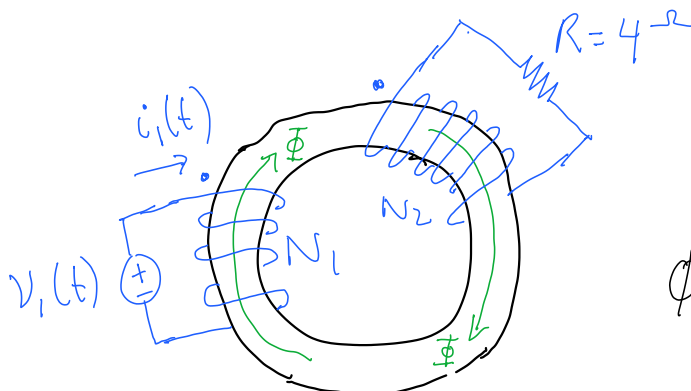

$$\Phi = \Phi_0 \sin(\omega t)$$

(a) $V_1(t)$

$$V_1(t) = N_1 \frac{d\phi}{dt} = \boxed{N_1 \phi_0 \omega \cos(\omega t)}$$

(b) $i_1(t)$

$$i_2(t) = \frac{V_2(t)}{4\Omega} = \frac{1}{4\Omega} \times N_2 \phi_0 \omega \cos(\omega t)$$

$$i_2 = \frac{1}{n} i_1 = \frac{N_1}{N_2} i_1 \Rightarrow i_1(t) = \frac{N_2}{N_1} i_2(t)$$

$$i_1(t) = \frac{N_2}{N_1} \times \frac{1}{4\Omega} \times N_2 \phi_0 \omega \cos(\omega t)$$


$$\boxed{i_1(t) = \frac{N_2^2}{N_1} \times \frac{1}{4\Omega} \times \phi_0 \omega \cos(\omega t)}$$

(c) $V_1(t) / i_1(t)$:

$$\frac{V_1(t)}{i_1(t)} = \frac{N_1 \cancel{\phi_0 \omega \cos(\omega t)}}{\left(\frac{N_2^2}{N_1} \times \frac{1}{4\Omega} \times \cancel{\phi_0 \omega \cos(\omega t)} \right)}$$

$$\boxed{\frac{V_1(t)}{i_1(t)} = \frac{N_1^2}{N_2^2} \times 4\Omega}$$



Problem #6

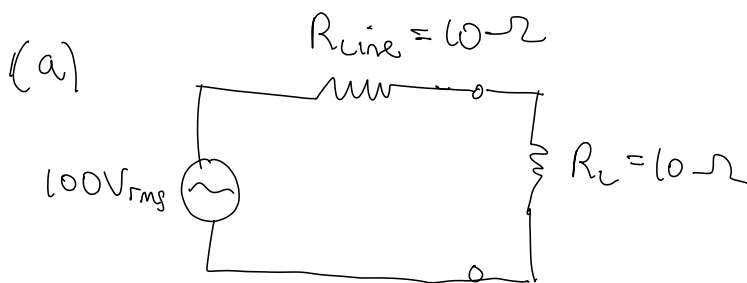


$$I = 5A_{rms}$$

- $P_{delivered} = 100V_{rms} \times 5A_{rms} = \underline{\underline{500W}}$ (average)
- $P_{dissipated-line} = I^2 R = (5A)^2 \times 10\Omega = \underline{\underline{250W}}$
- $P_{dissipated-load} = I^2 R = (5A)^2 \times 10\Omega = \underline{\underline{250W}}$
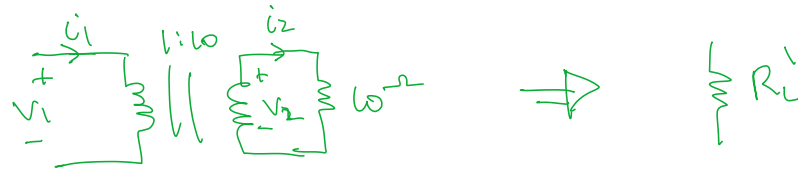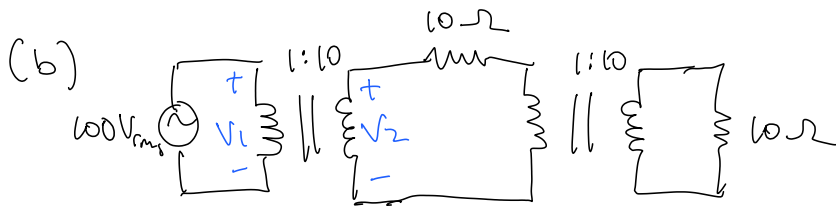
$$\bullet \text{ Efficiency} = \frac{P_{\text{Load}}}{P_{\text{delivered}}} = \frac{250 \text{ W}}{500 \text{ W}} = \boxed{50\%}$$



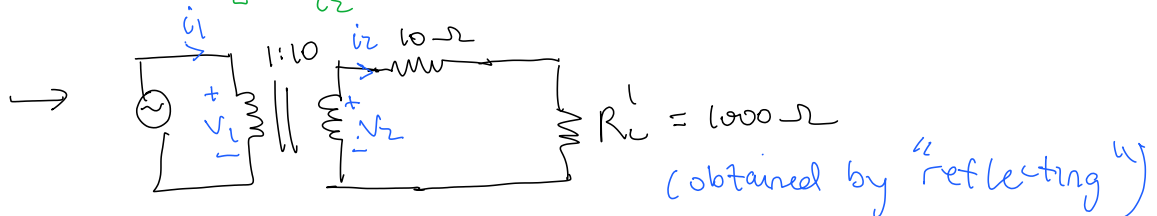
$$\left. \begin{array}{l} (1) \quad V_1 = 10 V_2 \\ (2) \quad i_1 = \frac{1}{10} i_2 \\ (3) \quad R_L = \frac{V_2}{i_2} = 10 \Omega \end{array} \right\} \quad \frac{V_1}{i_1} = \frac{10 V_2}{\left(\frac{1}{10} i_2\right)} = 100 \times \frac{V_2}{i_2} = 100 \times R_L = \underline{\underline{1000 \Omega}}$$



reflect again:

$$\begin{array}{l} (1) \quad V_1 = \frac{1}{10} V_2 \\ (2) \quad i_1 = 10 i_2 \\ (3) \quad \frac{V_2}{i_2} = (10 + 1000) \Omega = \underline{\underline{1010 \Omega}} \end{array}$$
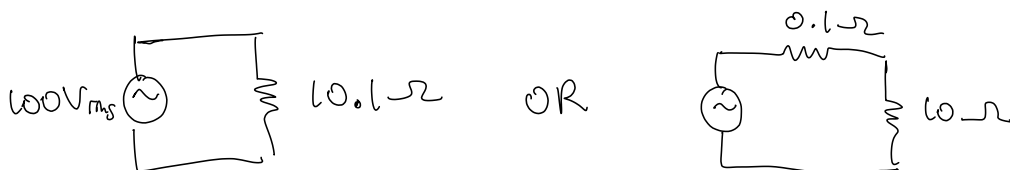
$$\Rightarrow \frac{V_1}{i_1} = \frac{1}{100} \times 1010 \Omega = \underline{\underline{10.1 \Omega}}$$




$$\bullet P_{\text{delivered}} = \frac{(100 \text{ V}_{\text{rms}})^2}{10.1 \Omega} \approx \underline{\underline{990.1 \text{ W}}}$$

$$\bullet P_{\text{dissipated-line}} = I^2 R = \left(\frac{100 \text{ V}_{\text{rms}}}{10.1 \Omega} \right)^2 \times 0.1 \Omega \approx \underline{\underline{9.8 \text{ W}}}$$

$$\bullet P_{\text{dissipated-load}} = I^2 R \approx \underline{\underline{980.3 \text{ W}}}$$

$$\bullet \text{ Efficiency} = \frac{P_{\text{load}}}{P_{\text{delivered}}} = \frac{980.3 \text{ W}}{990.1 \text{ W}} = \boxed{99\%}$$


Problem #7

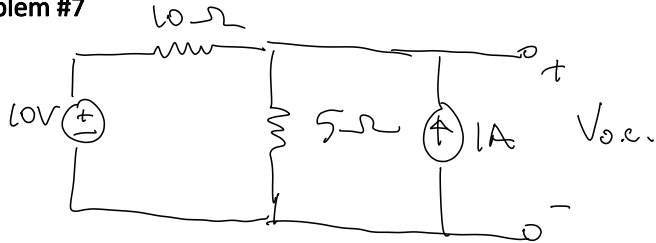


by KCL: $1\text{A} = \frac{V_{o.c.}}{5\Omega} + \frac{V_{o.c.} - 10\text{V}}{10\Omega}$

$$\underline{V_{o.c.} = 6.667\text{V}}$$


• zeroing sources:

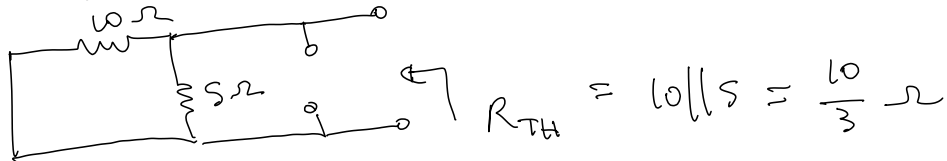



① Thevenin

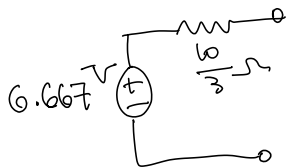

② Norton

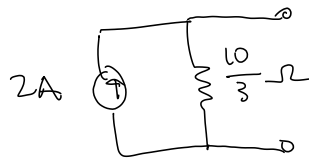

Problem #8

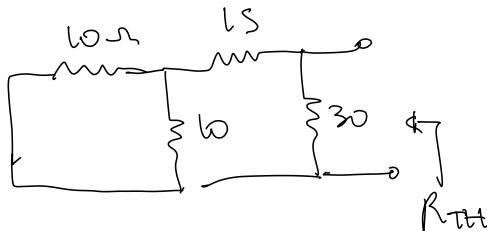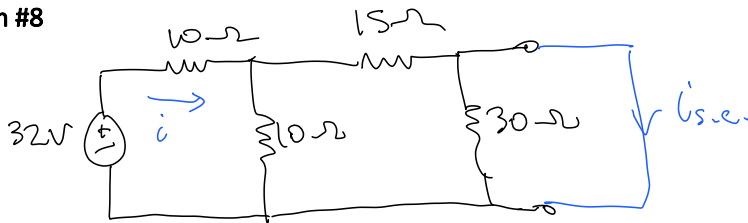


$$\begin{aligned} R_{TH} &= 30 || (15 + 10 || 10) \\ &= 30 || 20 = \underline{12\Omega} \end{aligned}$$

i : $i = \frac{32\text{V}}{R_{10\Omega || 15\Omega}} = \frac{32\text{V}}{16\Omega} = 2\text{A}$


$$L^{\infty} + w_{\parallel}^{\infty}$$

$$i_{s.c.} = \frac{10}{10+15} 2A = \boxed{\frac{4}{5}A}$$


Norton

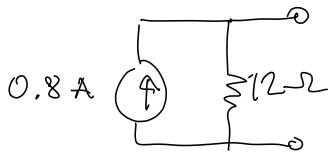

Thevenin

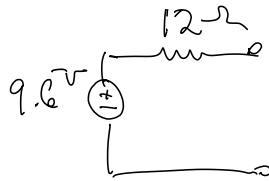

Problem #9

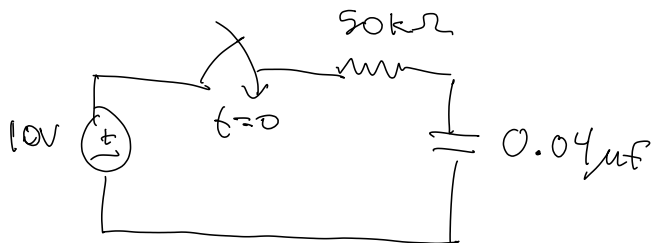

$$* V_C(0^+) = -10V$$

$$V_C[\infty] = 10V$$

$$V_C(t) = V[\infty] - (V[\infty] - V[0]) e^{-t/RC}$$

$$= 10V - (10 - (-10V)) e^{-t/RC}$$

$$V_C(t) = 10V - (20V) e^{-t/RC}$$

$$V_C(t_0) = 10 - 20 e^{-t_0/RC} = 0V$$

$$e^{-t_0/RC} = \frac{1}{2}$$

$$\rightarrow t_0 = -RC \times \ln\left(\frac{1}{2}\right) =$$

$$= - (50k\Omega)(0.04\mu F) \ln\left(\frac{1}{2}\right)$$

$$\approx \boxed{1.386ms}$$