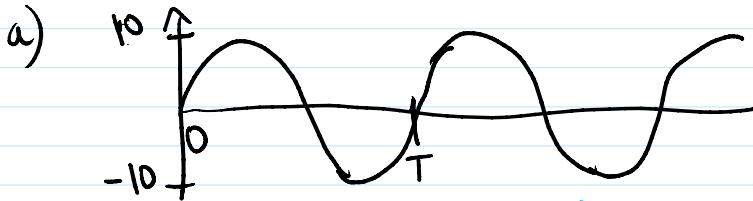


ECE 100 - Homework #1 Solutions

Problem 1

$$i(t) = 10 \sin(200\pi t) A$$



$$T = \frac{2\pi}{\omega} = \frac{2\pi}{200\pi} = \frac{1}{100} = 10 \text{ ms}$$

b)

$$Q = \int_0^{5 \text{ ms}} i dt$$

note: $i = \frac{dq}{dt}$


$$\begin{aligned} Q &= \int_0^{5 \text{ ms}} 10 \sin(200\pi t) dt \\ &= -\frac{10}{200\pi} \cos(200\pi t) \Big|_0^{5 \text{ ms}} \end{aligned}$$

$$= -\frac{1}{20\pi} [1 - \cos(1000\pi)] = \boxed{\frac{1}{20\pi} [C]} \quad \text{"half cycle"}$$

c)

$$\begin{aligned} Q &= \int_0^{10 \text{ ms}} 10 \sin(200\pi t) dt \\ &= -\frac{1}{20\pi} [1 - \cos(2000\pi)] = \boxed{0 [C]} \quad \text{"full cycle"} \end{aligned}$$

Problem 2

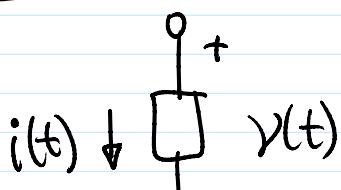

$$V(t) = 10V, \quad i(t) = 2e^{-t} A$$


$$P = V(t) \times i(t) = 20e^{-t} [W]$$

- $\int_{-\infty}^{\infty}$ ∞ t $+ \infty$ T T

$$E = \int_0^{\infty} P \cdot dt = \int_0^{\infty} 20e^{-t} = -20e^{-t} \Big|_0^{\infty} = -20[0 - 1] = 20 \text{ [J]}$$

\therefore absorbed by the element

Problem 3

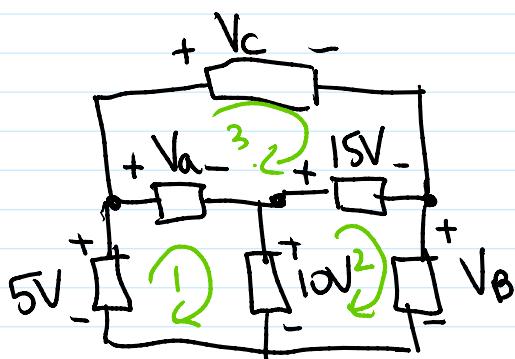

$$\textcircled{1} \quad 5V - V_A - 10V = 0$$

$$\hookrightarrow V_A = -5V$$

$$\textcircled{2} \quad 10V - 15V - V_B = 0$$


$$\hookrightarrow V_B = -5V$$

$$\textcircled{3} \quad V_A + 15V - V_C = 0$$

$$(-5V) + 15V = V_C \rightarrow V_C = 10V$$

Problem 4

(a) $P = 100W$ delivered to R

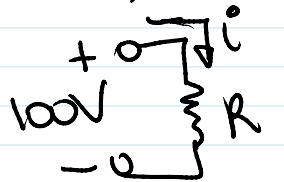

$$P = IV = 100W$$


$$\hookrightarrow I = \frac{100W}{100V} = 1 \text{ Amp}$$

$$\rightarrow V = IR \rightarrow R = \frac{V}{I} = \frac{100V}{1A} = 100 \text{ [}\Omega\text{]}$$

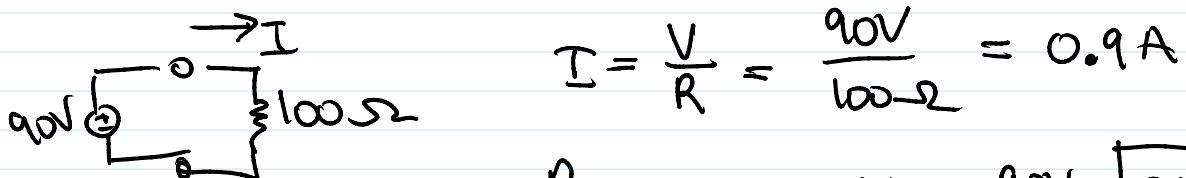(b) V reduced to 90V (by 10%)

$$\rightarrow I$$

$$\rightarrow V \cdot \frac{90V}{100V} = 0.9A$$




$$I = \frac{V}{R} = \frac{90V}{100\Omega} = 0.9A$$

$$P = IV = 0.9A \times 90V = 81W$$

\therefore power reduced by $>10\%$
(reduced by 19%)


Problem 5

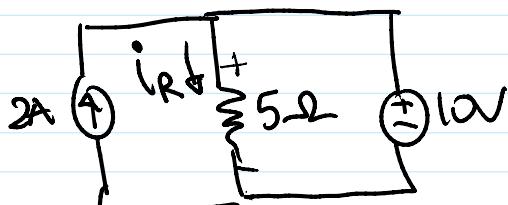

$$V = i_R \times 5\Omega = 10V$$

$$\Rightarrow i_R = 2A$$

Problem 6

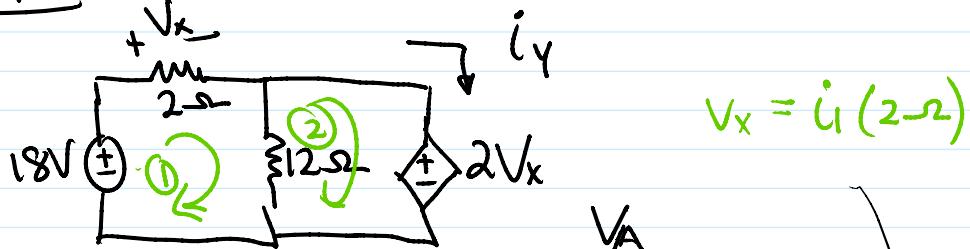

$$V_x = i_1(2\Omega)$$

$$① 18V - i_1(2\Omega) - (i_1 - i_2)(12\Omega) = 0$$

$$② 2V_x + (i_2 - i_1)(12\Omega) = 0$$

rewriting:

$$① 18V - i_1(2\Omega) = V_A$$


$$② 2V_x = +V_A \rightarrow V_A = +2V_x$$

$$\Rightarrow 18V - 2i_1 = +2V_x = +2(2i_1) = +4i_1$$

$$18V = 2i_1 + 4i_1 = +6i_1 \quad (6 \cdot i_1)$$

$$i_1 = \frac{18V}{+6\Omega} = 3A$$

$$V_x = i_1 \times 2\Omega = +8V$$

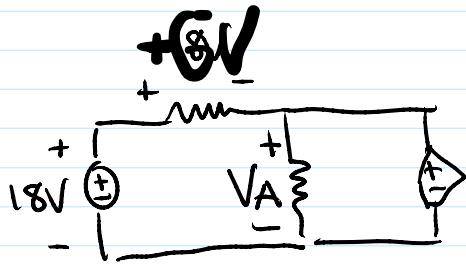

$$18V - (+8V) - V_A = 0$$

$$\rightarrow V_A = \text{box}$$


$$V_A = R_2 V = (i_1 - i_2) \times 12 - 2$$

note : $i_2 = i_y$

$$\frac{V}{R_2} = i_c - i_y \rightarrow i_y = i_c - \frac{V}{R_2}$$

$$\therefore iy = +3A - 6A = +3A$$

Problem 7

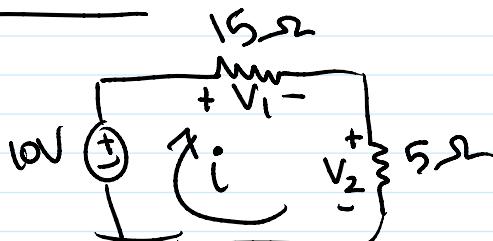

a.) KVL

$$WV = V_1 + V_2$$

b.) Ohm's Law

$$V_1 = i \times 15\Omega \quad V_2 = i \times 5\Omega$$

$$c) \quad 10V = i \times 15\Omega + i \times 5\Omega = i \times 20\Omega$$

\Downarrow

$$\therefore i = 0.5[A]$$

d)

Voltage source : $P_{\text{source}} = 10V \times 0.5A = \underline{\underline{5W}}$ (delivered)

Voltage source \rightarrow r_{source}

$$R_1: P_1 = V_1 i = 15 i^2 = \underline{\underline{3.75 \text{ W}}} \text{ (absorbed by } R_1)$$

$$R_2: P_2 = V_2 i = 5 i^2 = \underline{\underline{1.25 \text{ W}}} \text{ (absorbed by } R_2)$$

$$P_{\text{source}} = P_1 + P_2 \quad \checkmark$$