


**ECE100**  
**Homework-2 solutions**

**Total Points: 100**


**Required Readings: Chapter 1, 2 and class notes**

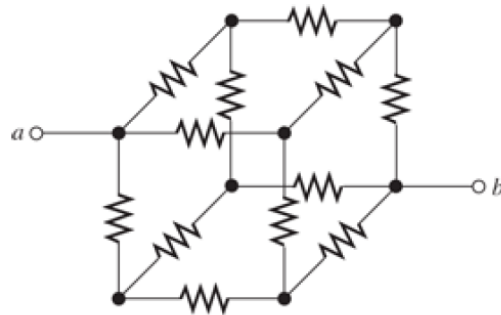**Submit your work in a pdf file electronically in the CCLE website before April 11<sup>th</sup> 11:59 pm. Late homework will not get credit!**

- Twelve  $1\ \Omega$  resistors are arranged on the edges of a cube, and terminals a and b are connected to diagonally opposite corners of the cube. The problem is to find the resistance between the terminals. Approach the problem this way: Assume that 1 A of current enters terminal a and exits through terminal b. Then, the voltage between terminals a and b is equal to the unknown resistance. By symmetry considerations, we can find the current in each resistor. Then, using KVL, we can find the voltage between a and b.



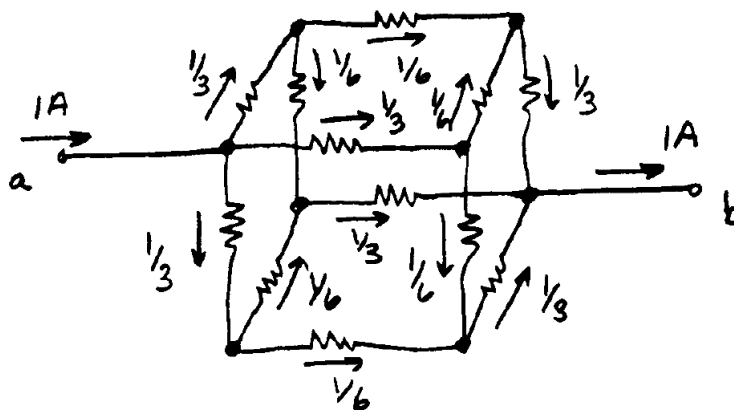
By symmetry, we find the currents in the resistors as shown below:



Then, the voltage between terminals a and b is


$$v_{ab} = R_{eq} = 1/3 + 1/6 + 1/3 = 5/6$$

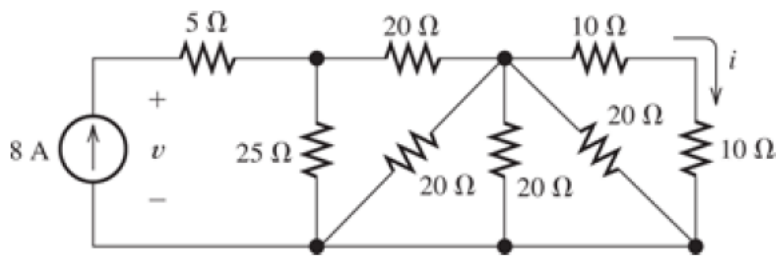2. Find the values of  $v$  and  $i$  for the circuit below






Combining resistors in series and parallel, we find that the equivalent resistance seen by the current source is  $R_{eq} = 17.5 \Omega$ . Thus,
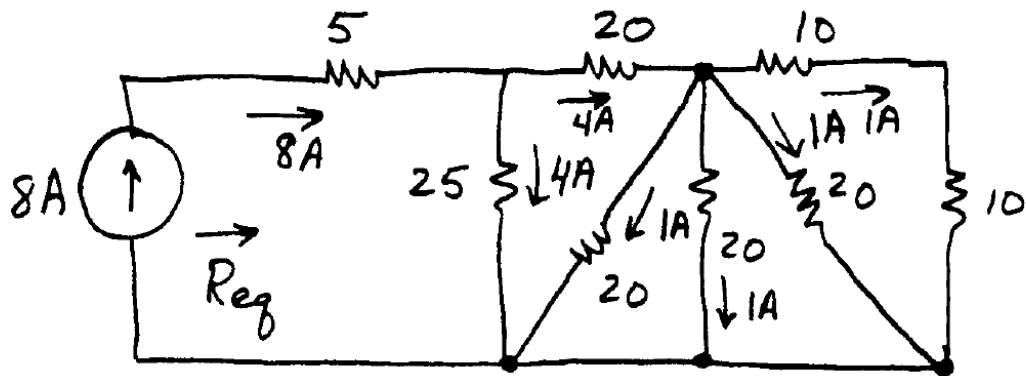
$$v = 8 \times 17.5 = 140 \text{ V. Also, } i = 1 \text{ A.}$$



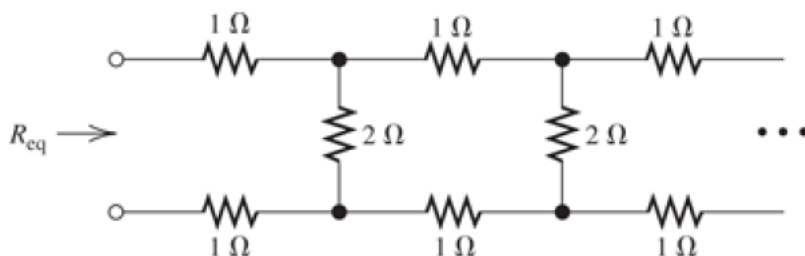3. Find the equivalent resistance for the infinite network shown in figure below



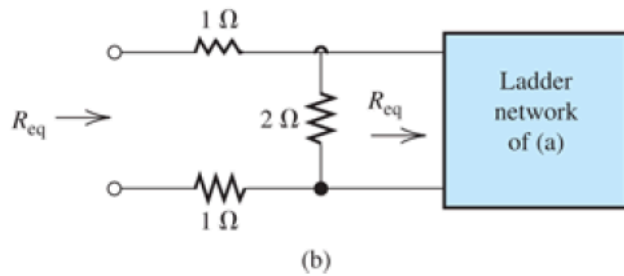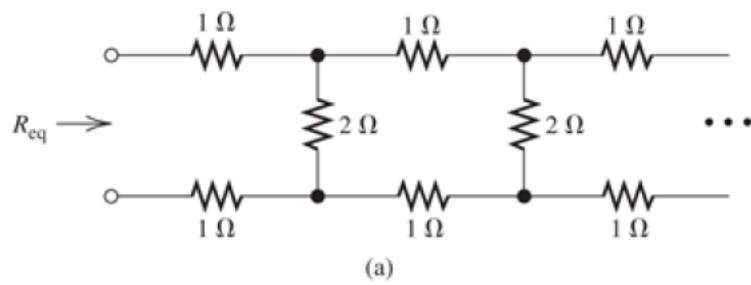

Combining the resistances shown in Figure

$$R_{eq} = 1 + \frac{1}{1/2 + 1/R_{eq}} + 1 = 2 + \frac{2R_{eq}}{2 + R_{eq}}$$


$$R_{eq}(2 + R_{eq}) = 2(2 + R_{eq}) + 2R_{eq}$$

$$(R_{eq})^2 - 2R_{eq} - 4 = 0$$

$$R_{eq} = 3.236 \, \Omega$$

( $R_{eq} = -1.236 \, \Omega$  is another root, but is not physically reasonable.)

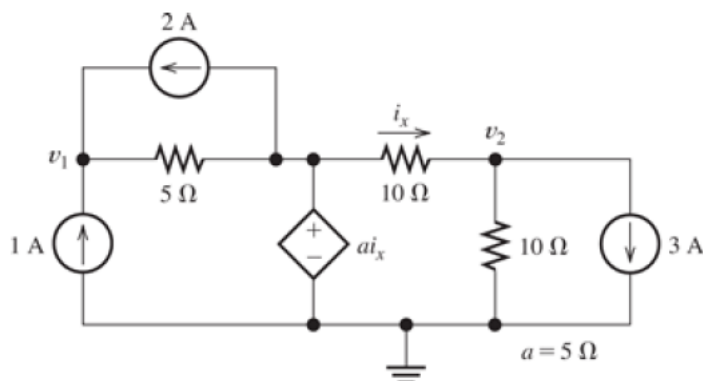4. Solve for the node voltages  $v_1$  and  $v_2$  shown in Figure below



First, we can write:

$$i_x = \frac{5i_x - v_2}{10}$$

Simplifying, we find  $i_x = -0.2v_2$ .

Then write KCL at nodes 1 and 2:


$$\frac{v_1 - 5i_x}{5} = 3 \qquad \frac{v_2}{10} - i_x = -1$$

Substituting for  $i_x$  and simplifying, we have


$$v_1 - v_2 = 15 \quad \text{and} \quad 0.3v_2 = -3$$

which yield  $v_1 = 25 \text{ V}$  and  $v_2 = -10 \text{ V}$ .

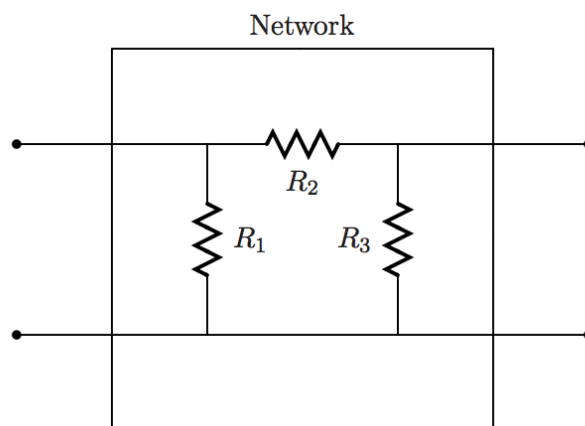5. The following network has two ports and three resistors. The resistor values  $R_1$ ,  $R_2$  and  $R_3$  are unknown.




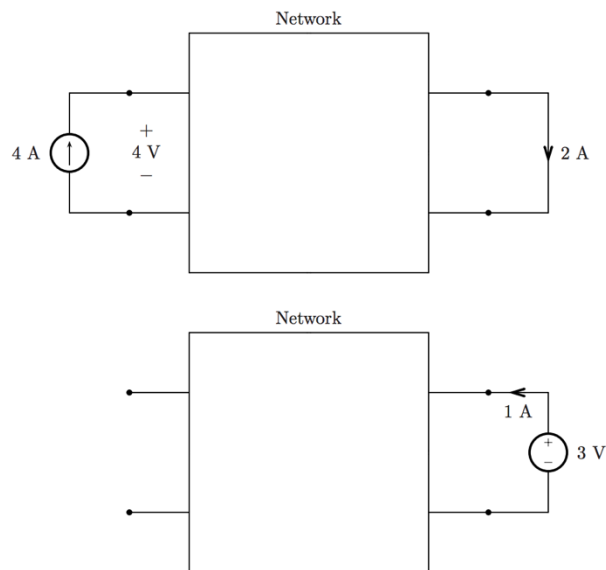Using the results of the following two experiments performed on the network, find the unknown values of the three resistors.



The first experiment allows us calculate the values of resistors  $R_1$  and  $R_2$ . We observe that the output terminal of the network on the right is shorted as shown in Fig: 1.9. This means that no current will flow in  $R_3$ . From inspection of the circuit we note that 2A of current flows through the short circuit. This current must pass through  $R_2$  and in doing so it causes a voltage drop of 4V across the resistor. Therefore from Ohm's law we calculate the value of  $R_2$  to be  $2\Omega$ . The remaining 2A of current from the current supply must flow through  $R_1$ , which also has a voltage drop of 4V across it. Therefore the value of  $R_1$  is also  $2\Omega$ .

Fig: 1.9

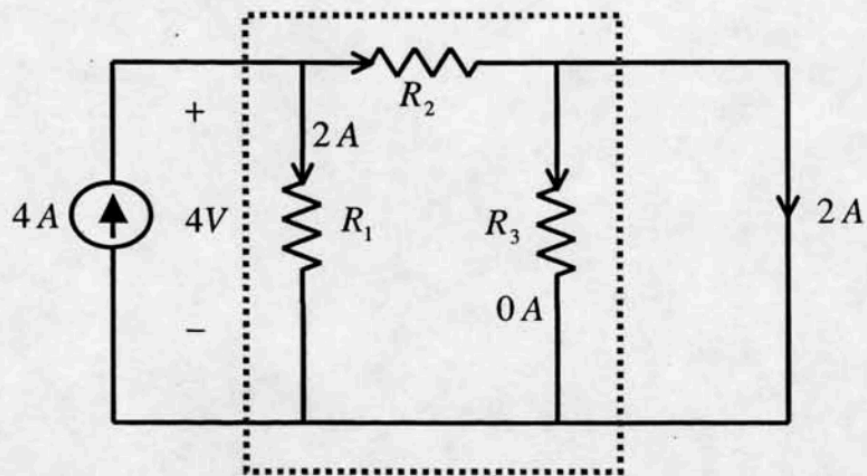

The second experiment allows us calculate the value of  $R_3$  assuming we have already calculated the values of the other resistors. We note that the output terminal of the network is open circuited and so no current can flow through the terminal. Therefore the current entering the network must be split between two parallel paths. The first path is through  $R_3$  and the second path is through the combination of  $R_2 + R_1$ . We already know the value of  $R_2 + R_3$  equals  $4\Omega$ . Indirectly we are told the overall resistance of the circuit because we are given the voltage across the circuit is  $3V$  and the current flowing into the circuit is  $1A$ .


$$\text{Equivalent resistance of circuit: } R_{eq} = \frac{3V}{1A} = 3\Omega \Rightarrow 3\Omega = \frac{(R_1 + R_2)R_3}{R_1 + R_2 + R_3}$$

$$R_1 + R_2 = 4\Omega \Rightarrow 12 + 3R_3 = 4R_3 \Rightarrow R_3 = 12\Omega$$

The final values of the resistors are as follows:

$$R_1 = 2\Omega \quad R_2 = 2\Omega \quad R_3 = 12\Omega$$

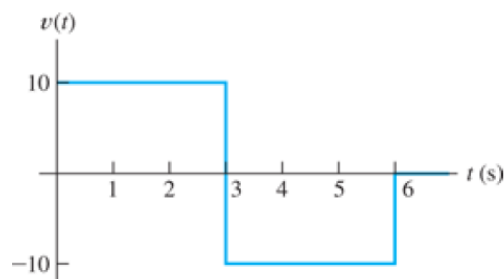6. The voltage across a 2-H inductance is shown in Figure below. The initial current in the inductance is  $i_L(0)=0$ . Sketch the current, power, and stored energy to scale versus time.



Given,

Inductance,  $L = 2\text{H}$

The voltages from the waveform are

$$v(t) = 10 \text{ V} \quad \text{for } 0 < t \leq 3 \text{ s}$$

$$v(t) = -10 \text{ V} \quad \text{for } 3\text{s} < t \leq 6 \text{ s}$$

Now,

Current through the inductor,  $i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$

For  $0 < t \leq 3 \text{ s}$

$$i(t) = \frac{1}{2} \int_0^t 10 dt + i(0)$$

$$i(t) = \frac{1}{2} [10t]_0^t + 0$$

$$i(t) = \frac{1}{2} [10t]$$

$$\therefore i(t) = 5t \text{ A}$$

For  $3 < t \leq 6\text{s}$

$$i(t) = \frac{1}{2} \int_3^t -10 dt + i(3\text{s})$$

$$i(t) = \frac{1}{2} [-10t]_3^t + 15$$

$$i(t) = -\frac{1}{2} [10t - 30] + 15$$

$$i(t) = -5t + 15 + 15$$

$$\therefore i(t) = -5t + 30 \text{ A}$$

Power,  $p(t) = v(t) \times i(t)$

For  $0 < t \leq 3 \text{ s}$

$$p(t) = 10 \times 5t$$

$$\therefore p(t) = 50t \text{ W}$$

For  $3\text{s} < t \leq 6\text{s}$

$$p(t) = -10 \times (-5t + 30)$$

$$\therefore p(t) = 50t - 300 \text{ W}$$

Energy stored

$$w(t) = \frac{1}{2} L i^2(t)$$

For  $0 < t \leq 3$  s

$$w(t) = \frac{1}{2} \times 2 \times (5t)^2$$

$$\therefore w(t) = 25t^2 \text{ J}$$


For  $3 \text{ s} < t \leq 6 \text{ s}$

$$w(t) = \frac{1}{2} \times 2 \times (-5t + 30)^2$$

$$\therefore w(t) = 25t^2 + 900 - 300t$$


Waveforms :-

Current:

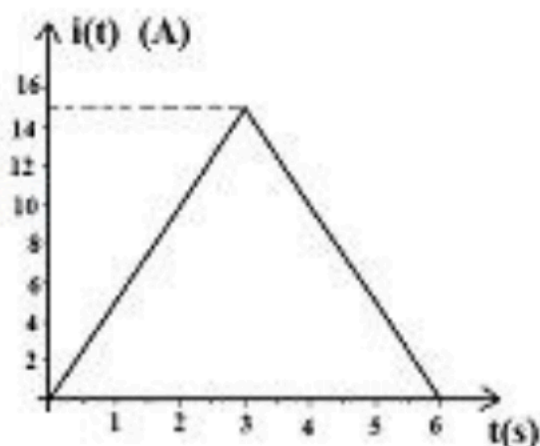



## Power:

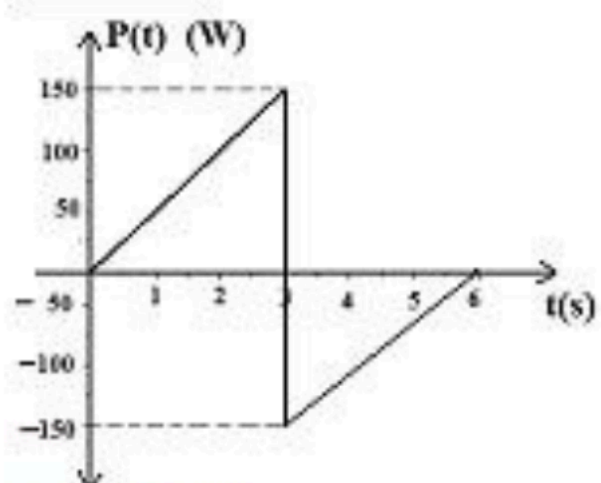

## Energy:

