

+ Finally, I had 28 pages.

Nhat Ho

+ And I also submitted our course evaluation.



#1

105355311

I do problem 3 first.


Problem 3:

For a RLC circuit, we have

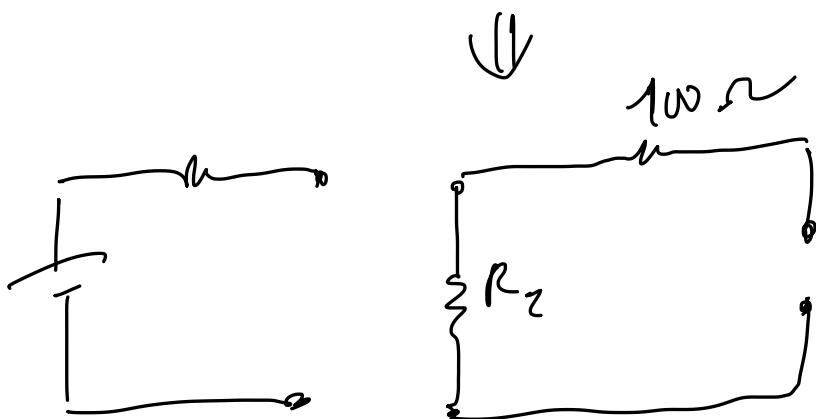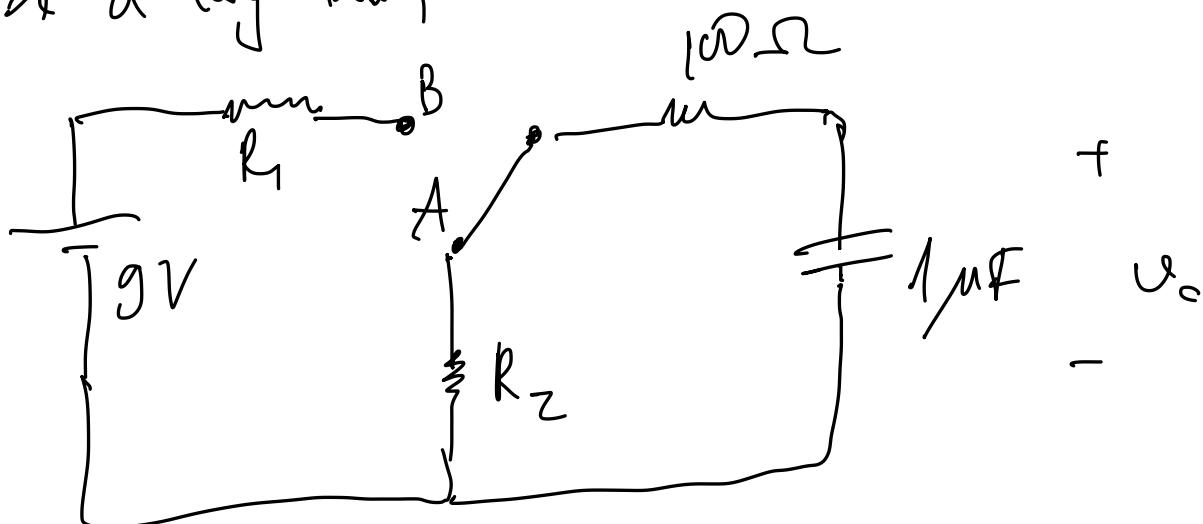

$$\Rightarrow \text{at } t=0^- \Rightarrow v_c(0^-) = 0(V)$$

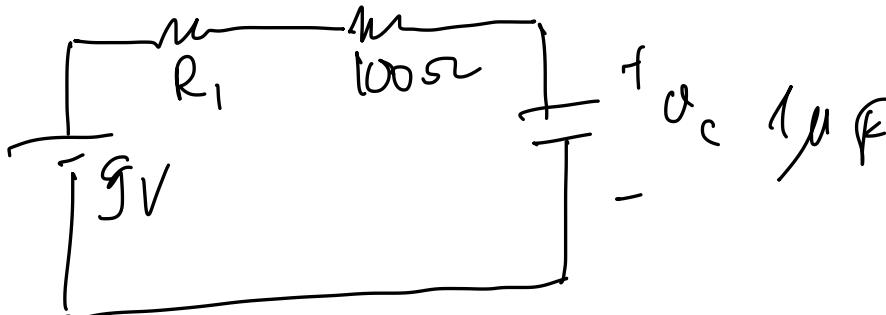
At  $t = 0$ , switch move to  $B$ , we have. [#2]



Since capacitor  
cannot change the  
voltage instantaneously

$$\Rightarrow V_c(0^+) = V_c(0^-) = 0(V)$$

with  $t \rightarrow \infty$ , we have:

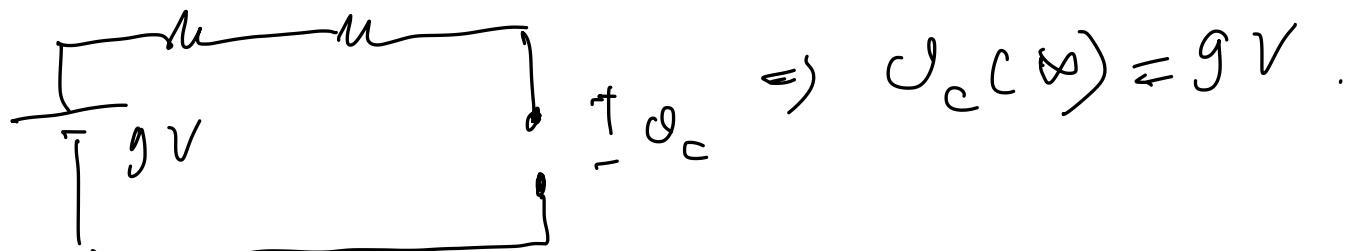

because this circuit contain the resistance and capacitor, then this circuit is a first order circuit. , we have :

$$V_c(t) = V_c[\infty] - (V_c[\infty] - V_c(0^+)) e^{-t/RC}$$

$$\text{We have: } RC = (R_1 + 100) \times 1 \times 10^{-6} (\text{s})$$

$$\Rightarrow V_c(t) = 9 - (9 - 0) e^{-t/RC}$$

$$V_c(t) = 9 - 9 e^{-t/RC}$$

$\Rightarrow$  from  $0 \leq t \leq 1 \text{ ms}$ , we have

#3

$$V_C(t) = 9 - 9e^{-t/RC}$$

$$\Rightarrow \text{at } t = 1 \text{ ms} \Rightarrow V_C(1^+) = 9 - 9e^{-10^3/RC} = 8 \text{ V}$$

$$\Rightarrow 9e^{-10^3/RC} = 1 \Rightarrow e^{-10^3/RC} = \frac{1}{9}$$


$$\Rightarrow \frac{-0.001}{(R_1 + 100) \times 10^{-6}} = R_h \frac{1}{9}$$

$$\Rightarrow (R_1 + 100) = 455.12$$

$$\Rightarrow R_1 = 355.12 \Omega$$

at  $t = 1 \text{ ms}$ , switch to position A, we have:

$$V_C(1^+) = V_C(1^-) = 8 \text{ V}$$

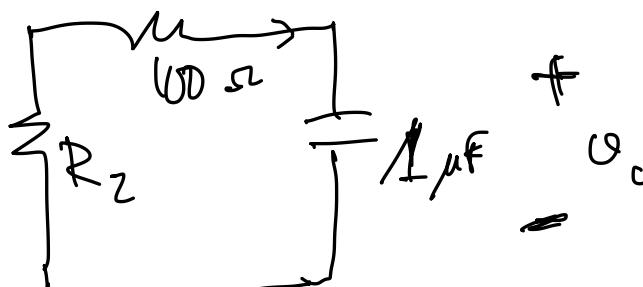

at  $t = 2 \text{ ms}$ ,

$$V_C(2 \text{ ms}) = 1 \text{ V}$$

at  $t = \infty \Rightarrow V_C = 0 \text{ V}$

$\Rightarrow$  continue discharged for capacitor.

$$\Rightarrow V_C(t) = 0 - (0 - 8) e^{-t/RC}$$

$$V_C(t) = 8e^{-t/RC} \quad \text{with } t = t_{\text{new}} = 1 \text{ ms}$$

$$\Rightarrow 8e^{-10^3/RC} = 1 \text{ V}$$

$$\Rightarrow e^{-0.001/RC} = \frac{1}{8}$$

$$\Rightarrow \frac{-0.001}{(R_2 + 100) \times 10^{-6}} = \ln \frac{1}{8}$$



$$\Rightarrow R_2 + 100 = 480.9$$

$$\Rightarrow R_2 = 380.9 \Omega$$

There is only one capacitor storing the power  
 $\Rightarrow$  this is a first order circuit.

Problem 4: at  $t = 0^-$ , we have:

#4

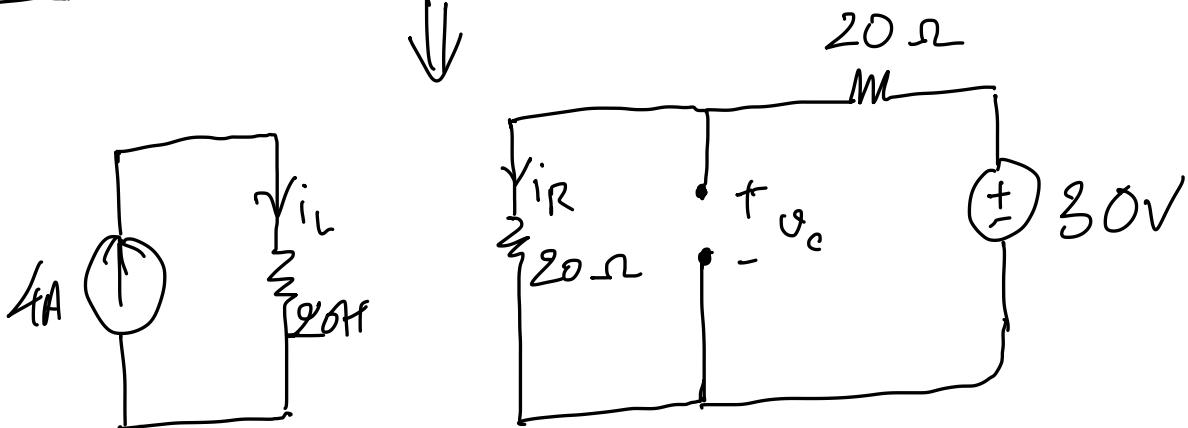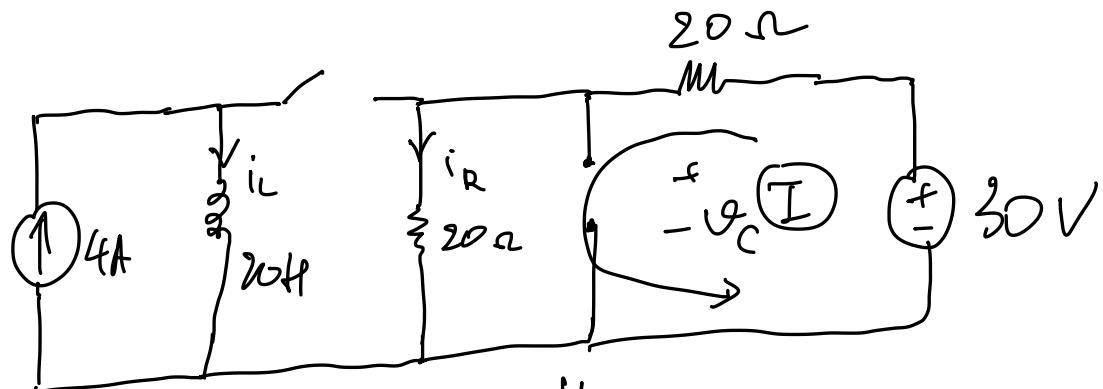

$$\Rightarrow i_L(0^-) = 4A$$

also, Apply KVL for Loop I, we have:

$$+30 = (20 + 20)i_R \Rightarrow i_R = \frac{30}{40} = 0.75(A)$$


$$\Rightarrow v_C(0^-) = i_R \times 20 = 20 \times 0.75 = 15V$$

At  $t = 0^+$ , we have:

$$i_L(0^+) = 4A \quad \& \quad v_C(0^+) = 15V.$$

#5




We have the circuit:

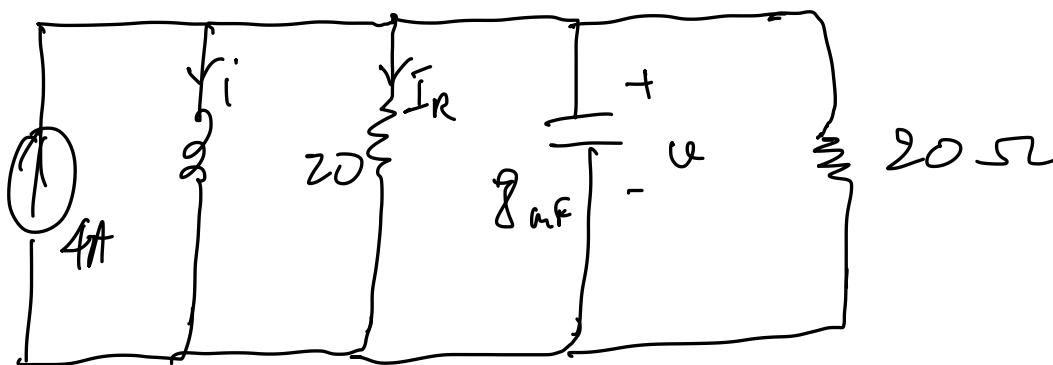

- a) The characterizes 2nd order circuit is conductor ( $L$ ) & capacitor ( $C$ ) & resistance ( $R$ ).  
 This circuit contain both  $L$  &  $C$  &  $R$ , then this is a second order circuit

- b) Draw the equivalent circuit for  $t < 0$  &  $t > 0$  as above.

c) We Have:

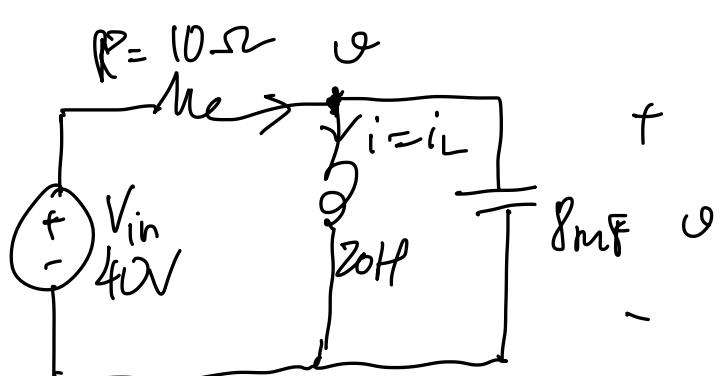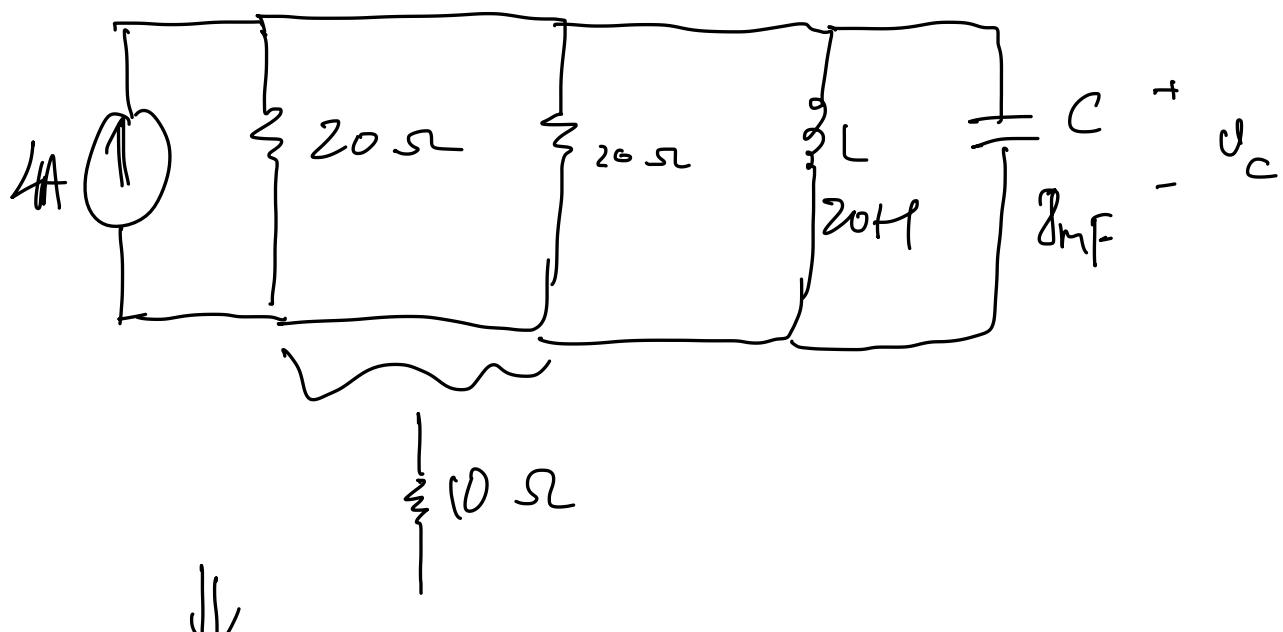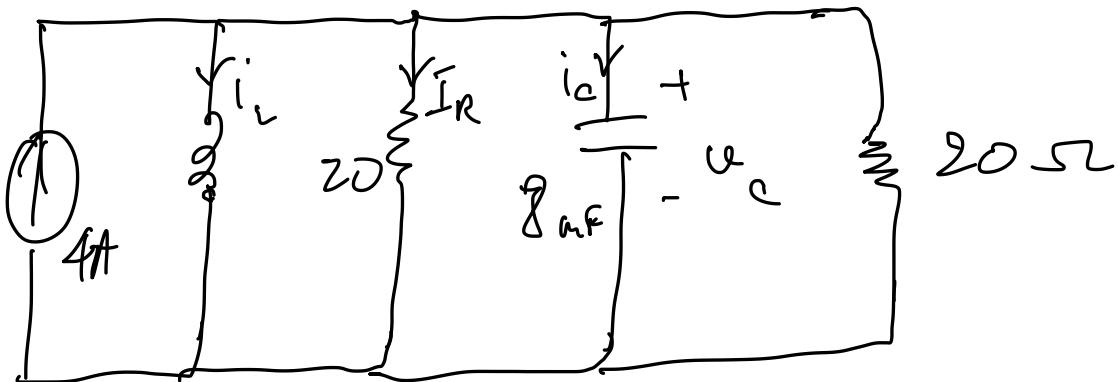

We have:  $\phi = \psi_L = \psi_C$

$$\frac{V_{in} - \phi}{R} = i_L + i_C$$

$$\Rightarrow \frac{\phi_{in}}{R} = \frac{\phi}{R} + i_L + i_C; \frac{\phi}{R} = \frac{\psi_L}{R} = \frac{L}{R} \frac{d\psi_L}{dt}$$

# 8

$$i_C = C \frac{d\varphi_C}{dt} = C \frac{d\varphi_L}{dt}, \quad \varphi_L = L \frac{di_L}{dt}$$

$$\Rightarrow i_C = CL \frac{d^2 i_L}{dt^2}$$

$$\Rightarrow \frac{\vartheta_{in}}{R} = \frac{L}{R} \frac{di_L}{dt} + i_L + CL \frac{d^2 i_L}{dt^2}$$

$$\Rightarrow CL \frac{d^2 i_L}{dt^2} + \frac{L}{R} \frac{di_L}{dt} + i_L = \frac{\vartheta_{in}}{R} = \frac{40}{10} = 4$$

$$\Rightarrow \frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{CL} i_L = 4$$

$$\Rightarrow s^2 + 2\omega_0 \xi s + \omega_0^2 = 4$$

d) As we did above, we have:

$$i(t=0^+) = i_L(0^+) = 4 A$$

$$\vartheta(t=0^+) = \vartheta_C(0^+) = 15(\text{v})$$

#9

e) Check  $S^2 + 2\omega_0 \xi S + \omega_0^2 = 0$

$$2\omega_0 \xi = \frac{1}{RC} = \frac{1}{10 \Omega \times 8 \times 10^{-3}} = 12.5$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{20 \times 8 \times 10^{-3}}} = 2.5 \text{ (rad/s)}$$

$$\Rightarrow \xi = \frac{12.5}{2 \times \omega_0} = \frac{12.5}{2 \times 2.5} = 2.5$$

f) Since  $\xi = 2.5 > 1 \Rightarrow$  over damped

g) We have:

$$i_L(t) = K_1 e^{S_1 t} + K_2 e^{S_2 t}$$

$$S_{1,2} = \left( -\xi \pm \sqrt{\xi^2 - 1} \right) \omega_0$$

#10

$$= \left( -2.5 \pm \sqrt{2.5^2 - 1} \right) \times 2.5$$

$$= (-2.5 \pm 2.3) \times 2.5$$

$$\Rightarrow \begin{cases} S_1 = -0.2 \times 2.5 = -0.5 \\ S_2 = -4.8 \times 2.5 = -12 \end{cases}$$

P)

$$\Rightarrow i_L(t) = K_1 e^{-0.5t} + K_2 e^{-12t}$$

We have  $i_L(0^+) = 4$

$$\Rightarrow K_1 + K_2 = 4 \quad ①$$

$$V_L(t) = L \frac{di_L}{dt} = 20 \left[ -0.5 K_1 e^{-0.5t} - 12 K_2 e^{-12t} \right]$$

$$V_L(t=0^+) = 15V$$

#11

$$\Rightarrow 15 = 20 [-0.5K_1 - 12K_2]$$

$$\Rightarrow 0.5K_1 + 12K_2 = -0.75 \quad (2)$$

From ① & ②

$$\begin{cases} K_1 = 4.24 \\ K_2 = -0.24 \end{cases}$$

$$\Rightarrow i_L(t) = 4.24e^{-0.5t} - 0.24e^{-12t} + i_{Lp}(t)$$

$$At \ t=0 \quad i_{Lp}(t) = i_{Lp}(t \rightarrow \infty) = 4(A)$$

$$\Rightarrow i_L(t) = 4.24e^{-0.5t} - 0.24e^{-12t} + 4$$

$$( ) \quad V_L(t) = L \frac{di}{dt}$$

$$= 20 \left[ -0.5 \times 4.24 e^{-0.5t} + 12 \times 0.24 e^{-12t} \right] \quad | \#12$$


$$= -4.24 e^{-0.5t} + 57.6 e^{-12t} \quad (\vee)$$

$$A(80) \quad \mathcal{O}_R(t) = \mathcal{O}_L(t)$$

$$\Rightarrow i_R = \frac{\mathcal{O}_L(t)}{20} = \frac{-4.24 e^{-0.5t} + 57.6 e^{-12t}}{20}$$

$$= \boxed{-0.212 e^{-0.5t} + 2.88 e^{-12t} \quad (A)}$$

j)  $\mathcal{O}_C(t) = \mathcal{O}_L(t)$

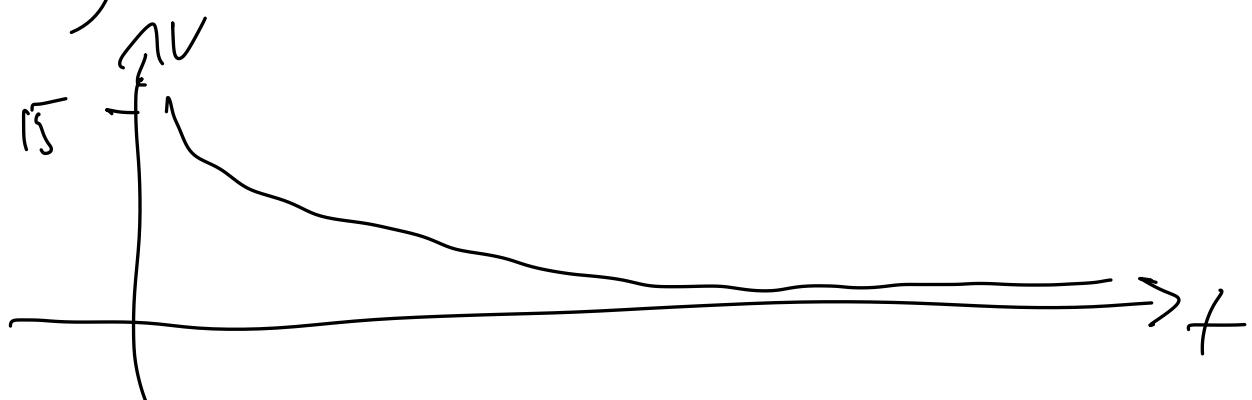


Problem 5 :

L#13

a) For K analysis, capacitor is opened

We have:

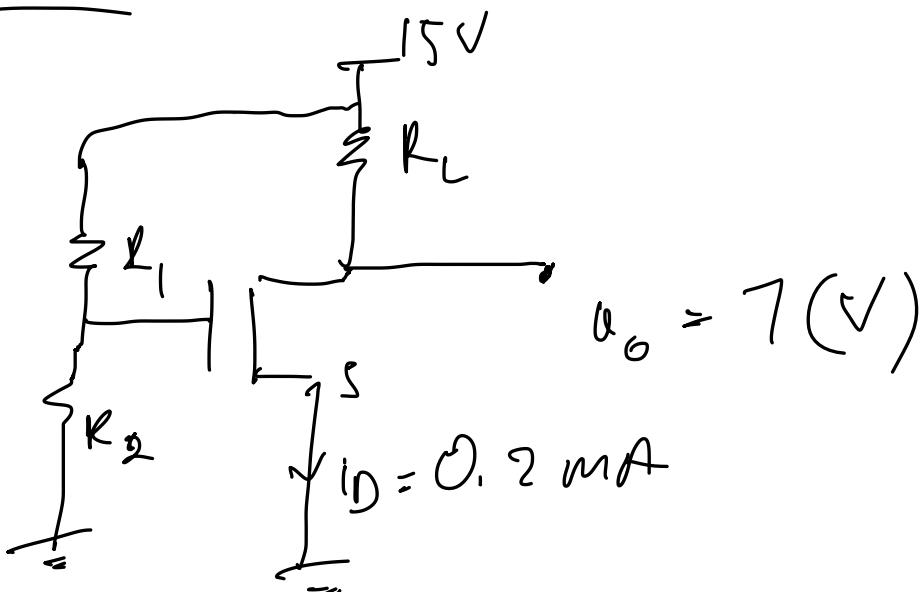

Apply KVL, we have:

$$15 - I_D R_L - U_o = 0$$

$$\Rightarrow R_L = \frac{15 - U_o}{I_D} = \frac{15 - 7}{0.2 \text{ mA}} = 4000 \Omega$$

$$\Rightarrow R_L = 40(\text{k}\Omega)$$

Also  $I_D = K(U_{qS} - U_{f0})^2 = 0.2 \frac{\mu\text{A}}{\text{V}^2} (U_{qS} - 2)^2$

$$\Rightarrow 0.2 \text{ mA} = 0.2 \frac{\mu\text{A}}{\text{V}^2} (V_{GS} - 2)^2 \quad | \#14$$

$$\Rightarrow (V_{GS} - 2)^2 = 1 \Rightarrow V_{GS} - 2 = \pm 1$$

$$\Rightarrow V_{GS} = 3(V) \quad (\text{Received})$$

$$V_{GS} = 1(V) \quad (\text{Rejected since } V_{GS} < V_T = 2V)$$

$$\Rightarrow V_{GS} = 3V$$

b) We have :  $I_D = K (V_{GS} - V_T)^2$

$$\Rightarrow g_m = \frac{\partial I_D}{\partial V_{GS}} = 2K (V_{GS} - V_T)$$

$$= 2 \times 0.2 \times (3 - 2)$$

$$= 0.4 \text{ mA/V}$$

c)  $R_1 + R_2 = 500 \text{ k}\Omega$

We have  $U_{gS} = 3V = U_g - U_S$

$$= U_g$$

#15

$$\Rightarrow U_g = 3V$$


Apply the Voltage divider:

$$V_g = \frac{15 \times R_2}{R_1 + R_2} = \frac{15 \times R_2}{500k\Omega} = 3V$$



$$\Rightarrow R_2 = 100k\Omega$$

$$\Rightarrow R_1 = 400k\Omega$$

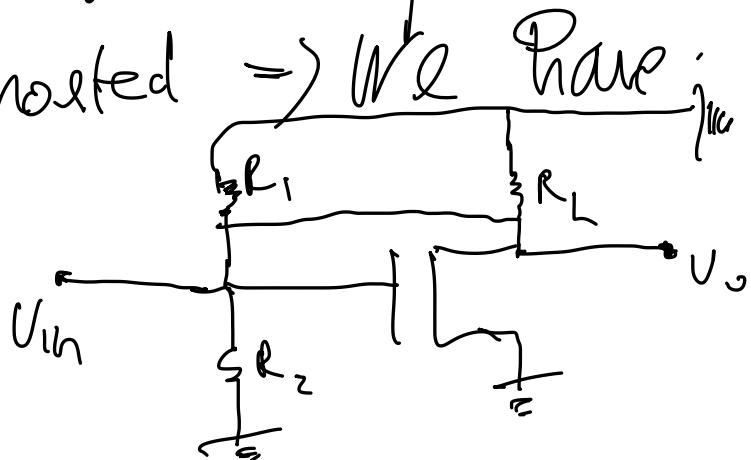d) Small Signal, all DC voltage source connected to ground & capacitor will be shorted  $\Rightarrow$  No Phase



#16

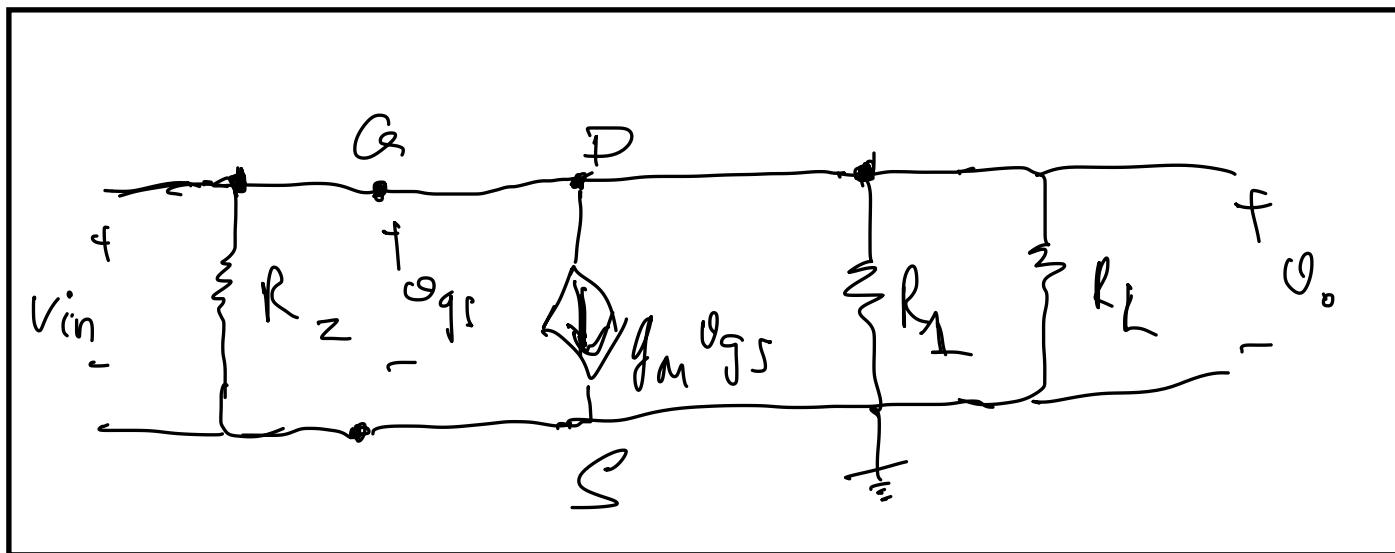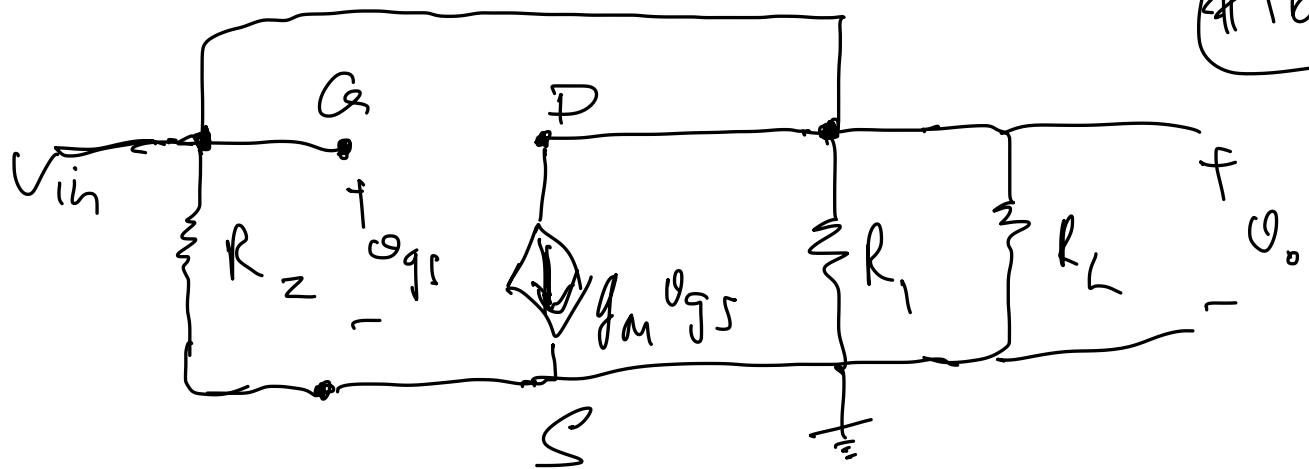
 $\Leftrightarrow$ 

Prob Lem 9:

Circuit:-


117

a)

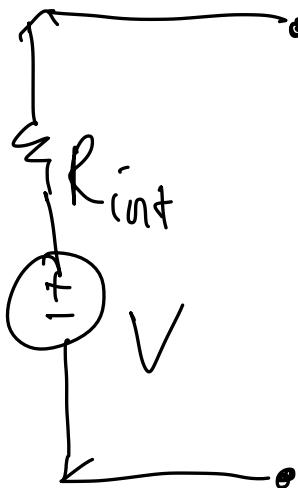


b)

We have : the circuit

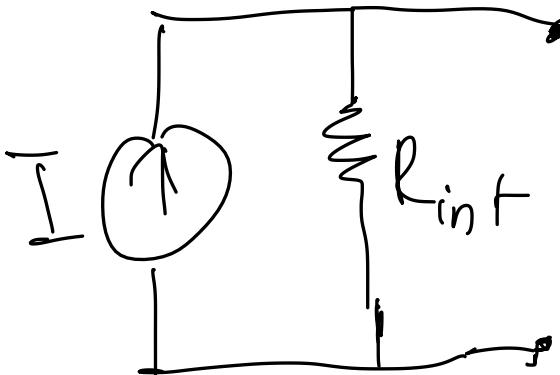

$$I = \frac{V}{R_{int}}$$

c)

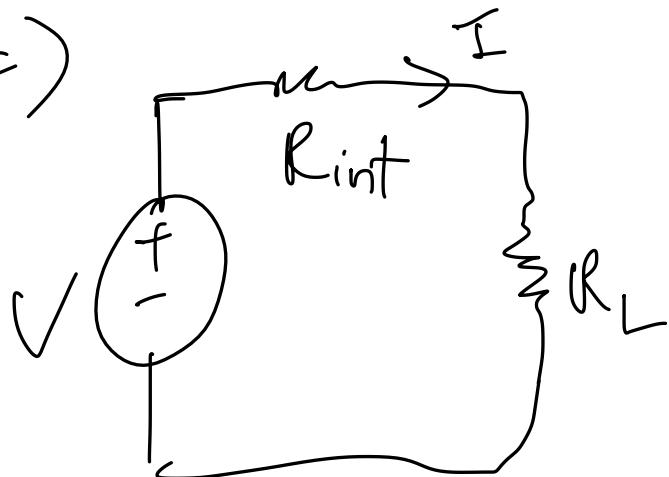

We have :

$$I = \frac{V}{R_{in} + R_L}$$

$$\Rightarrow \text{Power: } P = I^2 R_L = \left( \frac{V}{R_{in} + R_L} \right)^2 \times R_L \quad (\#8)$$

d) called  $R_L = x$ ,  $R_{in} = a$  (const),  $\lambda > 0$

$$\Rightarrow P = \left( \frac{V}{a+x} \right)^2 \cdot x = \frac{V^2 x}{(a+x)^2}$$

$$P'(x) = V^2 \left[ \frac{1(a+x)^2 - 2x(a+x)}{(a+x)^4} \right]$$

$$P' = 0 \Leftrightarrow (a+x)(a+x - 2x) = 0$$

$$\Rightarrow \begin{cases} a-x=0 \Leftrightarrow x=a \\ a+x=0 \text{ (refut since } x>0) \end{cases}$$

$\Rightarrow R_L$  has the power max when  $x=a$


$$\Leftrightarrow R_L = R_{in}$$

[19]

$$\Rightarrow P_{\max} = \left(\frac{V}{2R_L}\right)^2 \times R_L = \frac{V^2}{4R_L^2} \times R_L$$

$$\Rightarrow P_{\max} = \frac{V^2}{4R_L}$$

e) Equivalent current source:

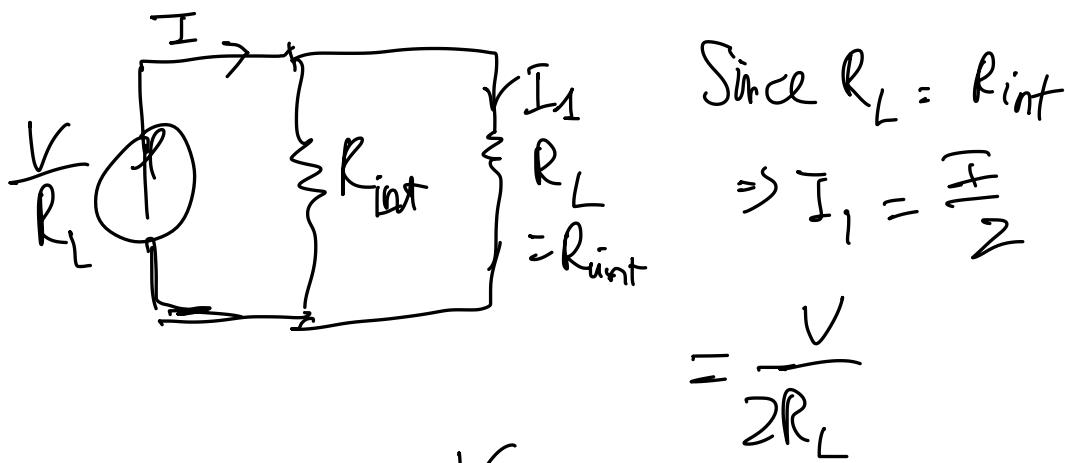

$$\Rightarrow I_1 = \frac{V}{2R_L}$$


$$\Rightarrow P_L = (I_1)^2 \times R_L = \frac{V^2}{4R_L^2} \times R_L = \frac{V^2}{4R_L}$$

$$\Rightarrow P_L \text{ is still equal } \frac{V^2}{4R_L} = P_{\max}$$

$\Rightarrow$  This is still true

# Problem 7:

We have:

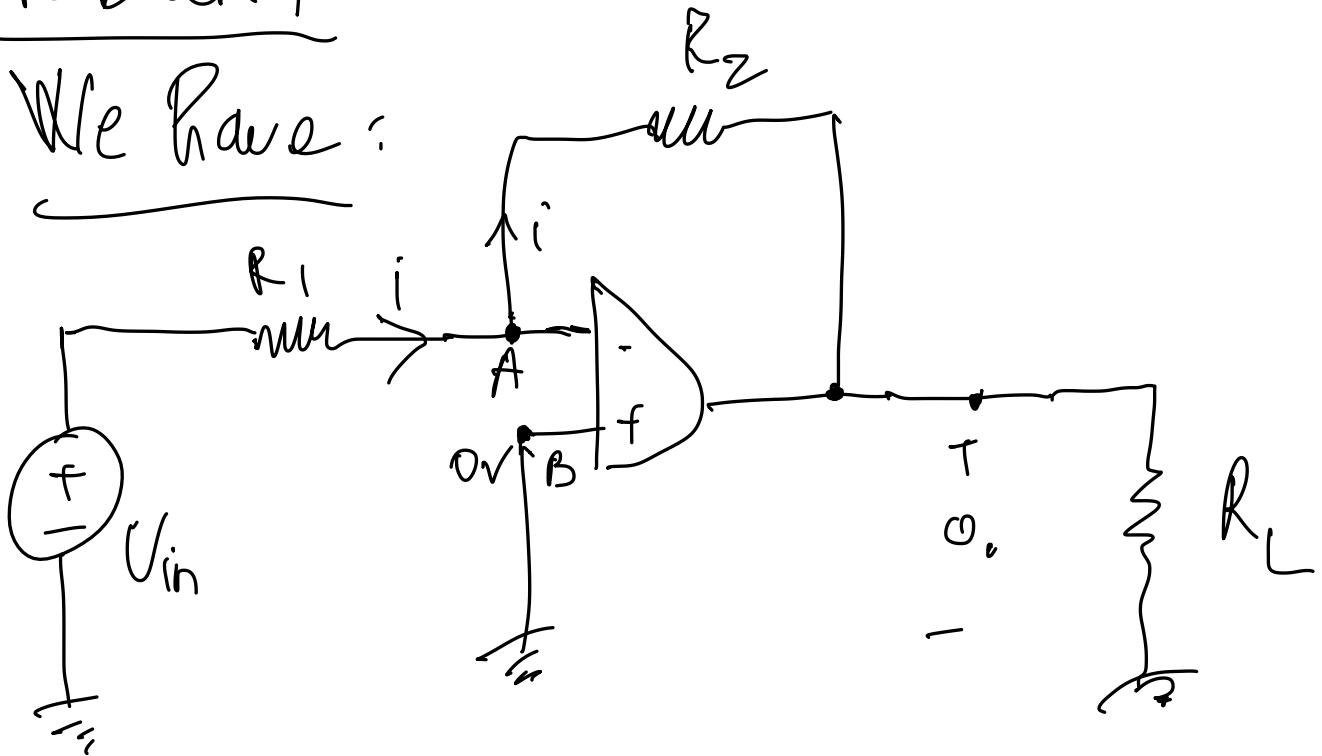

a) At point A,  $V_A = V_B = 0V$ .

$$\Rightarrow \frac{V_{in} - 0}{R_1} = \frac{0 - V_o}{R_2}$$

$$\Rightarrow \frac{V_{in}}{R_1} = -\frac{V_o}{R_2} \Rightarrow \frac{V_o}{V_{in}} = -\frac{R_2}{R_1}$$

$$\Rightarrow A_v = \frac{V_o}{V_{in}} = -\frac{R_2}{R_1}$$


$$\text{With } A_V = -5 \Rightarrow -\frac{R_2}{R_1} = -5$$

(2)


$$\Rightarrow R_2 = 5R_1$$

Since the gain  $A$  does not depend on  $R_L$   $\Rightarrow$  to get  $A_V = -5$ , we need focus on  $R_2$  &  $R_1$  with  $R_2 = 5R_1$  and does not matter  $R_L$

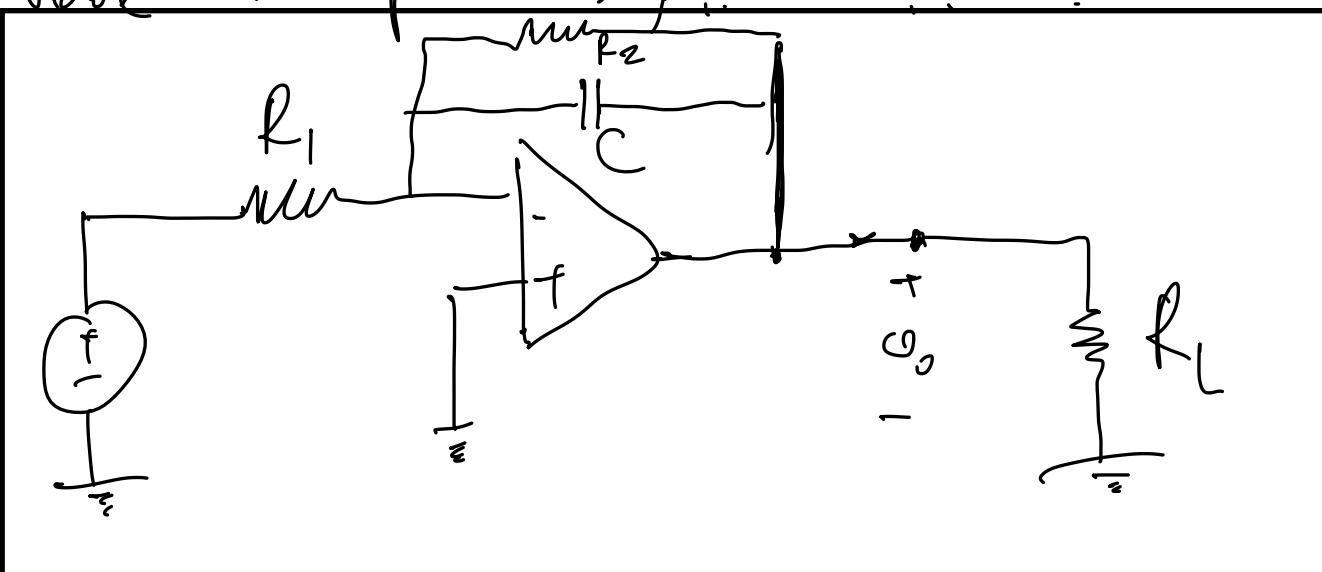
b) To have an integrator, we need to have a capacitor parallel with  $R_2$  like this one.



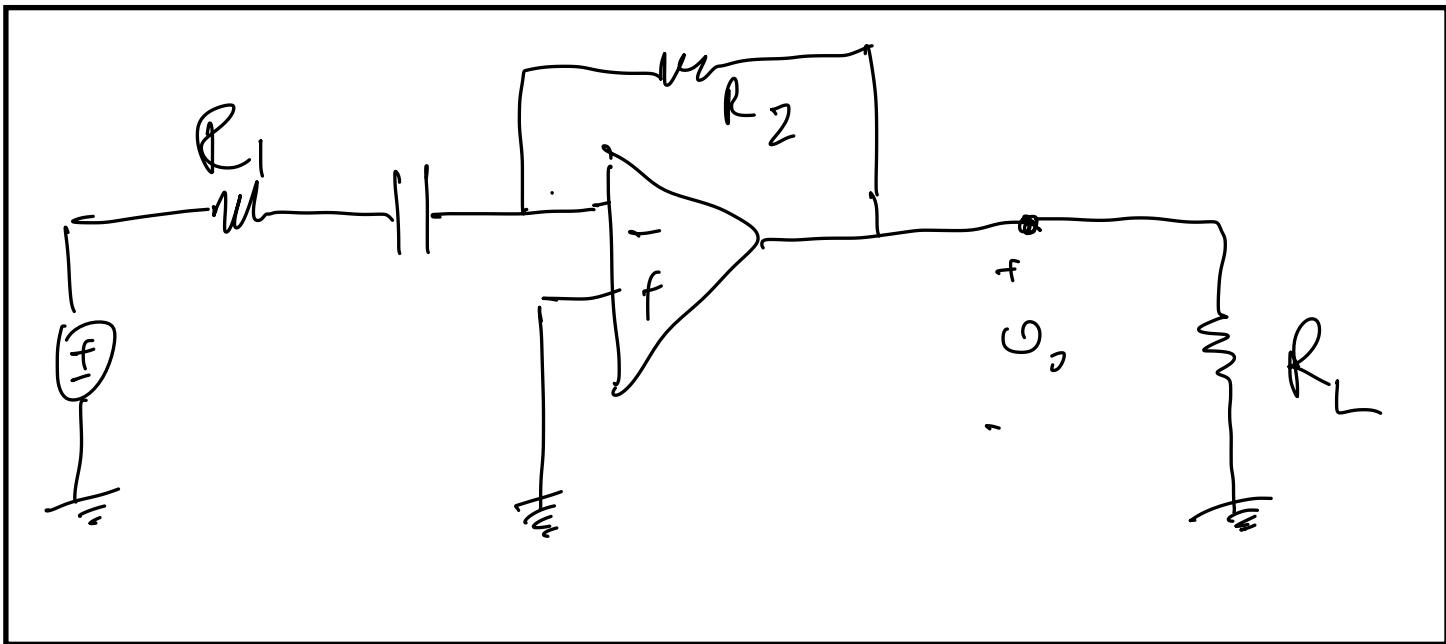
c) To have a differentiator, we need a capacitor at the input like this one.



d) To have a summation of 3 input:

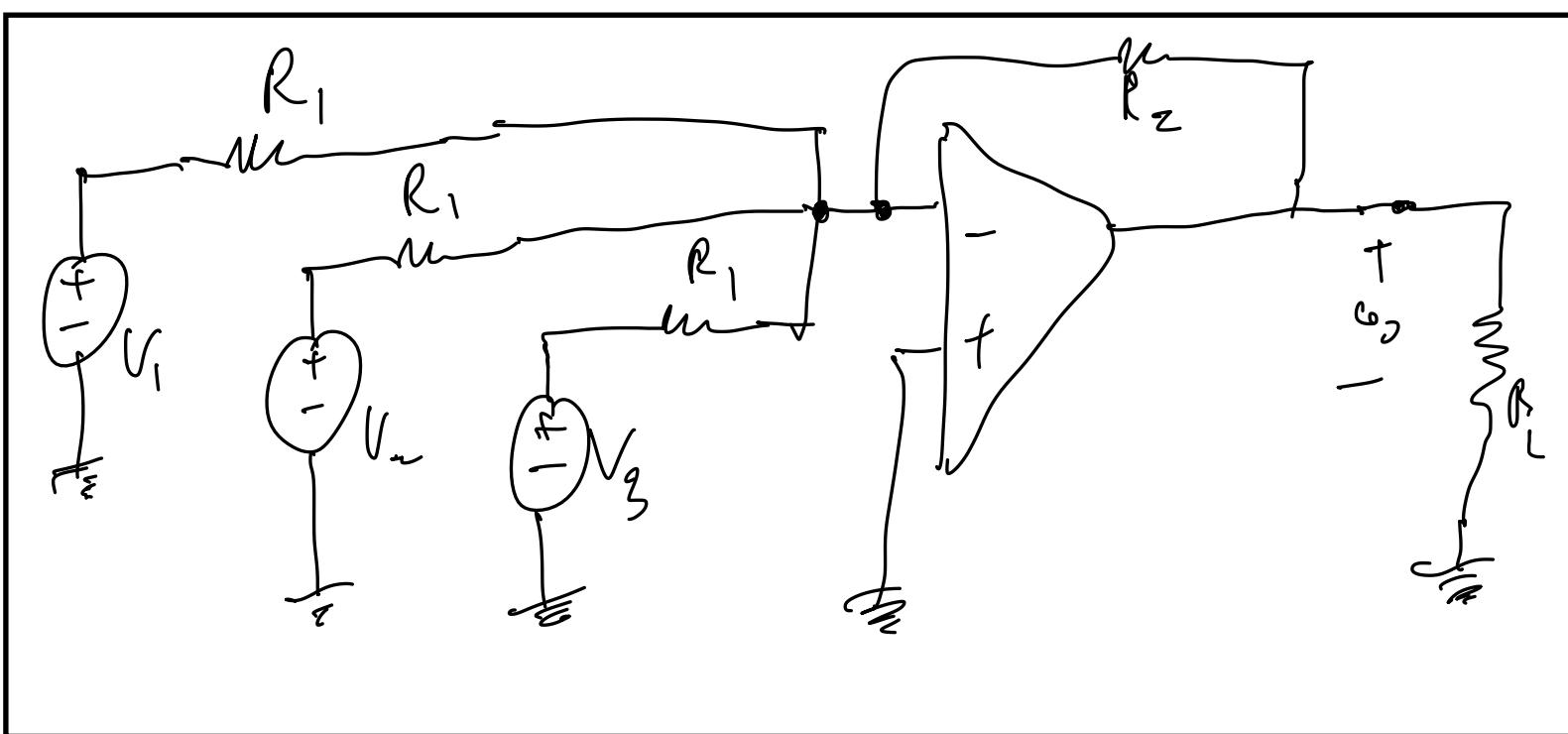


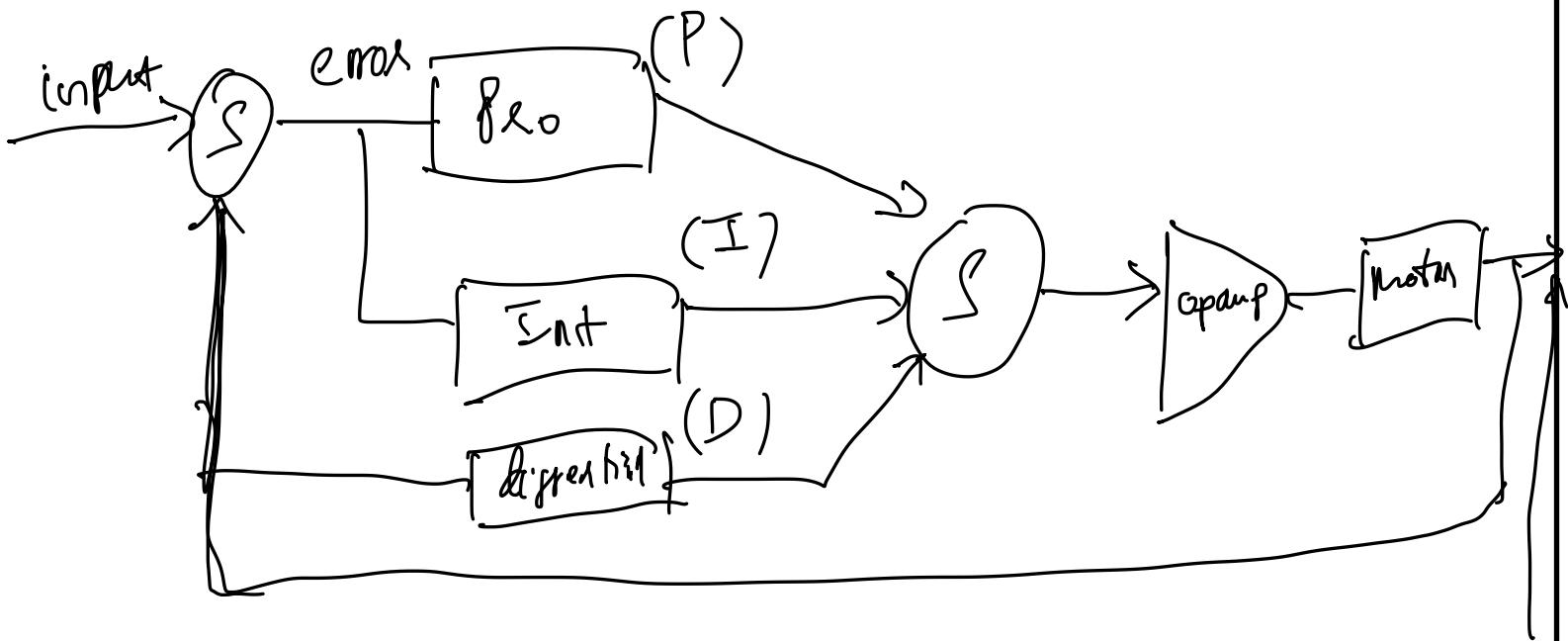c) Firstly, we have the block diagram (23)



The opamp will take the combination of 3 input as P, I, & D, and then control the motor, then it also get the output to find the error to make a better result in the next controlling.

Prob 1:

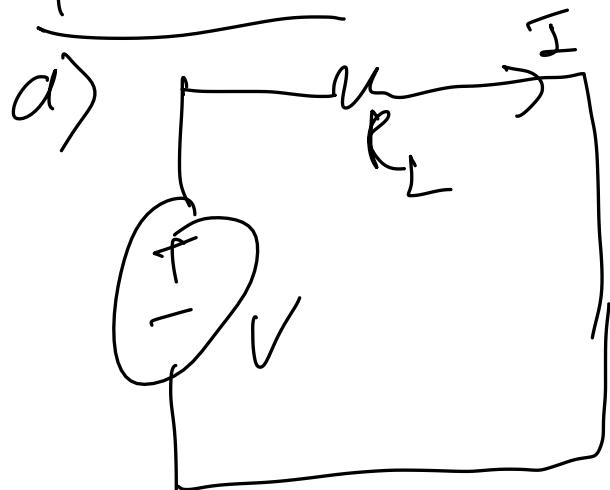

$$\Rightarrow P_{R_L} = I^2 R_L$$

$$I = \frac{V}{R_L} \Rightarrow I^2 = \frac{V^2}{R_L^2}$$

$$\Rightarrow P_R = \frac{V^2}{R_L^2} R_L = \boxed{\frac{V^2}{R_L}}$$

b) length: L  
mass: kg  
time: s  $\Rightarrow$  iii) Amperes

c)  $Z = R + jX$  with  $R$  is a real part,  $jX$  is a imaginary part.

then Ohm Law:

$$I = \frac{V}{Z} = \frac{V}{R + jX}$$

d) A phasor is a complex number representing a sinusoidal function whose amplitude  $A$ , angular frequency  $\omega$  and initial phase  $\theta$ .

#25

Voltage phasor  $V \Rightarrow I = \frac{V}{Z}$

$$V = V_0 \cos(\omega t + \phi) = V_0 \cos(\omega t)$$

$$R + jX = \sqrt{R^2 + X^2} \quad \angle \arctg(X/R)$$

$$\Rightarrow I = \frac{V_0}{Z} = \frac{V_0 \angle 0^\circ}{\sqrt{R^2 + X^2} \quad \angle \arctg(X/R)}$$

$$\rightarrow I = \frac{V_0}{\sqrt{R^2 + X^2}} \quad \angle \arctg(X/R)$$

$$\Rightarrow P_{\text{loss}} = VI = \frac{V_0^2}{\sqrt{R^2 + X^2}} \quad \angle \arctg(X/R)$$

The meaning of the imaginary component of power  
shows us that in addition to the  
resistance, the power also be stored by  
the capacitor or inductor.


e)

#27


f)

Problems :

#28

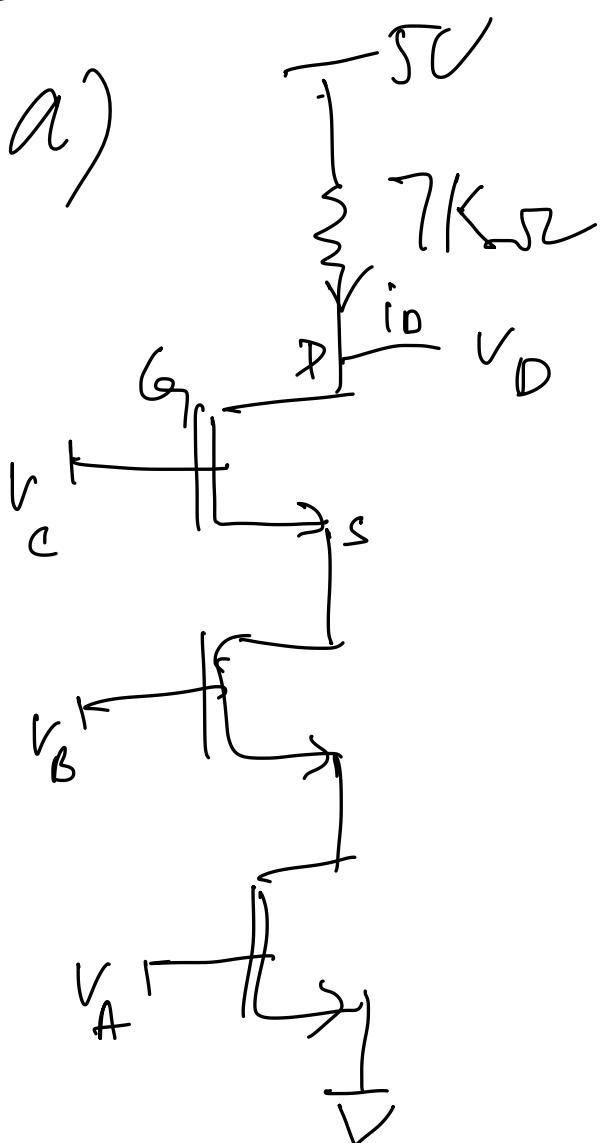

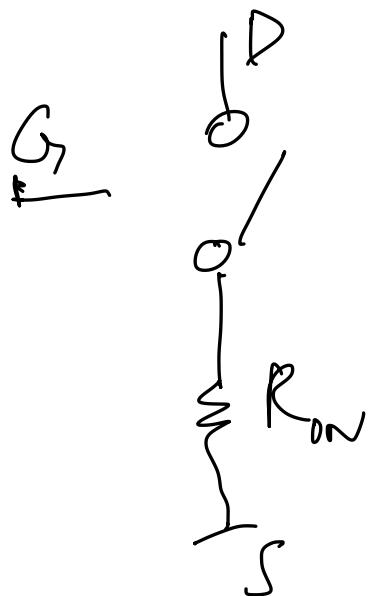$V > 4 \Rightarrow$  one  
 $V_L ( ) \Rightarrow 0$



$$V_{in} < V_{th}$$

$$5 - V_D = iR = 7i$$

$$\Rightarrow V_D = 5 - 7i$$

