

Problem 1:


What Ho
105355311

P1.12: Given $i(t) = 10 \sin(200\pi t)$ (A)

$$\Rightarrow \omega = 2\pi f = 200\pi \Rightarrow 2f = 200 \Rightarrow f = 100 \text{ (Hz)}$$

$$\Rightarrow T = \frac{1}{100 \text{ Hz}} = 0.01 \text{ (s)} = 10 \text{ (ms)}.$$

a) Sketch $i(t)$ to scale versus time.

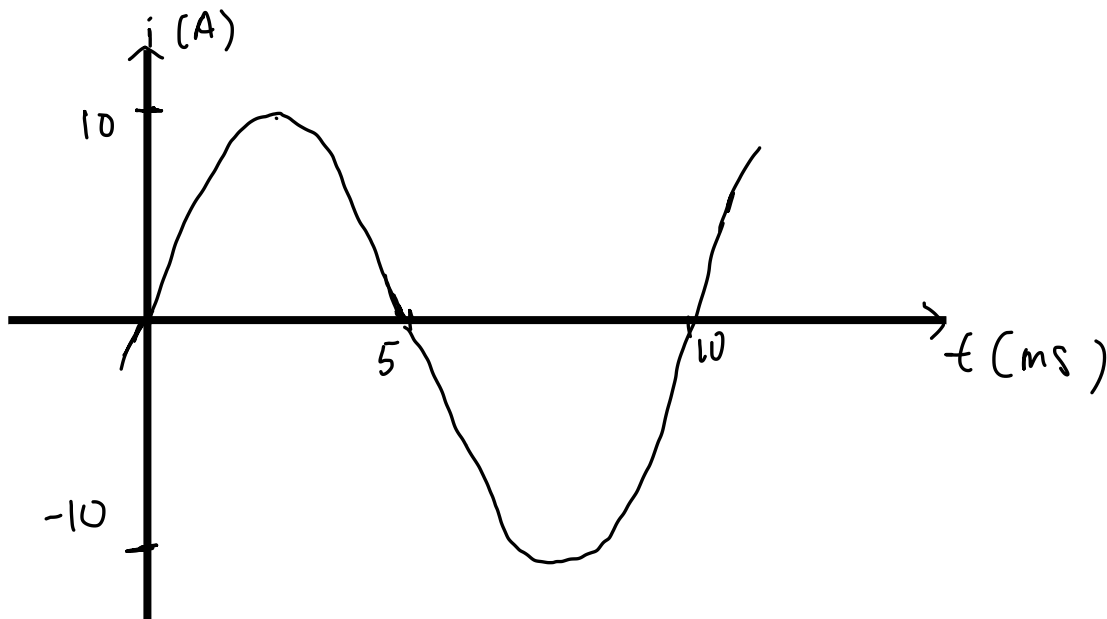

b) Determine the net charge that passes through the element between $t=0$ & $t=5 \text{ ms}$ ($\Rightarrow t_0 = 0 \text{ ms}$ & $t = 5 \text{ ms} =$

We have: $i(t) = \frac{dq(t)}{dt}$ or $q = \int_{t_0}^t i(t) dt = \int_0^{0.005} 10 \sin(200\pi t) dt$

$$= \frac{10}{200\pi} [\cos(200\pi t)] \Big|_0^{0.005} = \frac{1}{20\pi} \cos(200\pi t) \Big|_0^{0.005}$$

$$= \frac{1}{20\pi} [\cos 0 - \cos(200\pi \times 0.005)] = \frac{1}{20\pi} [1 - (-1)]$$

$$= \frac{2}{20\pi} = \frac{1}{10\pi} \approx 0.0318 \text{ (C)} = \boxed{31.83 \text{ mC}}$$

c) Repeat With $t_0 = 0 \text{ ms} \rightarrow t = 10 \text{ ms}$.

Based on b, we have the charge:


$$Q = \int_0^{0.01} 10 \sin(200\pi t) dt = \frac{1}{20\pi} \cos(200\pi t) \Big|_0^{0.01}$$

$$= \frac{1}{20\pi} [\cos 0 - \cos 2\pi] = \frac{1}{20\pi} [1 - 1] = \boxed{0 \text{ (C)}}$$

Problem 2:

P1.24: Given $\begin{cases} v(t) = 10 \text{ V} \\ i(t) = 2e^{-t} \text{ A} \end{cases}$

the element.

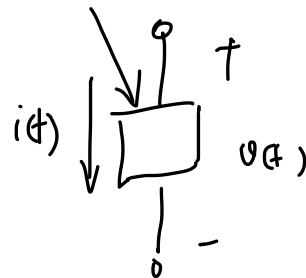

* Compute the power for the circuit:

We have the power: $P(t) = v(t) \times i(t) = 10 \times 2e^{-t} = \boxed{20e^{-t} \text{ (W)}}$

\Rightarrow The energy transferred between $t_0 = 0 \rightarrow t = \infty$: $E = \int_{t_0}^t P(t) dt$


$$\Rightarrow E = \int_0^{\infty} 20e^{-t} dt = -20e^{-t} \Big|_0^{\infty} = 20e^{-t} \Big|_0^{\infty}$$

$$= 20(e^0 - e^{-\infty}) = 20(1 - 0) = \boxed{20 \text{ (J)}}$$

because the energy $E = 20 \text{ (J)} > 0$, the energy is absorbed by the element.

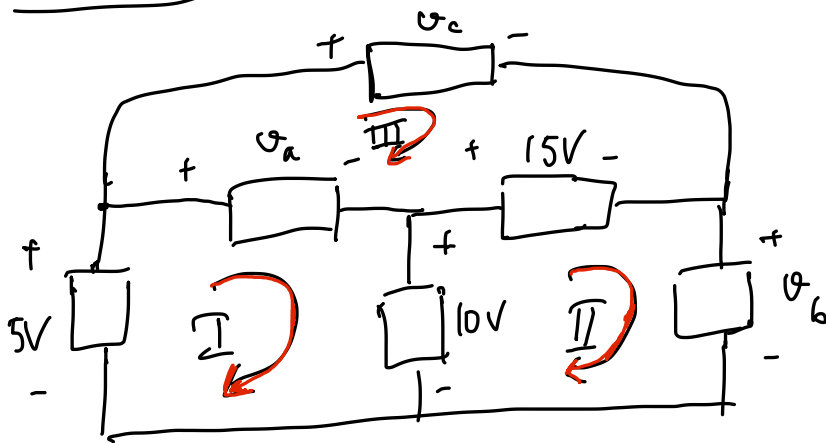Problem 3

P1.42: Use KVL to solve the voltage V_a , V_b & V_c .



Check for loop I, then applying KVL, we have:

$$-5V + V_a + 10V = 0 \Rightarrow V_a = 5 - 10 = -5V \Rightarrow \boxed{V_a = -5V}$$

Applying the KVL for loop II,

$$-10V + 15V + V_b = 0 \Rightarrow V_b = 10 - 15 = -5V$$

$$\Rightarrow \boxed{V_b = -5V}$$

Also applying the KVL for loop III.

$$-V_a + V_c - 15 = 0 \Rightarrow V_c = 15 + V_a = 15 - 5 = 10V$$

$$\Rightarrow \boxed{V_c = 10V}$$

Problem 4

P1.55: Given $P = 100\text{W}$, $V = 100\text{V} \Rightarrow$ find the resistance.

$$\text{We have } P = V \cdot I = V \cdot \frac{V}{R} = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P}$$

$$\Rightarrow R = \frac{(100\text{V})^2}{100\text{W}} = \frac{100^2}{100} = \boxed{100(\Omega)}$$

Then suppose the voltage is reduced by 10% (to 90V)

\Rightarrow What percentage the power is reduced..?

(assume the R remains constant)

$$\text{We have : } P_{\text{new}} = \frac{V_{\text{new}}^2}{R} = \frac{(90\text{V})^2}{100\Omega} = \frac{90^2}{100} = 81(\text{W})$$

$$\Rightarrow \Delta P = P - P_{\text{new}} = 100 - 81 = 19\text{W}$$


\Rightarrow the power is reduced 19W (to 81W)

\Rightarrow percentage the power is reduced:

$$\frac{\Delta P}{P} \times 100 = \frac{19\text{W}}{100\text{W}} \times 100 = \boxed{19\%}$$

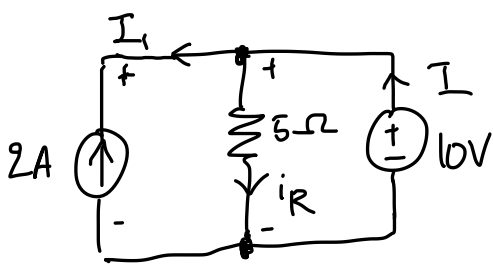Problem 5

P1.63: Find the current i_R through the resistor.



Based on the circuit, we have

$$V_R = 10V \Rightarrow i_R = \frac{V_R}{R} = \frac{10V}{5\Omega} = \boxed{2A}$$

Then find the power of each element in the circuit.

* For the 5Ω resistor:

$$P_R = V_R \cdot I_R = 10V \cdot 2A = \boxed{20(W) > 0}$$

\Rightarrow the resistor is receiving power, or the energy is absorbed by it.

* For the current source:

Based on the circuit, applying the KCL, we have:

$$I = i_R + I_1 = 2 + I_1, \text{ also } I_1 = -2A.$$

$$\Rightarrow I = 0(A)$$

\Rightarrow the power for the current source:

$$P = V I_1 = 10 \cdot (-2) = \boxed{-20(W) < 0}$$

\Rightarrow the current source supplies the energy or not receiving power.

* For the voltage source:


$$P = V \cdot I = (-10) \cdot 0 = \boxed{0(W)}$$

\Rightarrow the voltage source is not receiving the power

Finally, the resistor is receiving power.

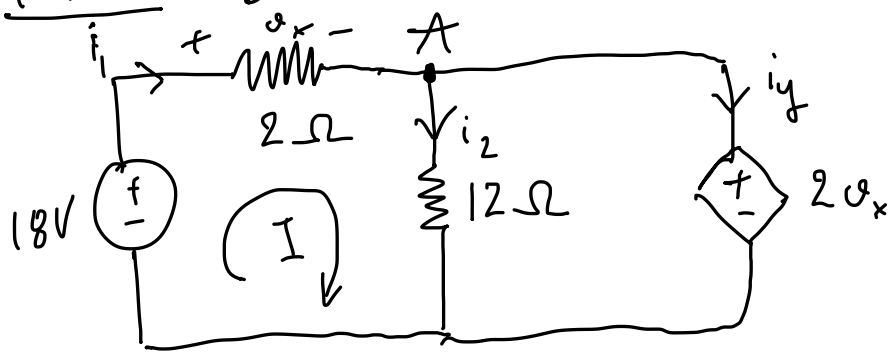Problem 6

P1.71: Determine the value of v_x & i_y in the circuit.



Firstly, we apply the KVL to the outer loop, we have:

$$-18V + v_x + 2v_x = 0 \Rightarrow 3v_x = 18V \Rightarrow \boxed{v_x = 6V}$$

$$\text{Also, } i_1 \times 2\Omega = v_x \Rightarrow i_1 = \frac{v_x}{2\Omega} = \frac{6V}{2\Omega} = 3A.$$

We continue applying the KVL for loop I, we have:

$$-18V + v_x + 12i_2 = 0 \Rightarrow 12i_2 = 18V - v_x = 18 - 6 = 12V$$


$$\Rightarrow i_2 = 1A.$$

Apply the KCL at A, we have:

$$i_1 = i_2 + i_y \Rightarrow i_y = i_1 - i_2 = 3A - 1A = \boxed{2A}.$$

Problem 7

P1.74 Given the circuit:

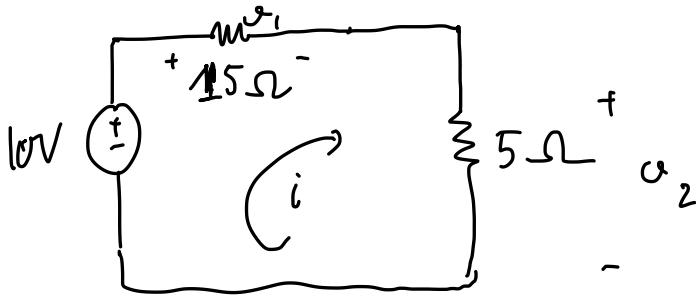

a) Use KVL to write an equation relating the voltages

Apply the KVL, we have: $-10V + u_1 + u_2 = 0$

$$\Rightarrow \boxed{u_1 + u_2 = 10V} \quad (1)$$

b) we have $V = IR$ (Ohm's Law)

$$\Rightarrow \begin{cases} u_1 = 15i \text{ (V)} \\ u_2 = 5i \text{ (V)} \end{cases} \quad (2)$$

c) From (1) & (2), we have: $u_1 + u_2 = 10V \Leftrightarrow 15i + 5i = 10V$

$$\Rightarrow 20i = 10V \rightarrow i = \frac{10V}{20} = 0.5A \rightarrow \boxed{i = 0.5A}$$

d) We have:

$$\text{* For } u_1: u_1 = 15\Omega \times i = 0.5 \times 15 = 7.5 \text{ (V)}$$

$$P_1 = u_1 \times i = 7.5V \times 0.5A = \boxed{3.75 \text{ (W)}} > 0$$

\Rightarrow The 15Ω -resistor absorbed the energy

$$\text{* For } u_2: u_2 = 5\Omega \times i = 5\Omega \times 0.5A = 2.5 \text{ (V)}$$

$$\Rightarrow P_2 = u_2 \times i = 2.5V \times 0.5A = \boxed{1.25 \text{ (W)}} > 0$$

\Rightarrow the 5Ω -resistor absorbed the energy

* For voltage source: $P = V \times I = -10V \times 0.5A = \boxed{-5(W)} < 0$
 \Rightarrow the voltage source delivered the power.

From above, we have the total power:

$$\sum P = P_1 + P_2 + P = 3.75 + 1.25 + (-5) = 0(W)$$

\Rightarrow the power is conserved (because the power delivered

by the voltage source is equal to the power absorbed by
2 resistors: $15\ \Omega$ & $5\ \Omega$)