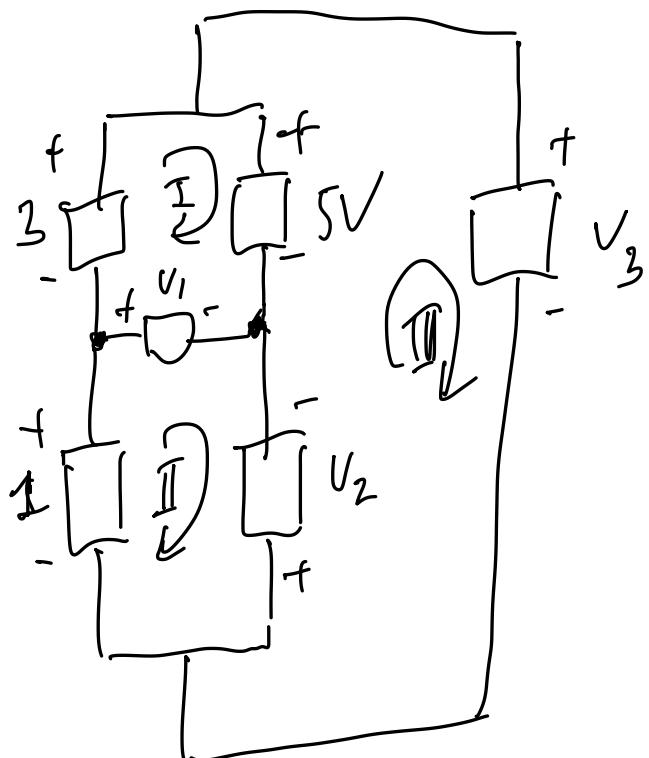


What to

Problem :

Apply KVL in I, we have

a) We have :



$$5 - V_1 - 3 = 0$$

$$\Rightarrow V_1 = 2(V)$$

Apply KVL in II, we have

$$V_1 - V_2 - 1 = 0$$


$$\Rightarrow 2 - 1 - V_2 = 0$$

$$\Rightarrow V_2 = 1(V)$$

Apply KVL in III, we have

$$-5 + V_3 + V_2 = 0 \Rightarrow V_3 = 5 - V_2$$

$$\Rightarrow V_3 = 5 - 1 = 4(V)$$

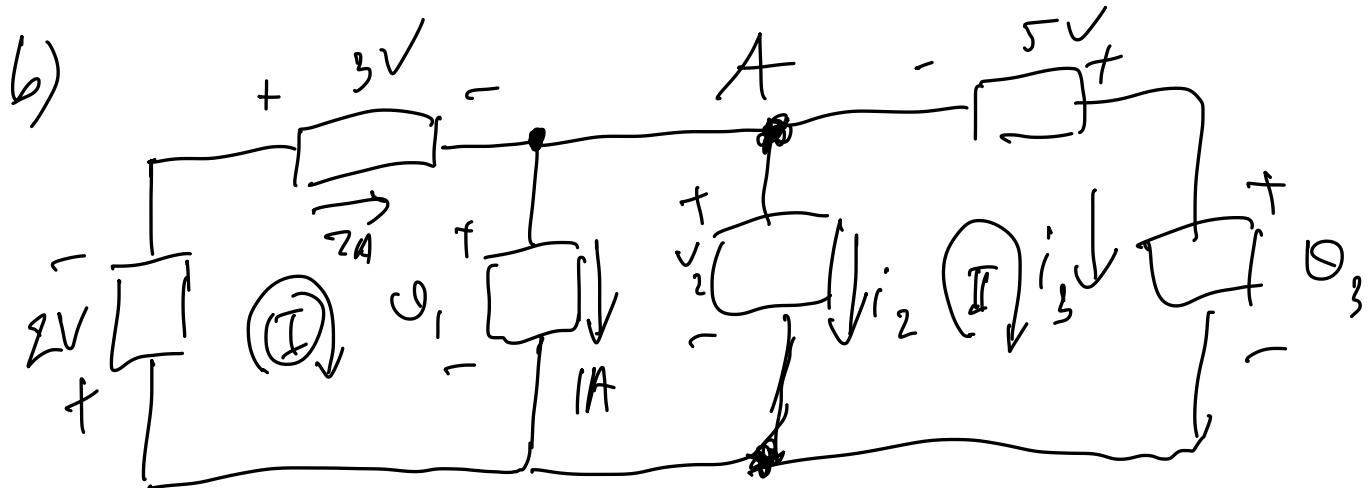

Apply KVL for (I), we have:

$$2V + 3V + \vartheta_1 = 0 \Rightarrow \vartheta_1 = -5V$$

Apply KVL for (II), we have:

$$-V_2 - 5V + \vartheta_3 = 0 \Rightarrow \vartheta_3 - V_2 = 5V$$

also $V_1 = V_2 \Rightarrow V_2 = -5V$

$$\Rightarrow \vartheta_3 = \vartheta_2 + 5 = -5 + 5 = 0$$

$$\Rightarrow \vartheta_3 = 0V$$


Apply KCL at A, we have:

$$2A = 1A + i_2 + i_3 \Rightarrow i_2 + i_3 = 1A$$


also $i_3 = -1A$ as the diagram

$$\Rightarrow i_2 = 1 - i_3 = \boxed{2 A}$$

Problem 2 :

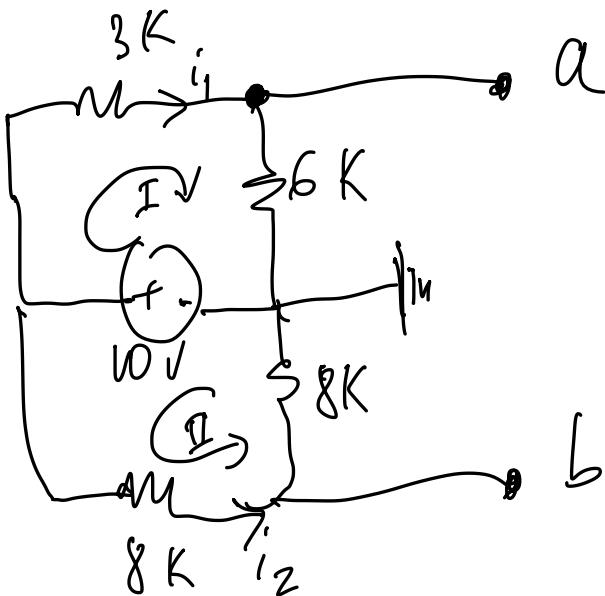

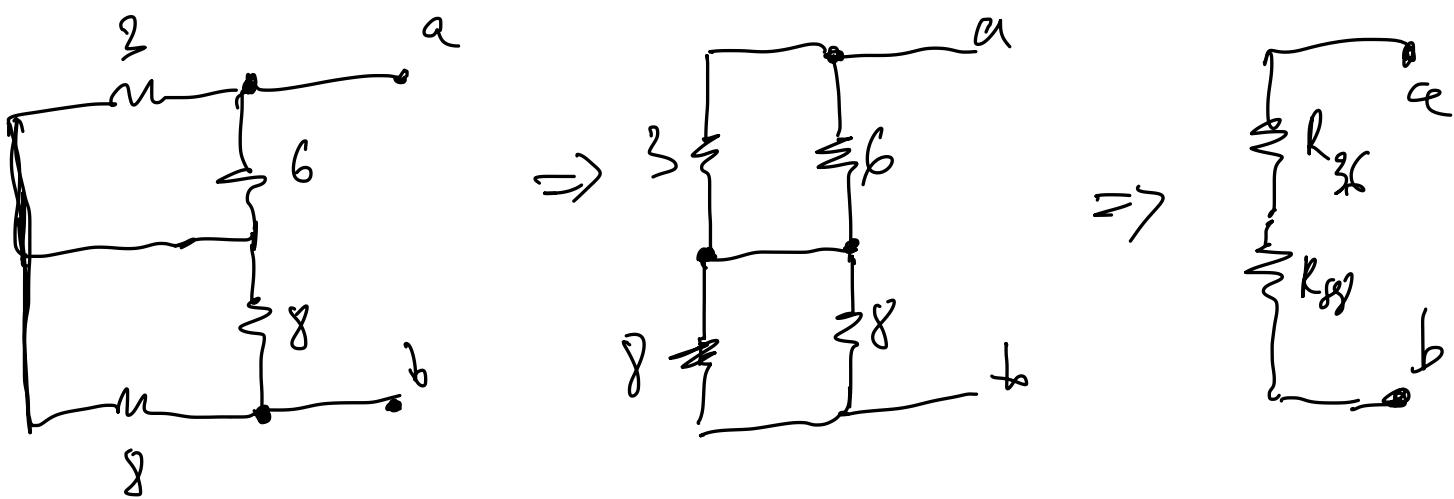To find R_{th} , we short the circuit for voltage source. We know.



$$\text{Since } 3 \parallel 6 \Rightarrow R_{36} = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2 \text{ K}$$

$$8 \parallel 8 \Rightarrow R_{8P} = \frac{8 \times 8}{8+8} = 4 \text{ K}$$

$$\Rightarrow R_{ab} = R_{th} = R_{36} + R_{8P} = 2 + 4 = \boxed{6 \text{ K}}$$

apply KVL for I₁ $\Rightarrow 10 = (3+6) i_1$

$$\Rightarrow i_1 = \frac{10}{9} \text{ mA} \Rightarrow V_a = i_1 \times 6K = \frac{10}{9} \times 6$$

$$\Rightarrow V_a = \frac{60}{9} V = \frac{20}{3} V$$


apply KVL for II $\Rightarrow 10 = 16 i_2 \Rightarrow i_2 = \frac{10}{16} \text{ mA}$

$$\Rightarrow V_b = i_2 \times 8 = \frac{10}{16} \times 8 = 5 V$$


$$\Rightarrow V_{ab} = V_a - V_b = \frac{20}{3} - 5 = \frac{5}{3} V$$

$$\Rightarrow V_{th} = \frac{5}{3} V \quad \text{also } R_{th} = 6K,$$


We have

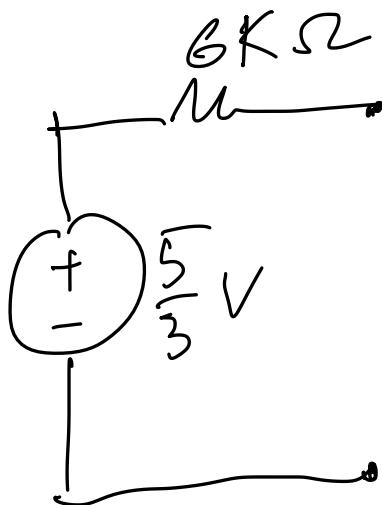

$$\Rightarrow \frac{5}{18} \text{ mA}$$

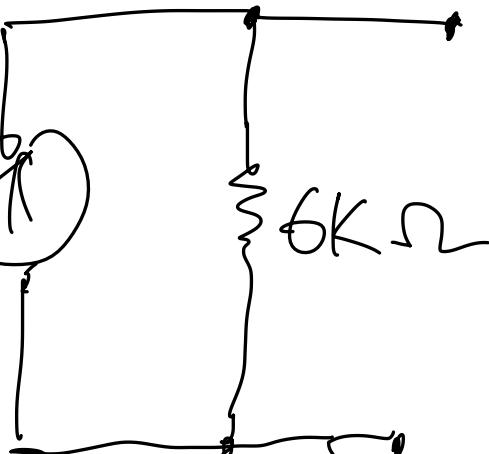

Thevenin

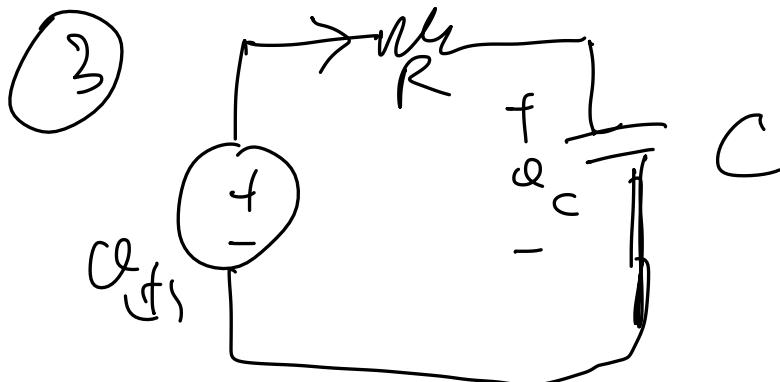


$$R = 1 \text{ k}$$

$$C = 1 \text{ mF}$$

$$t < 0 \quad v(t) = 0$$

$$t \geq 0 \quad v(t) = t$$

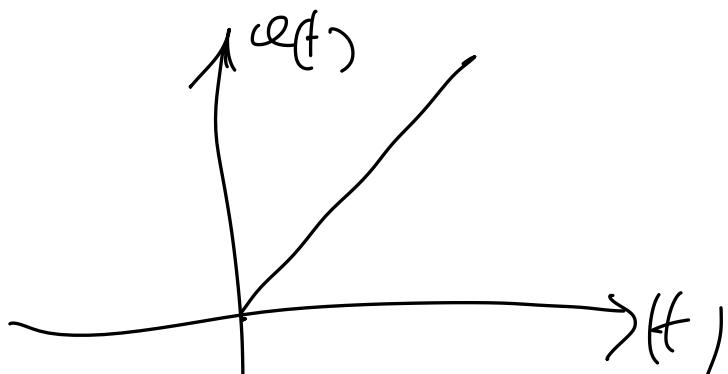

a) We have

$$-v(t) + iR + v_C = 0$$

$$\Rightarrow -v_{(t)} + RC \frac{dv_C}{dt} + v_C = 0$$


$$\Rightarrow RC \frac{dv_C}{dt} + v_C = v(t)$$

$$\Rightarrow \frac{dv_C}{dt} + \frac{1}{RC} v_C = \frac{1}{RC} v(t)$$

Based on this equation we have:

$$V_{df} = V_C(t) - [V_C(0) - V_C(0^+)] e^{-t/RC}$$

When $t \rightarrow \infty$, we have

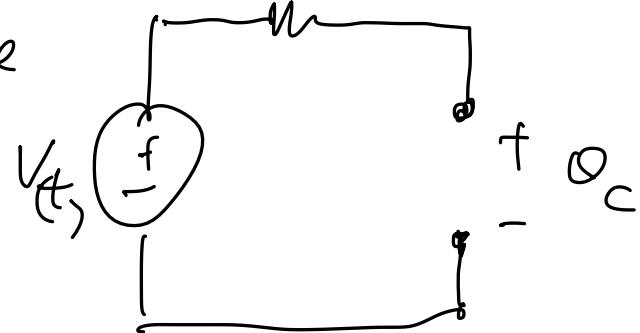

$$\Rightarrow V_C(\infty) = V(t) = t$$


At $t=0$, $V_C(0^+) = 0$

$$\Rightarrow V_C(t) = t - [t - 0] e^{-t/RC}$$

$$\Rightarrow V_C(t) = t - t e^{-t/RC}$$


$$RC = 1000 \times 1 \times 10^{-3} = 1 \text{ s}$$

$$\Rightarrow V_{df} = t - t e^{-t}$$

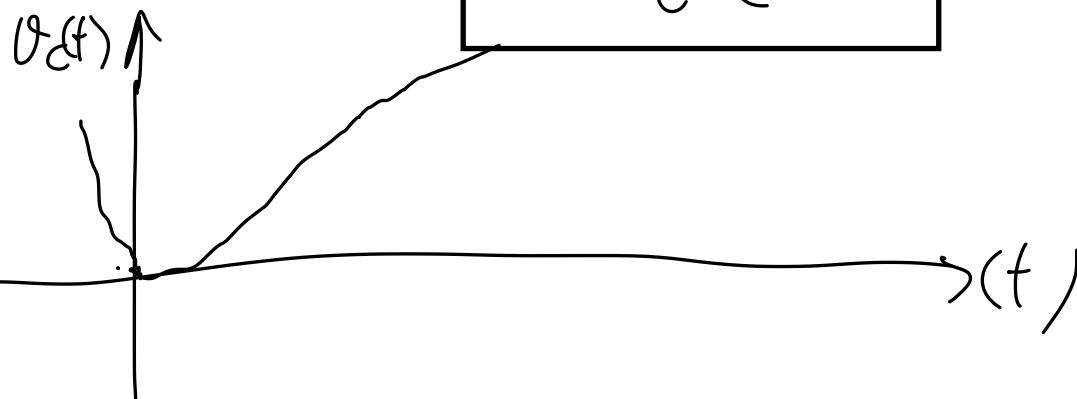

Problem 4: Switch open for a long time

=> We have:

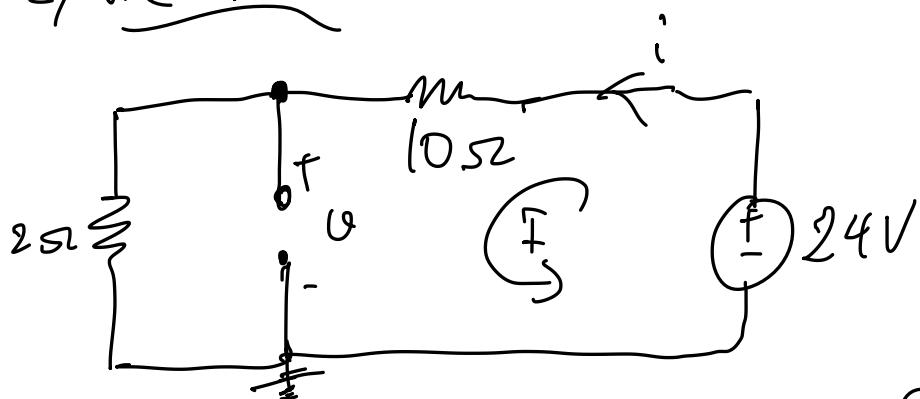

apply KVL for loop I, we have:

$$-24 + i(10 + 2) = 0$$

$$\Rightarrow i = \frac{24}{12} = 2(A)$$

$$\Rightarrow V = i \times 2 = 2 \times 2 = 4(V)$$


a) At $t = 0^-$, there is energy stored in the inductor and capacitor since $V_C = 4V$ and $i_L = 2A$. They are not zero

\Rightarrow stored the energy.

$$\Rightarrow E_L = \frac{1}{2} L i^2 = \frac{1}{2} \times 0.4 \times 2^2 = 0.8 J$$

$$\Rightarrow E_C = \frac{1}{2} C V^2 = \frac{1}{2} \times \frac{1}{20} \times 4^2 = 0.4 J$$

b) After switch close, new circuit:

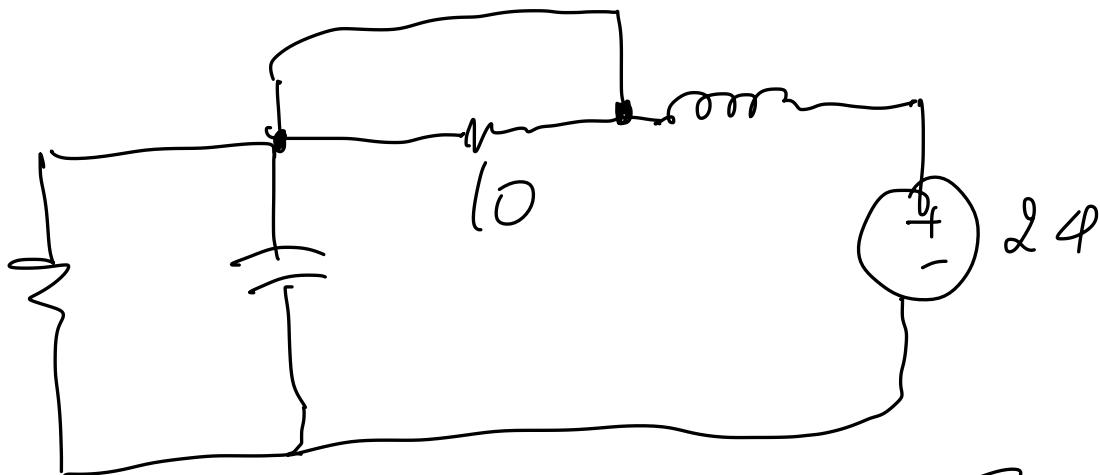

⇒ the $10\ \Omega$ will be shorted and no current go through it

Since ⇒

c) at $t \rightarrow 0^-$, we have $\vartheta_L(0^-) = 4V$
 $i_L(0^-) = 2A$. Since inductors can't change the current instantaneously and capacitors can not change the voltage instantaneously


$$\Rightarrow \boxed{\vartheta_c(0^+) = 4V} \quad \boxed{i_L(0^+) = 2A}$$

$$\text{We have: } v_L = L \frac{di}{dt}$$

$$\Rightarrow \frac{di(0^+)}{dt} = \frac{1}{L} v(0^+)$$

$$i_C = C \frac{dv_C}{dt} \Rightarrow \frac{dv_C(0^+)}{dt} = \frac{1}{C} i_C(0^+)$$

After switch close $f = 0^+$,

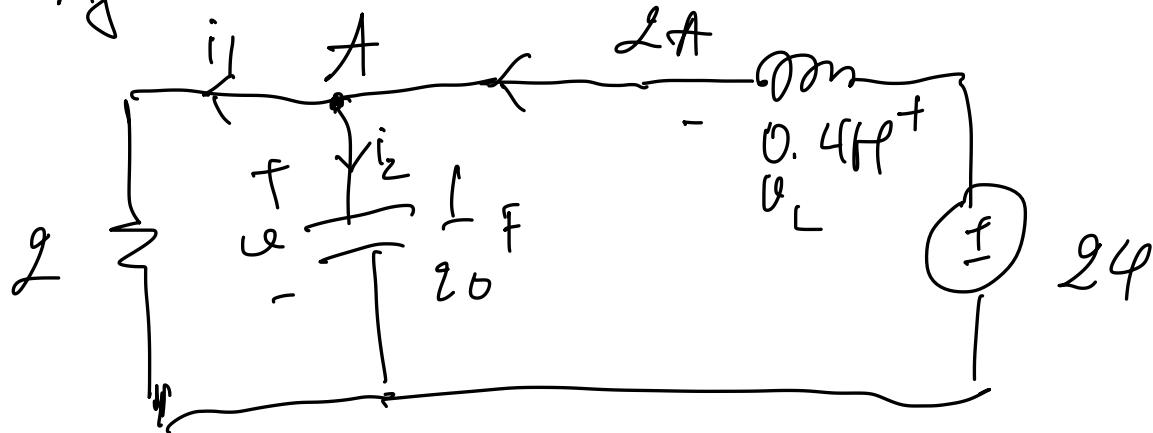

$$\Rightarrow i_1(0^+) = \frac{v}{2} = \frac{4}{2} = 2(A)$$

$$\Rightarrow i_2 = 2 - 2 = 0$$

$$\Rightarrow i_C(0^+) = 0 \Rightarrow$$

$$\frac{dv(0^+)}{dt} = \frac{1}{C} i_C(0^+) \\ = 0$$

Also, at $t = 0^+$, $\theta = 45^\circ$


$$-24 + \mathcal{O}(0^+) + 4 = 0$$

$$\Rightarrow V_L(0^+) = 24 - 4 = 20 \text{ V}$$

$$\Rightarrow \frac{di(0^+)}{dt} = \frac{1}{L} \mathcal{O}_L(0^+) = \frac{20}{0.4}$$

$$\Rightarrow \frac{di(0^+)}{dt} = 50$$

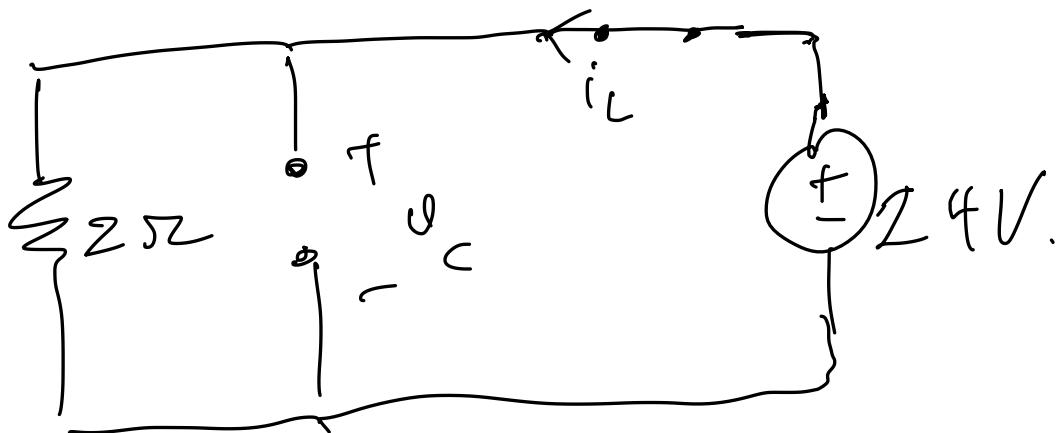d) When $t \rightarrow \infty$, the current




$$\Rightarrow i_L(\infty) = \frac{24}{2} = 12 \text{ A}$$

$$\mathcal{O}_C(\infty) = 12 \times 2 = 24 \text{ V}$$

Continue 1c .

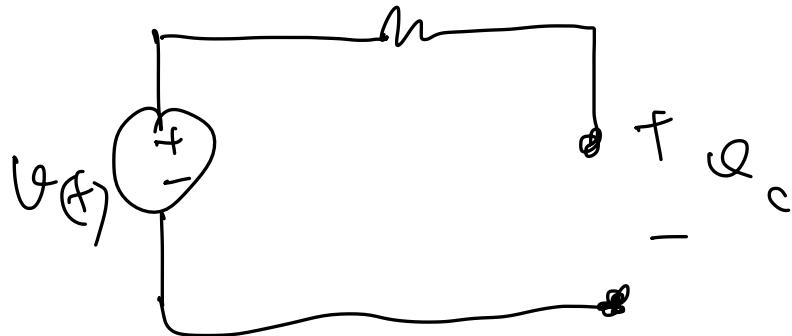When t is big enough time , we will have :



$$\text{So } V_c = v(t)$$

→ the capacitor voltage will be equal to the $v(t)$.

q) We have $i_c = C \frac{dV_c}{dt}$

also $V_c(t) = t - te^{-t}$

$$\Rightarrow \frac{dQ_c(t)}{dt} = 1 - [e^{-t} - te^{-t}]$$

$$= 1 - e^{-t} + te^{-t}$$

$$\Rightarrow i(t) = 10^{-3} \left(1 - e^{-t} + t e^{-t} \right) \text{ (A)}$$

a) We have:

$$P(t) = \varrho(t) i(t)$$

$$= 10^{-3} \cdot (t - t e^{-t}) (1 - e^{-t} + t e^{-t})$$


$$= 10^{-3} \left(t - t e^{-t} + t^2 e^{-t} - t^2 e^{-t} + t e^{-2t} - t^2 e^{-2t} \right)$$

$$= 10^{-3} \left(t - 2t e^{-t} + t^2 e^{-t} + t e^{-2t} - t^2 e^{-2t} \right)$$

f) The power delivered by the battery will be dissipated on the resistor

Problem 5: [I do b first]

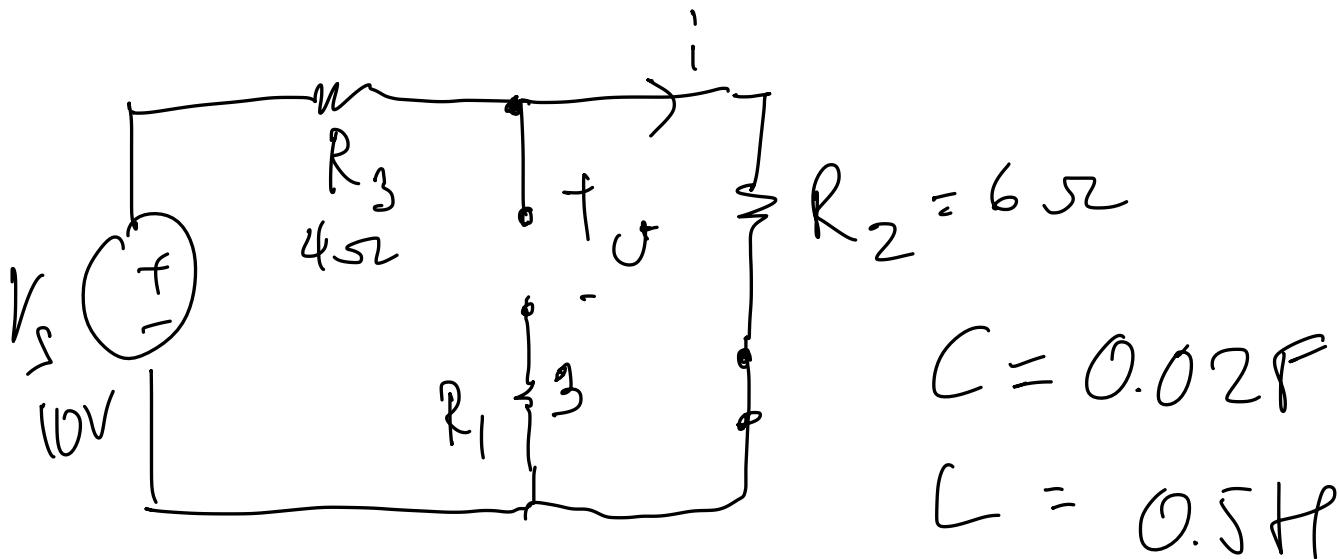b) at $t \rightarrow 0^-$, switch close for a long time, we have:



Apply KVL for the loop, we have:

$$10 = i(R_3 + R_2) = 10i$$

$$\Rightarrow i = 1 A \Rightarrow i_L(0^-) = 1 A$$

$$\Rightarrow \theta = iR_2 = 1 A \times 6 \Omega = 6 V$$

$$\Rightarrow \theta_C(0^-) = 6 V$$

After open switch at $t \rightarrow 0^+$, the capacitor could not change voltage instantaneously


$$\Rightarrow V_C(0^-) = V_C(0^+) = 6V$$

c) Find $\frac{dV_C(0^+)}{dt}$

We have : $i_C = C \frac{dV_C}{dt}$

$$\Rightarrow \frac{dV_C}{dt} \Big|_{t=0^+} = \frac{1}{C} \cdot i_C(0^+)$$

We know, after close switch, we have:

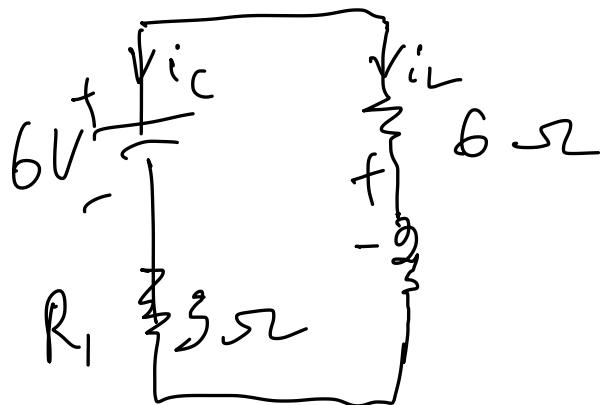

Since

$$i_C(0^+) = -i_L(0^+)$$

$$\Rightarrow i_C(0^+) = -i_L(0^+)$$


From above, we have already $i_L(0^-) = 1A$
 As the inductor could not change current
 instantaneously $\Rightarrow i_L(0^+) = i_L(0^-) = 1A$

$$\Rightarrow i_C(0^+) = -1A.$$


$$\Rightarrow \frac{dc}{dt} \Big|_{t=0^+} = \frac{1}{0.02} \times (-1)$$

$$= \boxed{-50}$$

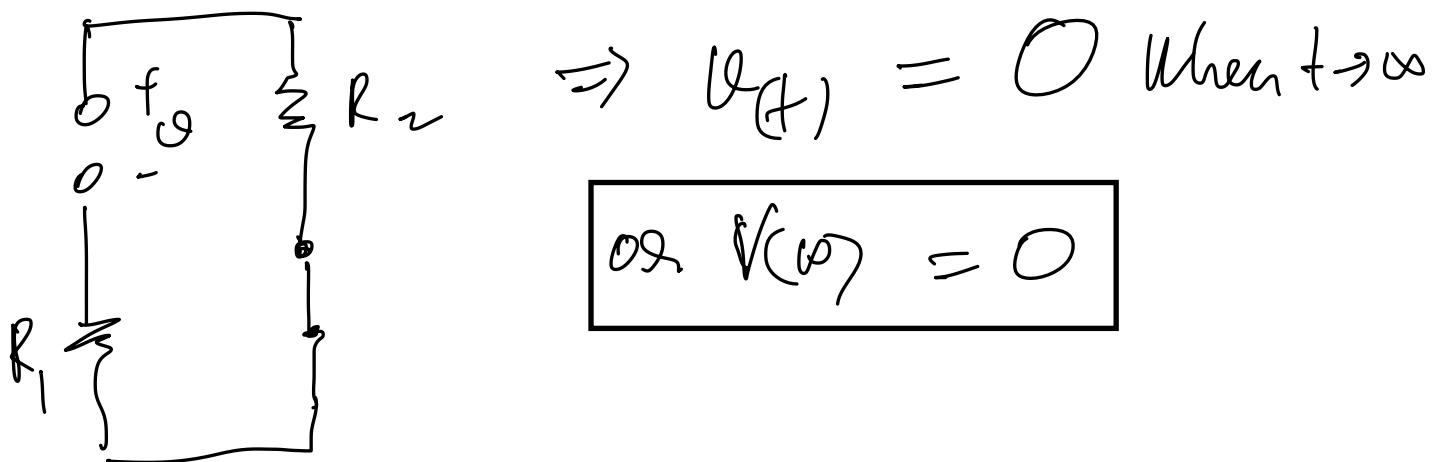f) When $t \rightarrow \infty$, we have :



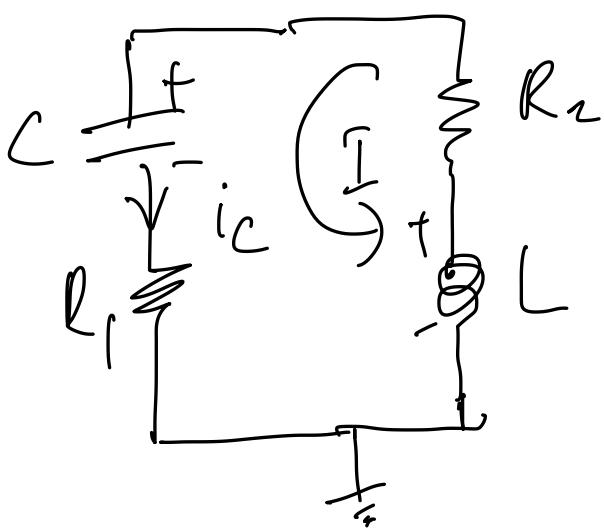back to 5a: We have already:
 $\left\{ \begin{array}{l} V_C(0^+) = 6V \\ I(0^+) = 1A \end{array} \right.$



Apply KVL for I ,
we have:

$$\text{also } i_C = -i_L$$

$$\Rightarrow i_L(t) = -C \frac{dV_C}{dt}$$

$$V_C + i_C(R_1 + R_2) - V_L = 0$$

$$\Rightarrow V_C + C \frac{dV_C}{dt} (R_1 + R_2) - L \frac{di_L}{dt} = 0$$

$$\Rightarrow V_C + C \frac{dV_C}{dt} (R_1 + R_2) - L \frac{d}{dt} \left(-C \frac{dV_C}{dt} \right) = 0$$

$$\text{Call } \ell = R_1 + R_2$$

$$\Rightarrow \varphi_c(t) + RC \frac{d\varphi_c}{dt} + [C \frac{d^2 \varphi_c(t)}{dt^2}] = 0$$

$$\Rightarrow \frac{d^2 \varphi_c(t)}{dt^2} + \frac{R}{L} \frac{d\varphi_c(t)}{dt} + \frac{1}{LC} \varphi_c(t) = 0$$

$$\Rightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\Leftrightarrow s^2 + 2\xi\omega_0 s + \omega_0^2 = 0$$

where $\omega_0 = \frac{1}{\sqrt{LC}}$; $\xi = \frac{1}{2} \cdot \frac{R}{\sqrt{LC}}$

$$L = 0.5 \text{ H}$$

$$C = 0.02 \text{ F} \Rightarrow LC = 0.01$$

$$\Rightarrow \omega_0 = 10$$

$$\xi = \frac{6}{2 \times 5} = 0.6$$

e) $\xi = 0.6 < 1 \Rightarrow$ underdamp.

f) We have already $\omega_0 = 10$

$$\omega_n = \sqrt{1 - \xi^2} \omega_0 = \sqrt{1 - 0.6^2} \cdot 10$$
$$= \boxed{8}$$

g) Roots are:

$$\zeta_1, \zeta_2 = -\xi \omega_0 \pm j \omega_0 \sqrt{1 - \xi^2}$$

$$= -0.6 \times 10 \pm j \times 10 \times 0.8$$

$$= \boxed{-0.6 \pm 8j}$$

$$\Rightarrow V_C(t) = K_1 e^{-0.6t} \cos(8t) + K_2 e^{-0.6t} \sin(8t)$$